



**Application Note**

# AS1343

**Where is the limit for the boost conversion?**

## Content Guide

1	Where is the limit for the boost conversion? .....	3
2	Where the boost conversion is used .....	3
3	Where is the limit for transformation factor in boost conversion .....	3
4	Real-world implementation and performance .....	4
5	Contact Information .....	6
6	Copyrights & Disclaimer .....	7
7	Revision Information .....	8

## 1 Where is the limit for the boost conversion?

Almost all portable devices are powered by low voltage batteries. However, in the same devices there are some circuits like LEDs that need high voltage supply. So, there is a need for voltage conversion. This article shows the possible solution with boost DCDC converters and the limits for this.

## 2 Where the boost conversion is used

The mostly batteries used in portable devices are lithium-ion batteries that operate at between 2.7V and 4.2V, and dual-cell alkaline (NiCd or NiMH) batteries that have a 1.6V-3.4V range. The next generations will have even lower battery supply voltage range.

However the typical application circuits require a stable high voltage supply bus of 12V or higher for supplying internal LEDs. Producing such a stable output from a low voltage battery is possible with boost converters that have big transformation factor.

## 3 Where is the limit for transformation factor in boost conversion

The mostly used DCDC boost converter is presented in Fig. 1. Usually, the switch S1 between coil and ground is realized as NMOS transistor and the switch S2 between coil and output as PMOS transistor or diode. To produce the high voltage, instead of PMOS usually the diode is used, and the operation of the circuit will be described with coil, NMOS and diode.

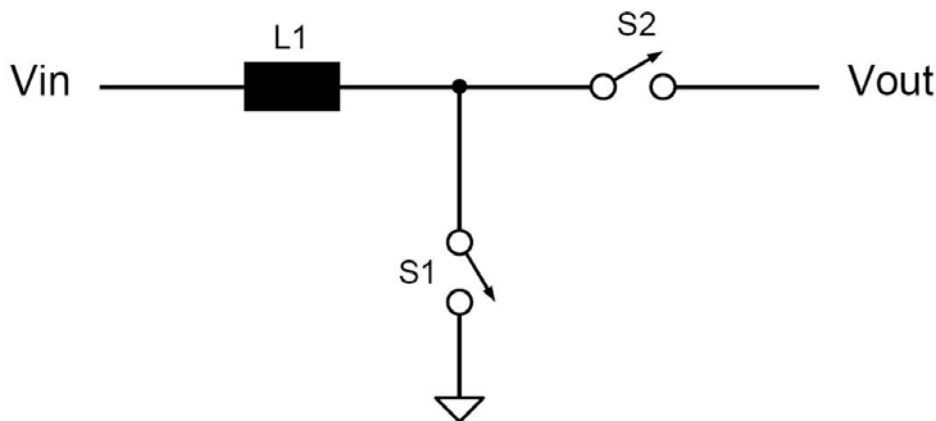


Fig. 1: Simple schematic of the boost converter

During the boost conversion there are two states. During the first one, the NMOS is ON, the current flowing through coil rises and the energy from the input is saved into the coil. During the second one the NMOS is OFF, but the current still must flow through coil and the saved energy is transferred to the output through diode.

The transformation factor  $V_{out}/V_{in}$  is mostly dependent on the duty cycle  $D$ . It represents the fraction of the commutation period  $T$  during which the NMOS switch is ON. In ideal case (no energy

losses)  $V_{out} = V_{in} / (1-D)$ . So if the NMOS is ON 50% of the period time,  $D=0.5$  and  $V_{out} = 2 * V_{in}$ . Similar if we need  $V_{out}$  that is 10 times higher than  $V_{in}$ , we have to realize in ideal case  $D=0.9$ , or NMOS ON time is 90%.

For the real case, we have to add different losses, like resistive and switching losses, what means that  $D$  should be bigger. However, the feedback loop is hard to stabilize if  $D > 0.9$ . Also the changes of the states (ON state to OFF state and vice versa) require some time, and during one period  $T$  usually few percents of it are spent on this.

Because of these reasons, many designer say it makes no sense to try to get transformation factor bigger than 6. But this means that if the supply bus of 12V is needed, minimum battery voltage of 2V is needed.

#### 4 Real-world implementation and performance

AS1343 is DCDC boost converter, with low voltage input and high voltage output. The output is adjustable with two external resistors (see Fig 2).

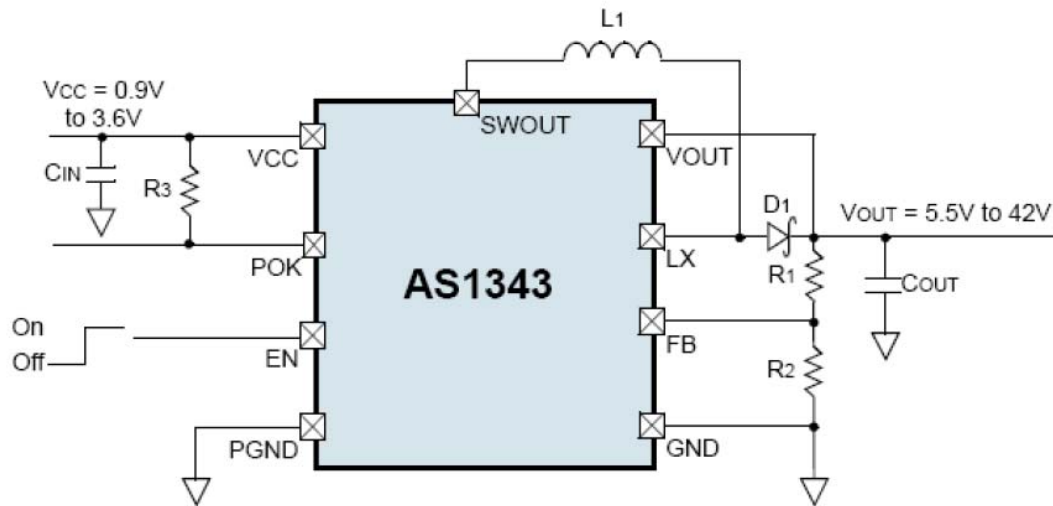


Fig. 2: AS1343 – Typical application diagram

The efficiency for some conditions is presented in the next figures. In Fig 3 we can see that even the transformation factor bigger than 10 (for example producing 15V from 1.2V) is possible with efficiency of 55% for 10mA load. However the Fig. 4 shows that big transformation factor (for example producing 18V from 2V or even 1.5V) is possible, but the energy losses for small loads are so big that the efficiency is less than 50%, what means that more than half of the energy is spent just to perform the conversion. So, the voltage conversion, where the output voltage is 10 or more times higher than input voltage, is possible, but we have to take in account big energy losses. But with two batteries (min. battery voltage 1.8V) we can supply even 15V buses with good efficiency.

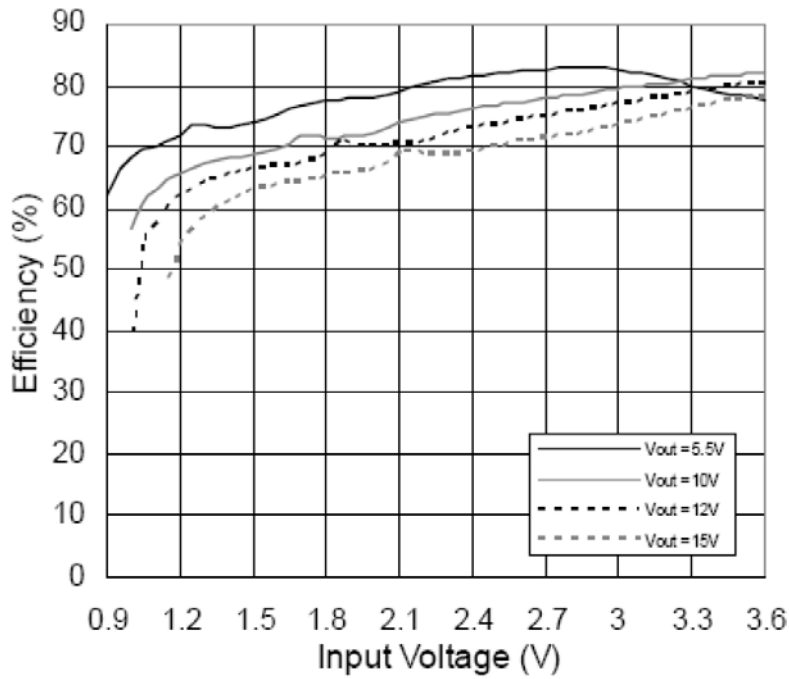


Fig 3: Typical efficiency (with constant Iout) of AS1343

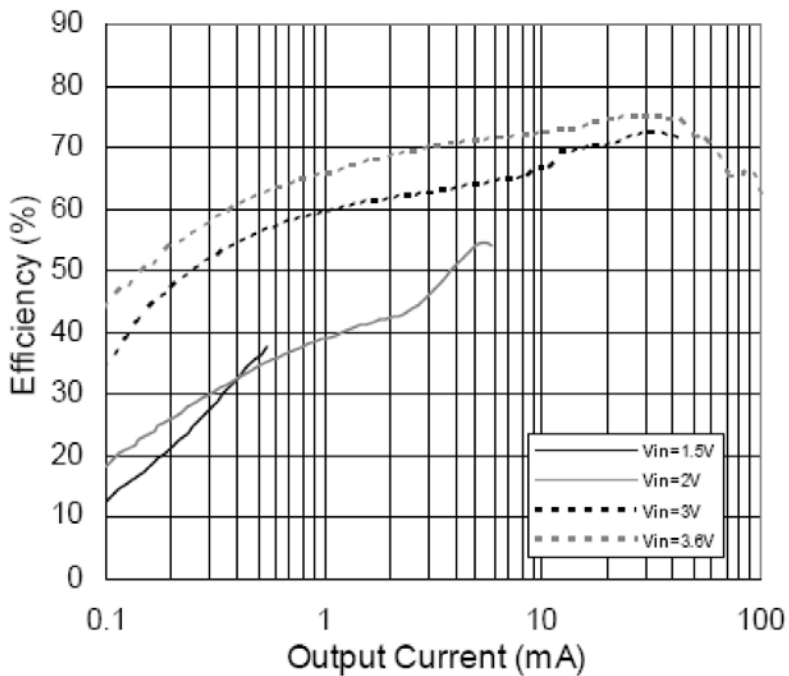


Fig 4: Typical efficiency (with constant Vout) of AS1343

## 5 Contact Information

**Buy our products or get free samples online at:**

[www.ams.com/ICdirect](http://www.ams.com/ICdirect)

**Technical Support is available at:**

[www.ams.com/Technical-Support](http://www.ams.com/Technical-Support)

**Provide feedback about this document at:**

[www.ams.com/Document-Feedback](http://www.ams.com/Document-Feedback)

**For further information and requests, e-mail us at:**

[ams\\_sales@ams.com](mailto:ams_sales@ams.com)

**For sales offices, distributors and representatives, please visit:**

[www.ams.com/contact](http://www.ams.com/contact)

### Headquarters

ams AG

Tobelbaderstrasse 30

8141 Unterpremstaetten

Austria, Europe

Tel: +43 (0) 3136 500 0

Website: [www.ams.com](http://www.ams.com)

## 6 Copyrights & Disclaimer

Copyright ams AG, Tobelbader Strasse 30, 8141 Unterpremstaetten, Austria-Europe. Trademarks Registered. All rights reserved. The material herein may not be reproduced, adapted, merged, translated, stored, or used without the prior written consent of the copyright owner.

Information in this document is believed to be accurate and reliable. However, ams AG does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

Applications that are described herein are for illustrative purposes only. ams AG makes no representation or warranty that such applications will be appropriate for the specified use without further testing or modification. ams AG takes no responsibility for the design, operation and testing of the applications and end-products as well as assistance with the applications or end-product designs when using ams AG products. ams AG is not liable for the suitability and fit of ams AG products in applications and end-products planned.

ams AG shall not be liable to recipient or any third party for any damages, including but not limited to personal injury, property damage, loss of profits, loss of use, interruption of business or indirect, special, incidental or consequential damages, of any kind, in connection with or arising out of the furnishing, performance or use of the technical data or applications described herein. No obligation or liability to recipient or any third party shall arise or flow out of ams AG rendering of technical or other services.

ams AG reserves the right to change information in this document at any time and without notice.

## 7 Revision Information

Changes from 0.1 to current revision 0-10 (2014-Jul-18)	Page
Content updated to latest ams design	

**Note:** Page numbers for the previous version may differ from page numbers in the current revision.