



Application Note

AS1750

Analog Switch with internal shunt switches and a comparator

Content Guide

1	Why the internal shunt switches are needed?	3
2	Why the internal comparator is needed?	3
3	Implementation of these features in AS1750	3
4	Results of the comparator.....	4
5	Contact Information	6
6	Copyrights & Disclaimer	7
7	Revision Information	8

1 Why the internal shunt switches are needed?

Due to the switching between audio sources, audible click-and-pop sounds occur. To reduce these sounds a shunt switch can be implemented and connected to the open terminal of the switch. This shunt switch automatically discharges any capacitance at the open terminal during the OFF state of the switch.

Audible clicks and pops are caused when a step DC voltage is switched into the speaker. By automatically discharging the side that is not connected, any residual DC voltage is removed, thereby reducing clicks and pops.

2 Why the internal comparator is needed?

To be able to implement a mute and headphone function there is the need for an internal comparator. The negative terminal of this comparator should be connected to the outside while the positive terminal should be internally set to some value between GND and VDD. The output of the comparator should be logic high when the negative terminal is below the threshold and logic low when it is above the threshold.

Headphone audio signals are typical biased to $VDD/2$ so a comparator threshold of $VDD/3$ is sufficient for the headphone detection.

For the mute function there are two options. One is to connect a negative terminal to GND (mute button is connected – mute is ON), and this would make the comparator output going to logic high, and the second is to connect the negative terminal to VDD (mute button is not connected – mute OFF), and this would make the comparator output going to logic low. So, the threshold of $VDD/3$ is also ok. This is presented in Fig. 1.

3 Implementation of these features in AS1750

Both functions are implemented in AS1750, as seen in Fig. 1. Typical the value of the shunt resistor is 25 Ohm, and the maximum is 50 Ohm. The Comparator threshold is set to $VDD/3$, with a switching time of typically 300 ns and a maximum of 400 ns.

Current consumption is typically 5 μA to a maximum of 10 μA , because of the comparator working. The Comparator input leakage is lower than 50 nA.

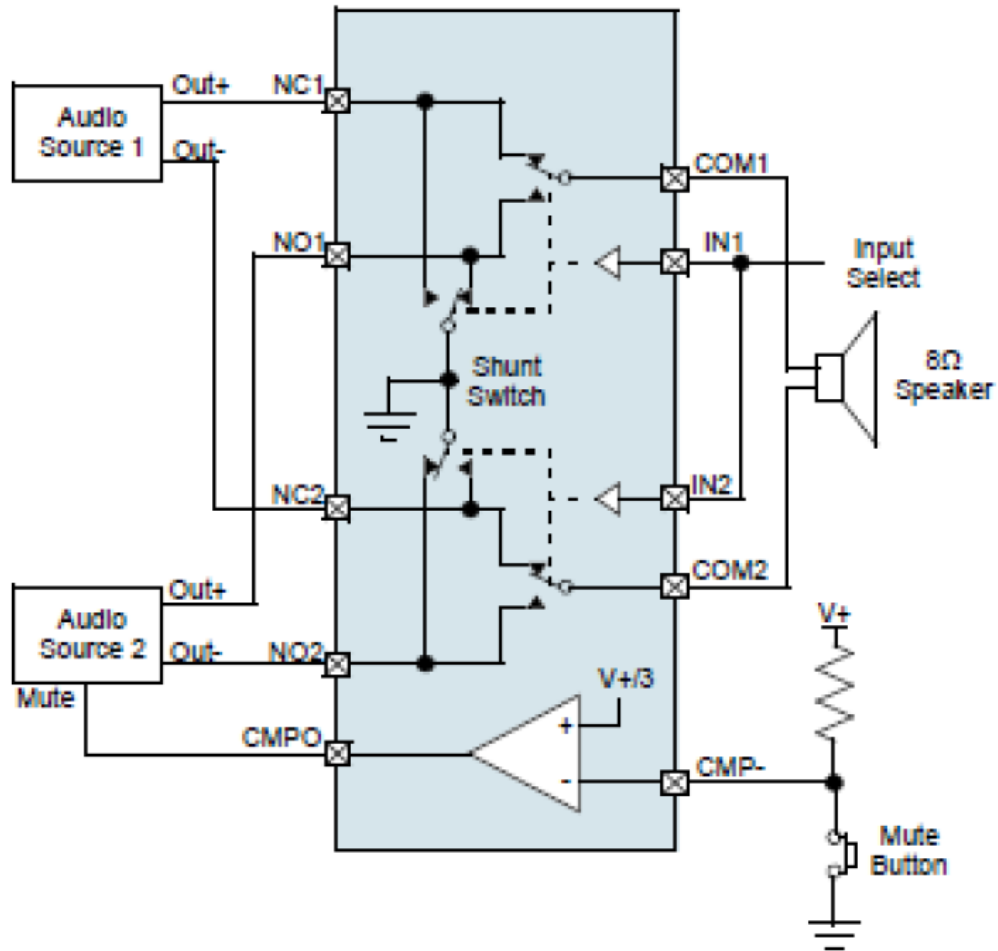


Figure 1: A typical Operating Circuit

4 Results of the comparator

The results of the comparator threshold are presented in Fig. 2 and Fig. 3. It is easy to see that the threshold is very stable at $V_{DD}/3$ for both supplies 3V and 5V over the whole temperature range.

The difference in switching for the rising and falling signal on the negative terminal is about 30 mV, and provides more stability.

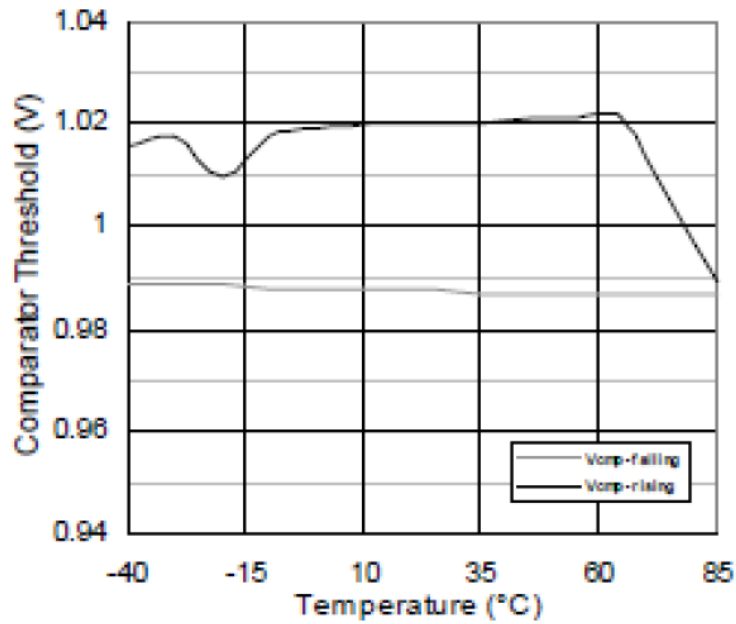


Figure 2: Comparator Threshold vs. Temp., VDD = 3V

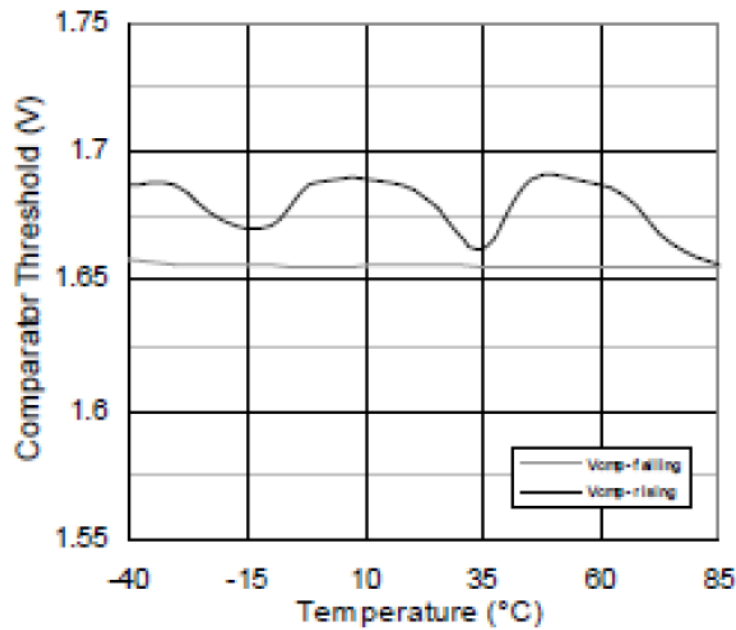


Figure 3: Comparator Threshold vs. Temp., VDD = 5V

5 Contact Information

Buy our products or get free samples online at:

www.ams.com/ICdirect

Technical Support is available at:

www.ams.com/Technical-Support

Provide feedback about this document at:

www.ams.com/Document-Feedback

For further information and requests, e-mail us at:

ams_sales@ams.com

For sales offices, distributors and representatives, please visit:

www.ams.com/contact

Headquarters

ams AG

Tobelbaderstrasse 30

8141 Unterpremstaetten

Austria, Europe

Tel: +43 (0) 3136 500 0

Website: www.ams.com

6 Copyrights & Disclaimer

Copyright ams AG, Tobelbader Strasse 30, 8141 Unterpremstaetten, Austria-Europe. Trademarks Registered. All rights reserved. The material herein may not be reproduced, adapted, merged, translated, stored, or used without the prior written consent of the copyright owner.

Information in this document is believed to be accurate and reliable. However, ams AG does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

Applications that are described herein are for illustrative purposes only. ams AG makes no representation or warranty that such applications will be appropriate for the specified use without further testing or modification. ams AG takes no responsibility for the design, operation and testing of the applications and end-products as well as assistance with the applications or end-product designs when using ams AG products. ams AG is not liable for the suitability and fit of ams AG products in applications and end-products planned.

ams AG shall not be liable to recipient or any third party for any damages, including but not limited to personal injury, property damage, loss of profits, loss of use, interruption of business or indirect, special, incidental or consequential damages, of any kind, in connection with or arising out of the furnishing, performance or use of the technical data or applications described herein. No obligation or liability to recipient or any third party shall arise or flow out of ams AG rendering of technical or other services.

ams AG reserves the right to change information in this document at any time and without notice.

7 Revision Information

Changes from 0.1 to current revision 0-10 (2014-Jul-18)	Page
Content updated to latest ams design	

Note: Page numbers for the previous version may differ from page numbers in the current revision.