

**Circuits
from the Lab™**
Reference Circuits

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0302.

Devices Connected/Referenced

ADF4159	13 GHz Fractional-N Frequency Synthesizer
AD8065	High Performance 145 MHz <i>FastFET™</i> Op amp

Ultra-Fast Settling PLL with RF to 13 GHz

EVALUATION AND DESIGN SUPPORT

Design and Integration Files

[Schematics, Layout Files, Bill of Materials,](#)
[ADIsimPLL Simulation File](#)

CIRCUIT FUNCTION AND BENEFITS

The PLL circuit shown in Figure 1 uses a 13 GHz Fractional-N synthesizer, wideband active loop filter and VCO, and has a phase settling time of less than 5 μ s to within 5° for a 200 MHz frequency jump.

The performance is achieved using an active loop filter with 2.4 MHz bandwidth. This wide bandwidth loop filter is achievable because of the [ADF4159](#) phase-frequency detector (PFD) maximum frequency of 110 MHz; and the [AD8065](#) op amp high gain-bandwidth product of 145 MHz.

The [AD8065](#) op amp used in the active filter can operate on a 24 V supply voltage that allows control of most wideband VCOs having tuning voltages from 0 V to 18 V.

 


Figure 1. Block Diagram of [ADF4159](#), [AD8065](#) Active Loop Filter, and 11.4 GHz to 12.8 GHz VCO.
(Simplified Schematic: All Connections and Decoupling Not Shown)

11903-001

Rev. 0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

CIRCUIT DESCRIPTION

In a PLL and VCO frequency synthesis system, achieving less than 5 μ s frequency and phase settling time requires a very wide loop bandwidth. The loop bandwidth (LBW) defines the speed of the control loop. A wider LBW allows for faster settling time, at the expense of less attenuation of phase noise and spurious signals.

The circuit in Figure 1 operates by locking the **ADF4159** to the RF_{OUT/2} signal (~6 GHz) of the 12 GHz VCO (MACOM MAOC-009269). However, VCOs up to 24 GHz that have a RF_{OUT/2} signal can be used with the **ADF4159**, since it accepts RF inputs up to 13 GHz.

ADF4159 Fractional-N Synthesizer

In a Fractional-N architecture PLL, the noise from the sigma-delta modulator (SDM) peaks at half the PFD frequency (f_{PFD}). For example, if a Fractional-N PLL has a PFD frequency of 32 MHz, then the unfiltered SDM noise peaks at 16 MHz. The SDM noise will make the loop unstable, and the PLL will not lock. Figure 2 shows a simulated phase noise plot of this condition.

 


Figure 2. Phase Noise Plot at 12 GHz Output with $f_{PFD} = 32$ MHz and $LBW = 2.4$ MHz

The **ADF4159** has a maximum PFD frequency of 110 MHz. This means that the unfiltered SDM noise peaks at 55 MHz. Figure 3 shows a phase noise plot with a PFD frequency of 110 MHz. The SDM noise occurs at a large offset from the carrier and is therefore filtered by the loop filter.

 


Figure 3. Phase Noise Plot at 12 GHz Output with $f_{PFD} = 110$ MHz and $LBW = 2.4$ MHz

The **ADF4159** high maximum PFD frequency is also important because it is recommended to keep the LBW less than 1/10 of the PFD frequency to ensure stability.

The **ADF4159** has a maximum RF input frequency of 13 GHz. In the configuration of this circuit, the **ADF4159** is actually being driven with the VCO RF_{OUT/2} signal. This means that when the VCO primary output is 12 GHz, the **ADF4159** is actually locking to 6 GHz.

This configuration means a 24 GHz VCO can be used so that the RF_{OUT/2} signal, of 12 GHz, is fed back to the **ADF4159**. The evaluation board has a footprint capable of supporting a variety of 32-lead 5 mm × 5 mm LFCSP VCOs.

The supply voltage for the **ADF4159** internal charge pump is 3.3 V. However, many wide-band VCOs require a tuning voltage of up to 18 V. To handle this, an active loop filter is required. The active filter multiplies the output tuning range of the **ADF4159** by the gain of the op amp. For more detail, see the **AD8065** section of this circuit note.

The **ADF4159** supports a programmable charge pump current feature. This feature allows the user to easily modify the loop filter dynamic without changing the physical components. In this circuit, the LBW was designed for 2.4 MHz at a charge pump current of 2.5 mA. The charge pump current can be reduced in order to reduce the LBW without physically changing the loop filter components.

The **ADIsimPLL** simulation for the circuit can be found at the **CN0302 Design Support Package** located at (<http://www.analog.com/CN0302-DesignSupport>).

Active Filter Using the AD8065

The AD8065 op amp has a 24 V supply voltage range, a gain bandwidth product (GBP) of approximately 145 MHz, and low noise ($7 \text{ nV}/\sqrt{\text{Hz}}$). These features make it ideal for an active filter.

For most PLL applications, a phase margin of 45° to 55° is recommended to maintain a stable loop and to minimize settling time. In an active loop filter, i.e. when there is an op amp in a loop filter, an additional pole occurs at the unity gain frequency (or gain bandwidth product) of the op amp. This additional pole adds extra phase lag, so, depending on the frequency of the pole, it can render the loop unstable.

Table 1. Phase Lag as a Function of GBP:LBW Ratio

GBP/LBW Ratio	Extra Phase Lag ($^\circ$)
5 (e.g. GBW = 1 MHz, LBW = 200 kHz)	11.3
10	5.7
20	2.9

The higher the ratio of GBP to LBW, the less phase lag. For example, Table 1 shows that a GBP/LBW ratio of 10 will reduce the phase margin by 5.7° . If the GBP/LBW ratio is too low, the phase margin will also become too low and result in an unstable loop.

This circuit uses a 2.4 MHz LBW, so the AD8065 145 MHz GBP results in negligible phase lag (GBP/LBW = 60).

Comparison with OP184 Active Filter

The OP184 is a frequently used op amp in active filter PLL applications. However, the OP184 is not suitable for very wide LBW applications due to its 4 MHz GBP. Some optimization of the phase margin will allow the use of the OP184 at wide LBWs, but ultimately, the OP184 will limit the maximum LBW.

The op amp in the active filter is configured in the inverting mode, therefore the ADF4159 is programmed with a negative phase-detector polarity. The inverting configuration is easier to implement because the op amp positive input can be biased at a fixed voltage that does not change with the op amp output (as it would in the non-inverting configuration).

The AD8065 also acts as a buffer to mitigate the input capacitance of the VCO. For a 2.4 MHz LBW passive filter, the combined capacitance of the VCO input and the last capacitor in the filter must be approximately 1.5 pF. However, the VCO measured input capacitance alone is 52 pF.

Ceramic C0G/NP0 capacitors (which discharge quicker than standard capacitors) are recommended for the loop filter capacitors to minimize phase settling time.

Excellent layout, grounding, and decoupling techniques are required for the circuit as described in Tutorials MT-031 and MT-101. A complete schematic, layout files, and bill of materials can be found in the CN-0302 Design Support Package (www.analog.com/CN0302-DesignSupport).

Test Results

The measured phase noise of the circuit is shown in Figure 4. Frequency and phase settling time for a 200 MHz jump in frequency are shown in Figure 5 and Figure 6, respectively.

 


Figure 4. Phase Noise at 12.002 GHz; LBW = 2.4 MHz

 


Figure 5. Frequency Settling for a 200 MHz Jump from 12.2 GHz to 12.0 GHz

 


Figure 6. Phase Settling for a 200 MHz Jump from 12.2 GHz to 12.0 GHz

CIRCUIT EVALUATION AND TEST

PC Board Modifications for 2.4 MHz Active Filter

The following modifications to the standard [EV-ADF4159EB1Z](#) are required to implement the 2.4 MHz active filter using the [AD8065](#) rather than the [OP184](#):

- Replace U4 with AD8065ARZ (8-lead, SOIC)
- Replace R1 with 220 Ω , 1%, 0603
- Replace R2 with 3 k Ω , 1%, 0603
- Replace R3 with 120 Ω , 1%, 0603
- Replace C1 with 12 pF, 10%, 0603
- Replace C2 with 82 pF, 10%, 0603
- Replace C3 with 2.7 pF, 5%, 0603
- C4 is not changed and remains 180 pF

Equipment Required

- [EV-ADF4159EB1Z](#) evaluation board modified for [AD8065](#) op amp and 2.4 MHz LBW filter components
- [ADF4159](#) evaluation software
- Windows® PC with USB port
- +15 V power supply
- +5.5 V power supply
- Spectrum Analyzer: R&S: FSUP26, FSQ26, FSW26, Agilent E5052B or equivalent.

Functional Block Diagram of Test Setup

A functional diagram of the test setup is shown in Figure 7, and a photo of the setup is shown in Figure 8. Refer to [User Guide UG-383](#) for details on running the tests and setting up the software.

 


Figure 7. Functional Block Diagram of Test Setup

11903-007



Figure 8. Photo of EV-ADF4159EB1Z Board and Test Setup Showing External Connections

Learn More

CN-0302 Design Support Package:
<http://www.analog.com/CN0302-DesignSupport>

ADIsimPLL Design Tool

AN-30 Application Note, Ask the Application Engineer—PLL
Synthesizers, Analog Devices

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”*, Analog Devices.

MT-086 Tutorial, *Fundamentals of Phase Locked Loops (PLLs)*,
Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

UG-383: Evaluating the ADF4159 Frequency Synthesizer for
Phase-Locked Loops

Data Sheets and Evaluation Boards

ADF4159 Data Sheet and Evaluation Board
AD8065 Data Sheet

REVISION HISTORY

10/13—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.