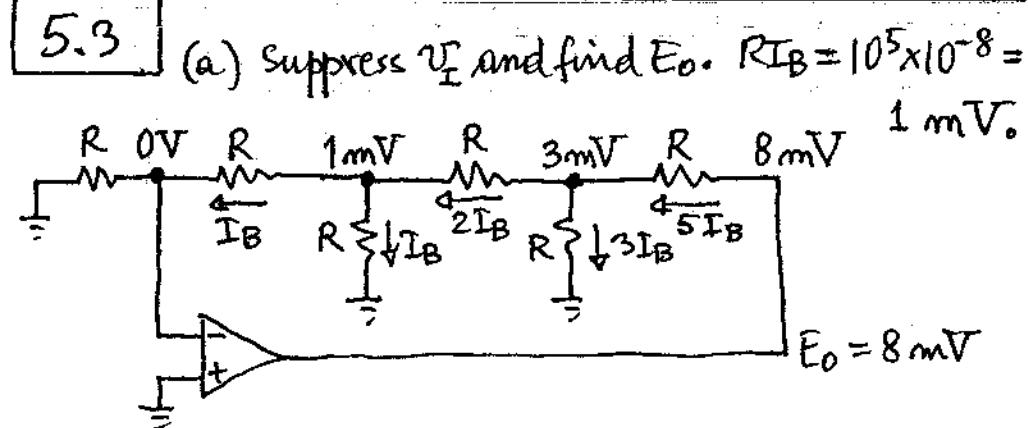



**5.1** By Eq. (5.7), doubling  $I_A$  will double  $g_{m1}$ , thus increasing the open-loop gain  $a$ . This will also double the input bias currents  $I_p$  &  $I_N$ , and halve the input resistance  $r_d$  and the first-stage output resistance  $r_{o1}$ . The reduction in  $r_{o1}$  will affect loading of the first stage by the second stage, thus affecting  $a$ . Furthermore, the first-stage output-current saturation levels will also double; in Ch. 6 we'll see that this doubles the slew rate.

**5.2**  $R_2 = 10R_1$ . With  $R_p = R_1//R_2 = 0.91R_1$  in place,  $E_{o(\max)} = (1+R_2/R_1)(R_1//R_2)I_{os(\max)} = 11 \times 0.91R_1 \times 200 \times 10^{-9} = 10 \times 10^{-3}$ . This yields  $R_1 = 5\text{k}\Omega$ . Use  $R_1 = 4.99\text{k}\Omega$ ,  $R_2 = 49.9\text{k}\Omega$ , and  $R_p = 45.3\text{k}\Omega$ , all 1%.



(b) We readily find the noise gain to be  $1/3 = 13 \text{ V/V}$ . We thus need  $R_p I_B = (8 \text{ mV})/13 \Rightarrow R_p = 61.5 \text{ k}\Omega$  (Use  $62 \text{ k}\Omega$ ).

5.4

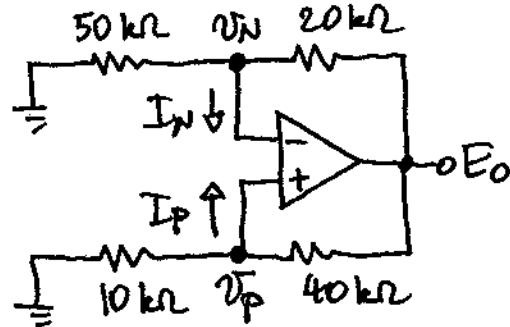


$$V_N = V_P; \frac{V_O - V_N}{20 \text{ k}\Omega} = I_N + \frac{V_N}{50 \text{ k}\Omega}; \frac{V_O - V_P}{40 \text{ k}\Omega} = I_P + \frac{V_P}{10 \text{ k}\Omega}$$

$$\Rightarrow V_O = \frac{250 \times 10^3 I_N - 140 \times 10^3 I_P}{9}$$

With  $I_P = 105 \text{ mA}$  and  $I_N = 95 \text{ mA}$  we get  $V_O = 1.005 \text{ mV}$ ; with  $I_P = 95 \text{ mA}$  and  $I_N = 105 \text{ mA}$  we get  $V_O = 1.438 \text{ mV}$ . We thus expect  $V_O$  within the range of  $1.005 \text{ mV}$  to  $1.438 \text{ mV}$ . With  $I_{OS} = 0$ ,  $V_O = 1.2 \text{ mV}$ .

5.5

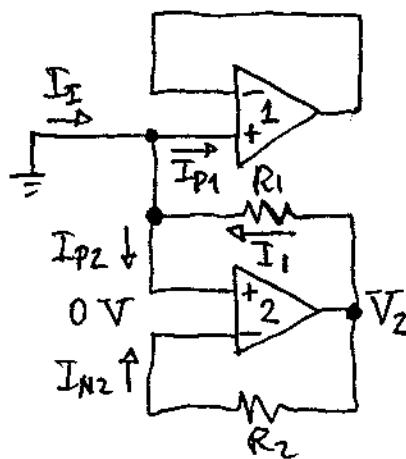

$$I_I = I_{P1} + I_{P2} - I_1 \\ = I_{P1} + I_{P2} - V_2 / R_1 \\ = I_{P1} + I_{P2} - R_2 I_{N2} / R_1.$$

(a) For matched op amps,


$$I_I = 2I_P - (R_2/R_1) I_N \\ = (2 - R_2/R_1) I_B \\ \Rightarrow R_2 = 2R_1.$$

(b) Assume  $I_{P1} = I_B$ ,  $I_{P2} = I_{N2} = I_B (1 \pm 0.01)$ .

Then  $I_I = I_B + I_B (1 \pm 0.01) - 2I_B (1 \pm 0.01) = \mp 0.01 I_B$ , indicating an input current on the order of the mismatch itself.

5.3

5.6 (a)

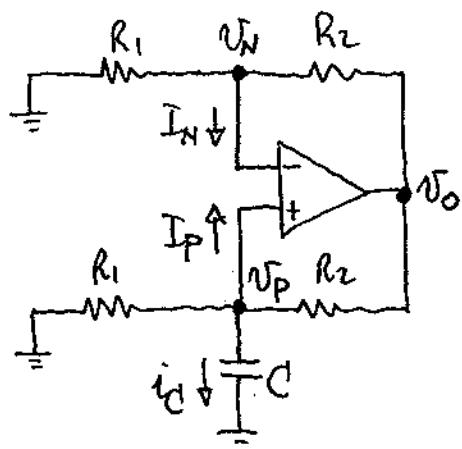

$$\frac{v_O - v_N}{R_2} = I_N + \frac{v_N}{R_1}$$

$$\frac{v_O - v_P}{R_2} = I_P + i_C + \frac{v_P}{R_1}$$

$v_N = v_P$ . Combining,

$$i_C = I_N - I_P = -I_{OS}$$

regardless of the resistance values. Consequently,


$$v_O(t) = \left(1 + \frac{R_2}{R_1}\right) v_P = -\left(1 + \frac{R_2}{R_1}\right) \frac{I_{OS}}{C} t + v_O(0).$$

$$(b) v_O(t) = \mp 2 \times \frac{10^{-9}}{10^{-9}} t + 1 = \mp 2t + 1 \text{ V.}$$

Dependence on whether  $I_{OS} > 0$  or  $I_{OS} < 0$ .  $v_O$  will

5.4

5.8

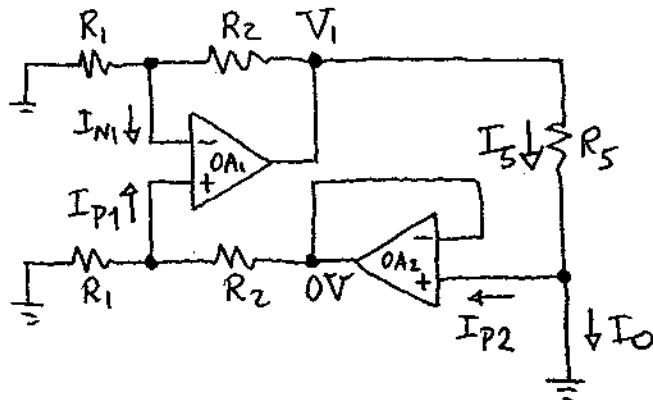

The presence of the bias and offset currents does not affect the resistances, so we expect  $i_o = A(V_2 - V_1) - V_L/R_o + I_o$ ,  $A = R_2/R_1R_5$ ,  $R_o = \infty$ .


To find the error  $I_o$ , consider the case of a short-circuit load for simplicity. Then,

$$V_1 = R_2 I_{N1} + (1 + R_2/R_1) [-(R_1//R_2) I_{P1}] = -R_2 I_{OS1}.$$

$$I_o = I_{S1} - I_{P2} = V_1/R_5 - I_{P2} = -(R_2/R_5) I_{OS1} - I_{P2}.$$

Writing  $I_o = A \times [-(R_1 I_{OS1} + R_1 I_{P2} R_5/R_2)]$  indicates the presence of an equivalent input voltage error  $E_I = -R_1 [I_{OS1} + (R_5/R_2) I_{OS2}]$ .

To make the second term proportional to

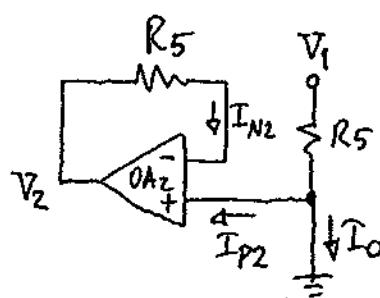

$I_{OS2}$  rather than  $I_{OS2}$ , install a dummy feedback resistance  $R_5$ , as shown.


$$\text{Then, } V_1 = -R_2 I_{OS1} + R_5 I_{N2}$$

$$I_o = \frac{-R_2 I_{OS1} + R_5 I_{N2}}{R_5} - I_{P2} = -\frac{R_2}{R_5} I_{OS1} - I_{OS2}$$

$$E_I = -R_1 [I_{OS1} + (R_2/R_5) I_{OS2}].$$

5.5

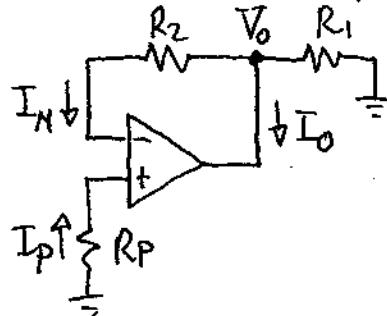**5.9** Since  $I_B$  and  $I_{OS}$  do not affect the resistances, we expect  $i_o = A i_I - V_L / R_o + I_O$ ,  $A = 1 + R_2 / R_1$ ,  $R_o = \infty$ . To find  $I_O$ , consider a short-circuited load for simplicity.




$$\frac{0 - V_o}{R_1} = I_N + I_O \Rightarrow I_O = -\left(\frac{V_o}{R_1} + I_N\right)$$

$$V_o = V_N + R_2 I_N = V_p + R_2 I_N = -R_p I_p + R_2 I_N.$$

Eliminating  $V_o$  gives

$I_O = \frac{R_p}{R_1} I_p - \left(1 + \frac{R_2}{R_1}\right) I_N$ . With  $R_p = 0$  we get  $I_O \approx -\left(1 + R_2 / R_1\right) I_B$ , indicating an equivalent input error  $I_I = -I_B$ . Installing a dummy resistance  $R_p = R_1 + R_2$  gives  $I_O = (1 + R_2 / R_1) I_{OS}$ , for an equivalent input error  $I_I = I_{OS}$ .

5.10

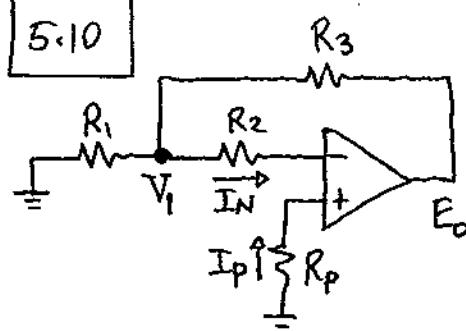

At dc caps = open ckt.

$$\frac{E_0 - V_1}{R_3} + \frac{0 - V_1}{R_1} = I_N \Rightarrow$$

$$E_0 = \left(1 + \frac{R_3}{R_1}\right) V_1 + R_3 I_N$$

$$V_1 = R_2 I_N + V_N = R_2 I_N - R_p I_p$$


$$\text{Eliminating } V_1, E_0 = \left(1 + \frac{R_3}{R_1}\right) \left[ (R_2 + R_1 // R_3) I_N - R_p I_p \right].$$

Without  $R_p$ ,  $E_0 \approx (1 + R_3 / R_1) (R_2 + R_1 // R_3) I_B = 2 \times 150 \times 10^3 \times 50 \times 10^{-9} = 15 \text{ mV}$ . Installing a dummy resistance  $R_p = R_2 + R_1 // R_3 = 150 \text{ k}\Omega$  gives  $E_0 = -\left(1 + \frac{R_3}{R_1}\right) (R_2 + R_1 // R_3) I_{OS} = -300 \times 10^3 I_{OS}$ .

5.6

5.11

$$(a) I_B = C |dV_0/dt| = 10^{-8} \times 10^{-3} / 1 = 10 \text{ pA} \Rightarrow \text{FET-input op.amp.}$$

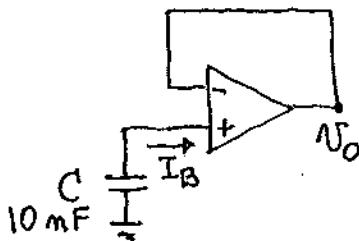


(b) To increase  $I_B$  by a factor of 100 we need

$$100 = 2^{\Delta T/10} \Rightarrow \Delta T = 66.4^\circ\text{C.}$$

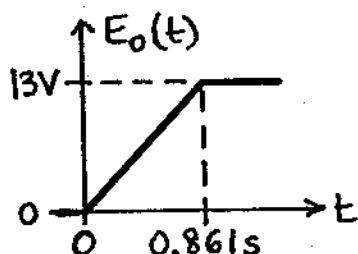5.12

$$V_{os} = E_0 / (1 + R_2/R_1) = 0.5 / (1 + 33/0.1) =$$




1.51 mV.

$$E_0(t) = \frac{1}{RC} V_{os} t =$$

$$\frac{1}{10^5 \times 10^{-9}} \times 1.51 \times 10^{-3} t = 15.1 t.$$

The output saturates at  $t = 13/15.1 = 0.861\text{s}$ .

5.13

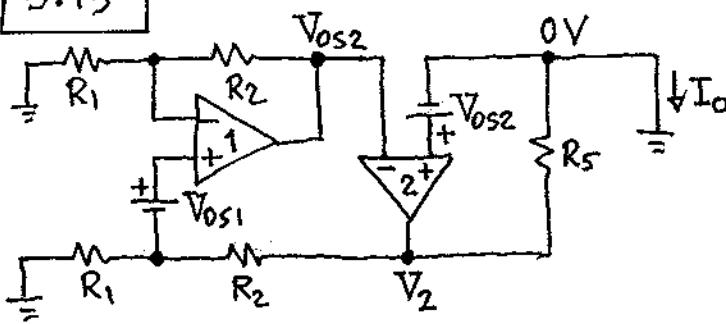

The presence of  $V_{os1}$  and  $V_{os2}$  does not affect the resistances of

the circuit, so we expect  $i_o = A V_I - V_L / R_o + I_o$ ,  $A = R_2/R_1 R_5$ ,  $R_o = \infty$ . To find  $I_o$ , consider a short-circuit load for simplicity.  $I_o = V_2 / R_5$ ; moreover,  $V_{N1} = [R_1/(R_1+R_2)] V_{os2} = V_{P1} = [R_1/(R_1+R_2)] V_2 + V_{os1}$ .


This gives  $I_o = \left(\frac{1}{R_5}\right) \left[ V_{os2} - \left(1 + \frac{R_2}{R_1}\right) V_{os1} \right]$ , indicating an equivalent input error  $I_I = \frac{R_1 R_5}{R_2} I_o = \frac{R_1}{R_2} V_{os2} - \left(1 + \frac{R_1}{R_2}\right) V_{os1}$ .

5.1

**5.14** (a)  $E_0 \equiv (1 + 10^5/10)V_{OS} = 10^4 V_{OS}$ ;  $|E_0(0^\circ C)| \approx 10^4 (5 \times 10^{-6} \times 25) = 1.25 \text{ V}$ ;  $|E_0(25^\circ C)| \approx 10^4 (5 \times 10^{-6}) \times (70 - 25) = 2.25 \text{ V}$ ; opposite polarities.

(b)  $V_0(t) = \pm (V_{OS}/RC)t + V_0(0) = \pm [5 \times 10^{-6} \times 25 / (10^5 \times 10^{-9})]t + V_0(0) = \pm 1.25t + V_0(0)$ ;  $v_0(t) = \mp 2.25t + V_0(0)$ .

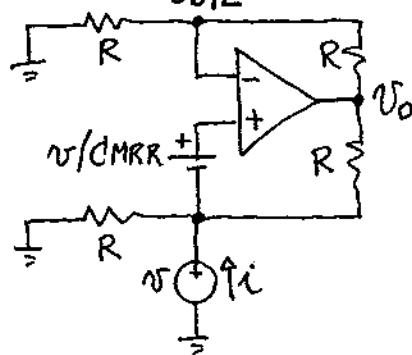**5.15**  $V_{OS}/2$  CMRR<sub>dB</sub> = 100 dB  $\Rightarrow 1/\text{CMRR} = 10^{-5} \text{ V/V}$ .




$$\frac{V_0}{2} = V + \frac{V}{\text{CMRR}} = \frac{1 + \text{CMRR}}{\text{CMRR}} V$$

$$i = \frac{V}{R} + \frac{V - V_0}{R} = -\frac{2V/R}{\text{CMRR}}$$

$$R_o = V/i = -\frac{R}{2} \text{ CMRR} = -500 \text{ M}\Omega$$

The output resistance is

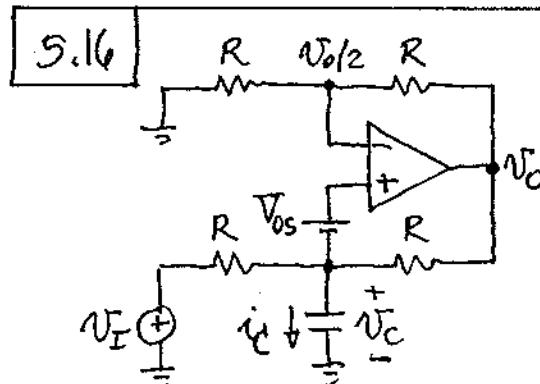negative (or positive), depending on whether  $V_{OS}$  increases (or decreases) with  $V_{CM}$ .



$$V_0 = \left(1 + \frac{R}{R}\right)(V_d + V_{OS})$$


$$= 2(V_d + V_{OS})$$

$$i_C = \frac{V_I - V_d}{R} + \frac{V_0 - V_d}{R}$$

$$= V_I/R + 2V_{OS}/R.$$

Letting  $V_{OS} = V_{OS0} + \frac{V_d}{\text{CMRR}}$  gives  $i_C = \frac{V_I}{R} + \frac{2V_{OS0}}{R} - \frac{V_d}{\text{CMRR} \times R/2}$ .

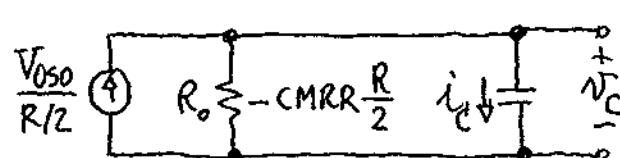For  $V_d = 0$ , it's the Norton equivalent:



$$V_{OS0}/(R/2) = 2 \text{ mA}$$

$$|R_o| = 5 \text{ G}\Omega$$


5.8

Assuming C is initially discharged, we have two cases:

1.  $V_{OS}$  decreases with  $V_{CM}$ ; then  $R_o = +5 \text{ G}\Omega$ ,  $\infty = R_o C = +5s$ ,  $V_d(\infty) = 10 \text{ V}$ ;  $V_d(t) = 10(1 - e^{-t/5}) \text{ V}$ ;  $V_o = 2(V_C + V_{OS})$ . These expressions hold only as long as the op amp is within the linear region.

2.  $V_{OS}$  increases with  $V_{CM}$ ; then  $R_o = -5 \text{ G}\Omega$ ,  $\infty = -5s$ ,  $V_d(t) = 10(e^{+t/5} - 1) \text{ V}$ ,  $V_o = 2(V_C + V_{OS})$ .

5.17

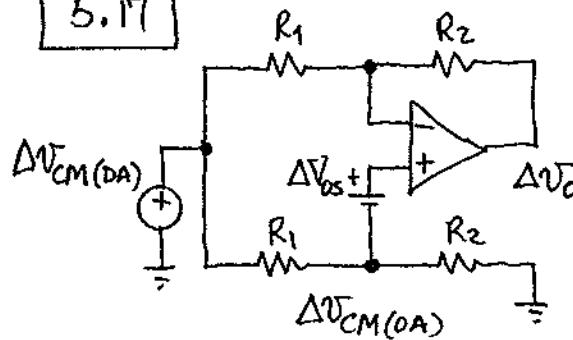

$$A_{dm} = R_2 / R_1$$

$$\Delta V_{CM(DA)} = \frac{R_2}{R_1 + R_2} \Delta V_{CM(DA)}$$

$$\Delta V_{OS} = \frac{\Delta V_{CM(DA)}}{CMRR_{OA}}$$

$$\Delta V_o = \left(1 + \frac{R_2}{R_1}\right) \Delta V_{OS} = \left(1 + \frac{R_2}{R_1}\right) \frac{R_2}{R_1 + R_2} \frac{\Delta V_{CM(DA)}}{CMRR_{OA}}$$

$$A_{cm} = \frac{\Delta V_o}{\Delta V_{CM(DA)}} = \frac{R_2}{R_1} \frac{1}{CMRR_{OA}} = A_{dm} \frac{1}{CMRR_{OA}}$$

$$CMRR_{DA} \cong A_{dm} / A_{cm} = CMRR_{OA} .$$

5.18

$$(a) CMRR_{DA(min)} = CMRR_{OA(min)} = 70 \text{ dB.}$$

(b) Applying  $\Delta V_{CM(DA)} = 1 \text{ V}$  yields

$$|\Delta V_{o1}|_{max} = A_{dm} \frac{1 \text{ V}}{CMRR_{OA(min)}} = \frac{100 \times 1}{10^{70/20}} = 31.6 \text{ mV}$$

due to the op amp finite CMRR. Moreover, by

Eq. (2.24c), bridge imbalance yields


$$|\Delta V_{o2}|_{max} = \frac{R_2}{R_1 + R_2} |\epsilon|_{max} \times (1 \text{ V}) = \frac{100}{1+100} 0.04 \times 1 =$$

39.6 mV. The worst-case scenario occurs when

5.9

the output terms are maximized and combine additively to give  $|\Delta V_o|_{\max} = 31.6 + 39.6 = 71.2 \text{ mV}$ . Then,  $|A_{cm}|_{\max} = |\Delta V_o|_{\max} / \Delta V_{CM(DA)} = 0.0712 / 1 = 0.0712 \text{ V/V}$ , and  $CMRR_{\text{net(max)}} = 20 \log_{10} \frac{100}{0.0712} = 63 \text{ dB}$ . In the present circuit, a 1% resistance tolerance can degrade the CMRR due to the basic opamp by as much as 7 dB.

**5.19** Assuming perfectly matched resistances, we have, by Prob. 5.17,  $CMRR_{DA} = CMRR_{741} = 90 \text{ dB}$  at 1 Hz, 76 dB at 1 kHz, and 66 dB at 10 kHz. The corresponding peak variations of  $V_o$ s are, respectively,  $(1 \text{ V}) / 10^{90/20} = 31.6 \mu\text{V}$ ,  $158 \mu\text{V}$ , and  $501 \mu\text{V}$ . Multiplying by the noise gain, which is 101 VN, gives respectively,  $v_o \cong 3.2 \times \sin 2\pi t \text{ mV}$ ,  $16 \sin 2\pi 10^3 t \text{ mV}$ ,  $50.6 \sin 2\pi 10^4 t \text{ mV}$ .

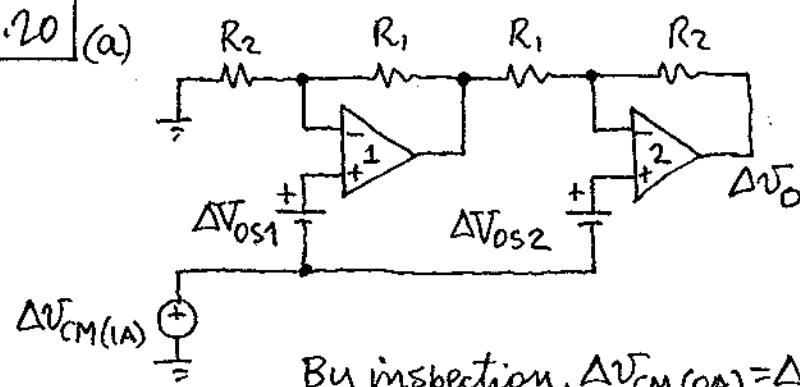**5.20 (a)**

$$\text{By inspection, } \Delta V_{CM(DA)} = \Delta V_{CM(1A)}$$

$$\Delta V_{OS1} \cong \Delta V_{OS2} = \frac{\Delta V_{CM(1A)}}{CMRR_{DA}} ; \Delta V_o = A_{\text{adm}} (\Delta V_{OS2} - \Delta V_{OS1})$$

The worst-case scenario occurs when the two terms combine additively to give

5.10


$$|\Delta V_o|_{\max} = A_{\text{dm}} \times 2 |\Delta V_{\text{os}}|_{\max} = 2 A_{\text{dm}} \Delta V_{\text{CM(IA)}} / (\text{CMRR}_{\text{OA(min)}}) \Rightarrow$$

$$A_{\text{cm(max)}} = |\Delta V_o|_{\max} / \Delta V_{\text{CM(IA)}} = 2 A_{\text{dm}} / (\text{CMRR}_{\text{OA(min)}}) \Rightarrow$$

$$(\text{CMRR}_{\text{IA(min)}}) \triangleq \frac{A_{\text{dm}}}{A_{\text{cm(max)}}} = \frac{1}{2} (\text{CMRR}_{\text{OA(min)}}).$$

$$(b) \Delta V_o(\max) = 100 \times 2 \times \frac{10 \text{ V}}{10^{114/120}} \approx 4 \text{ mV.}$$

5.21

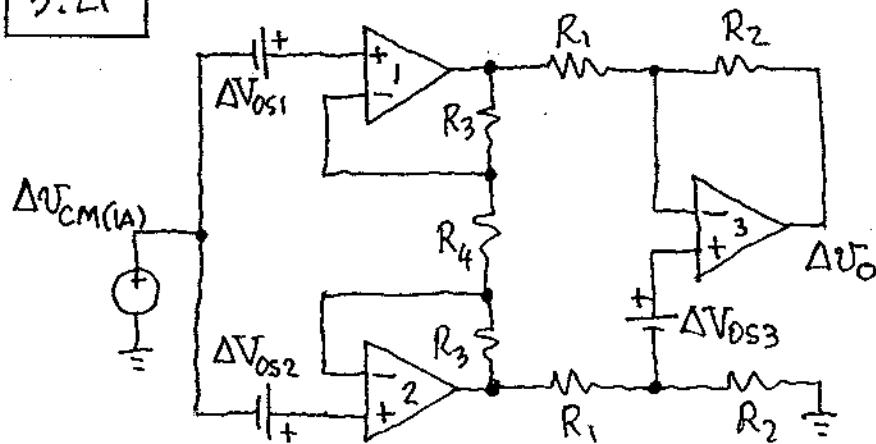

$$\text{CMRR}_{\text{IA}} = \left| \frac{A_{\text{dm}}}{A_{\text{cm}}} \right|; A_{\text{dm}} = A_I \times A_{\text{II}} = \left( 1 + \frac{2R_3}{R_4} \right) \times \left( \frac{R_2}{R_1} \right).$$

By inspection,  $\Delta V_{\text{CM(OA}_1)} = \Delta V_{\text{CM(OA}_2)} = \Delta V_{\text{CM(II)}} = \Delta V_{\text{CM(IA)}}.$

By Problem 5.17,  $\text{CMRR}_{\text{II}} = \text{CMRR}_{\text{OA}_3}$ , so the contribution of  $\text{OA}_3$  to the output is

$$\Delta V_o(\text{II}) = A_{\text{cm(II)}} \Delta V_{\text{CM(II)}} = A_{\text{II}} \Delta V_{\text{CM(IA)}} / (\text{CMRR}_{\text{OA}_3}).$$

The first-stage contribution to the output is

$$\begin{aligned} \Delta V_o(\pm) &= A_I A_{\text{II}} (\Delta V_{\text{os2}} - \Delta V_{\text{os1}}) \\ &= A_I A_{\text{II}} \left( \Delta V_{\text{CM(IA)}} / (\text{CMRR}_{\text{OA}_1}) - \Delta V_{\text{CM(IA)}} / (\text{CMRR}_{\text{OA}_2}) \right). \end{aligned}$$

The worst-case scenario occurs when the contributions are maximized and combine additively:

$$\begin{aligned} |\Delta V_o|_{\max} &= |\Delta V_o(\pm)|_{\max} + |\Delta V_o(\text{II})|_{\max} \\ &= \Delta V_{\text{CM(IA)}} \left[ A_I A_{\text{II}} \left( \frac{1}{\text{CMRR}_{\text{OA}_1(\min)}} + \frac{1}{\text{CMRR}_{\text{OA}_2(\min)}} \right) \right] \end{aligned}$$

5.11

$$+ A_{II} \frac{1}{CMRR_{OA_3(\min)}} \Big] = A_{dm} \Delta V_{CM(IA)} \left[ \frac{1}{CMRR_{OA_1(\min)}} + \frac{1}{CMRR_{OA_2(\min)}} + \frac{1}{A_I CMRR_{OA_3(\min)}} \right] \Rightarrow$$

$$A_{cm(max)} = |\Delta V_0|_{max} / \Delta V_{CM(IA)} = A_{dm} \times [\dots]$$


$$\frac{1}{CMRR_{IA(\min)}} = \frac{A_{cm(max)}}{A_{dm}} = \frac{1}{CMRR_{OA_1(\min)}} + \frac{1}{CMRR_{OA_2(\min)}} + \frac{1}{(1+2R_3/R_4) CMRR_{OA_3(\min)}}.$$

For matched op amps this simplifies to

$$CMRR_{IA(\min)} = CMRR_{OA(\min)} / \left[ 2 + \frac{1}{1+2R_3/R_4} \right].$$

For a sufficiently high first-stage gain, the second-stage CMRR limitation can be ignored compared to the first stage's.

5.22

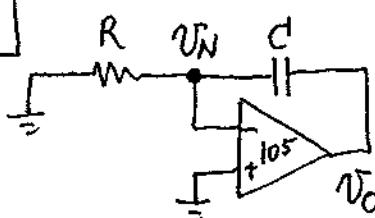

$$V_o(0) = 10 \text{ V};$$


$$\alpha = 10^5 \text{ V/V};$$

$$V_N = -V_o/\alpha.$$

$(0 - V_N)/R = C d(V_N - V_o)/dt$ . Eliminating  $V_N$  and collecting gives  $V_o(t) = -\tau dV_o(t)/dt$ , where  $\tau = (1+\alpha)RC \cong 10^5 \times 10^5 \times 10^{-8} = 100 \text{ s}$ . The solution is  $V_o(t) = 10 e^{-t/(100 \text{ s})} \text{ V}$ , which represents an exponential decay with a 100-s time constant.

5.12

5.23

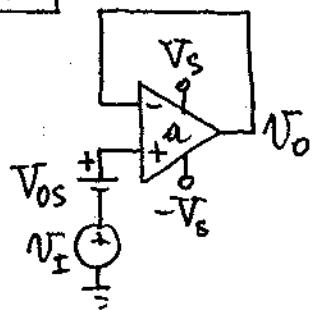

$$V_O = a(V_I + V_{OS} - V_O) \Rightarrow$$

$$V_O = \frac{a}{1+a} (V_I + V_{OS})$$

$$V_O - V_I \approx V_{OS} - V_I/a.$$

Ideally,  $V_O = V_I$ ; max departure of  $V_O$  from  $V_I$  is thus  $\Delta V_O(\max) = -[|V_{OS}|_{\max} + |V_I|/a]$ .

$$(a) V_I = 0 \Rightarrow \Delta V_O(\max) = -V_{OS0} = -3 \text{ mV.}$$

$$(b) V_I = 10 \text{ V} \Rightarrow \Delta V_O(\max) = -(V_{OS0} + 10/10^4 + 10/10^{74/20}) = -(3 + 1 + 2) \text{ mV} = -5 \text{ mV.}$$

$$(c) \Delta V_S = 3 \text{ V} \Rightarrow \Delta V_{OS} = 3/10^{74/20} = 0.6 \text{ mV.}$$

Thus, in (a) we have  $\Delta V_O(\max) = -3.6 \text{ mV}$ , and in (b) we have  $\Delta V_O(\max) = -5.6 \text{ mV}$ .

5.24

(a) By Eq. (5.32), a 10% mismatch between  $A_{E1}$  and  $A_{E2}$  yields a 10% mismatch between  $I_{S1}$  and  $I_{S2}$ . By Eq. (5.30), this gives  $\Delta V_{OS} = V_T \ln 1.01 \approx 0.01 \times 26 \text{ mV} = 0.26 \text{ mV}$ .

(b) A well known rule of thumb states that the voltage drop across a pn junction varies by about  $2 \text{ mV}/^\circ\text{C}$ . We thus anticipate that a  $1^\circ\text{C}$  gradient across  $Q_1$  and  $Q_2$  will yield  $\Delta V_{OS} \gtrsim 2 \text{ mV}$ .

5.13

**5.25** Use  $R_p = R = 100 \text{ k}\Omega$ . Then,  $E_{I(\max)} = 6 \text{ mV} + 100 \times 10^3 \times 200 \times 10^{-9} = 26 \text{ mV}$ . Impose  $-30 \text{ mV} \leq V_X \leq 30 \text{ mV}$  for safety. Use  $R_c = 100 \text{ k}\Omega$ ,  $R_B = 100 \text{ k}\Omega$ ,  $R_A = 200 \text{ }\Omega$ .

**5.26**  $R_1 = R_2 = 0 \Rightarrow E_o = (1 + 10^4/10) V_{os} = 1000 V_{os} \Rightarrow V_{os} = 0.48 \text{ mV}$ .  $R_1 = 1 \text{ M}\Omega$  and  $R_2 = 0 \Rightarrow E_o = 1000 (V_{os} + R_1 I_N)$ . Thus,  $I_N = (0.230/1000 - 0.48 \times 10^{-3})/10^6 = -0.25 \text{ mA}$ , indicating that  $I_N$  flows out of the op amp.  $R_1 = 0$  and  $R_2 = 1 \text{ M}\Omega \Rightarrow E_o = 1000 \times (V_{os} - R_2 I_p) \Rightarrow I_p = -(0.780/1000 - 0.48 \times 10^{-3})/10^6 = -0.3 \text{ mA}$ , flowing out of the op amp. Thus,  $I_B = -(0.25 + 0.3)/2 = 0.275 \text{ mA}$ , out of op amp;  $I_{os} = -50 \text{ pA}$ .

**5.27** At dc, the output  $V_o$  of DUT is such that  $(V_o - 0)/10^5 = (0 - V_1)/10^5$ , or  $V_o = -V_1$ . The inputs are, respectively,  $V_N = -R_n I_N$  and  $V_p = [100/(100 + 49,900)] V_2 - R_p I_p$ , where  $R_n$  and  $R_p$  are the dc resistances presented at DUT's inputs. Imposing  $V_N = V_p + V_{oso} - V_o/a$  gives  $V_2 = 500 [R_p I_p - R_n I_N - V_{oso} - \frac{V_1}{a}] \quad \text{Eq.(1)}$

(a) With  $SW_1 = SW_2 = \text{closed}$  we have  $R_p =$

5.14


$R_m = 100 \Omega \approx 0 \Omega$ . With  $V_1 = 0$ , Eq. (1) reduces to  $V_2 = 500(-V_{OS})$ ; imposing  $-0.75 = 500(-V_{OS})$  gives  $V_{OS} = 1.5 \text{ mV}$ .

(b) We now have  $R_p = 10^5 \Omega$ , and Eq. (1) becomes  $V_2 = 500(R_p I_p - V_{OS})$ , or  $0.30 = 500(10^5 I_p - 1.5 \text{ mV})$ , which gives  $I_p = 21 \text{ mA}$ .

(c)  $R_m = 10^5 \Omega$ ,  $V_2 = 500(-R_m I_N - V_{OS})$ ,  $-1.70 = 500(-10^5 I_N - 1.5 \text{ mV})$ ,  $I_N = 19 \text{ mA}$ ;  $I_{OS} = I_p - I_N = 2 \text{ mA}$ .

(d)  $V_2 = [-V_{OS} - (-10)/a]$ ,  $-0.25 = 500 \times [-1.5 \text{ mV} + 10/a] \Rightarrow a = 10^4 \text{ V/V}$ .

5.28

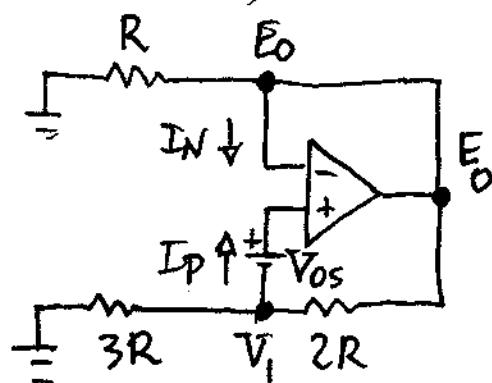(a)  $E_0 = V_1 + V_{OS}$ . Summing currents at node  $V_1$ ,

$$\frac{0-V_1}{3R} = I_p + \frac{V_1-E_0}{2R}$$

Eliminating  $V_1$ ,


$$E_0 = 2.5 V_{OS} - 3R I_p.$$

(b)

$$E_0 = 4R I_N + V_N = 4R I_N + V_P$$

$$= 4R I_N + (-V_{OS} - R I_p)$$


$$= R(4I_N - I_p) - V_{OS}.$$

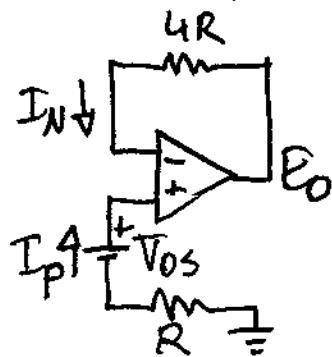

5.15

5.29

(a)

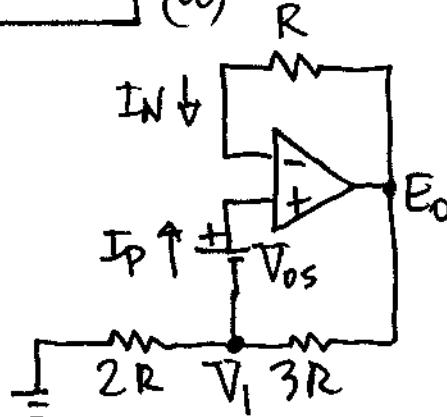

$$E_o = RIN + V_N = RIN + V_{os}$$

$$= RIN + V_{os} + V_1.$$


Summing currents @ V1:

$$\frac{0 - V_1}{2R} = I_p + \frac{V_1 - E_o}{3R}$$

Eliminating V1,

$$E_o = \frac{1}{3} [5V_{os} + R(5IN - 6I_p)].$$

(b)

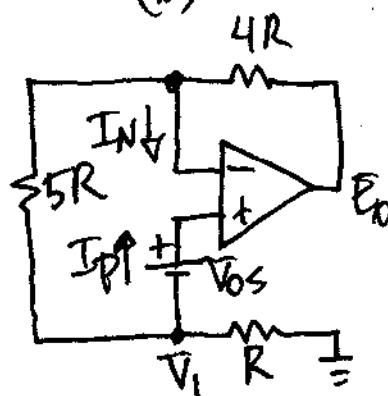

KVL:  $V_N = V_1 + V_{os}$ ; KCL:


$$\frac{E_o - (V_1 + V_{os})}{4R} = \frac{V_{os}}{5R} + IN$$

KCL again:

$$\frac{V_{os}}{5R} = I_p + \frac{V_1}{R}.$$

Eliminating V1:  $E_o = 2V_{os} + R(4IN - I_p)$

5.30

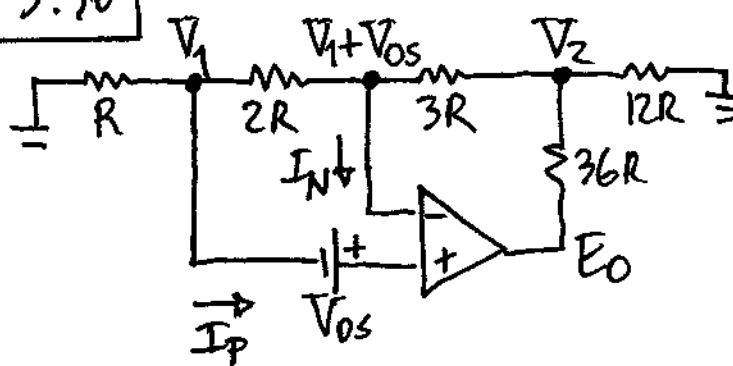

$$KCL @ V_1: \frac{0 - V_1}{R} = I_p + \frac{V_1 - (V_1 + V_{os})}{2R} = I_p - \frac{V_{os}}{2R}$$

$$KCL @ V_N: \frac{V_1 - (V_1 + V_{os})}{2R} = IN + \frac{V_1 + V_{os} - V_2}{3R}$$


5.16

$$\text{KCL at } V_2: \frac{V_1 + V_{OS} - V_2}{3R} = \frac{V_2 - E_0}{36R} + \frac{V_2}{12R}$$

Eliminating  $V_1$  and  $V_2$  gives

$$E_0 = 54V_{OS} + 4R(2I_N - 5I_P).$$

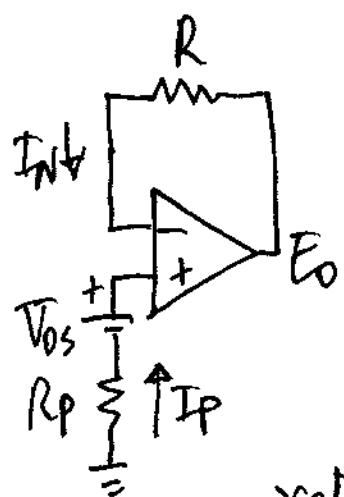**5.31** (a) With  $R_p = 0$ ,  $E_0 = R I_N + V_N$



$$\approx R I_B + V_{OS}$$



(b) With  $R_p = R$ ,

$$E_0 = V_{OS} - R I_{OS}$$

$$(c) E_0(\max) = 10^{-3} + 10^6 \times 10^{-9}$$

= 2mV. To null  $E_0$ ,

return  $R_p$  to a variable voltage  
 $-3mV \leq V_x \leq +3mV$ .

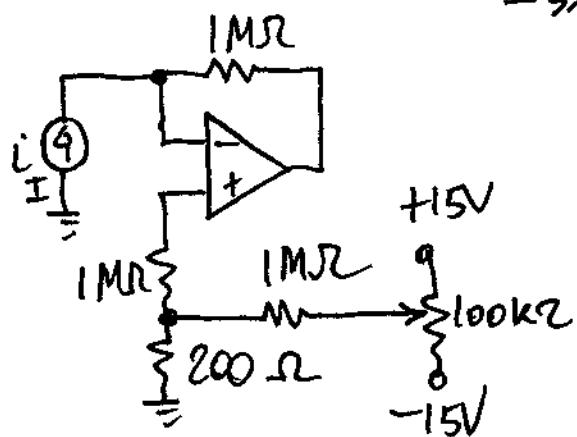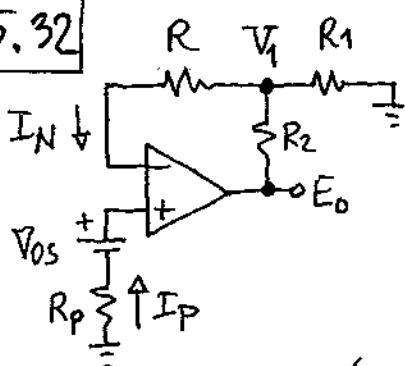**5.32**

Superposition and KCL:

$$V_1 = V_{OS} + R I_N - R_p I_P$$

$$(E_0 - V_1)/R_2 = I_N + V_1/R_1.$$

Eliminating  $V_1$  gives

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) [V_{OS} - R_p I_P + (R + R_1 || R_2) I_N].$$

5.11


To minimize input-bias current errors, use a FET-input opamp, and install a dummy resistance  $R_p = R + R_1 \parallel R_2 \approx 1 \text{ M}\Omega$ , after which

$$E_0 = (1 + R_2/R_1) [V_{OS} - (R + R_1 \parallel R_2) I_{BS}] = 101 [V_{OS} - 10^6 I_{BS}].$$

To null  $E_0$ , return  $R_p$  to a variable voltage  $V_x$  within the range  $-V_2 \leq V_x \leq V_2$ , where

$$V_2 \geq V_{OS(\max)} + 10^6 I_{BS(\max)}.$$

5.33

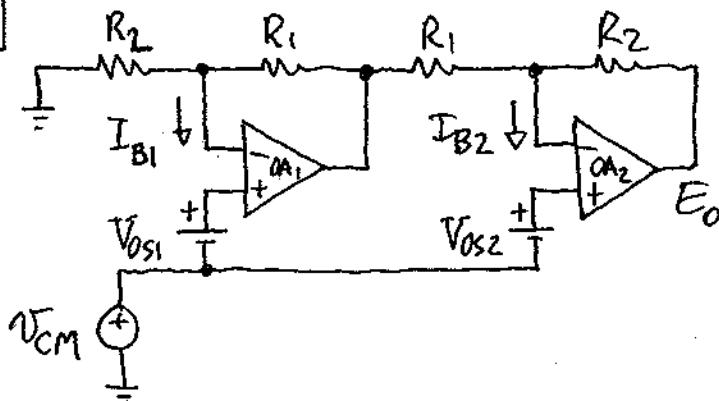

Since the OP-227 uses input bias-current cancellation, there is no point using dummy resistances at the noninverting inputs. The superposition principle gives, for  $V_{CM} = 0$ ,

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) (V_{OS2} - V_{OS1}) - \frac{R_2}{R_1} R_1 I_{B1} + R_2 I_{B2}$$

$$= \left(1 + \frac{R_2}{R_1}\right) [V_{OS2} - V_{OS1} + (R_1 \parallel R_2)(I_{B2} - I_{B1})]$$

$$E_0(\max) = 100 [2V_{OS(\max)} + 2(R_1 \parallel R_2)I_{B(\max)}]$$

$$= 200 [V_{OS(\max)} + (R_1 \parallel R_2)I_{B(\max)}].$$


Specify  $R_1$  and  $R_2$  so that  $(R_1 \parallel R_2)I_{B(\max)} \ll V_{OS(\max)}$ , or  $R_1 \parallel R_2 = R_1/(99R_1) \cong R_1 \ll (80 \mu\text{V})/(40 \text{ mA}) = 2 \text{ k}\Omega$ . For instance, use  $R_1 = 200 \Omega$ ,  $R_2 =$

5.18

19.8 k $\Omega$ . Then, with  $V_{CM} = 0$  V,  $E_0(\text{max}) = 17.6$  mV.

Rising  $V_{CM}$  to 10 V changes  $V_{OS1}$  and  $V_{OS2}$  by as much as  $(10 \text{ V}) / 10^{114/20} \approx 20 \mu\text{V/V}$ . Moreover,  $V_{OS1}$  experiences an additional change of  $V_{OI}/a_{1(\text{min})} = 10/10^6 = 1 \mu\text{V}$ . We thus have, for  $V_{CM} = 10$  V,  $E_0(\text{max}) \approx 17.6 \text{ mV} + 100(21 + 20) \mu\text{V} = 21.7 \text{ mV}$ .

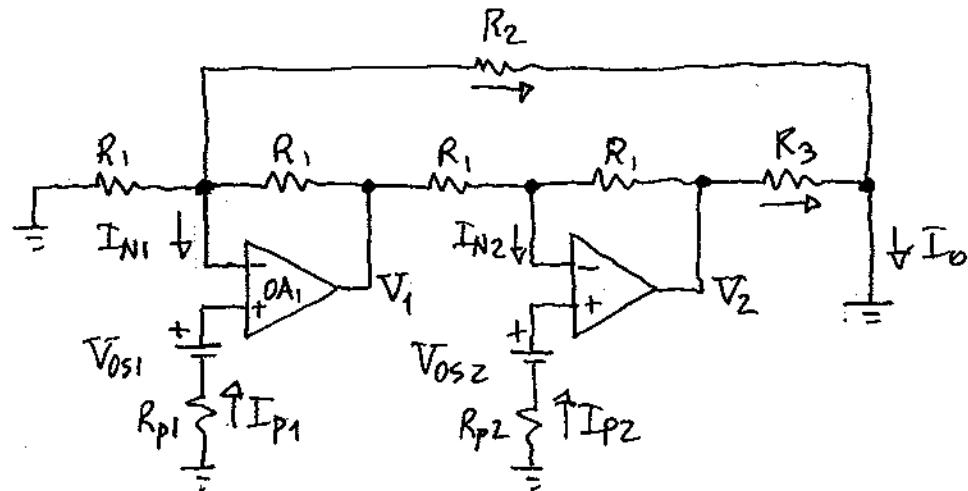**5.34** The presence of the bias currents and offset voltages does not affect the resistances of the circuit, so we expect A and  $R_o$  to remain the same. The only effect is to produce an output error  $I_o$ .



$I_o = V_{N1}/R_2 + V_2/R_3$ . In a well-designed circuit we usually have  $R_3 \ll R_2$  for efficiency, so we need to minimize  $V_2$ . Superposition:

$$\begin{aligned} V_2 &= (1 + R_1/R_1)(V_{OS2} - R_{P2}I_{P2}) + R_1I_{N2} - (R_1/R_1)V_1 \\ &= 2[V_{OS2} - R_{P2}I_{P2} + (R_1/2)I_{N2}] - V_1. \end{aligned}$$

$\Rightarrow$  Use  $R_{P2} = R_1/2$  to minimize effect of  $I_{B2}$ .

$$V_1 = [1 + R_1/(R_1||R_2)](V_{OS1} - R_{P1}I_{P1}) + R_1I_{N1}$$

5.19

$$= \left(2 + R_1/R_2\right) \left\{ V_{OS1} - R_{P1} I_{P1} + \left[\left(R_1/2\right) \parallel R_2\right] I_{N1} \right\}$$


$\Rightarrow$  Use  $R_{P1} = (R_1/2) \parallel R_2$  to minimize effect of  $I_{B1}$ .

Worst-case output error is then

$$I_0(\max) = \frac{V_{OS1} + R_{P1} \bar{I}_{B1}}{R_2} + \frac{1}{R_3} \left\{ 2V_{OS2} + \frac{R_1}{2} I_{OS2} + \left(2 + \frac{R_1}{R_2}\right) (V_{OS1} + R_{P1} I_{OS1}) \right\}.$$

To null  $I_0$ , return  $R_{P2}$  to a variable voltage  $V_x$ ,  
 $-V_3 \leq V_x \leq V_3$ ,  $V_3 \geq \overline{2V_{OS2}} + (R_1/2)\overline{I_{OS2}} + 3(\overline{V_{OS1}} + R_{P1} \overline{I_{OS1}})$ , where the overbar indicates max value.

5.35

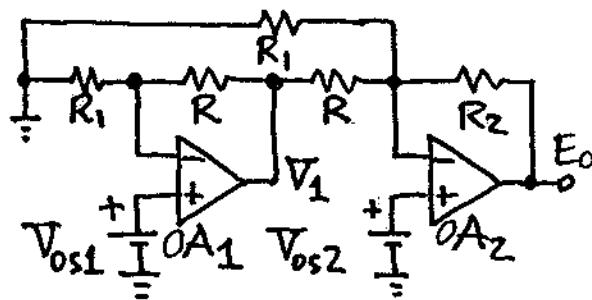(a)  $V_1 = (1 + R/R_1)V_{OS1}$ . Superposition:

$$E_o = -\frac{R_2}{R} V_1 + \left(1 + \frac{R_2}{R_1 \parallel R}\right) V_{OS2}$$

Eliminating  $V_1$  and manipulating,


$$E_o = V_{OS2} + \frac{R_2}{R_1 \parallel R} (V_{OS2} - V_{OS1}).$$

(b) Lift  $OA_2$ 's noninverting input and return it to a variable voltage  $V_x$ ,  
 $-V_2 \leq V_x \leq V_2$ ,  $V_2 = E_o(\max) / [1 + R_2 / (R_1 \parallel R)]$ .

5.20

5.36

(a)

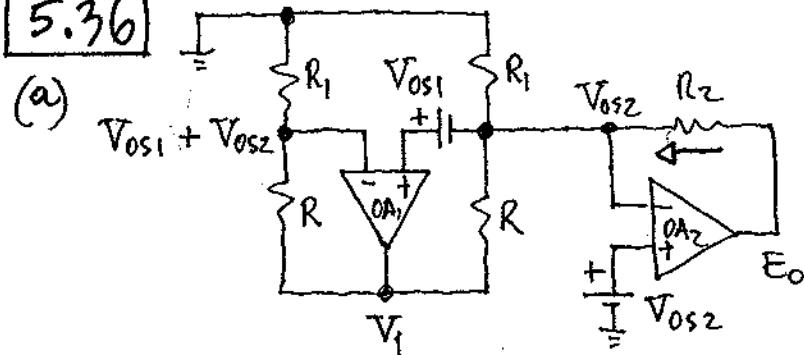

KCL:  $(E_o - V_{os2})/R_2 = V_{os2}/R_1 + (V_{os2} - V_1)/R$ , where  $V_1 = (1 + R/R_1)(V_{os1} + V_{os2})$ . Eliminating  $V_1$ ,  $E_o = V_{os2} - [R_2/(R_1 + R)]V_{os1}$ .


(b) Loft OA2's noninverting input and return it to a variable voltage  $V_x$ ,  $-V_2 \leq V_x \leq V_2$ ,  $V_2 \approx V_{os2(\max)} + [R_2/(R_1 + R)]V_{os1(\max)}$ .

5.37

Fig. 2.1 :  $E_o = V_{os} - RI_{os}$ .  $E_o(\max) = 10^{-3} + 10^6 \times 2 \times 10^{-9} = 3 \text{ mV}$ . Fig. 2.2 : using the superposition principle,  $E_o = R_{eq} I_N + (1 + R_2/R_1)(V_{os} - R_p I_p)$ , where  $R_{eq} = (1 + 20/100 + 20/2.26)100 = 1 \text{ M}\Omega$ ,  $1 + R_2/R_1 = 9.8$ ,  $(1 + R_2/R_1)R_p = 1 \text{ M}\Omega$ . Thus,  $E_o = (1 + R_2/R_1)V_{os} - R_{eq}I_{os}$ , and  $E_o(\max) = 9.8 \times 10^{-3} + 10^6 \times 2 \times 10^{-9} = 9.8 + 2 = 11.8 \text{ mV}$ . While the contribution from  $I_{os}$  is the same, that from  $V_{os}$  is much larger in the second circuit due to the fact that the noise gain is unity in the first circuit, but  $1 + R_2/R_1$  in the second.

5.38

Dc equivalent is as shown:

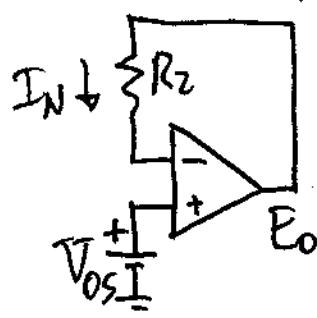


$$\begin{aligned} E_o &= V_{os} + R_2 I_N \approx V_{os} + R_2 I_B \\ &\approx 10^{-3} + 316 \times 10^3 \times 50 \times 10^{-9} \\ &= 16.8 \text{ mV}. \end{aligned}$$

To minimize the output error,

return the noninverting input to ground via a dummy resistance  $R_p = R_2 = 316 \text{ k}\Omega$ . Then,  $E_o = V_{os} - R_2 I_{os}$ , and  $|E_o|_{\max} = 10^{-3} + 316 \times 10^3 \times 5 \times 10^{-9} = 2.58 \text{ mV}$ . To null this residual error, return  $R_p$  to a variable voltage  $V_x$ ,  $-3 \text{ mV} \leq V_x \leq 3 \text{ mV}$ .

5.39

Since noninverting input sees a dc

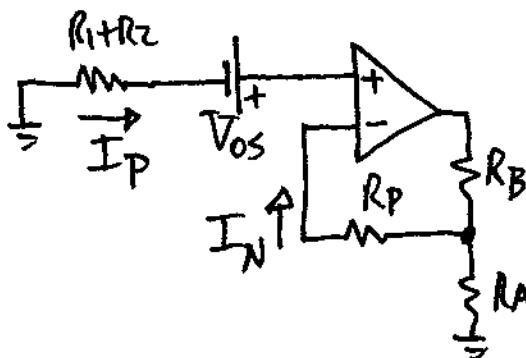


resistance of  $R_1 + R_2 = 31.6 \text{ k}\Omega$ , and the inverting input sees a dc resistance of  $R_A // R_B = 6.40 \text{ k}\Omega$ ,

we either scale  $R_A$  and  $R_B$  to achieve  $R_A // R_B = R_1 + R_2$  while retaining the same ratio, in order to leave Q unchanged, or we leave them as they are, but insert a dummy resistance  $R_p = R_1 + R_2 - R_A // R_B = 25.2 \text{ k}\Omega$ , as shown. In either case we have:

(5.22)

$$E_0 = \left(1 + \frac{R_B}{R_A}\right) [V_{OS} - (R_1 + R_2) I_{OS}], |E_0|_{max} =$$

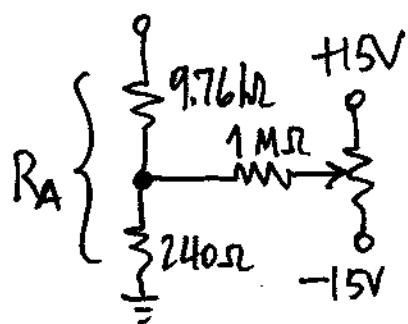
$$2.8 (10^{-3} + 31.6 \times 10^3 \times 5 \times 10^{-9}) = 3.24 \text{ mV. To}$$



null it, return RA to a variable voltage  $V_x$ ,  $-3.5 \text{ mV} \leq V_x \leq 3.5 \text{ mV}$  as shown

5.40

Both the circuits have a dc equiv-

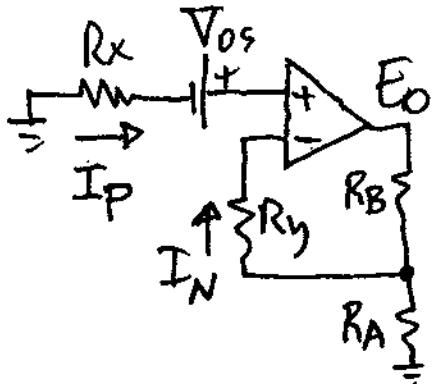


To minimize the error, insert a dummy resistor  $R_y = R_x - (R_A // R_B)$ .

Then, the output

$$\text{error is } E_0 = \left(1 + R_B / R_A\right) (V_{OS} - R_x I_{OS}).$$

Example 3.13:  $R_x = R_2 = 22.5 \text{ k}\Omega$ ,  $R_y = 22.5 - (10 // 28.7) = 15 \text{ k}\Omega$ .  $|E_0|_{max} = 3.86 \times (1 + 22.5 \times 10^3 \times 5 \times 10^{-9}) = 4.3 \text{ mV}$

Example 3.14:  $R_x = 2R = 53.1 \text{ k}\Omega$ ;  $R_y = 53.1 - 0.870 = 52 \text{ k}\Omega$ .  $|E_0|_{max} = (47/12) \times (10^{-3} + 53.1 \times 10^3 \times 5 \times 10^{-9}) = 4.94 \text{ mV}$ .

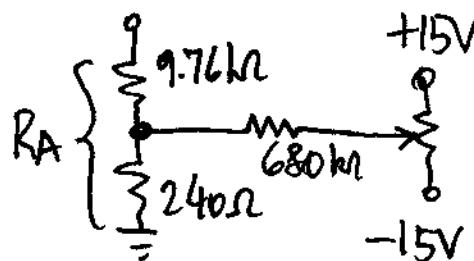


To null the error, split RA and use external nulling as shown.

5.23

5.41

DC equivalent:

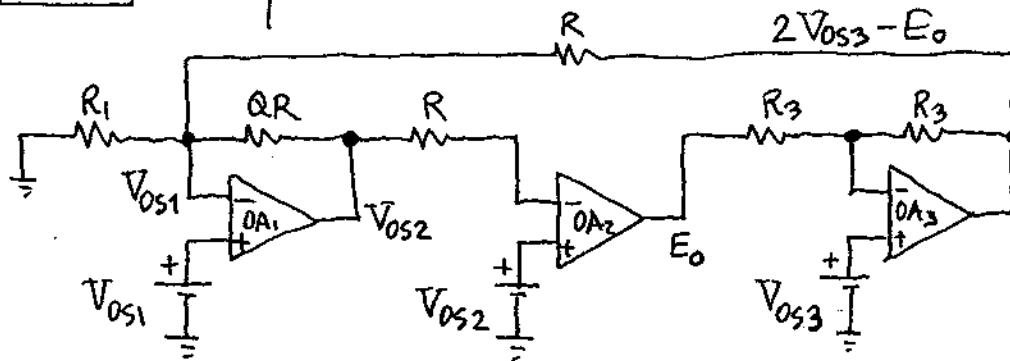

$$\text{KCL: } \frac{V_{OS2} - V_{OS1}}{QR} + \frac{0 - V_{OS1}}{R_1} + \frac{(2V_{OS3} - E_o) - V_{OS1}}{R} = 0$$

$$\Rightarrow E_o = 2V_{OS3} - \left(1 + \frac{1}{Q} + \frac{R}{R_1}\right)V_{OS1} + \frac{V_{OS2}}{Q}$$



$$E_o(\max) = \left[2 + \left(1 + \frac{1}{40} + \frac{20}{78.7}\right) + \frac{1}{40}\right] 5 \times 10^{-3} = 16.3 \text{ mV.}$$

To null  $E_o$ , return  $OA_3$ 's noninverting input to an adjustable voltage  $V_x$  such that

$$2(V_{OS3} + V_x) - 1.28V_{OS1} + 0.025V_{OS2} = 0 \Rightarrow |V_x|_{\max} =$$

$8.2 \text{ mV}$ . For safety, make  $-10 \text{ mV} \leq V_x \leq 10 \text{ mV}$ .

5.42

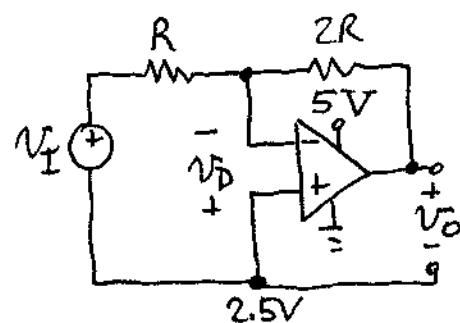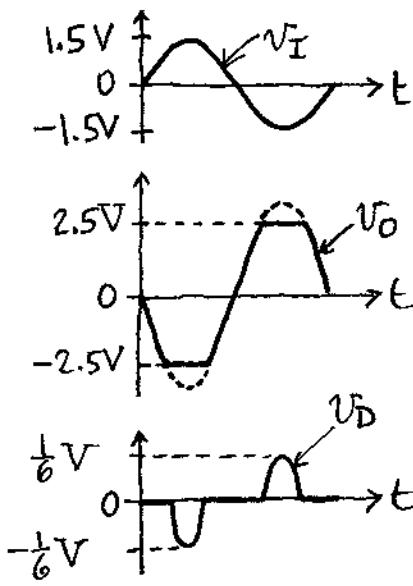

(a) As  $V_O$  tries to swing to  $\pm 3 \text{ V}$ , it clips at  $\pm 2.5 \text{ V}$ ; also,  $V_D$  peaks at  $\pm \left(\frac{2}{3} 1.5 - \frac{1}{3} 2.5\right) = \pm \frac{1}{6} \text{ V}$ .

(b)  $V_I = 1.25 \sin \omega t \text{ V}$ .

5.24

**5.43** (a)  $i_0 = 10/2 = 5 \text{ mA}$ ;  $V_{R_G} = 0.027 \times 5 = 0.135 \text{ V}$ ;  $Q_{15} = \text{off}$ ;  $i_{C15} = 0$ ;  $i_{C14} = i_0 = 5 \text{ mA}$ ;  
 $P_{Q14} = [15 - (10 + 0.135)]5 = 24.3 \text{ mW}$ ;  $V_{B22} = 10 + 0.135 + 0.7 - 3 \times 0.7 = 8.735 \text{ V}$ .

(b)  $10/0.2 = 50 \text{ mA} > 0.7/27 \approx 26 \text{ mA} \Rightarrow$   
 $i_0 \approx 26 \text{ mA}$ ;  $V_0 \approx 0.2 \times 26 = 5.2 \text{ V}$ ;  $i_{C14} \approx i_0 \approx 26 \text{ mA}$ ;  $i_{C15} = 0.18 - 26/250 = 76 \mu\text{A}$ ;  $P_{Q14} \approx (15 - 5.2)26 = 255 \text{ mW}$ ;  $V_{B22}$  close to  $V_{cc}$ .