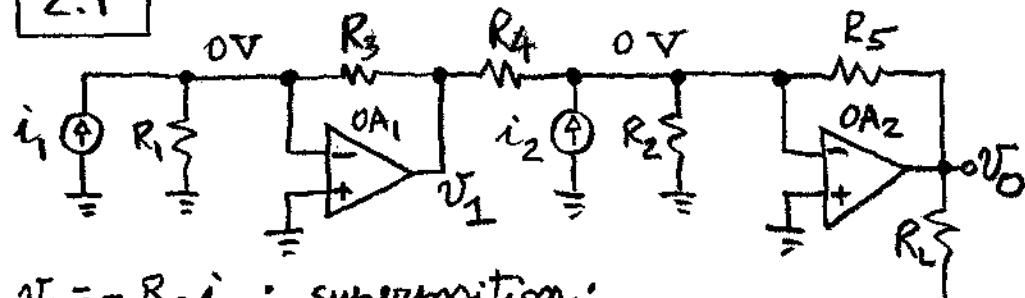


2.1

2.1




$$V_1 = -R_3 i_s; \text{ superposition:}$$

$$V_o = -R_5 i_s - (R_5 / R_4) V_1 = R_5 \left( \frac{R_3}{R_4} V_1 - i_s \right). \text{ Use}$$

$$R_3 = R_4 = R_5 = 0.1 / 10^{-6} = 100 \text{ k}\Omega.$$

2.2

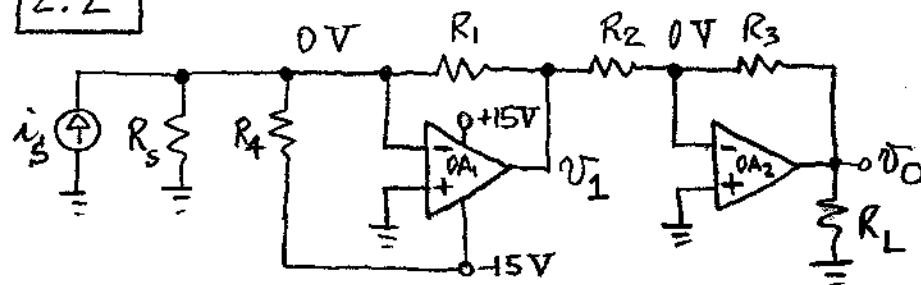


$$V_o = -\frac{R_3}{R_2} V_1 = -\frac{R_3}{R_2} \left[ -R_1 i_s - \frac{R_1}{R_4} (-15 \text{ V}) \right].$$

$$i_s = 4 \text{ mA} \Rightarrow V_o = 0 \Rightarrow \frac{15}{R_4} = 4 \Rightarrow R_4 = 3.75 \text{ k}\Omega$$

(Use 3.74 kΩ, 1%). For simplicity, let  $R_2 = R_3 = 10.0 \text{ k}\Omega$ , so  $V_o = R_1 (i_s - 4 \text{ mA})$ .  $i_s = 20 \text{ mA}$   $\Rightarrow V_o = 10 \text{ V} = R_1 (20 - 4) \Rightarrow R_1 = 10 / 16 = 625 \Omega$ .

2.3

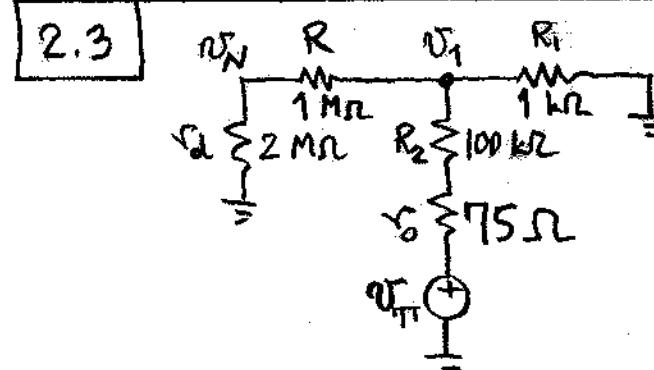

$$V_N = \frac{R}{R_a + R} V_1 = \frac{2}{3} V_1;$$

$$V_1 = \frac{(V_2 + R) \parallel R_1}{[(R_a + R) \parallel R_1] + R_2 + R_5} V_T \approx \frac{1}{1 + 100} V_T = \frac{V_T}{101};$$


2.2

$$\beta \approx \frac{2}{3} \times \frac{1}{101} = \frac{2}{303} \text{ V/V}; T = \alpha\beta = 2 \times 10^5 \times \frac{2}{303} = 1320.$$

$$A \approx A_{\text{ideal}} (1 - 1/T) = A_{\text{ideal}} \times (-0.9992);$$

$$R_i \approx \frac{R_1 R_2}{1+T} = 505 \Omega; R_o \approx \frac{R_2}{1+T} = 57 \text{ m}\Omega.$$

2.4 (a)

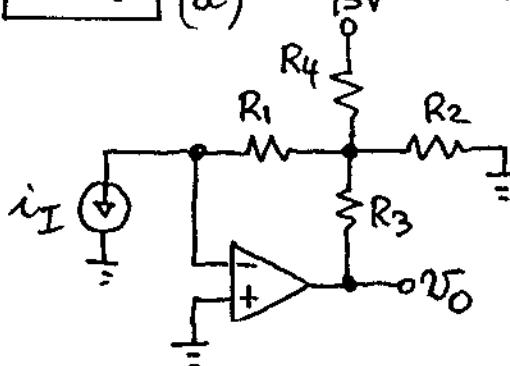

$$v_o = R_2 i_I - 5V; i_I = 0$$

$$\Rightarrow v_o = -(R_3/R_4) 15$$

$$= -5V \Rightarrow R_4 = 3R_3.$$

$$R = \Delta v_o / \Delta i_I = 10 / 10^{-6} = 10 \text{ M}\Omega. \text{ Let } R_1 = 1 \text{ M}\Omega.$$

Let  $X$  be the node where the resistors meet. Then,

$i_I = 1 \mu\text{A} \Rightarrow v_x = 10^6 \times 10^{-6} = 1 \text{ V}$  and  $v_o = +5 \text{ V}$ . KCL:  $(5-1)/R_3 + (15-1)/R_4 = 10^{-6} + 1/R_2$ . Let  $R_2 = 1 \text{ k}\Omega$ . Then,  $R_3 = 8.658 \text{ k}\Omega$  (use  $8.66 \text{ k}\Omega$ ) and  $R_4 = 25.97 \text{ k}\Omega$  (use  $26.1 \text{ k}\Omega$ ).

(b)  $\beta \approx (R_2 // R_4) / [(R_2 // R_4) + R_3] = 1/11 \text{ V/V}$ .  $100/\alpha\beta \leq 1 \Rightarrow \alpha \geq 1,100 \text{ V/V}$ .

2.5 (a)


$$i_o = i_{R_2} + i_{R_3} = i_{R_1} + i_{R_3} = \frac{v_I}{R_1} + \left( \frac{R_2 v_I}{R_1 R_3} \right) \frac{1}{R_3} = \frac{v_I}{R_1} \left( 1 + \frac{R_2}{R_3} \right) = \frac{v_I}{R}, R = \frac{R_1 R_3}{1 + R_2/R_3}.$$

(b)  $R_i = R_1 \Rightarrow R_1 = 1 \text{ M}\Omega$ . Let  $R_2 = R_3 = 1 \text{ M}\Omega$ . Then, for  $R = (1 \text{ V}) / (1 \text{ mA}) = 10^3 \Omega$ , we need  $10^3 = 10^6 / (1 + 10^6/R_3)$ , or  $R_3 \approx 1 \text{ k}\Omega$ .

(c)  $|v_L| \leq 13 - |v_I| \text{ V}$ .

2.3

2.6

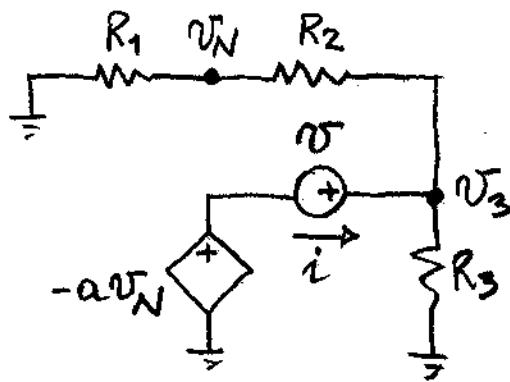


$$\begin{aligned}V_3 &= (1 + R_2/R_1)V_N = 1.99V_N; \quad -aV_N + V = V_3 \\ \Rightarrow V_N &= V/(1.99 + 10^3); \quad i = V_3/(R_1 + R_2) + \\ V_3/R_3 &= [1.99 \cdot V/(1.99 + 10^3)] / [(199 \parallel 1)10^3] \\ &= V/(500,995). \quad R_o = V/i \approx 501 \text{ k}\Omega.\end{aligned}$$

2.7

Eq. (2.7) gives  $\lim_{a \rightarrow \infty} R_o = \infty$ , so (c) is correct. (a) is wrong because it ignores negative feedback. (b) is wrong because the op amp keeps a virtual short between  $V_N$  and  $V_P$ , not between  $V_N$  and  $V_O$ .

2.8

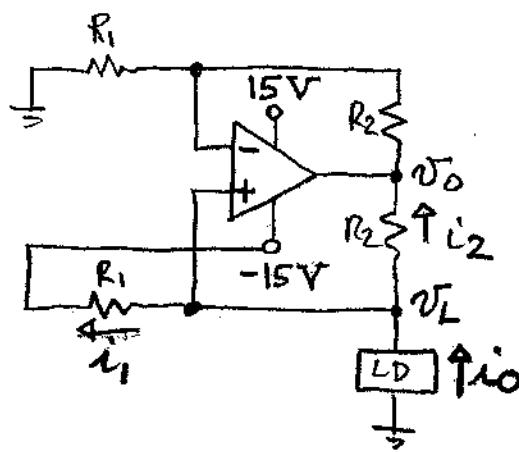

$R_1 = 15/1.5 = 10.0 \text{ k}\Omega, 1\% ; R_2 \leq 0.3 R_1$ . Use  $R_2 = 2.00 \text{ k}\Omega, 1\%$ . Then,  $V_0 = (1 + 2/10)V_L = 1.2V_L$ .

(a)  $V_L = -2 \times 1.5 = -3 \text{ V} ; V_0 = -3.6 \text{ V} ;$   
 $i_1 = [3 - (-15)]/10 = 1.2 \text{ mA} ; i_2 = [-3 - (-3.6)]/2 =$

2.4

0.3 mA; clearly,  $i_0 = i_1 + i_2 = 1.2 + 0.3 = 1.5 \text{ mA}$ .


(b)  $V_L = -9 \text{ V}$ ,  $V_O = -10.8 \text{ V}$ ,  $i_1 = 0.6 \text{ mA}$ ,  $i_2 = 0.9 \text{ mA}$ .

(c) With the cathode at ground, the zener gives  $V_L = -5 \text{ V}$ ,  $V_O = -6 \text{ V}$ ,  $i_1 = 1 \text{ mA}$ ,  $i_2 = 0.5 \text{ mA}$ .

(d)  $V_O = V_L = 0$ ,  $i_1 = 1.5 \text{ mA}$ ,  $i_2 = 0$ .

(e) With a 10-k $\Omega$  load the op amp saturates at  $-13 \text{ V}$ . By KCL,  $(0 - V_L)/10 = (V_L + 15)/10 + (V_L + 13)/2$ , or  $V_L = -80/17 \text{ V}$ . So,  $i_0 = 1.143 \text{ mA}$ ,  $i_1 = 0.357 \text{ mA}$ ,  $i_2 = 0.786 \text{ mA}$ . Because of saturation, we no longer have  $i_0 = 1.5 \text{ mA}$ .

2.9

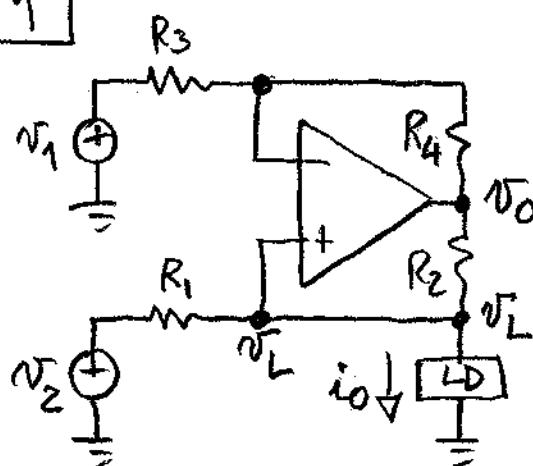

$$\text{Superposition: } V_O = -\frac{R_4}{R_3} V_1 + \left(1 + \frac{R_4}{R_3}\right) V_L ; \text{ KCL:}$$


$$\begin{aligned} i_0 &= \frac{V_2 - V_L}{R_1} + \frac{V_O - V_L}{R_2} = \frac{V_2}{R_1} + \frac{V_O}{R_2} - \left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_L \\ &= \frac{V_2}{R_1} - \frac{R_4}{R_2 R_3} V_1 - V_L \left(\frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{R_2} - \frac{R_4}{R_2 R_3}\right) \\ &= \frac{1}{R_1} \left(V_2 - \frac{R_1 R_4}{R_2 R_3} V_1\right) - \frac{V_L}{R_2} \left(\frac{R_2}{R_1} - \frac{R_4}{R_3}\right) \end{aligned}$$

2.5

$$= \frac{1}{R_1} \left( V_2 - \frac{R_4/R_3}{R_2/R_1} V_1 \right) - \frac{V_L}{R_o}, R_o = \frac{R_2}{R_2/R_1 - R_4/R_3}$$

If  $R_4/R_3 = R_2/R_1$ , then  $i_o = \frac{1}{R_1}(V_2 - V_1)$ , and  $R_o = 0\Omega$ .

2.10

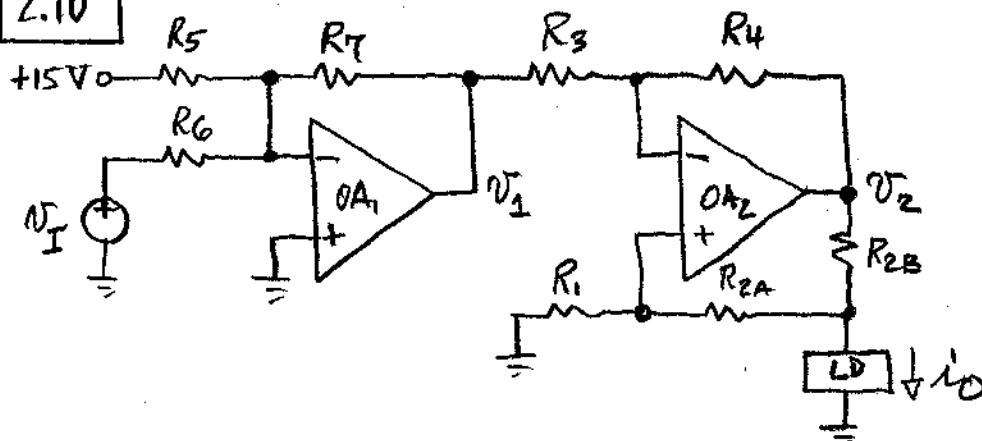


Let  $R_1 = R_3 = R_4 = 10\text{k}\Omega$ . Assume a maximum drop of 2 V across  $R_{2B}$ , so  $R_{2B} = 2/20 = 100\Omega$ . Then,  $R_{2A} = 10\text{k}\Omega - 100\Omega = 9.9\text{k}\Omega$ .

$$V_I = 0 \Rightarrow V_1 = -(R_7/R_5)15 = -0.4 \Rightarrow R_5/R_7 = 37.5$$

$$V_I = 10\text{V} \Rightarrow V_1 = -0.4 - (R_7/R_6)10 = -2 \Rightarrow R_6/R_7 =$$

6.25. Use  $R_7 = 2\text{k}\Omega$ ,  $R_6 = 12.5\text{k}\Omega$ ,  $R_5 = 75\text{k}\Omega$ .

2.11

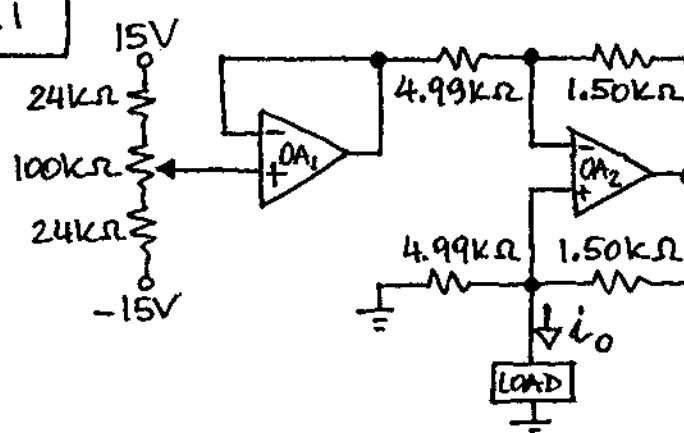


OA<sub>1</sub> provides a variable voltage from -10V to +10V, which OA<sub>2</sub> converts to a variable current from -2mA to +2mA.

2.6

2.12

(a)

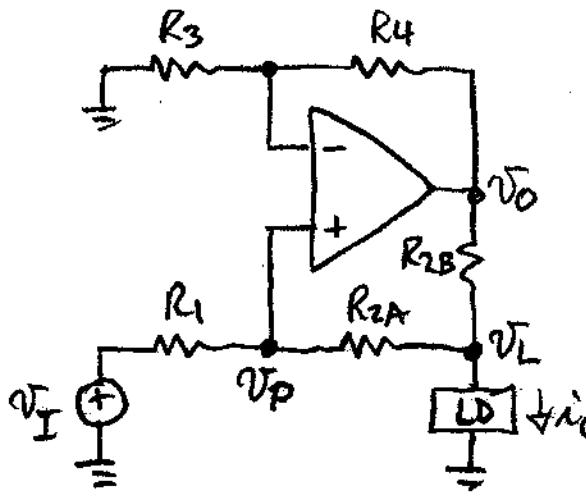

$$V_P = \left(1 + \frac{R_4}{R_3}\right) V_I$$

$$V_P = \frac{R_{2A} V_I + R_1 V_L}{R_1 + R_{2A}}$$

$$i_O = \frac{V_I - V_L}{R_1 + R_{2A}} + \frac{V_O - V_L}{R_{2B}}$$

Eliminating  
 $V_O$  and  $V_P$   
gives

$$i_O = \frac{1}{R} V_I - \frac{1}{R_0} V_L, \text{ where}$$

$$R = \frac{R_3 R_{2B} (R_1 + R_{2A})}{R_3 (R_{2A} + R_{2B}) + R_4 R_{2A}}, R_0 = \frac{R_{2B} (1 + R_{2A}/R_1)}{R_4/R_3 - (R_{2A} + R_{2B})/R_1}.$$


To make  $R_0 = \infty$  impose  $R_4/R_3 = R_2/R_1$ , where  
 $R_2 = R_{2A} + R_{2B}$ . This gives

$$R = \frac{R_3 R_{2B} (R_1 + R_{2A})}{R_4 (R_1 + R_{2A})} = \frac{R_3}{R_4} R_{2B} \Rightarrow \frac{1}{R} = \frac{R_4/R_3}{R_{2B}}.$$

(b) Impposing  $10 = 13 - (R_4/R_3)i_O$

gives  $R_4/R_3 = 0.3$ . Let  $R_1 = R_3 = 100\text{k}\Omega$ ,  $R_4 = R_{2A} + R_{2B} = 30.1\text{k}\Omega$ . Then, imposing  $(R_4/R_3)/R_{2B} = 0.301/R_{2B} = 1\text{mA/V}$  gives  $R_{2B} = 301\text{\Omega}$ . Finally,  
 $R_{2A} = 30.1 - 0.301 = 29.8\text{k}\Omega$  (use  $30.1\text{k}\Omega, 1\%$ ).

2.13

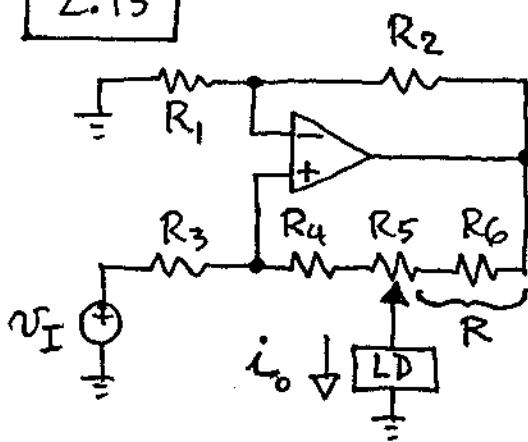

$$i_O = \frac{R_2/R_1}{R} V_I$$

Wiper to the right:

$$\frac{R_2/R_1}{R_6} = \frac{1}{10^3}.$$

Wiper to the left:

2.7

$\frac{R_2/R_1}{R_5+R_6} = \frac{1}{10^4}$ . Let  $R_5 = 10-k\Omega$  pot. Substituting and solving yields  $R_2/R_1 = 10/9$  and  $R_6 = 10/9 k\Omega$ . Use  $R_1 = 90.9 k\Omega$ ,  $R_2 = 100 k\Omega$ ,  $R_3 = 90.9 k\Omega$ ,  $R_5 = 10.0 k\Omega$ ,  $R_6 = 1.10 k\Omega$ ,  $R_4 = 100 - 10 - 1.1 = 88.7 k\Omega$ , all 1%.

2.14 (a) Denote the output of OA<sub>1</sub> as  $V_{O1}$ , and that of OA<sub>2</sub> as  $V_{O2}$ . By inspection, we have  $V_{O2} = V_L$ . By the superposition principle,

$$\begin{aligned} V_{O1} &= -\frac{R_4}{R_3} V_1 + \left(1 + \frac{R_4}{R_3}\right) \frac{R_2 V_2 + R_1 V_L}{R_1 + R_2} \\ &= \frac{1 + R_4/R_3}{1 + R_1/R_2} V_2 - \frac{R_4}{R_3} V_1 + \frac{1 + R_4/R_3}{1 + R_2/R_1} V_L. \end{aligned}$$

$$i_o = \frac{V_{O1} - V_L}{R_5} = A_2 V_2 - A_1 V_1 - \frac{1}{R_0} V_L, \text{ where}$$

$$A_2 = \frac{1 + R_4/R_3}{1 + R_1/R_2} \frac{1}{R_5}, A_1 = \frac{R_4}{R_3} \frac{1}{R_5}, \text{ and}$$

$$\frac{1}{R_0} = \frac{1}{R_5} \left(1 - \frac{1 + R_4/R_3}{1 + R_2/R_1}\right) = \frac{1}{(1 + R_2/R_1)R_5} \left(\frac{R_2}{R_1} - \frac{R_4}{R_3}\right)$$

To make  $R_0 \rightarrow \infty$  impose  $R_4/R_3 = R_2/R_1$ , after which it is readily seen that  $A_1 = A_2 = \frac{R_2/R_1}{R_5}$ .

In summary, imposing  $R_4/R_3 = R_2/R_1$  gives

$$i_o = A V_I - \frac{1}{R_0} V_L, A = \frac{R_2/R_1}{R_5}, V_I = V_2 - V_1, R_0 = \infty.$$

(b) If the resistances are mismatched,  $A_1$  and  $A_2$  will also be mismatched, so we no longer have true difference operation.

2.8

$$\text{Writing } R_o = \frac{(1+R_2/R_1)R_5}{R_2/R_1 - (R_2/R_1)(1-\varepsilon)} = \left(1 + \frac{R_2}{R_1}\right) \frac{R_5}{\varepsilon}$$

gives, for 1% resistors,  $|R_o| \geq 25(1+R_2/R_1)R_5$ .

2.15

(a) Denote the output of OA<sub>1</sub> as  $V_{O1}$ , that of OA<sub>2</sub> as  $V_{O2}$ . By OA<sub>2</sub>'s action,  $V_{O1} = V_L$  and  $V_{O2} = V_L + R_5 i_o$ . By the superposition principle,

$$V_{O1} = -\frac{R_4}{R_3} V_I + \left(1 + \frac{R_4}{R_3}\right) \frac{R_1}{R_1 + R_2} (V_L + R_5 i_o) = V_L.$$

Solving for  $i_o$  gives  $i_o = A V_I - (1/R_o) V_L$ ,

$$A = \frac{1+R_2/R_1}{1+R_4/R_3} \frac{R_4/R_3}{R_5}, R_o = \frac{(1+R_4/R_3) R_5}{R_2/R_1 - R_4/R_3}.$$

Imposing  $R_4/R_3 = R_2/R_1$  gives  $R_o = \infty$  and  $A = (R_2/R_1)/R_5$ .

$$(b) \text{ Writing } R_o = \frac{(1+R_2/R_1)R_5}{R_2/R_1 - (R_2/R_1)(1-\varepsilon)}$$

$= (1+R_1/R_2)R_5/\varepsilon$ . With 1% resistors we can expect  $|R_o| \geq 25(1+R_1/R_2)R_5$ .

2.16

(a) Denote the outputs of OA<sub>1</sub> and OA<sub>2</sub> as  $V_{O1}$  and  $V_{O2}$ . We have  $V_{O2} = -V_{O1} = -[-V_I - (R_1/R_2)V_L] = V_I + (R_1/R_2)V_L$ ;  $i_o =$


$$\frac{V_{O2} - V_L}{R_3} - \frac{V_L}{R_2} = \frac{V_I}{R_3} - V_L \left[ \frac{1}{R_3} + \frac{1}{R_2} - \frac{R_1/R_2}{R_3} \right],$$

$$\text{or } i_o = A V_I - \frac{1}{R_o} V_L, A = \frac{1}{R_3}, R_o = \frac{R_2 R_3}{R_2 + R_3 - R_1}.$$

To achieve  $R_o = \infty$ , impose  $R_2 + R_3 = R_1$ .

2.9

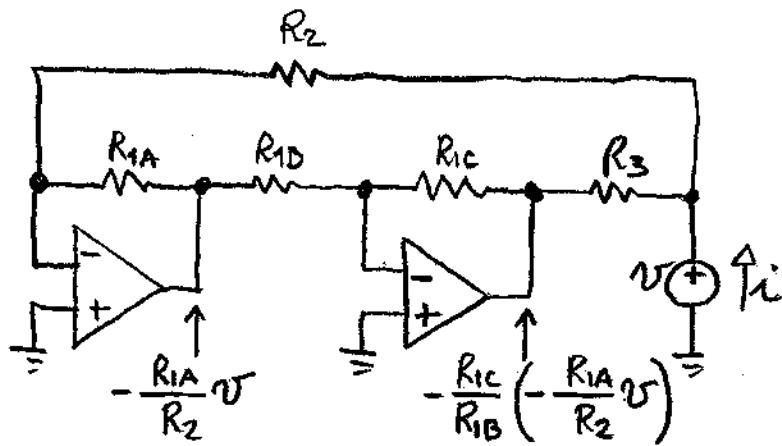(b) To find the effect of mismatches upon  $R_o$ , apply a test voltage at the output, as shown:



$$i = \frac{v}{R_2} + \frac{v - (R_{1A}R_{1B}/(R_2R_{1B}))v}{R_3}$$

$$= v \left[ \frac{1}{R_2} + \frac{1}{R_3} - \frac{R_{1A}(R_{1B}/R_2)}{R_2R_3} \right]$$

$$R_o = \frac{v}{i} = \frac{R_2R_3}{R_2 + R_3 - R_{1A}(R_{1B}/R_2)}$$

$R_o$  is maximized when  $R_2$ ,  $R_3$ , and  $R_{1B}$  are maximized, and  $R_{1A}$  and  $R_{1C}$  are minimized.

For 1% resistors, rewrite as

$$R_o(\text{max}) = \frac{(R_2 \times R_3) 1.01^2}{(R_2 + R_3) 1.01 - (R_2 + R_3) 0.99 (0.99/1.01)} \\ \approx 25 \frac{R_3}{1 + R_3/R_2}.$$


2.10

**2.17** (a)  $i_0 = 1 \text{ mA}$ ,  $R_o = \infty$ .  $v_C(t) = (i_0/C)t = (10^{-3}/10^{-7})t = 10^4 t$ .  $v_o(t) = (1 + R_2/R_1)v_C(t) = 1.295 \times 10^4 t$ . A linear ramp.

(b)  $13 = 1.295 \times 10^4 t \Rightarrow t \approx 1 \text{ ms}$ .

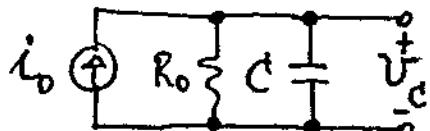2.18


The capacitor sees the equivalent circuit on the left.



(a)  $i_0 = 1 \text{ mA}$ ;  $R_o = R_2 / (R_2/R_1 - R_4/R_3) = 4.42 / (4.42/15 - 3.978/15) = 150 \text{ k}\Omega$ ;  $R_o i_0 = 150 \times 1 = 150 \text{ V}$ ;  $\tau = R_o C = 150 \times 10^3 \times 10^{-7} = 15 \text{ ms}$ ;  $(1 + R_2/R_1)R_o i_0 = (1 + 3.980/15)150 \approx 190 \text{ V}$ .


$v_o(t) = 190 \text{ V} [1 - \exp(-t/15 \text{ ms})]$ .  $13 = 190 \times [1 - \exp(-t/15 \text{ ms})] \Rightarrow t = 1.06 \text{ ms}$ .

(b) Now  $R_o = -150 \text{ k}\Omega$ ,  $(1 + R_2/R_1) \times |R_o| i_0 \approx 200 \text{ V}$ ,  $v_o(t) = 200 \text{ V} [\exp(t/15 \text{ ms}) - 1]$ .  $13 = 200 [\exp(t/15 \text{ ms}) - 1] \Rightarrow t = 0.95 \text{ ms}$ .

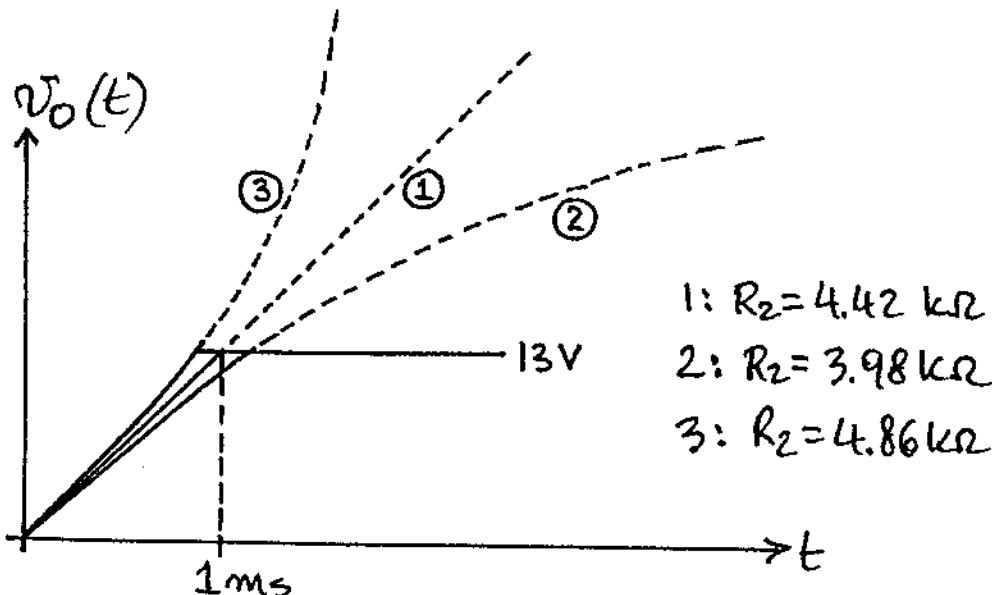

2.11

2.19

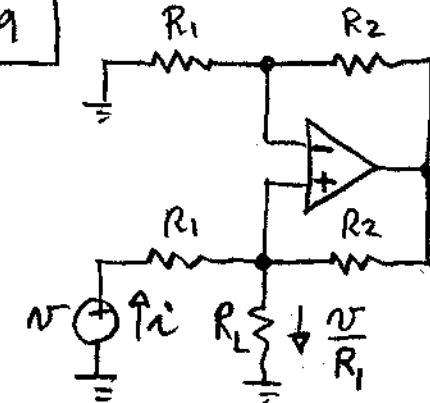

$$i = \frac{V - (V/R_1)R_L}{R_1}$$


$$= \frac{V}{R_1} \left( 1 - \frac{R_L}{R_1} \right);$$

$$R_i = \frac{V}{i} = \frac{R_1}{1 - R_L/R_1}.$$

$R_L < R_1 \Rightarrow R_o > 0$ ;  $R_L > R_1 \Rightarrow R_i < 0$ ;  $R_L = R_1 \Rightarrow R_i = \infty$ .

2.20

(a)

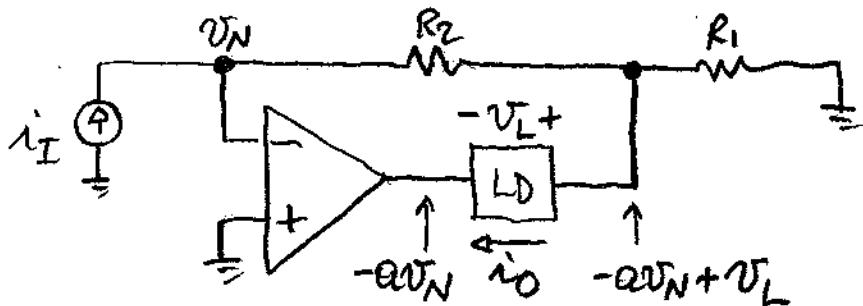

$$\text{D: } V_N - (-aV_N + V_L) = R_2 i_I$$

$$\Rightarrow V_N = (R_2 i_I + V_L) / (1+a). \text{ KCL:}$$

$$i_O = i_I + \frac{aV_N - V_L}{R_1} = i_I + \frac{a(R_2 i_I + V_L)}{(1+a)R_1} - \frac{V_L}{R_1}$$

$$= i_I \left( 1 + \frac{R_2/R_1}{1+1/a} \right) - \frac{1}{R_1} V_L \left( 1 - \frac{1}{1+a} \right) = A i_I - \frac{V_L}{R_o},$$

$$A = 1 + \frac{R_2/R_1}{1+1/a}, R_o = R_1 (1+a)$$

(b) Use  $R_1 = 2 \text{ k}\Omega$ ,  $R_2 = 18 \text{ k}\Omega$ .

$$A_{ideal} = 10 \text{ A/A}; A_{actual} = 1 + 9/(1 + 1/200,000)$$

$$= 9.999955; \text{ gain error} = -0.00045\%.$$

$$R_o \approx 2 \times 10^3 \times (1 + 200,000) = 400 \text{ M}\Omega.$$

2.12


**2.21** The op amp keeps  $V_o = V_N = V_p$ . By the superposition principle,  $V_p = (R_s // R_2) i_S + \frac{R_s}{R_s + R_2} V_L$ . By KCL,  $i_O = (V_p - V_L) / (R_L // R_2)$ . Substituting,

$$i_O = \frac{R_s // R_2}{R_L // R_2} i_S - \frac{V_L}{R_L // R_2} \left[ 1 - \frac{R_s}{R_s + R_2} \right] = A i_S - \frac{V_L}{R_o},$$

$$A = \frac{1 + R_2 / R_1}{1 + R_2 / R_s}, R_o = \frac{R_s + R_2}{1 + R_2 / R_1}.$$

For  $R_s \rightarrow \infty$  we get  $A = 1 + R_2 / R_1$  and  $R_o = \infty$ .

2.22

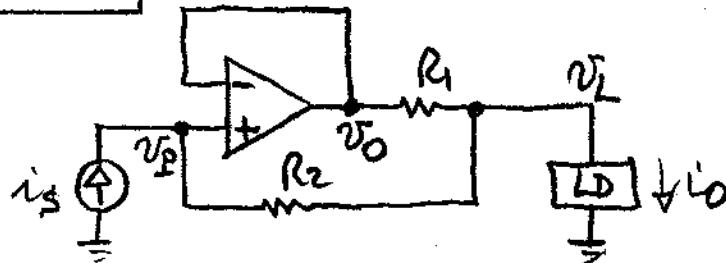


$$V_p = V_L + R_2 i_S; V_0 = a(V_p - V_L) \Rightarrow V_0 = \frac{a}{1+a} V_p$$

$$V_0 = \frac{a}{1+a} (V_L + R_2 i_S). i_O = i_S + \frac{V_0 - V_L}{R_L} \Rightarrow$$

$$i_O = i_S + \frac{1}{R_L} \left[ \frac{a}{1+a} V_L - V_L + \frac{a}{1+a} R_2 i_S \right] = A i_S - \frac{1}{R_L} V_L,$$

$$A = 1 + (R_2 / R_1) / (1 + 1/a), R_o = R_1 (1 + a).$$

2.23

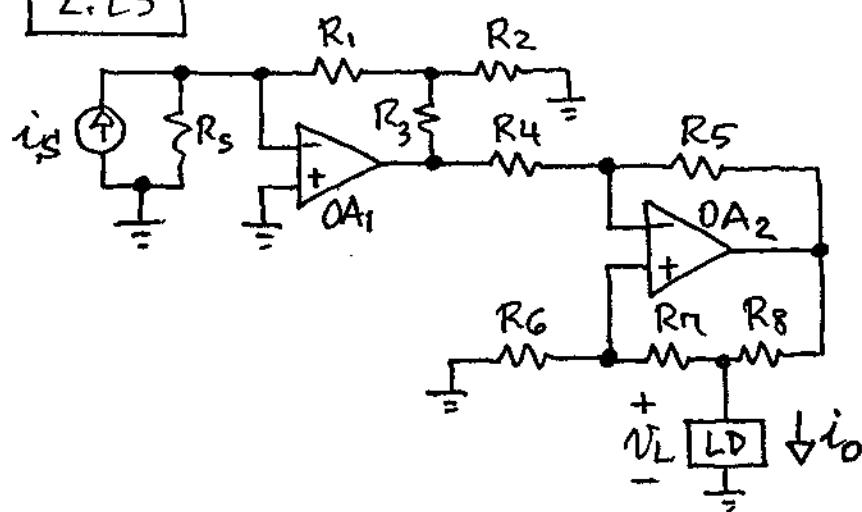


2.13

Choose the I-V converter components for a 10-V full scale at OA<sub>1</sub>'s output. Thus, let  $R_1 = 1\text{ M}\Omega$ ,  $R_2 = 1\text{ k}\Omega$ ,  $R_3 = 100\text{ k}\Omega$ .

$i_{O(\max)} = 10^5 \times 100 \times 10^{-9} = 10\text{ mA}$ . Impressing  $R_g = 100\text{ }\mu\Omega$  yields a voltage compliance of  $B - 0.1 \times 10 = 12\text{ V} > 5\text{ V}$ . Finally, let  $R_4 = R_5 = R_6 = 100\text{ k}\Omega$ ,  $R_7 = 99.9\text{ k}\Omega$ .

2.24

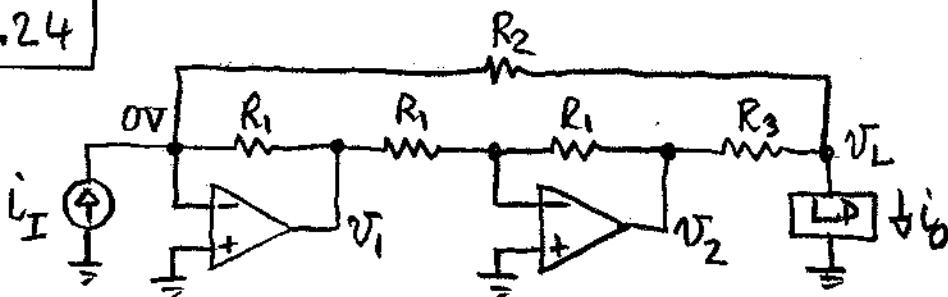

$$v_1 = -R_1 i_I - (R_1 / R_2) v_L; v_2 = -v_1 = R_1 i_I + \frac{R_1}{R_2} v_L.$$

$$i_O = \frac{v_2 - v_L}{R_3} - \frac{v_L}{R_2} = \frac{R_1}{R_3} i_I - v_L \left[ \frac{1}{R_2} + \frac{1}{R_3} - \frac{R_1}{R_2 R_3} \right].$$

Impose  $R_2 + R_3 = R_1$  to achieve  $R_o = \infty$ , and  $R_1/R_3 = 10$  to achieve the desired gain. Moreover,  $R_i = 0$  because of the input virtual ground. Use  $R_1 = 10.0\text{ k}\Omega$ ,  $R_3 = 1.00\text{ k}\Omega$ , and  $R_2 = 9.09\text{ k}\Omega$ .

2.25


The output of OA<sub>1</sub> is  $v_1 = -\frac{R}{R_2} v_2 - \frac{R}{R_4} v_4$ . By the superposition principle,

$$v_o = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_3} v_3 - \frac{R_F}{R} v_1 =$$

$$= \frac{R_F}{R_2} v_2 + \frac{R_F}{R_4} v_4 - \frac{R_F}{R_1} v_1 - \frac{R_F}{R_3} v_3.$$

The circuit sums the even-numbered inputs with positive gains, and the odd-numbered inputs with negative gains. Since the summing junctions of both op amps are at virtual ground, leaving an input floating has no effect. By contrast, leaving any input floating in Fig. Pl.31 affects the output because in general  $V_N = V_P \neq 0$ .

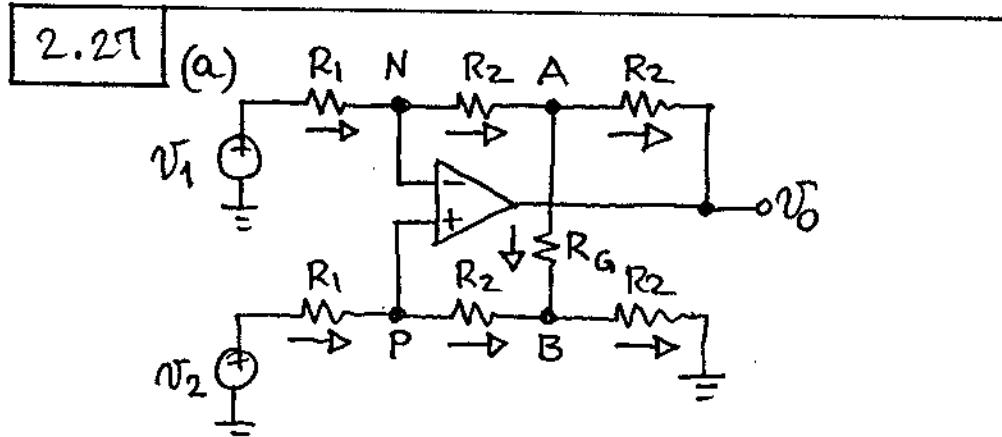**2.26** Applying a test voltage  $v$  in Fig. 2.14(a) yields, by the virtual short concept,  $i = v/(R_1 + 0 + R_1) = v/2R_1$ . Hence,  $R_{id} = 2R_1$ . In Fig. 2.14(b) both resistances  $R_1$  carry the same current. Hence, applying a test voltage  $v$  yields  $i = 2i_{R_1} = 2v/(R_1 + R_2)$ . Consequently,  $R_{id} = (R_1 + R_2)/2$ .



$$\text{KCL at } N: \frac{V_1 - V_N}{R_1} = \frac{V_N - V_A}{R_2}$$

$$\text{KCL at } P: \frac{V_2 - V_P}{R_1} = \frac{V_P - V_B}{R_2}.$$

2.15

Letting  $V_N = V_P$  and subtracting,

$$V_A - V_B = \left(\frac{R_2}{R_1}\right)(V_2 - V_1) \dots \dots \dots (1)$$

$$\text{KCL at A: } \frac{V_1 - V_A}{R_1 + R_2} = \frac{V_A - V_B}{R_G} + \frac{V_A - V_O}{R_2}.$$

$$\text{KCL at B: } \frac{V_2 - V_B}{R_1 + R_2} + \frac{V_A - V_B}{R_G} = \frac{V_B}{R_2}. \text{ Subtracting,}$$

$$\frac{(V_2 - V_1) + (V_A - V_B)}{R_1 + R_2} + 2 \frac{V_A - V_B}{R_G} = \frac{(V_B - V_A) + V_O}{R_2}.$$

Combining with Eq. (1),

$$(V_2 - V_1) \left( \frac{1 + R_2/R_1}{R_1 + R_2} + 2 \frac{R_2/R_1}{R_G} + \frac{1}{R_1} \right) = \frac{V_O}{R_2}.$$

Solving for  $V_O$  and simplifying,

$$V_O = 2 \frac{R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) (V_2 - V_1).$$

(b) Let  $R_G = 100\text{k}\Omega$  pot in series with a  $5\text{k}\Omega$  resistor. Then,  $100 = 2(R_2/R_1)(1+R_2/5)$  and  $10 = 2(R_2/R_1)[1+R_2/(100+5)]$ . Dividing,  $100/10 = (1+R_2/5)/(1+R_2/105)$ . Solving,  $R_2 = 85.9\text{k}\Omega$ . Back substituting yields  $R_1 = 31.24\text{k}\Omega$ . Use  $R_1 = 31.6\text{k}\Omega$ ,  $R_2 = 86.6\text{k}\Omega$ ,  $R_G = 100\text{k}\Omega$  pot +  $4.99\text{k}\Omega$ , all 1%.

2.28

(a)  $V_{O2} = -(R_3/R_G)V_O$ . Superposition:

$V_{P1} = \frac{R_2 V_2 + R_1 V_{O2}}{R_1 + R_2}$ . Voltage divider:  $V_{N1} = [R_2/(R_1 + R_2)]V_1$ .

Eliminating  $V_{O2}$  and letting  $V_{N1} = V_{P1}$  gives  $V_O = \frac{R_2}{R_1} \frac{R_G}{R_3} (V_2 - V_1)$ .

2.16

(b) Let  $R_1 = R_2 = 10 \text{ k}\Omega$ . Then,  $A = R_G/R_3$ .  
 Let  $R_3 = 1 \text{ k}\Omega$  and let  $R_G$  be a  $100-\text{k}\Omega$  pot in series with a  $1-\text{k}\Omega$  resistor. Then,  
 $A_{(\min)} = 1 \text{ V/V}$ ,  $A_{(\max)} = (1+100)/1 \cong 100 \text{ V/V}$ .

2.29 (a)  $(V_1 + V_2)/2 = 10 \cos 2\pi 60t \text{ V}$ ;  
 $V_2 - V_1 = 0.01 \cos 2\pi 10^3 t \text{ V}$ ;  $A_{dm} = 2/0.01 = 200 \text{ V/V}$ ;  
 $A_{cm} = 0.1/10 = 0.01 \text{ V/V}$ ;  $\text{CMRR} = 20 \log_{10} (200/0.01) = 86 \text{ dB}$ .

(b)  $(V_1 + V_2)/2 = 10.005 \cos 2\pi 60t \text{ V}$ ;  
 $V_2 - V_1 = -0.01 \sin 2\pi 60t + 0.01 \sin 2\pi 10^3 t \text{ V}$ ;  
 $A_{dm} = 2.5/0.01 = 250 \text{ V/V}$ . At 60 Hz, we have  $0.5 = 250 \times (-0.01) + A_{cm} \times 10.005$ , or  $A_{cm} \cong 0.3 \text{ V/V}$ ;  $\text{CMRR} = 20 \log_{10} (250/0.3) = 58.4 \text{ dB}$ .

2.30  $A_{dm} \cong (100 \text{ k}\Omega)/(1 \text{ k}\Omega) = 100 \text{ V/V} = 40 \text{ dB}$ .  
 To find  $A_{dm}$ , tie the inputs together and apply a common signal. Then,

$$A_{dm} = -\frac{99.7}{1.01} + \left(1 + \frac{99.7}{1.01}\right) \frac{102}{102 + 0.995} = 0.0367 \text{ V/V}$$

$$= -28.7 \text{ dB}. \quad \text{CMRR} \cong 40 - (-28.7) = 68.7 \text{ dB}.$$

2.31  $|A_{dm}| = 10^3 \text{ V/V}$ ;  $\text{CMRR} = 10^5$ ;  $|A_{cm}| = 10^{-2} \text{ V/V}$ .


$$V_{id} = V_2 - V_1 = 2 \text{ mV}; \quad V_{ic} = (V_1 + V_2)/2 = 4 \text{ V};$$

$$|V_{od}| = 10^3 \times 2 \times 10^{-3} = 2 \text{ V}; \quad |V_{oc}| = 10^{-2} \times 4 = 0.04 \text{ V}.$$

$$\text{Error} = 100|V_{oc}|/|V_{od}| = 2\%.$$

2.17

2.32

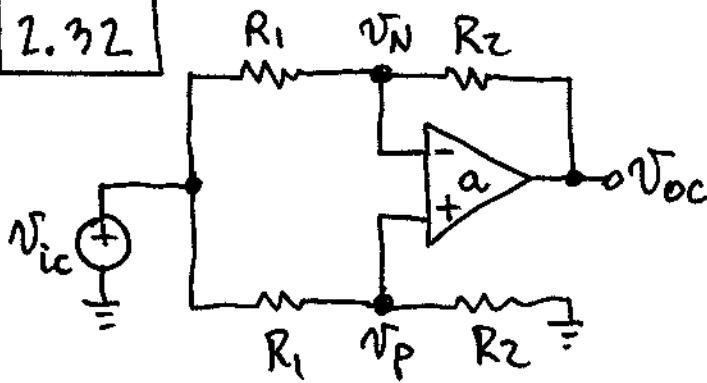

$$\begin{aligned} V_{oc} &= a(V_p - V_N) = a \left[ \frac{R_2}{R_1 + R_2} V_{ic} - \frac{R_2 V_{ic} + R_1 V_{oc}}{R_1 + R_2} \right] \\ &= a \left[ \cancel{\frac{R_2}{R_1 + R_2} V_{ic}} - \cancel{\frac{R_2}{R_1 + R_2} V_{ic}} - \frac{R_1}{R_1 + R_2} V_{oc} \right] \end{aligned}$$

$$\Rightarrow V_{oc}(1 + a\beta) = 0 \Rightarrow V_{oc} = 0 \text{ regardless of } V_{ic}.$$

$\Rightarrow CMRR = \infty$ . Intuitively:  $V_{oc}$  can only be zero. Suppose  $V_{oc}$  was positive. Then,  $V_N$  would be  $> V_p$ , implying  $V_o = a(V_p - V_N) < 0$ , a contradiction.

2.33

$$V_{N1} = V_{P1} = V_1 = 5V - 5 \sin \omega t \text{ mV};$$

$$V_{N2} = V_{P2} = V_2 = 5V + 5 \sin \omega t \text{ mV};$$

$$\begin{aligned} V_{O1} &= V_{N1} + R_3 \frac{V_{N1} - V_{N2}}{R_G} = 5V - 5 \sin \omega t \text{ mV} + \\ &\quad \frac{10^6}{2 \times 10^3} (-10 \sin \omega t \text{ mV}) = 5V - 5.005 \sin \omega t \text{ V}; \end{aligned}$$

$$V_{O2} = 5V + 5.005 \sin \omega t \text{ V};$$

$$V_{N3} = V_{P3} = \frac{R_2}{R_1 + R_2} V_{O2} = 2.5V + 2.5025 \sin \omega t \text{ V};$$


$$V_O = \frac{R_2}{R_1} (V_{O2} - V_{O1}) = 10.01 \sin \omega t \text{ V}.$$

2.18

2.34  $V_O = V_{O1} - V_{O2} = \alpha_1 (V_{P1} - V_{N1}) - \alpha_2 (V_{P2} - V_{N2}) = \alpha [(V_{P1} - V_{P2}) - (V_{N1} - V_{N2})] = \alpha [V_I - R_G V_O / (R_G + 2R_3)]$ . This is of the type  $V_O = \alpha (V_I - \beta V_O)$ ,  $\beta = R_G / (R_G + 2R_3)$ .

2.35 From Problem 2.34,  $\beta_I = 1/A_I = 1/50$  V/V; moreover,  $\beta_{II} = 1/A_{II} = 1/20$  V/V. We can guarantee a 0.1% maximum deviation of  $A = A_I \times A_{II}$  from ideality by imposing a 0.05% maximum deviation of  $A_I$  and  $A_{II}$ . Thus,  $100/\alpha_I \beta_I \leq 0.05 \Rightarrow \alpha_I \geq 100 \times 50/0.05 = 10^5$  V/V; likewise,  $\alpha_{II} \geq 4 \times 10^4$  V/V.

2.36

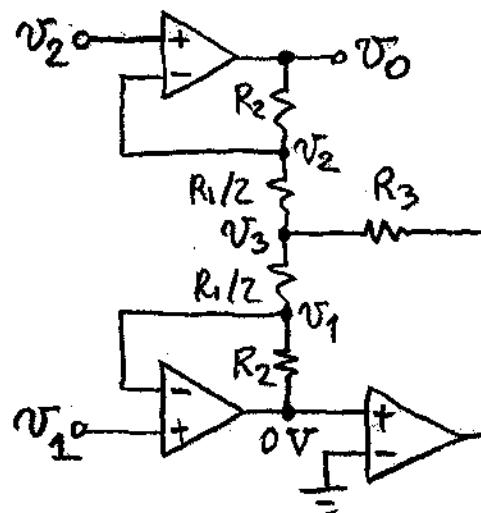

$$V_1 = \frac{R_2}{R_2 + R_1/2} V_3 \Rightarrow$$

$$V_3 = \left(1 + \frac{R_1}{2R_2}\right) V_1 ;$$

$$\frac{V_O - V_2}{R_2} = \frac{V_2 - V_3}{R_1/2} .$$

Eliminating  $V_3$ ,

$$V_O = \left(1 + \frac{2R_2}{R_1}\right) (V_2 - V_1) .$$

2.37

(a) Superposition:

$$V_O = \left[1 + \frac{R_2}{R_1}\right] \left[V_{CM} + \frac{V_{DM}}{2}\right] - \frac{R_2}{R_1} \left[1 + \frac{R_1}{R_2}(1-\varepsilon)\right] \left[V_{CM} - \frac{V_{DM}}{2}\right]$$


$$= \left(1 + \frac{R_2}{R_1} - \frac{\varepsilon}{2}\right) V_{DM} + \varepsilon V_{CM}$$

2.19

(b) With 1% resistors,  $\epsilon$  can be as large as 0.04. Since this is much less than 100, we can write  $\text{CMRR} \geq 20 \log_{10} (100/0.04) = 68 \text{ dB}$ .

2.38

(a)

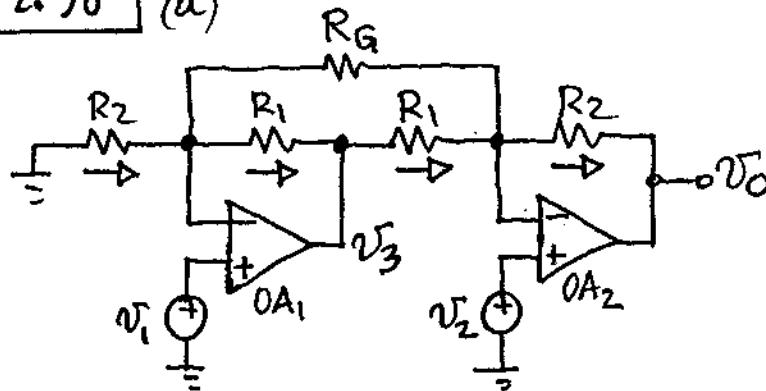

$V_{N1} = V_{P1} = V_1$ ,  $V_{N2} = V_{P2} = V_2$ . Applying KCL:

$$\frac{V_0 - V_1}{R_2} = \frac{V_1 - V_2}{R_G} + \frac{V_1 - V_3}{R_1}; \quad \frac{V_2 - V_0}{R_2} = \frac{V_1 - V_2}{R_G} + \frac{V_3 - V_2}{R_1}.$$

Adding the two equations pairwise gives

$$\frac{V_2 - V_1}{R_2} - \frac{V_0}{R_2} = 2 \frac{V_1 - V_2}{R_G} + \frac{V_1 - V_2}{R_1}. \text{ Solving}$$

for  $V_0$  yields  $V_0 = \left(1 + \frac{R_2}{R_1} + 2 \frac{R_2}{R_G}\right)(V_2 - V_1)$ .

(b) Let  $R_G = R_{GA} + R_{GB}$ , where  $R_{GA} = 10\text{k}\Omega$  pot. Arbitrarily impose  $R_2/R_1 = 1$ , so that  $A = 2(1 + R_2/R_G)$ .  $10 \leq A \leq 100 \Rightarrow$

$$5 \leq (1 + R_2/R_G) \leq 50 \Rightarrow 4 \leq R_2/R_G \leq 49.$$

$R_G = 0 + R_{GB} \Rightarrow R_2/R_{GB} = 49$ ;  $R_G = 10 + R_{GB} \Rightarrow R_2/(10 + R_{GB}) = 4$ . Solving,  $R_{GB} = 889\Omega$  (use  $887\Omega$ , 1%);  $R_2 = 49 R_{GB} = 43.5\text{k}\Omega = R_1$  (use  $R_1 = R_2 = 43.2\text{k}\Omega$ , 1%).

2.20

**2.39** (a) The op amps keeps  $V_{P1} = V_{N1} = V_1$ ,  $V_{N2} = V_{P2} = V_2$ . Let  $V_3$  be the output of OA<sub>2</sub>.

Summing currents at  $V_{P1}$  and  $V_{N2}$  gives

$$\frac{V_0 - V_2}{R} + \frac{V_1 - V_2}{R_G} + \frac{V_3 - V_2}{R} = 0$$

$$\frac{V_3 - V_1}{R} + \frac{V_2 - V_1}{R_G} + \frac{0 - V_1}{R} = 0$$

Eliminating  $V_3$  and collecting gives

$$V_0 = 2 \left( 1 + \frac{R}{R_G} \right) (V_2 - V_1)$$

(b) Let  $R_G$  be a 10-kΩ pot in series with a resistance  $R_s$ . Then,

$$2 \left( 1 + \frac{R}{R_s} \right) = 100 \Rightarrow R = 49 R_s$$

$$2 \left( 1 + \frac{R}{10 + R_s} \right) = 10 \Rightarrow R = 4(10 + R_s). \text{ Solving,}$$


$R_s = 888 \Omega$  (use 887 Ω, 1%),  $R = 43.5 \text{ k}\Omega$  (use 43.2 kΩ, 1%).

**2.40** Regard the capacitor as an open circuit in dc analysis. By op amp action,  $V_{P1} = V_{N1} = V_1$ ,  $V_{N2} = V_{P2} = V_2$ . Moreover, the output of OA<sub>2</sub> is  $V_3 = (1 + R_1/R_2)V_1 = -\frac{R_1}{R_2}V_0 + \left( 1 + \frac{R_1}{R_2} \right) V_2$ .

Thus,  $V_0 = \left( 1 + \frac{R_2}{R_1} \right) (V_2 - V_1)$ .

2.21

2.41

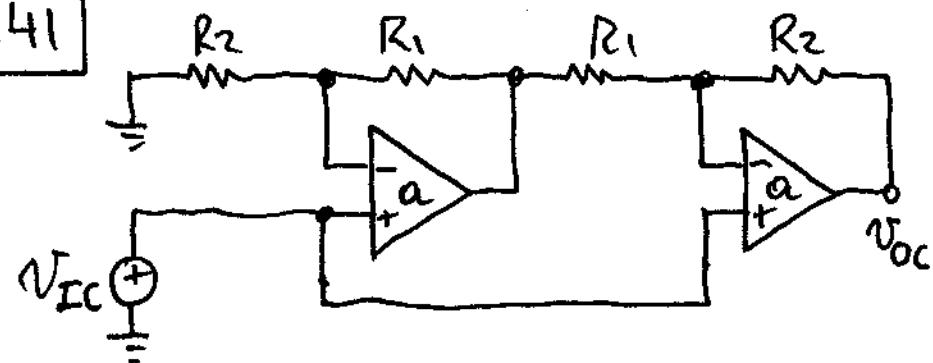

$$A = 1 + R_2/R_1 \Rightarrow R_2/R_1 = A - 1, R_1/R_2 = 1/(A-1)$$

$$V_1 = \frac{1 + R_1/R_2}{1 + \frac{1 + R_1/R_2}{a}} V_{IC} = \frac{A}{A - 1 + A/a} V_{IC}$$

$$V_{OC} = \frac{1}{1 + \frac{1 + R_2/R_1}{a}} \left[ \left( 1 + \frac{R_2}{R_1} \right) V_{IC} - \frac{R_2}{R_1} V_1 \right]$$

$$= \frac{A}{1 + A/a} \left[ 1 - \frac{A-1}{A-1+A/a} \right] V_{IC}$$

$$= \frac{A}{A(1+1/a) + a(1-1/A)} V_{IC} = A_{cm} V_{IC}$$

$$CMRR = \frac{A}{A_{cm}} = a \left( 1 - \frac{1}{A} \right) + A \left( 1 + \frac{1}{a} \right) \approx \frac{A-1}{A} a$$

Since in general  $A \ll a$ . We readily see that for sufficiently large gains, or  $A \gg 1$ , we have  $CMRR \approx a$ , regardless of  $A$ .

$$A = 10^3 V/V \Rightarrow CMRR_{dB} = \left| \frac{999}{1000} 10^5 \right|_{dB} = 99.99 \text{ dB}$$


$$A = 10 V/V \Rightarrow CMRR_{dB} = \left| \frac{9}{10} 10^5 \right|_{dB} = 99.08 \text{ dB},$$

indicating an insignificant change.

2.22

2.42

When the "1000" switches are closed,

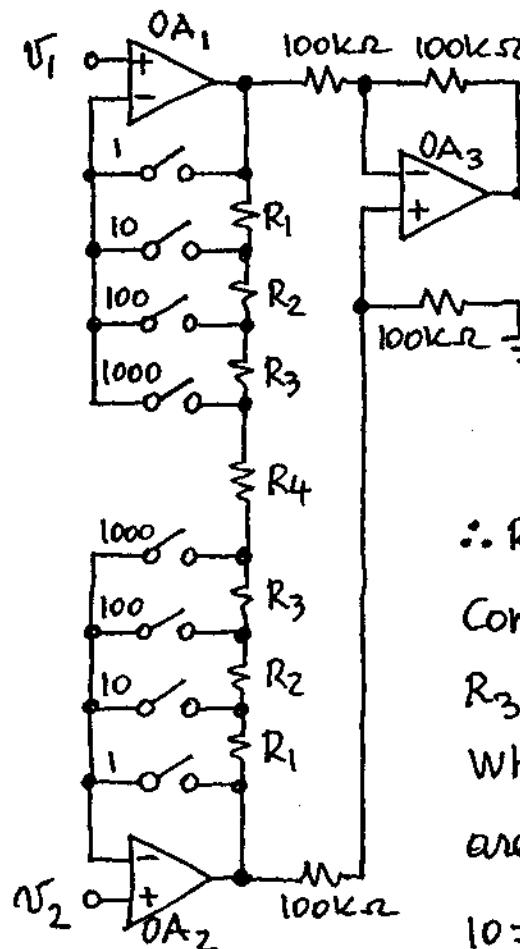

$$1000 = 1 + 2 \frac{R_1 + R_2 + R_3}{1}$$

$$\therefore R_1 + R_2 + R_3 = 499.5 \text{ k}\Omega.$$

When the "100"  
switches are closed,

$$100 = 1 + 2 \frac{R_1 + R_2}{2R_3 + 1}.$$

$$\therefore R_1 + R_2 = 99R_3 + 49.5 \text{ k}\Omega.$$

Combining yields

$$R_3 = 4.5 \text{ k}\Omega.$$


When the "10" switches  
are closed,

$$10 = 1 + 2 \frac{R_1}{2R_2 + 2R_3 + 1}.$$

$\therefore R_1 = 9R_2 + 45 \text{ k}\Omega$ . Combining yields  
 $R_2 = 45 \text{ k}\Omega$  and  $R_1 = 450 \text{ k}\Omega$ . Summarizing,  
 $R_1 = 450 \text{ k}\Omega$ ,  $R_2 = 45 \text{ k}\Omega$ ,  $R_3 = 4.5 \text{ k}\Omega$ ,  $R_4 = 1 \text{ k}\Omega$ .  
All other resistors =  $100 \text{ k}\Omega$ .

2.43

2.13

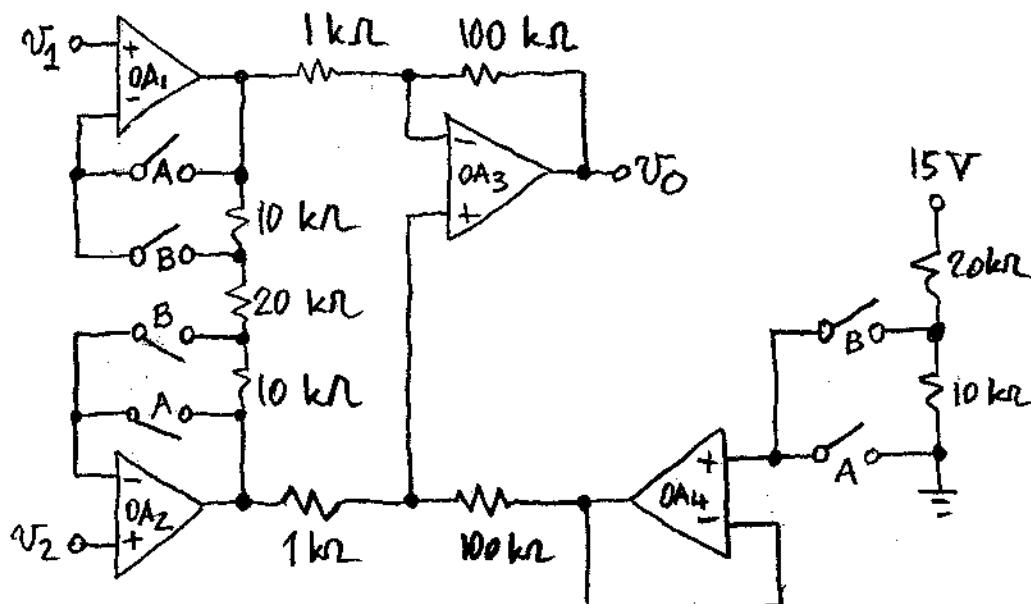

"A" switches closed  $\Rightarrow V_0 = 1 \times 100(V_2 - V_1) + 0 \text{ V}.$

"B" switches closed  $\Rightarrow V_0 = (1 + 2 \frac{10}{20}) \times 100(V_2 - V_1) + 5 \text{ V}.$

2.44 (a) Let the outputs of OA<sub>1</sub> and OA<sub>2</sub> be  $V_{O1}$  and  $V_{O2}$ . Superposition:

$$V_{O1} = \left(1 + \frac{R_1}{R_3}\right)V_1 - \frac{R_1}{R_3}V_L$$

$$V_{O2} = \left(1 + \frac{R_5}{R_4}\right)V_2 - \frac{R_5}{R_4} \left[\left(1 + \frac{R_1}{R_3}\right)V_1 - \frac{R_1}{R_3}V_L\right]$$

$$\text{KCL: } i_0 = \frac{V_1 - V_L}{R_3} + \frac{V_{O2} - V_L}{R_2}. \text{ Eliminating } V_{O2},$$

$$i_0 = \frac{V_2}{R_2} \left[1 + \frac{R_5}{R_4}\right] - \frac{V_1}{R_2} \left[\frac{R_5}{R_4} \left(1 + \frac{R_1}{R_3}\right) - \frac{R_2}{R_3}\right] - V_L \times$$

$$\frac{R_2 + R_3 - R_1 R_5 / R_4}{R_2 R_3}. \text{ It is readily seen that}$$

imposing  $R_2 + R_3 = R_1 R_5 / R_4$  gives

$$i_0 = \frac{1}{R}(V_2 - V_1), \quad \frac{1}{R} = \frac{1 + R_5 / R_4}{R_2}.$$

(b) Use  $R_1 = R_4 = R_5 = 100 \text{ k}\Omega$ ,  $R_2 = 2.00$ .


$kR$ , and  $R_3 = 100 - 2 = 98.0 \text{ k}\Omega$ .

(2.24)

(c) If the resistances are mismatched, the gains with which the circuit processes  $v_1$  and  $v_2$  will also be mismatched. Moreover,  $R_0 \neq 0$ .  $R_0$  is minimized when  $R_2, R_3$ , and  $R_4$  are maximized,  $R_1$  and  $R_5$  are minimized.

$$R_0(\min) \cong \frac{2 \times 10^3 \times 98 \times 10^3}{10^5 \times 1.001 - (10^5 \times 0.999)^2 / (10^5 \times 1.001)} \\ = 490 \text{ k}\Omega.$$

2.45

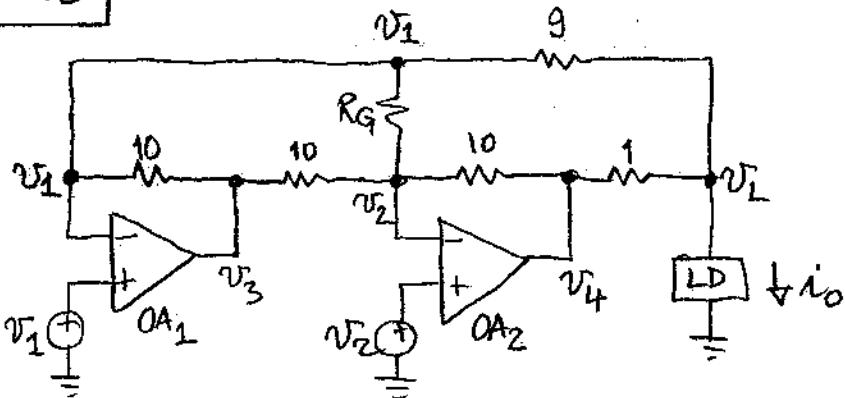

Summing currents at the inverting inputs of the op amps,

$$\frac{v_L - v_1}{9} + \frac{v_2 - v_1}{R_G} + \frac{v_3 - v_1}{10} = 0$$

$$\frac{v_1 - v_2}{R_G} + \frac{v_3 - v_2}{10} + \frac{v_4 - v_2}{10} = 0$$

Solving for  $v_4$  gives


$$v_4 = \frac{10}{9}v_L + v_2\left(\frac{20}{R_G} + 2\right) - v_1\left(\frac{20}{R_G} + \frac{19}{9}\right). \text{ KCL:}$$

$$i_O = \frac{v_1 - v_L}{9} + \frac{v_4 - v_L}{1}. \text{ Substituting } v_4 \text{ gives}$$

$$i_O = 2\left(1 + \frac{10}{R_G}\right)(v_2 - v_1).$$

2.25

2.46

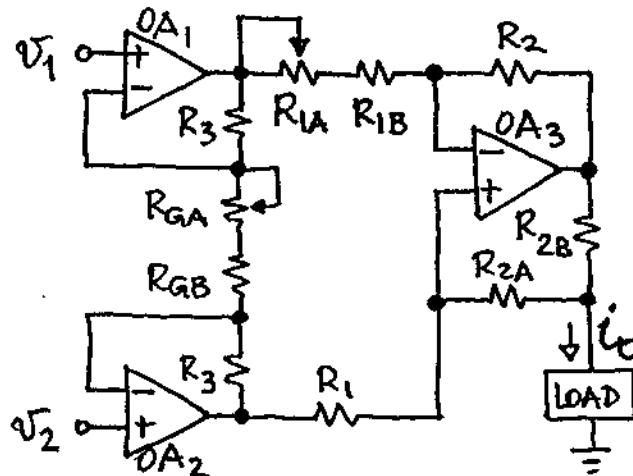(a)  $1/R = A_1/R_1, A_1 = 1 + 2R_3/R_G$ . Since

$1/R$  must vary over a  $100 : 1$  range and since  $A_1 > 1$ , impose  $2 \leq A_1 \leq 200$ . Then,

$$200 = 1 + 2 \frac{R_3}{R + R_{GB}},$$

$$2 = 1 + 2 \frac{R_3}{100 + R_{GB}}. \text{ Solving yields}$$

$$R_3 = 50.25 \text{ k}\Omega \text{ (use } 49.9 \text{ k}\Omega\text{), and}$$

$$R_{GB} = 0.505 \text{ k}\Omega \text{ (use } 499 \text{ }\Omega\text{). When } A_1 = 2 \text{ we want } 1/R = 2/R_1 = 1 \text{ mA/V} \Rightarrow R_1 = 2 \text{ k}\Omega.$$

Use the improved Howland circuit with  $R_1 = R_2 = 100 \text{ k}\Omega$  and  $R_{2B} = 2 \text{ k}\Omega$ . Then,

$$R_{2A} = 100 - 2 = 98 \text{ k}\Omega \text{ (use } 97.6 \text{ k}\Omega\text{). Now}$$

4% of  $100 \text{ k}\Omega$  is  $4 \text{ k}\Omega$ . Use  $R_{1A} = 10 \text{ k}\Omega$

to be on the safe side, and  $R_{1B} = 95.3 \text{ k}\Omega$ .

Summarizing,  $R_1 = R_2 = 100 \text{ k}\Omega$ ,

$R_{1A} = 10 \text{ k}\Omega$  pot,  $R_{1B} = 95.3 \text{ k}\Omega$ ,  $R_{2A} = 97.6$

$\text{k}\Omega$ ,  $R_{2B} = 2.00 \text{ k}\Omega$ ,  $R_3 = 49.9 \text{ k}\Omega$ ,  $R_{GA} =$


$100 \text{ k}\Omega$  pot,  $R_{GB} = 499 \text{ }\Omega$ .

(b) Let  $V_1 = V_2 = 0V$  and adjust  $R_{1A}$  as in Fig. 2.9.

2.26

**2.47** With reference to Fig. 2.34, we want

$2R_2R_3/R_1 = 10 \text{ V/mA} = 10 \text{ k}\Omega$ . Let  $R_1 = R_2 = 10.0 \text{ k}\Omega$ . Then,  $R_3 = 10/2 = 5 \text{ k}\Omega$  (inc 4.99 k $\Omega$ , 1%). Moreover,  $R_4 = 4.99 \text{ k}\Omega$ , 1%.

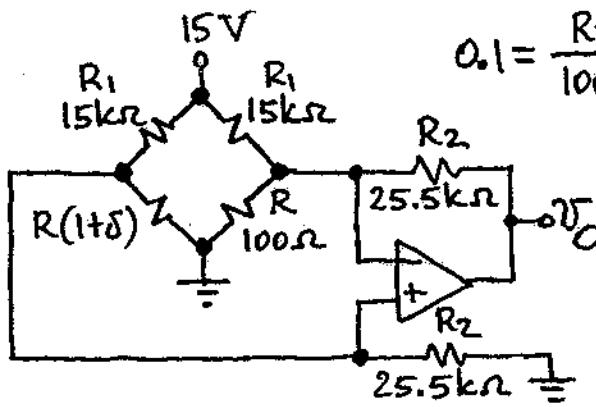**2.48**(a) Let  $R_1 = 15 \text{ k}\Omega$ . Then,

$$0.1 = \frac{R_2}{100} \cdot 15 \cdot \frac{0.00392}{1 + \frac{15,000}{100} + \frac{15,000}{R_2}}$$

This yields  $R_2 = 170.7 \left( 151 + \frac{15000}{R_2} \right)$ . Starting out with  $R_2 = 10 \text{ k}\Omega$

and solving by iteration yields  $R_2 = 25.8 \text{ k}\Omega$ .

$$(b) V_O = \frac{25.5}{0.1} \cdot 15 \cdot \frac{0.392}{\frac{15}{0.1} + \left( 1 + \frac{15}{25.5} \right) \left( 1 + 0.392 \right)} =$$

9.96V, which corresponds to a 0.4°C error.

**2.49** (a) KCL at the op amp input nodes:

$$\frac{V_{REF} - V_N}{R_1} = \frac{V_N}{R_2} + \frac{V_N - V_O}{R_2} \quad \text{and} \quad \frac{V_{REF} - V_P}{R_1} = \frac{V_P}{R(1+\delta)} + \frac{V_O}{R_2}$$

Letting  $V_N = V_P$  and solving for  $V_O$  yields  $V_O = (R_2/R) [\delta/(1+\delta)] V_P$ . Voltage divider:

$$\frac{V_P}{V_{REF}} = \frac{[R(1+\delta)] // R_2}{[R(1+\delta)] // R_2 + R_1} = \frac{1}{1 + \frac{R_1}{[R(1+\delta)] // R_2}} =$$

$$\frac{1}{1 + R_1 \frac{R(1+\delta) + R_2}{R(1+\delta)R_2}} = \frac{1}{1 + \frac{R_1}{R_2} \left( 1 + \frac{R_2}{R} \frac{1}{1+\delta} \right)} =$$

2.27

$\frac{1+\delta}{1+\delta\left(1+\frac{R_1}{R_2}\right)+\frac{R_1}{R}} \cdot$  Eliminating  $V_P$  yields

$$V_O = \frac{R_2}{R} V_{REF} \frac{\delta}{\frac{R_1}{R} + \left(1 + \frac{R_1}{R_2}\right)(1+\delta)};$$

$$\lim_{\delta \rightarrow 0} V_O = \frac{R_2}{R} V_{REF} \frac{\delta}{1 + R_1/R + R_1/R_2}.$$

(b) The output of OA<sub>1</sub> is  $V_I = -\frac{R(1+\delta)}{R_1} V_{REF}$ .

Superposition:  $V_O = -(R_2/R)V_I - (R_2/R_1)V_{REF}$ .

Eliminating  $V_I$ ,  $V_O = (R_2/R_1)V_{REF}\delta$ .

2.50

Impose 1mA through each side of the bridge. Thus,  $R_1 = 2.5/2 = 1.25\text{ k}\Omega$ . Let  $R_2 = 30\text{ k}\Omega$  and  $R = 100\Omega$ , both 1%. Then,

$$0.1 = A \frac{100}{2 \times 1250} 2.5 \times 0.00392 \Rightarrow A = 255 \text{ V/V.}$$

2.51

(a) Let  $i_{RTD} = 1\text{ mA}$ , so  $R_1 = 15\text{ k}\Omega$ . Then,

$$0.1 = \frac{R_2}{15,000} 15 \times 0.00392 \Rightarrow R_2 = 25.5\text{ k}\Omega.$$

(b) Use the same topology, components, and calibration procedure as in Example 2.13.

2.52


Since  $V_N = V_P$ , it follows that the two legs of the bridge must conduct identical currents,

$$\frac{V_{REF} - V_O}{R_1 + R(1+\delta)} = \frac{V_{REF}}{R_1 + R}. \text{ Thus, } V_O = -\frac{R}{R_1 + R} V_{REF}\delta.$$

2.28

The disadvantage is very low sensitivity, thus requiring an additional gain stage.

2.53

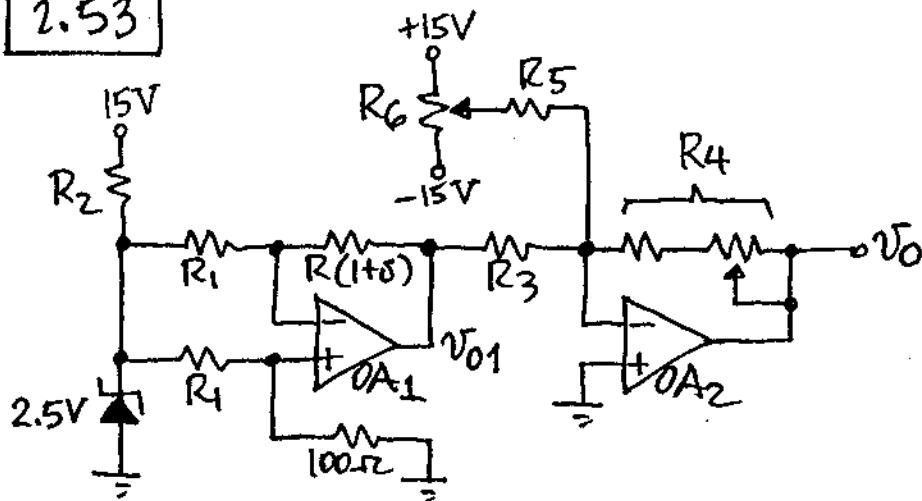

Let  $R_1 = 2.49\text{ k}\Omega$ . Then,  $\Delta T = 1^\circ\text{C} \Rightarrow \Delta V_{01} = [100/(100+2490)] \times 2.5 \times 0.00392 = 378.38\text{ }\mu\text{V}$ .  
 $\Delta V_0 = (R_4/R_3) \Delta V_{01} = 0.1\text{ V} \Rightarrow R_4/R_3 = 264.3$ .  
 Use  $R_3 = 1\text{ k}\Omega$ ,  $R_4 = 237\text{ k}\Omega$  in series with a  $50\text{-k}\Omega$  pot. Let  $R_5 = 3.3\text{ M}\Omega$ ,  $R_6 = 100\text{-k}\Omega$  pot,  $R_2 = 3.9\text{ k}\Omega$ . To calibrate:  
 With  $T = 0^\circ\text{C}$ , adjust  $R_6$  for  $V_0 = 0\text{ V}$ .  
 With  $T = 100^\circ\text{C}$ , adjust  $R_4$  for  $V_0 = 10.0\text{ V}$ .

2.54

$$v_{N1} = v_{P1} = v_{N2} = v_{P2} = 0\text{ V.}$$

$$v_{01} = -[R(1+\delta)/R_1] v_{REF}. \quad v_0 = -R_2 [V_{REF}/R_1 + v_0/R] = -R_2 \{V_{REF}/R_1 - [(1+\delta)/R_1] V_{REF}\}, \text{ i.e. } v_0 = (R_2/R_1) V_{REF} \delta.$$