

8.1

$$\boxed{8.1} \quad \angle T = -[\tan^{-1}(f/10^5) + \tan^{-1}(f/2 \times 10^6)];$$

$$|T| = 10^3 / \sqrt{[1 + (f/10^5)^2] \times [1 + (f/2 \times 10^6)^2]}.$$

Trial-and-error: $f_x = 14.07 \text{ MHz}$; $\angle T(jf_x) = 171.5^\circ$; $\phi_m = 8.5^\circ$; $\cos \phi_m = \sqrt{4\zeta^2 + 1} - 2\zeta^2 \Rightarrow$
 $\zeta = 0.0743$; $Q = 1/2\zeta = 6.74$; $GP = 16.58 \text{ dB}$;
 $OS = 79\%$; $A = 1/(1 + 1/T) = 1/[1 + 10^{-3} \times (1 + jf/f_1)(1 + jf/f_2)] = 10^3 / [1 + 10^3 + jf(\frac{1}{f_1} + \frac{1}{f_2}) - \frac{f^2}{f_1 f_2}]$

$$A \approx \frac{10^3}{10^3 + 1} \frac{1}{1 - f^2/(1001 f_1 f_2) + jf(1/f_1 + 1/f_2)/1001}$$

$$= 0.999 \frac{1}{1 - \left(\frac{f}{14.15 \times 10^6}\right)^2 + \frac{jf}{14.15 \times 10^6} / 6.74}$$

$$\boxed{8.2} \quad T = T_0 / [1 + jf/f_1]^3, \quad T_0 = a_0 \beta. \quad \text{Imposing } 180^\circ = 3 \tan^{-1}(f_{-180^\circ}/f_1) \text{ gives } f_{-180^\circ} = 1.732 f_1.$$

$$\angle T(jf_{-180^\circ}) = \frac{-T_0}{(1 + 1.732^2)^{3/2}} = \frac{-T_0}{8}.$$

$$\boxed{8.3} \quad (a) \quad \angle T = -\tan^{-1}\left(\frac{f}{10^5}\right) - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{2 \times 10^6}\right)$$

$$|T| = \frac{10^2}{\sqrt{[1 + (f/10^5)^2][1 + (f/10^6)^2][1 + (f/2 \times 10^6)^2]}}$$

By trial and error it is found that $|T|=1$ for $f = f_x = 2.42 \text{ MHz}$, and that $\angle T(jf_x) =$

8.2

-205.6°, so that $\phi_m = -25.6^\circ$, an unstable system.

(b) By trial and error it is found that $\angle T = -135^\circ$ for $f = f_{-135^\circ} = 685 \text{ kHz}$, and that $|T(jf_{-135^\circ})| = T_0/8.87$. Imposing $|T(jf_{-135^\circ})| = 1$ yields $T_{0(\text{new})} = 8.87$.

$$(c) \angle T = -\tan^{-1}\left(\frac{f}{f_1}\right) - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{2 \times 10^6}\right)$$

$$|T| = \frac{10^2}{\sqrt{[1 + (f/f_1)^2][1 + (f/10^6)^2][1 + (f/(2 \times 10^6))^2]}}$$

Using Bode-plot reasoning, we find, as initial guess, $f_1 = f_2/T_0 = 10^6/10^2 = 10 \text{ kHz}$.

For this value of f_1 , it is found that $f_x = 750 \text{ kHz}$ and $\phi_m = 33.3^\circ$, which is a bit too low. Retry with a lower value of f_1 . Eventually it is found that $f_1 = 6.8 \text{ kHz}$ yields $f_x = 570 \text{ kHz}$ and $\phi_m = 45^\circ$.

$$(d) f_{-120^\circ} = 508 \text{ kHz}; T_0 = 6.0.$$

$$f_1 = 4.0 \text{ kHz}, f_x = 369^\circ, \angle T = -120^\circ.$$

8.4

(a) $\phi_m \geq 45^\circ$ for $f \leq 1.33 \text{ kHz}$ and $f \geq 7.65 \text{ kHz}$. Since $|a(j1.33 \text{ kHz})| \approx 456 \text{ V/V}$ and $|a(j7.65 \text{ kHz})| \approx 21.3 \text{ V/V}$, the permis-

8.3

stable ranges for β are $\beta \leq 1/456 \text{ V/V}$ and $\beta \geq 1/21.3 \text{ V/V}$.

(b) $f \leq 694 \text{ Hz}$ and $f \geq 14.9 \text{ kHz}$;

$\beta \leq 1/1187 \text{ V/V}$ and $\beta \geq 1/8.06 \text{ V/V}$.

(c) $f = 3.16 \text{ kHz}$, $\phi_m(\text{min}) \approx 35^\circ$.

Problem 8.4

Vi 1 0 ac 1

R1 1 0 1

eHn 2 0 Laplace {V(1,0)}={1.0E5*(1+s/62830)}

R2 2 0 1


eHd 3 0 Laplace {V(2,0)}={1/((1+s/62.83)*(1+s/6283))}

R3 3 0 1

.ac dec 10 1 100k

.probe

.end

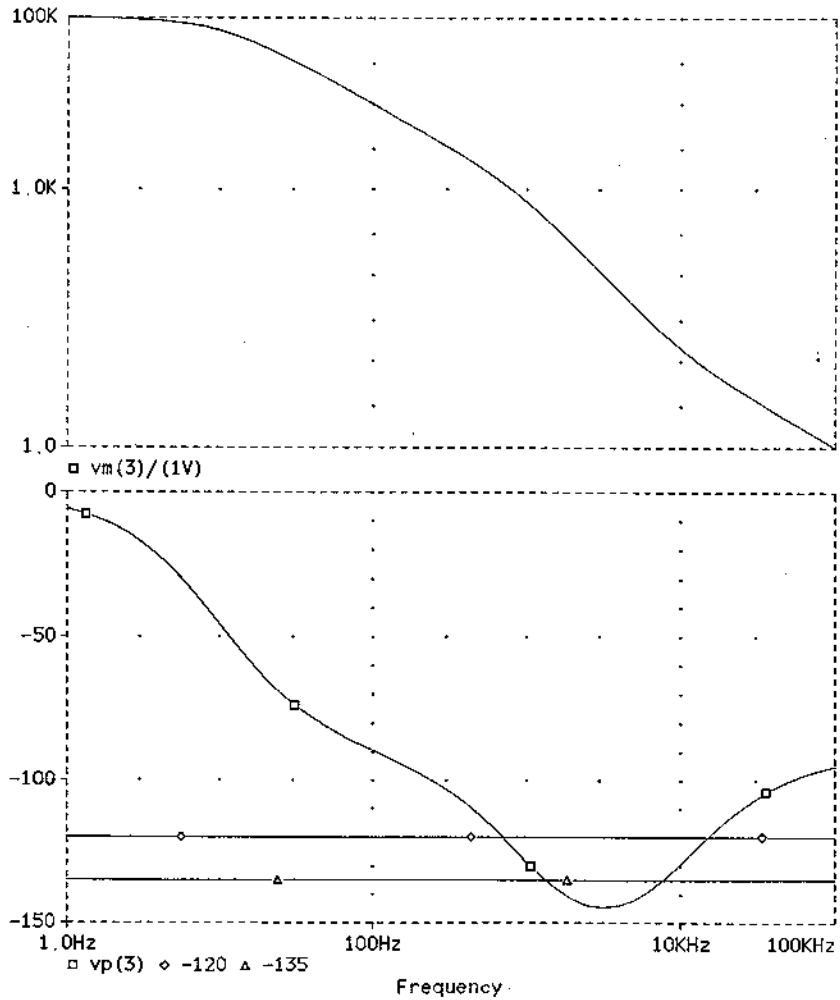

8.4

8.5 System 1: Error Function = $1/(1+1/T) = 1/(1+1/10) = 1.11/10^0$. System 2: Error

8.5

exhibits an overall phase shift of 270° , the same as a three-pole function.

Problem 8.7

*LHP zero

Vi 1 0 ac 1V

Ri 1 0 1

e1 2 0 Laplace {V(1,0)}={1+s/6283}

R1 2 0 1

e2 3 0 Laplace {V(2,0)}={1/((1+s/62.83)*(1+s/628.3))}

R2 3 0 1

.ac dec 10 1 100k

.probe

.end

Problem 8.7

*RHP zero

Vi 1 0 ac 1V

Ri 1 0 1

e1 2 0 Laplace {V(1,0)}={1-s/6283}

R1 2 0 1


e2 3 0 Laplace {V(2,0)}={1/((1+s/62.83)*(1+s/628.3))}

R2 3 0 1


.ac dec 10 1 100k

.probe

.end

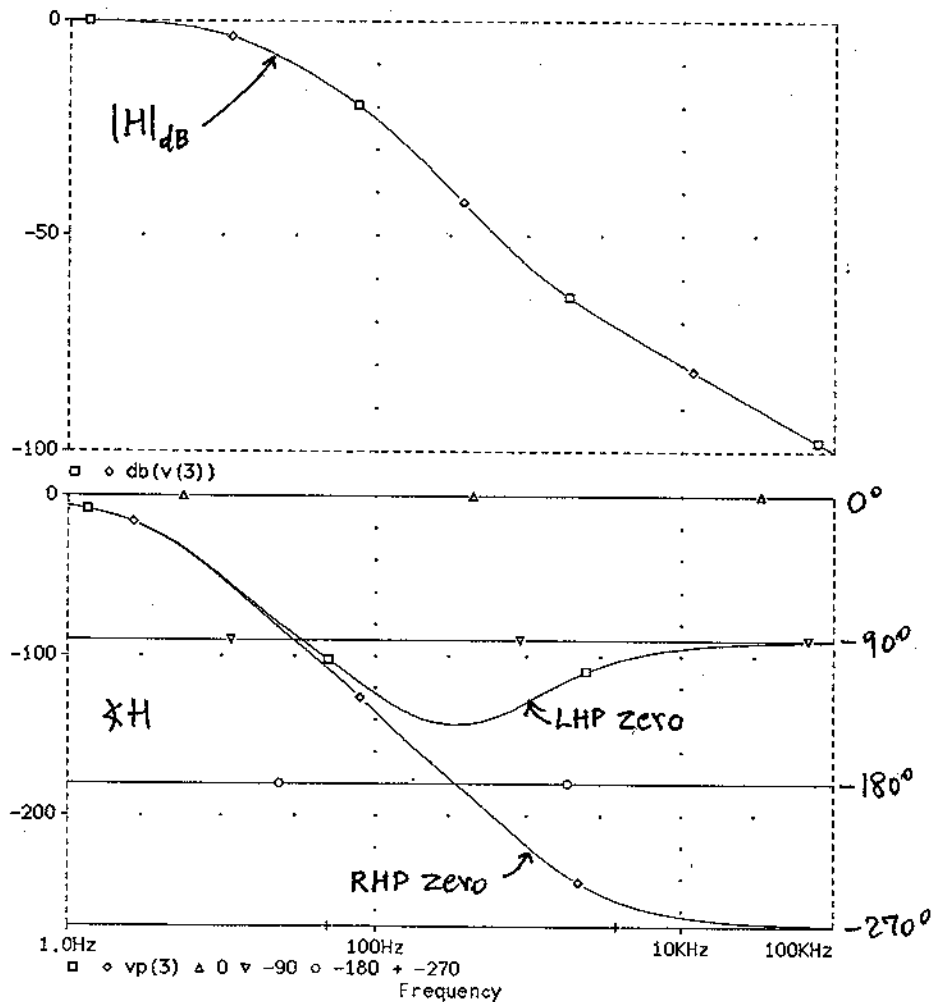

8.6

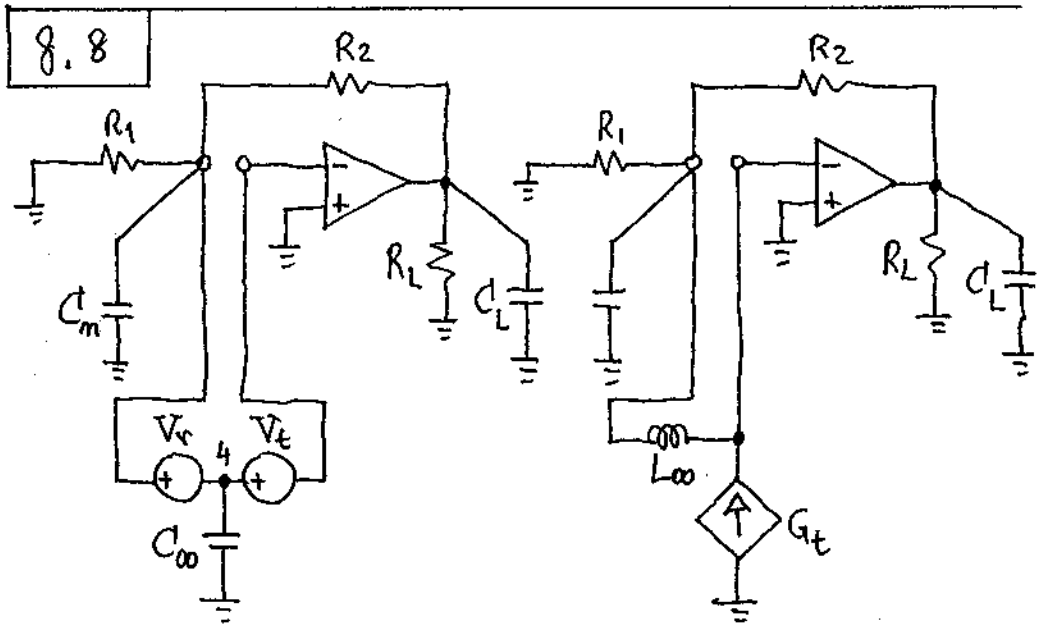

Problem 8.8

.lib eval.lib

VCC 10 0 dc 15V

VEE 11 0 dc -15V

*Circuit to find Tsc:

R1sc 0 2 100k

R2sc 2 1 100k

Cnsc 2 0 5pF

RLsc 1 0 2k

CLsc 1 0 100pF

XOAsc 0 3 10 11 1 ua741

Vr 2 4 dc 0V

Vt 4 3 ac 1V

C00 4 0 0.1kF

*Circuit to find Toc:

R1oc 0 6 100k

R2oc 6 5 100k

Cnoc 6 0 5pF

RLoc 5 0 2k

CLoc 5 0 100pF

XOAoc 0 7 10 11 5 ua741

L00 6 7 1MegH


Gt 0 7 4 3 1u

.ac dec 10 1 10MegHz


.probe ;Tsc = I(Vr)/I(Vt), Toc = V(6)/V(7)

.end

8.7

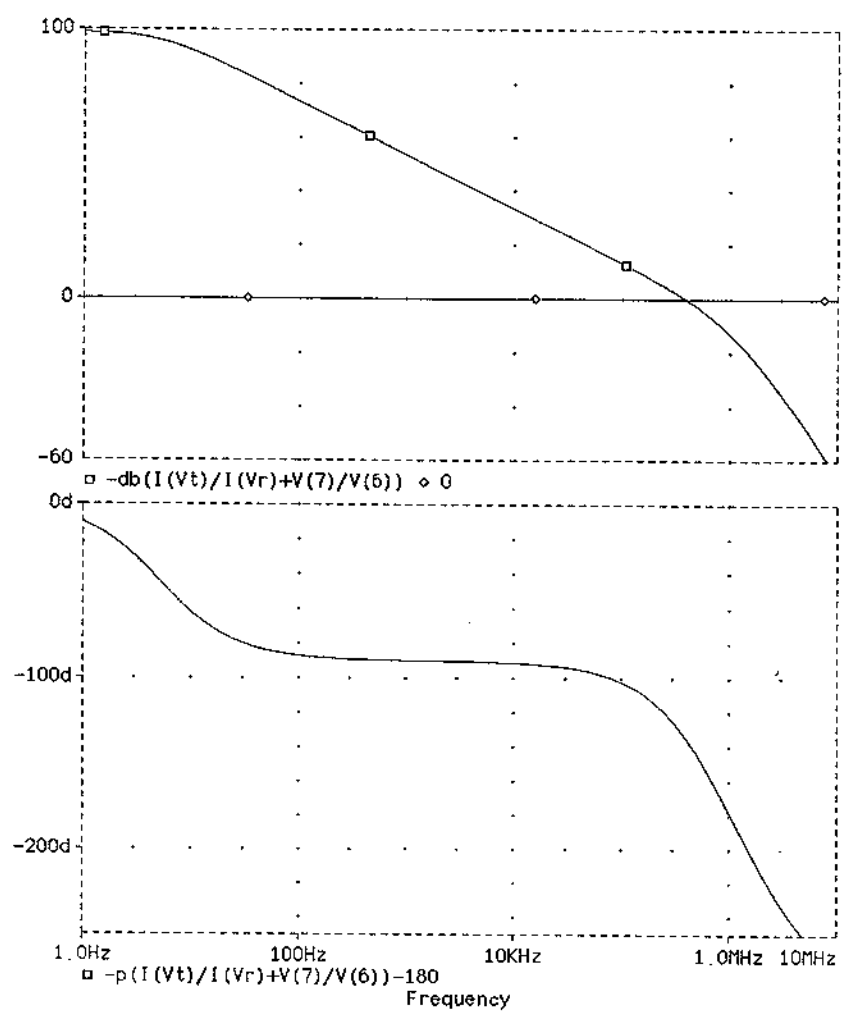

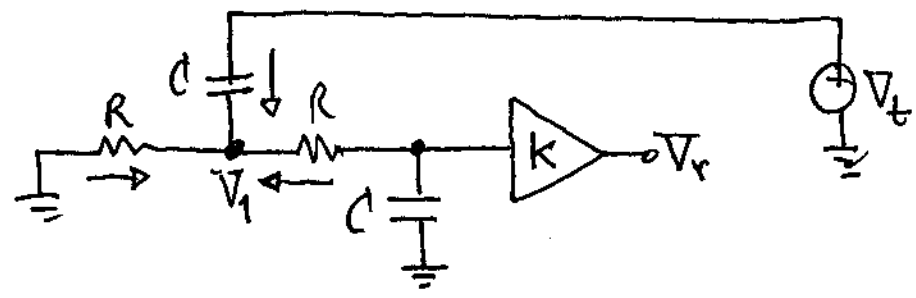8.9 Suppress the input, break the loop at the op amp's output, and inject a test signal V_t :



The return signal is $V_r = K \frac{1}{1+sRC} V_1$. KCL:

$$\frac{0-V_1}{R} + (V_t-V_1)sc + \frac{V_r/K - V_1}{R} = 0$$

8.8

Eliminating V_i we get

$$T = \frac{V_r}{V_t} = \frac{-KsRC}{1 + (sRC)^2 + 3sRC}$$

Letting $s \rightarrow j2\pi f$, $RC \rightarrow 1/(2\pi 10^3)$, $K \rightarrow 2.8$,

$$T = \frac{-2.8 j f / 10^3}{1 - (f/10^3)^2 + 3 j f / 10^3}$$

We observe that $|T|$ is maximized for $f = 10^3$ Hz, where we have $T(j10^3) = -2.8/3$, or

$T = \frac{2.8}{3} \angle -180^\circ$. The circuit has therefore a gain margin of $20 \log(3/2.8) = 0.6$ dB.

8.10 (a) For $f \gg 10$ Hz we can approximate

$$\pi = a\beta = a \approx \frac{10^6}{j f (1 + j f / 10^6)}$$
 By trial-and-error

as in Example 8.1 we find that $|\pi| = 1$ for $f = f_x = 786$ MHz, where $\angle \pi = -128.2^\circ$. Thus, $\phi_m = 51.8^\circ$.

(b) We now have $\pi \approx \frac{10^6}{j f (1 + j f / 10^6)}$. Since

$f_c > 10^6$ Hz. Try $f_c =$

840 kHz and $\phi_m =$

?. We thus need to try

$60^\circ > 51.8^\circ$, we must have

1.3 MHz. This gives $f_x =$

57.1° , which is too small

8.9

a higher value for f_2 . After a few more attempts we find that for $\phi_m = 60^\circ$ we need $f_2 = 1.5 \text{ MHz}$. Moreover, $f_x = 866 \text{ kHz}$.

(c) Since $45^\circ < 51.8^\circ$, we need $f_2 < 1 \text{ MHz}$. By a similar trial-and-error technique we find $f_2 = 1/\sqrt{2} \text{ MHz}$ and $f_x = f_2 = 707 \text{ kHz}$.


8.11 $T = a\beta = \frac{10^5 \beta_0}{(1+jf/10)(1+jf/10^5)^2}$

(a) $\angle T = -[\tan^{-1}(f/10) + 2 \tan^{-1}(f/10^5)]$; $\angle T = -180^\circ$ for $f = f_{-180^\circ} = 100 \text{ kHz}$, where $|T| = 5\beta_0$. The onset of oscillation occurs for $\beta_0 = 1/5 = 0.2 \text{ V/V}$.

(b) $f_{-135^\circ} = 41.4 \text{ kHz}$, $|T(j 41.4 \text{ kHz})| = 20.6\beta_0$, $\beta_0 = 1/20.6 \text{ V/V}$.

(c) $f_{-120^\circ} = 26.8 \text{ kHz}$, $\beta = 1/34.8 \text{ V/V}$.

8.12

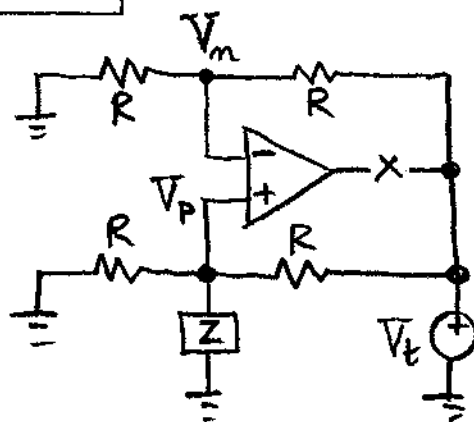

$$\begin{aligned} \beta &= (V_m - V_p) / V_t \\ &= \frac{1}{2} - \frac{Z \parallel R}{Z \parallel R + R} \\ &= \frac{1}{2} \frac{1}{1 + 2Z/R}; \\ \frac{1}{\beta} &= 2(1 + 2Z/R). \end{aligned}$$




$Z = R_L \Rightarrow 1/\beta > 2$, $1/\beta$ frequency-independent
 \Rightarrow stable circuit with $f_x < f_t/2$.

$Z = C_L \Rightarrow 1/\beta = 2(1 + 2/sRC) = 2[1 + 1/(j\omega/\omega_0)]$,

8.10

$f_0 = 1/\pi RC$. $1/\beta_{\infty} \rightarrow 2 V/V \Rightarrow$ stable circuit with $f_x = f_0/2$.

$Z = L_L \Rightarrow 1/\beta = 2(1 + 2sL/R) = 2(1 + jf/f_0)$, $f_0 = R/4\pi L$. Since $1/\beta$ has a zero frequency at f_0 , the $|1/\beta|$ curve bends upward and invites instability.

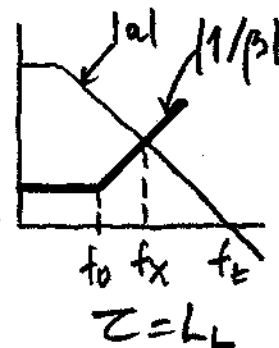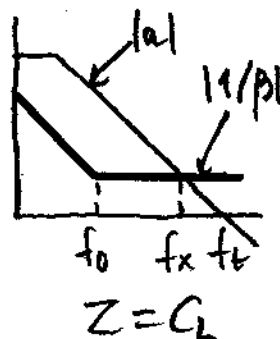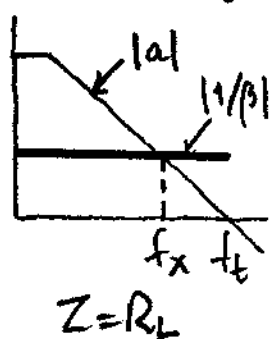

Compensate by placing a resistance R_s in series with L_L so that at high frequencies the $|1/\beta|$ curve flattens out to $|1/\beta_{\infty}| = 2 \times (1 + 2R_s/R)$.

8.13 With R_s in place we have

$$\frac{1}{\beta} = 1 + \frac{R}{R_s + 1/sC} = \frac{1 + jf/f_z}{1 + jf/f_p}, \quad f_z = \frac{1}{2\pi(R + R_s)C}, \quad f_p =$$

$1/2\pi R_s C$. Since we expect $R_s \ll R$, it follows that $f_z \cong f_0 = 100 \text{ Hz}$, so we can write

$$\pi = a\beta \cong \frac{10^6}{j f} \frac{1 + jf/f_0}{1 + jf/100}. \quad \text{Since } 60^\circ > 45^\circ, \text{ we}$$

expect $f_p < 10 \text{ kHz}$. Start out with the estimate $f_p = 8 \text{ kHz}$, and then use the trial-and-error technique to find f_x and ϕ_m . This

8.11


gives $f_x = 14.3 \text{ kHz}$ and $\phi_m \cong 61^\circ$, which is close enough without warranting further trials. So, $R_s = 1/(2\pi \times 8 \times 10^3 \times 10 \times 10^{-9}) \cong 2.0 \text{ k}\Omega$. The Xfer function is $H = H_{ideal} / (1 + 1/T) = (j \frac{f}{f_0}) / (1 + 1/T)$,

$$\frac{1}{1 + 1/T} \cong \frac{1}{1 + \frac{j f (1 + j f / 100)}{10^6 (1 + j f / 8,000)}} \cong \frac{1 + j f / 8,000}{1 - (\frac{f}{10^4})^2 + (j \frac{f}{10^4}) / 0.8}$$

$\therefore Q \cong 0.8$

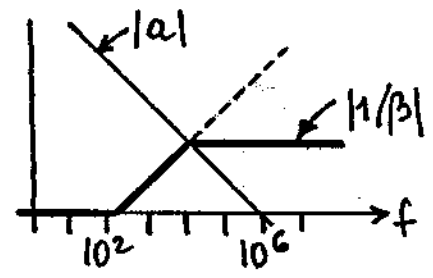8.14

$$f_0 = 1 / (2\pi \times 78.7 \times 10^3 \times 10^{-8}) \cong 200 \text{ Hz.}$$




Eq. (8.14 b): $f_x = (200 \times 10^6)^{1/2} = 14.1 \text{ kHz.}$

For $\phi_m = 45^\circ$ impose $1/(2\pi RC_f) = f_x$. This

yields $C_f = 143 \text{ pF}$ (use 150 pF).

8.15

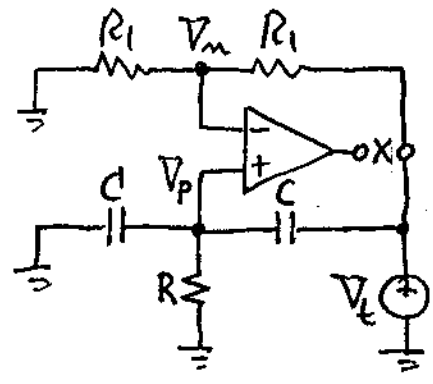


$$\beta = \frac{V_m - V_p}{V_t} = \frac{1}{2} - \frac{R \parallel 1/sC}{R \parallel 1/sC + 1/sC}$$

Expanding gives

$$\frac{1}{\beta} = 2 \left(1 + j \frac{f}{f_0} \right)$$
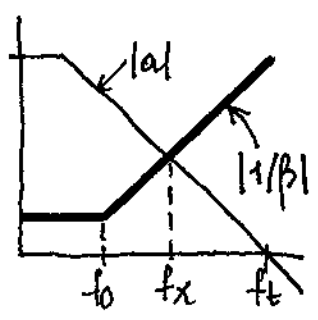
$$f_0 = \frac{1}{4\pi RC} \cong 100 \text{ Hz.}$$



Using ROC considerations, we see that the circuit is on the verge of oscillation.

8.12

To stabilize the circuit we need to flatten out the $|1/\beta|$ curve above f_x . This can be achieved by connecting a suitable capacitance C_c between the

8.13

$$\boxed{8.17} \quad \mathcal{T} = a\beta = \frac{\beta_0 f_t}{j f} \frac{1 + j f / f_p}{1 + j f / f_z}; \quad \frac{1}{f_p} = 2\pi R_2 C_f =$$

$$60\pi 10^3 C_f; \quad \frac{1}{f_z} = 2\pi (R_1 \parallel R_2) (C_m + C_f) = 30\pi 10^3 (C_m + C_f) =$$

$$\frac{1}{663 \times 10^3} + \frac{1}{2 f_p}. \quad \text{Substituting actual values;}$$

$$\mathcal{T} = \frac{10^7}{j f} \frac{1 + j f / f_p}{1 + j f (1/663 \times 10^3 + 1/2 f_p)}. \quad \text{Our goal is to find}$$

f_p such that $\angle \mathcal{T}(j f_x) = -120^\circ$. Starting out with the initial estimate $f_p = \sqrt{663 \times 10^3 \times 10 \times 10^6}$, and then using trial-and-error, we find $f_p = 2.56 \text{ MHz}$.

This gives $f_z = 587 \text{ kHz}$, $f_x = 2.96 \text{ MHz}$, and $C_f = 2.07 \text{ pF}$.

With $\phi_m = 60^\circ$, we have $GP \cong 0.3 \text{ dB}$ and $OS \cong 9\%$. Moreover, $A = (-R_2/R_1) \text{HLP}$, where HLP is the second-order low-pass response with (See Problem 8.16) $f_0 = (587 \times 10^3 \times 10^7)^{1/2} = 2.42 \text{ MHz}$, and $Q = [10^7 / (587 \times 10^3)]^{1/2} / [1 + 10^7 / (2.56 \times 10^6)] = 0.841$.

$$\boxed{8.18} \quad \text{(a) For } \phi_m = 45^\circ \text{ impose } f_z = f_x = \beta_0 f_t = 10 \text{ MHz,}$$

$$\text{or } 1/[2\pi (R_1 \parallel R_2) \times 16 \times 10^{-12}] = 10^7 \Rightarrow R_1 \parallel R_2 = 994 \Omega$$

$$\Rightarrow R_1 = R_2 = 2.00 \text{ k}\Omega$$

$$\text{(b) } \mathcal{T} = a\beta = (\beta_0 f_t / j f) / (1 + j f / f_z) = \frac{10^7}{j f (1 + j f / f_z)}$$


Use trial-and-error to find f_z such that $\angle \mathcal{T} = -120^\circ$ at $f = f_x$. Start out with initial estimate $f_z = 12 \text{ MHz}$. The result is $f_z = 15 \text{ MHz}$,

8.14

$f_x = 8.63 \text{ MHz}$, and $R_1 \parallel R_2 = 663 \Omega \Rightarrow R_1 = R_2 = 1.30 \text{ k}\Omega$.

(c) The advantage is the avoidance of using C_f ; the disadvantage is the need for low resistance values, which may pose power dissipation problems in certain applications.

8.19 (a)

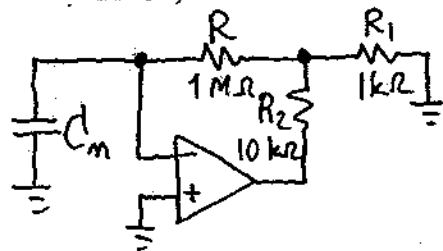

Since $R \gg R_1 \parallel R_2$, we can write


$$\beta \approx \frac{R_1}{R_1 + R_2} \frac{1}{1 + sRC_m}$$

$$= \frac{1/11}{1 + jf/(15.9 \times 10^3)}$$

$$\Gamma = a\beta \approx \frac{4 \times 10^6 / 11}{jf [1 + jf/(15.9 \times 10^3)]} \quad \text{Trial-and-error:}$$

$f_x = 75 \text{ kHz}$; $\phi_m \approx 12^\circ$, not enough.

(b) Summing currents at node V_m gives

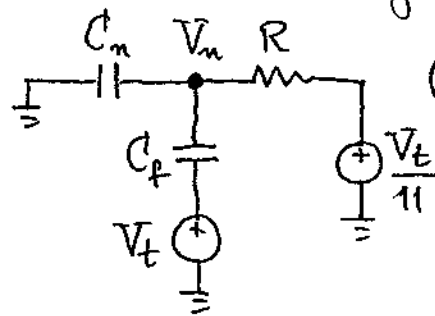

$$0 = \frac{0 - V_m}{1/sC_m} + \frac{V_t - V_m}{1/sC_f} + \frac{V_t/11 - V_m}{R}$$

Collecting and solving,

$$\beta = \frac{V_m}{V_t} = \frac{1}{11} \frac{1 + s11RC_f}{1 + sR(C_m + C_f)}$$

To make β frequency independent impose $11C_f = C_m + C_f \Rightarrow C_f = C_m/10 = 1 \text{ pF}$.

To find the bandwidth, find A_{ideal} .

Summing currents at the virtual-ground node,
 $I_i + V_o/(1/sC_f) + (V_o/11)/R = 0 \Rightarrow A_{ideal} = V_o/I_i =$

8.15

$-11R/(1+jf/f_p)$, $f_p = 1/(2\pi 11RC_f) = 14.5 \text{ kHz}$. The actual gain, besides a pole at 14.5 kHz, has an additional one at $4 \times 10^6/11 \approx 364 \text{ kHz}$.

8.20

$$T = a\beta \approx \frac{10^7}{jf(1+jf/f_p)} \frac{R_1}{R_1+R_2}, f_p \approx \frac{1}{2\pi R_0 C_L}$$

For $\phi_m \approx 45^\circ$, impose $f_p = \frac{R_1}{R_1+R_2} 10^7$. We thus get

(a) $f_p = 5 \text{ MHz}$, $C_L \leq 318 \text{ pF}$; (b) $f_p = 1 \text{ MHz}$, $C_L \leq 1.59 \text{ nF}$; (c) $C_L \leq 159 \text{ pF}$.

(d) $T = 10^7/[jf(1+jf/f_p)]$. Using trial and error, find f_p so that $\angle T(jf_c) = -120^\circ$, starting with $f_p = 10 \text{ MHz}$ as initial estimate. The result is $f_p = 15 \text{ MHz}$. So, $C_L \leq 106 \text{ pF}$.



8.21

```

Problem 8.21 (a)
Vi 1 0 ac 1V pulse (0 1V 0 1ns 1ns 1us 2us)
R1 0 2 30k
Cext 2 0 3pF
Cc/2 2 0 6pF
Cd 2 1 7pF
R2 2 3 30k
Cf 2 3 9pF
ea0 5 0 1 2 1Meg ;dc gain
Req 5 6 1Meg ;pole frequency at
Ceq 6 0 7.958nF ;fb=20Hz
eout 3 0 6 0 1 ;output buffer
*feedback network:
R2f 1 4 30k
Cff 1 4 9pF
R1f 4 0 30k
Cnf 4 0 16pF
.ac dec 50 1k 100Meg
.probe
.tran 1ns 1us 0ns 1ns
*a=V(3)/V(1,2), A=V(3)/V(1), 1/beta=V(1)/V(4)
.end

```



8.16

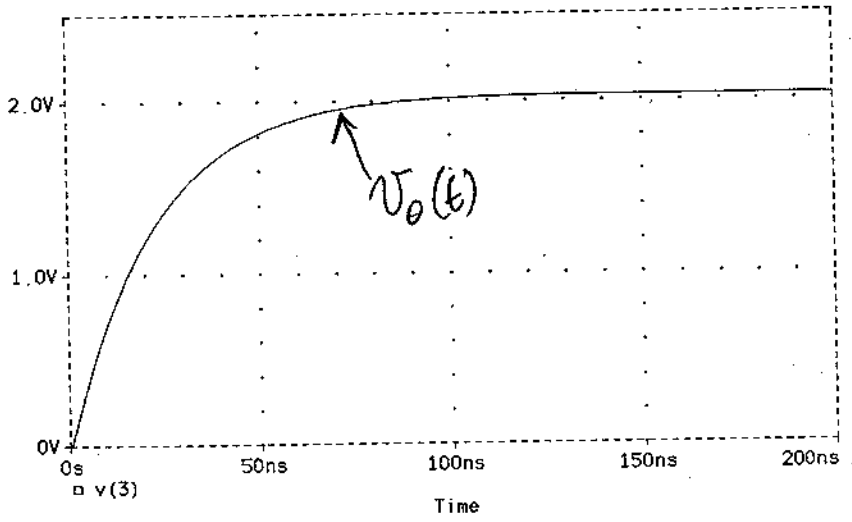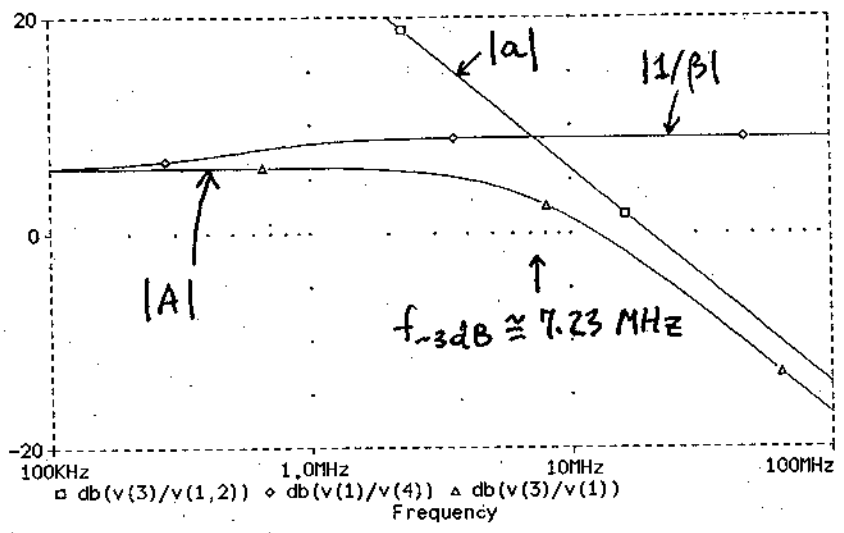


```

Problem 8.21 (b)
Vi 1 0 ac 1V pulse (0 1 0 10n 10n 5us 10us)
R1 1 2 10k
R2 2 4 20k
Cf 2 3 56.25pF
Rs 3 4 50
CL 4 0 5nD
*a0 1 Meg, fa = 10 Hz
ea0 10 0 0 2 1Meg
Req 10 11 1Meg
Ceq 11 0 15.92nF
ebuf 12 0 11 0 1
ro 12 3 100
*1/beta:
rof 1 33 100
Cff 33 22 56.25pF
Rsf 33 44 50
CLf 44 0 5nF
R2f 44 22 20k
R1f 22 0 10k
.ac dec 10 10k 1G
.tran 10ns 5us 0ns 10ns
.probe
.end
  
```


8.17

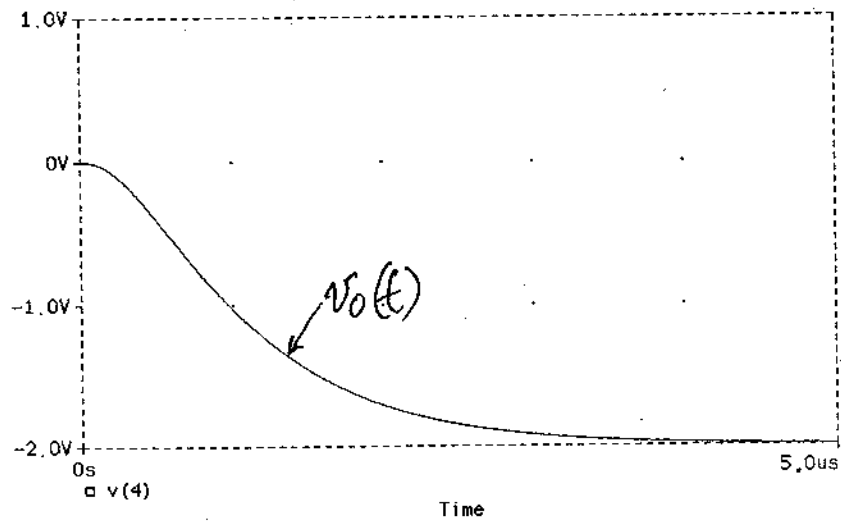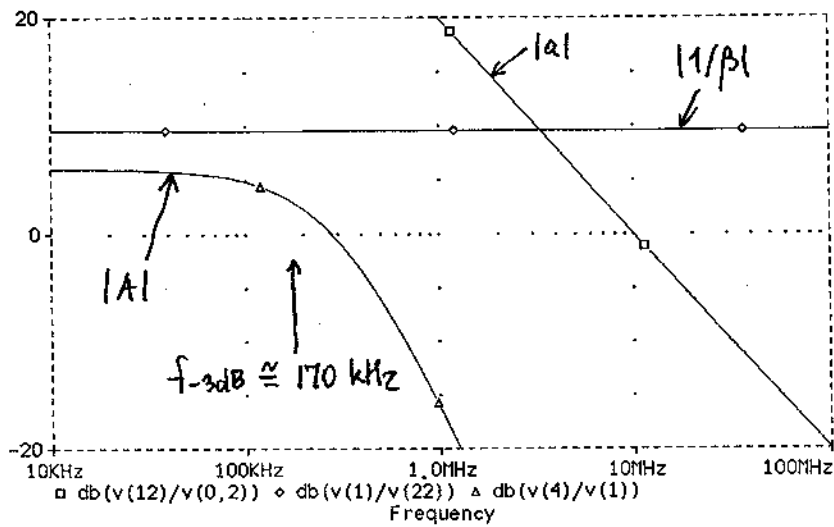

8.22


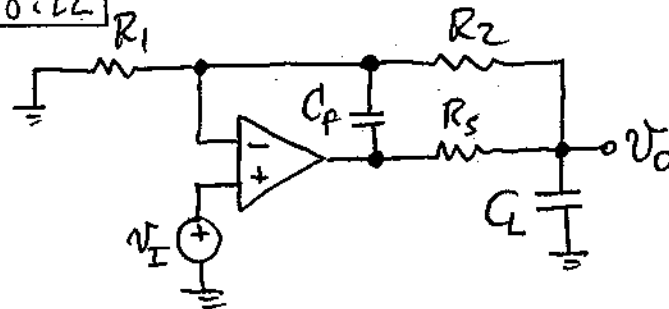


$$R_1 = 20 \text{ k}\Omega, R_2 = 180 \text{ k}\Omega, C_f = 6.26 \text{ }\mu\text{F}, R_s = 11.11 \text{ }\Omega.$$

8.18

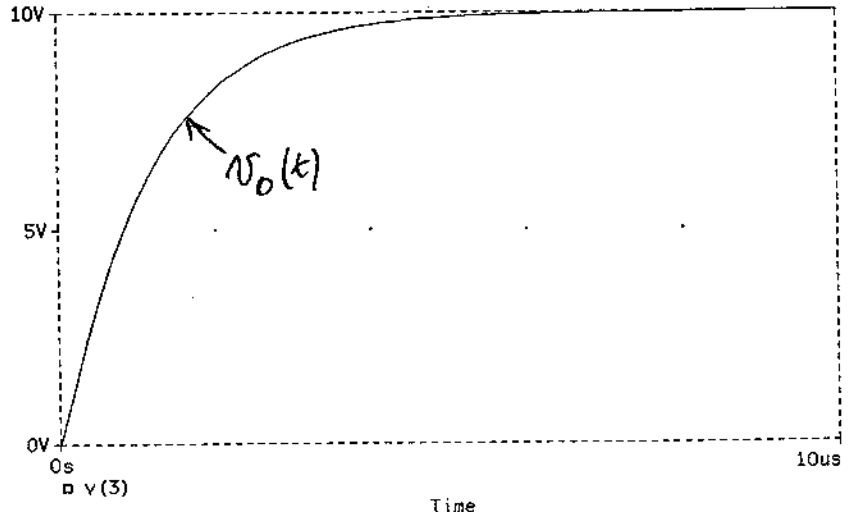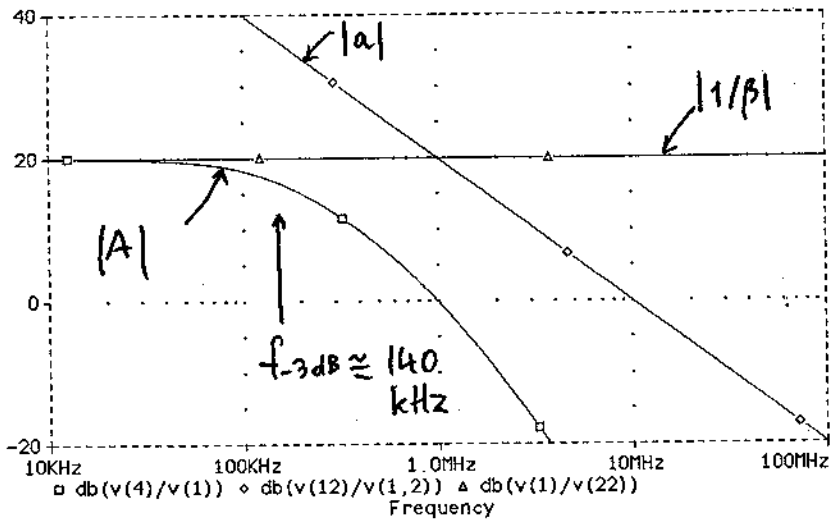
Problem 8.22.

```
*a0 = 1Meg, fb = 10Hz
ea0 10 0 1 2 1Meg
Req 10 11 1Meg
Ceq 11 0 15.92nF
ebuf 12 0 11 0 1
ro 12 3 100
Vi 1 0 ac 1V pulse (0 1V 0 10ns 10ns 10us 20us)
Rvi 1 0 1
R1 0 2 20k
R2 2 4 180k
Cf 2 3 6.86pF
Rs 3 4 11.11
CL 4 0 10nF
*1/beta:
rof 1 33 100
Cff 33 22 6.86pF
Rsf 33 44 11.11
CLf 44 0 10nF
R2f 44 22 180k
R1f 22 0 20k
.ac dec 10 10k 1G
.tran 0.1us 10us 0 0.1us
.probe
.end
```



8.19

8.23

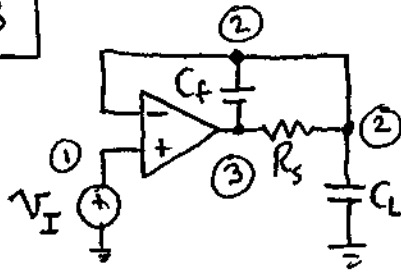

$$R_s = 30v_o = 3 \text{ k}\Omega$$

$$C_f = \left(\frac{5 \times 10^9}{18\pi \times 100 \times 10^7} \right)^{1/2} \approx 300 \text{ pF.}$$

Problem 8.23

ea0 10 0 1 2 1Meg

Req 10 11 1Meg

Ceq 11 0 15.92nF

ebuf 12 0 11 0 1

ro 12 3 100

Vi 1 0 ac 1V Pulse (0 1V 0 1ns 1ns 4us 8us)

RVi 1 0 1

Cf 2 3 300pF

Rs 2 3 3k



CL 2 0 5nF

.ac dec 50 10k 1Meg

.tran 25ns 4us 0ns 25ns

.probe

.end

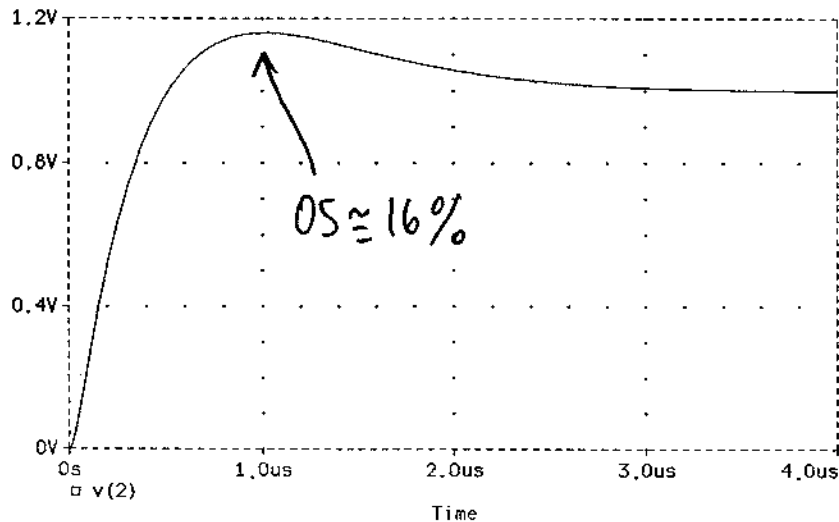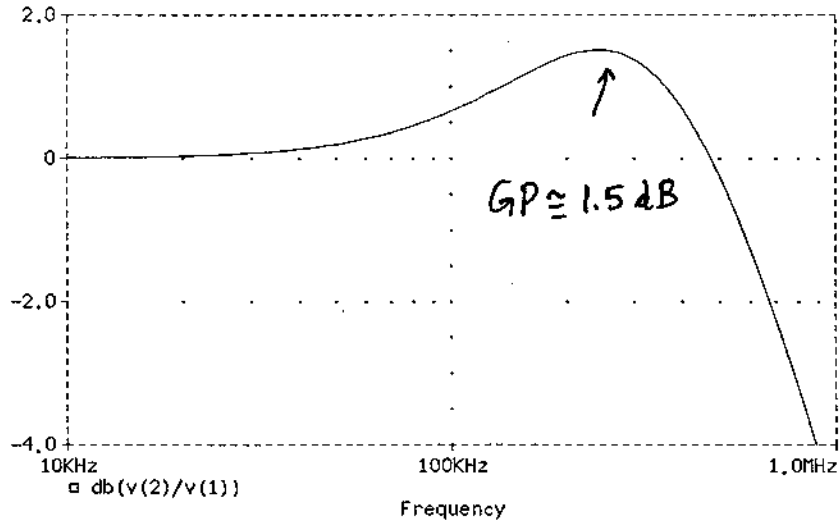


8.20

8.24 (a) $\beta_{\infty} = 1$ V/V because C_2 acts as a short in the limit $f \rightarrow \infty$. Consequently, $f_x = \beta_{\infty} f_t = f_t$, indicating that as long as the op amp is unity-gain stable, so is the wideband band-pass filter.

(b) At high frequencies the caps act as shorts, so $\beta_{\infty} = 1/(1 + KR_4/R_4) = 1/(1 + K)$, indicating a stable circuit with $f_x = f_t/(1 + K)$.

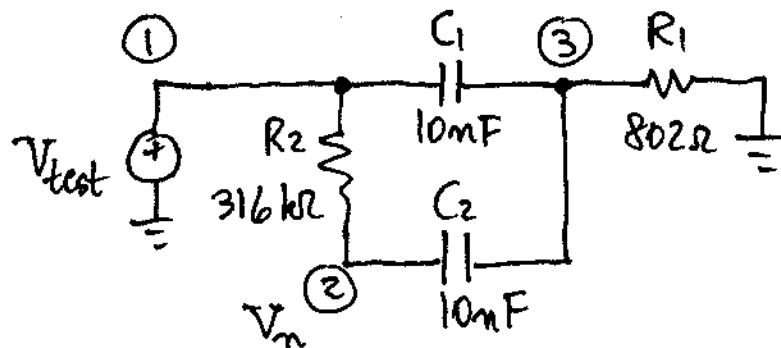8.25 (a) Suppress V_i , break the loop at the op amp's output, insert a test source V_{test} , and plot $1/\beta = V_{test}/V_m$.




```

PROBLEM 8.25a
Vtest 1 0 AC 1
R1 0 3 802
C1 3 1 10n
C2 3 2 10n
R2 2 1 316k
EOA 4 0 Laplace {V(1,0)}={100k/(1+s/62.83)}
.ac dec 10 1 10Meg
.probe
.end


```

8.21

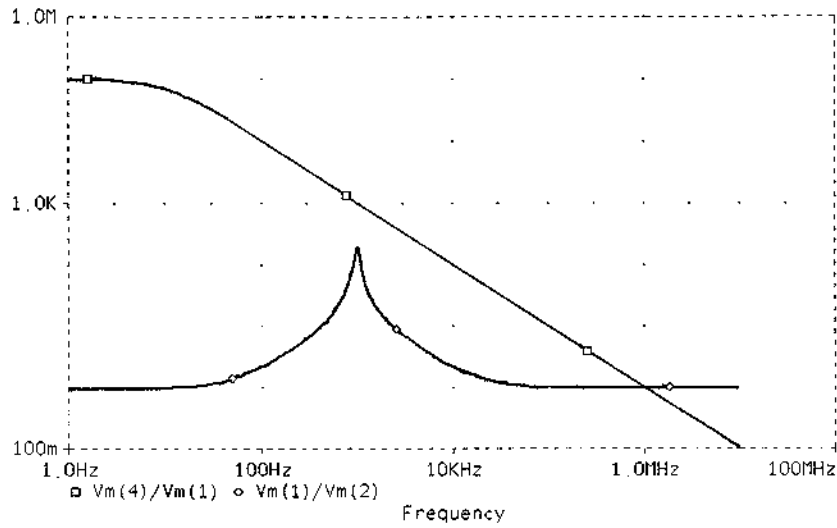

The above plot reveals a stable circuit with $f_x = f_t$ and $\phi_m = 90^\circ$.

(b) Proceeding as in (a), we have:

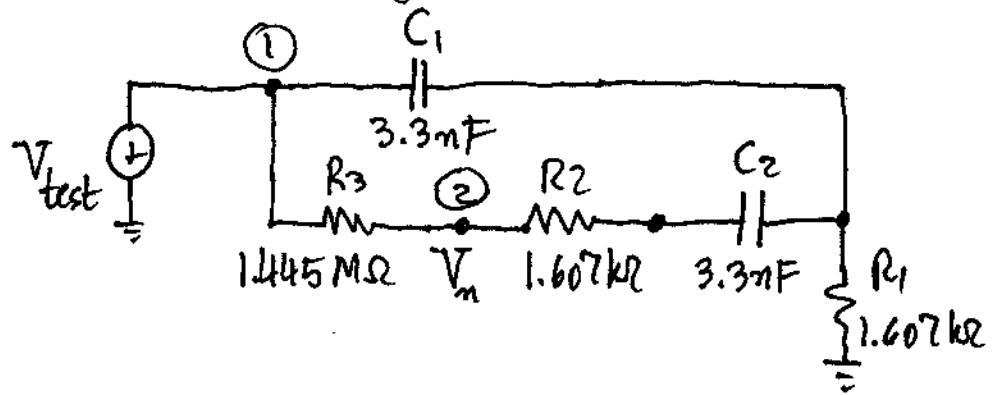


```

PROBLEM 8.25b
Vtest 1 0 AC 1
R1 4 0 1.6k
R2 2 3 1.6k
R3 1 2 1.445Meg
C1 1 4 3.3n
C2 3 4 3.3n
EOA 5 0 Laplace (V(1,0))=(100k/(1+s/62.83))
.ac dec 10 1 10Meg
.probe
.end

```

The result is again a stable circuit with $f_x = f_t$ and $\phi_m = 90^\circ$.

8.22

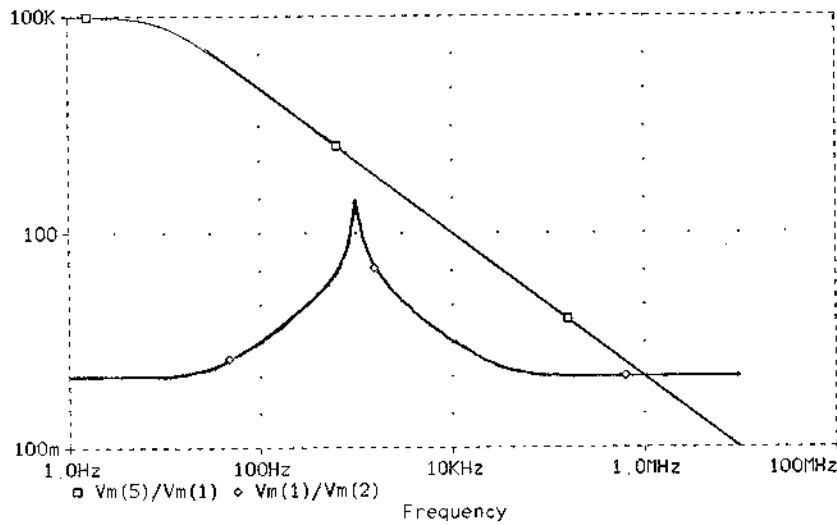

8.26
$$a_{old} = \frac{3600}{(1+jf/10^6)(1+jf/4 \times 10^6)(1+jf/40 \times 10^6)}$$

$$a_{new} = \frac{1}{1+jf/f_d} a_{old} ; \quad T = \beta a_{new} = \frac{1}{10} a_{new} ;$$

for $f \gg f_d$, $\angle a_{new} \cong \angle a_{old} + 90^\circ$.

(a) For $\phi_m = 60$, find the frequency f_{-300} at which $\angle a = -300^\circ$. Using trial and error (PSPICE plots also help), we find $f_{-300} = 430 \text{ kHz}$, where $|\beta a_{old}| = 329$. So, $f_d = 430 \times 10^3 / 329 \cong 1.31 \text{ kHz}$.


(b) The frequency at which $\angle a_{old} = -90^\circ$ is $f_{-90} = 1.87 \text{ MHz}$, where $|\beta a_{old}| = 154$. For $GM = 12 \text{ dB}$, we want $|T(jf_{-90})| = 10^{-12/20} = \frac{1}{4}$, indicating that $f_d = 1.87 \times 10^6 / (154 \times 4) = 3.04 \text{ kHz}$.

(c) With a second-order approximation, Eq. (8.4) indicates that for $GM = 2 \text{ dB}$ we need $Q = 1.13$, or $\phi_m \cong 47^\circ$, by Eq. (8.6). So, use $f_d \cong 650 \times 10^3 / 298 = 2.2 \text{ kHz}$.

8.23

(d) $OS = 5\% \Rightarrow \zeta = 0.69 \Rightarrow \phi_m = 64.6^\circ \Rightarrow f_d = 360 \times 10^3 / 337 = 1.07 \text{ kHz}$.

8.27

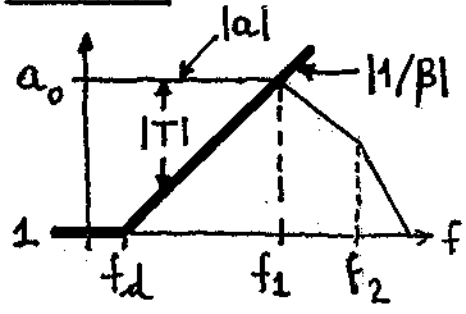

(a) Introduce a pole at $f = f_d$. Thus, $a_0 f_d = 1 f_1 \Rightarrow f_d = 10^6 / 10^3 = 1 \text{ kHz} = 1 / (2\pi RC)$. Let $C =$

1 mF . Then, $R = 158 \text{ k}\Omega$.

(b) $SSBW \approx f_1 = 1 \text{ MHz}$.

8.28


$$a = \frac{10^4}{(1 + jf/10^3)(1 + jf/f_2)} \text{ V/V}$$

$$A_0 = 60 \text{ dB} = 1000 \text{ V/V} \Rightarrow 10^3 = \frac{10^4}{1 + 10^4 \beta} \Rightarrow \beta = 9 \times 10^{-4}$$

V/V . $T = 9 / [(1 + jf/10^3)(1 + jf/f_2)]$. $Q = 1/\sqrt{2} \Rightarrow \phi_m = 65.5^\circ$. Use trial and error to find f_2 such that $\angle T(jf_c) = -114.5^\circ$. Trial and error: $f_2 = 12 \text{ kHz}$, $f_c = 7.55 \text{ kHz}$.

8.29

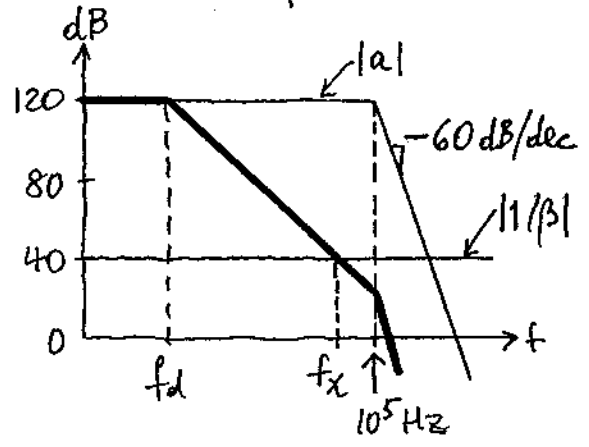(a) $1/\beta = 1 + R_2/R_1 = 101 \approx 40 \text{ dB}$. The ROC



between the f_d and $|1/\beta|$ curves is $-60 \text{ dB/dec} \Rightarrow \phi_m \approx -90^\circ \Rightarrow \text{unstable}$.

8.24

(b) Since f_d contributes -90° at $f = f_x$, if we want $\phi_m = -45^\circ$, the phase contribution of a at f_x must be -45° . Since a has three identical poles, the contribution of each pole at f_x must be $-45^\circ/3 = -15^\circ$. Imposing $-15^\circ = \tan^{-1} f_x/10^5$ gives $f_x = 26.8 \text{ kHz}$. Finally, $f_d = f_x / (\beta A_0) = 26.8 \times 10^3 / (10^6/101) = 2.7 \text{ Hz}$. Use $C = 0.1 \mu\text{F}$, $R = 620 \text{ k}\Omega$.

8.30

$$g_1 V_d + \frac{V_1}{R_1} + sC_1 V_1 + sC_c (V_1 - V_2) = 0$$

$$g_2 V_1 + \frac{V_2}{R_2} + sC_2 V_2 + sC_c (V_2 - V_1) = 0$$

Eliminating V_1 and collecting,

$$\frac{V_2}{V_d} = g_1 g_2 R_1 R_2 \frac{1 - sC_c/g_2}{1 + As + Bs^2}, \text{ where}$$

$$A = R_1 R_2 g_2 C_c + R_1 (C_1 + C_c) + R_2 (C_2 + C_c)$$

$$B = R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c).$$

Writing

$$1 + As + Bs^2 = \left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_b}\right) \cong 1 + \frac{s}{\omega_a} + \frac{s^2}{\omega_a \omega_b}$$

allows us to derive $\omega_1 = 1/A$ and $\omega_2 = 1/B\omega_1$, or

$$\omega_1 = \frac{1}{R_2 (C_2 + C_c) + R_1 (C_1 + C_c) + g_2 R_1 R_2 C_c} \cong \frac{1}{R_1 g_2 R_2 C_c}$$

$$\omega_2 \cong \frac{g_2 C_c}{C_1 C_2 + (C_1 + C_2) C_c}$$

Where we have exploited the fact that the

8.25

Miller effect renders the last denominator term of a_d much bigger than the others. Letting $\omega_z = g_2/c_c$ we thus have

$$\frac{V_z}{V_d} = g_1 R_1 g_2 R_2 \frac{1 - s/\omega_z}{(1 + s/\omega_1)(1 + s/\omega_2)}$$

8.31


$$\pi = 10^5 \frac{1 - jf/50 \times 10^6}{(1 + jf/100)(1 + jf/10^7)(1 + jf/77 \times 10^6)}$$

Using trial and error, we find $f_x = 7.9 \text{ MHz}$ and $\angle T(jf_x) = -\tan^{-1}(7.9/50) - [\tan^{-1}(7.9 \times 10^6/100) + \tan^{-1}(7.9/10) + \tan^{-1}(7.9/77)] = -9^\circ - 90^\circ - 38.3^\circ - 5.9^\circ = -143.1^\circ \Rightarrow \phi_m = 36.9^\circ$.

8.32

In both cases assume the follower configuration, since it is the hardest to compensate.

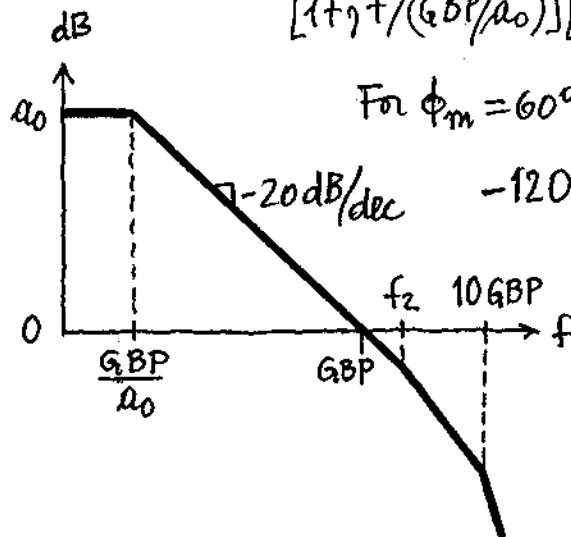(a) $\pi = \frac{a_0}{[1 + jf/(GBP/a_0)][1 + jf/f_2][1 + jf/(10GBP)]}$



For $\phi_m = 60^\circ$ we need $\angle T(jGBP) =$

$$-120^\circ, \text{ or } -[\tan^{-1} a_0 +$$

$$\tan^{-1}(GBP/f_2) +$$

$$\tan^{-1}(0.1) = -120^\circ,$$

$$\text{or } f_2 = \frac{GBP}{\tan 24.29^\circ}$$

$$= 2.2 \times GBP.$$

8.26

$$(b) \quad \pi = \frac{a_0 [1 - jf / (10 \text{ GBP})]}{[1 + jf / (\text{GBP}/a_0)] \times [1 + jf / f_2]}$$

For $\phi_{out} = 45^\circ$ impose $\angle T(j \text{ GBP}) = -135^\circ$, or $-\left[\tan^{-1} 0.1 - \tan^{-1} a_0 - \tan^{-1} (\text{GBP}/f_2)\right] = -135^\circ \Rightarrow f_2 = 1.2 \text{ GBP}$.

8.33 $V_1 = -g_1 V_d Z$, where Z is such that

$$\frac{1}{Z} = \frac{1}{R_1} + sC_1 + \frac{1}{R_c + 1/sC_c} = \frac{1 + s[R_1(C_1 + C_c) + R_c C_c] + s^2 R_1 C_1 R_c C_c}{R_1(1 + sR_c C_c)}$$

$$\frac{V_1}{V_d} = -g_1 R_1 \frac{1 + sR_c C_c}{1 + s[R_1(C_1 + C_c) + R_c C_c] + s^2 R_1 C_1 R_c C_c} \text{ . Rewriting}$$

$$\frac{V_1}{V_d} = -g_1 R_1 \frac{1 + s/\omega_z}{(1 + s/\omega_a)(1 + s/\omega_b)} \approx \frac{1 + s/\omega_z}{1 + s/\omega_a + s^2/\omega_a \omega_b} \text{ gives}$$

$$\omega_z = 1/R_c C_c, \omega_a = 1/[R_1(C_1 + C_c) + R_c C_c] \approx 1/R_1 C_c,$$

$$\omega_b = [R_1(C_1 + C_c) + R_c C_c] / R_1 C_1 R_c C_c \approx 1/R_c C_c.$$

8.34

Problem 8.34

rd 1 2 1Meg

g1 4 0 1 2 2m

R1 4 0 100k

C1 4 0 15.92pF

*Pole-zero comp:

Cc 4 44 15.9nF

Rc 44 0 10

g2 5 0 4 0 10m

R2 5 0 50k

C2 5 0 3.183pF

e3 6 0 5 0 1

R3 6 7 10k

C3 7 0 1.592pF

e0 8 0 7 0 1

ro 8 3 100

vi 1 0 ac 1 pulse (0 1V 0 1ns 1ns 0.4us 0.8us)

Rf 2 3 1k



.ac dec 10 1 100Meg

.tran 2ns 0.4us 0 2ns


.probe

.end

8.27

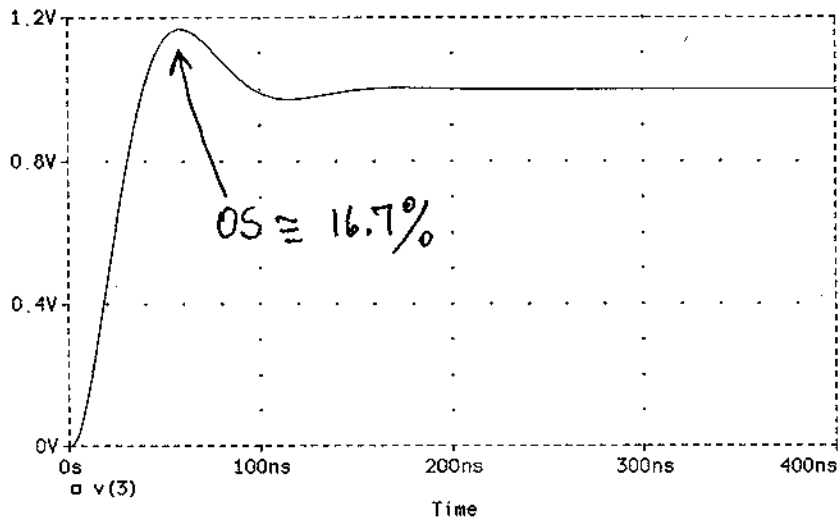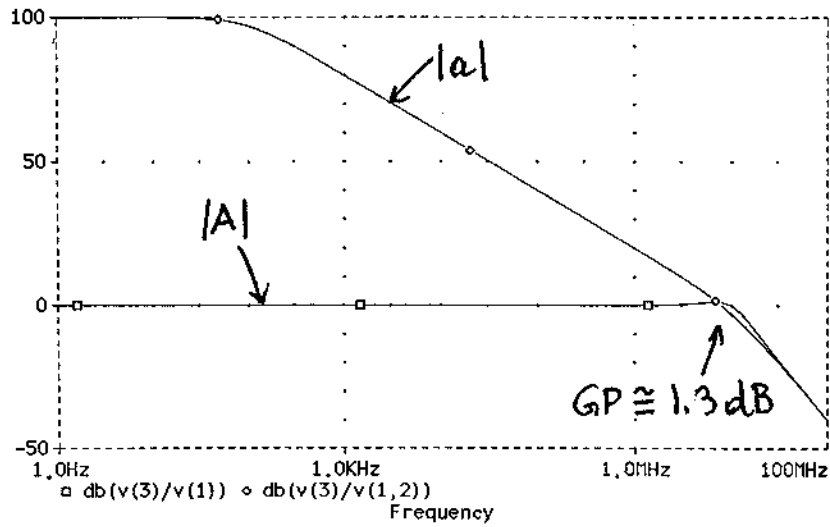

8.35

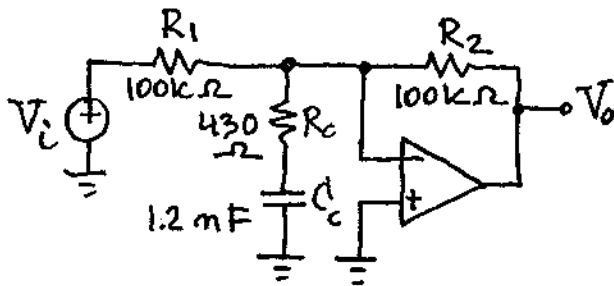

$$R_c = \frac{100 \text{ k}\Omega}{234.5 - (1 + 100/100)} \approx 430 \Omega$$

$$C_c = \frac{5}{\pi \times 430 \times 3 \times 10^6} \approx 1.2 \text{ mF}$$

8.28

To find $A(jf)$, refer to Fig. 8.25(b) and note that for $f < f_2/10$, $|T|$ is fairly large, indicating that $A(jf) \cong A_{ideal} = -1V/V$ there. For $f > f_2/10$ we can write $1/\beta \cong |a(jf_2)|$ and $a \cong a_0 / [(jf/f_1)(1+jf/f_2)(1+jf/f_3)]$, so

$$\frac{1}{T} = \frac{1}{a\beta} \cong \frac{|a(jf_2)|}{a_0} (jf/f_1)(1+jf/f_2)(1+jf/f_3).$$

But, $|a(jf_2)| \times f_2 = a_0 f_1$, so $A = -1/(1+1/T)$, or

$$A(jf) = \frac{-1}{1 + (jf/f_2)(1+jf/f_2)(1+jf/f_3)}$$

$$= \frac{-1}{1 + jf/f_2 - (f/f_2)^2 + (jf/f_3)[jf/f_2 - (f/f_2)^2]}$$


In the neighbourhood of f_2 ($f_2 \ll f_3$) we can approximate

$$A(jf) \cong \frac{-1}{1 + jf/f_2 - (f/f_2)^2} = -HLP, f_0 = f_2, Q = 1$$

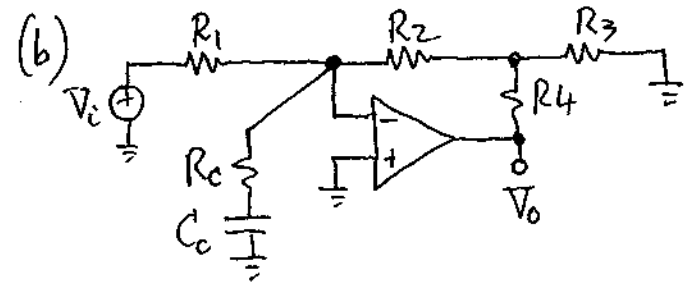8.36 (a) $\beta = \frac{R_1}{R_1 + R_2} \times \frac{(R_1 + R_2) \parallel R_3}{R_4 + (R_1 + R_2) \parallel R_3} = \frac{1}{23} V/V.$

$$T = \frac{10^5/23}{(1 + jf/10^4)(1 + jf/2 \times 10^5)(1 + jf/2 \times 10^6)}$$

Trial and error: $f_x = 2.36 \text{ MR}$, $\phi_m = -44.6^\circ$.



8.29



At high frequencies, where C_c acts as a short, we have $1/\beta_{\infty} = (1 + R_2/R_p) \times [1 + R_4/(R_p + R_2) \parallel R_3] =$

$(1 + R_2/R_p) \times [1 + R_4/(R_p + R_2) + R_4/R_3]$, where $R_p = R_1 \parallel R_c$.

Imposing $1/\beta_{\infty} = |a(jf_2)|$, or $(1 + 100/R_p) \times [1 + 10 + 100/(R_p + 100)] = 3514$ gives $R_p = 342.7 \Omega$. Then, $1/R_c = 1/R_p - 1/R_1 = 344 \Omega$, $C_c = 5/\pi f_2 R_c = 23.1 \text{ mF}$.

(c) $f_{-3dB} \cong f_2 = 200 \text{ kHz}$.


8.37

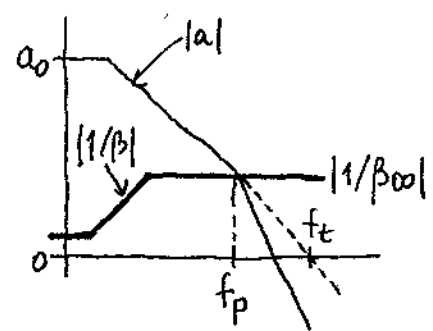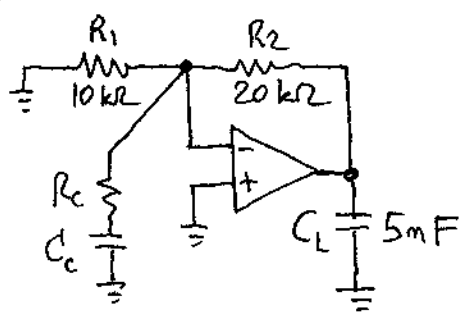

$f_p = \frac{1}{2\pi R_1 C_c} = 318 \text{ kHz}$. Near f_p , $a \cong 10^7 / [j f (1 + j f / 318 \text{ kHz})]$

So $|a(jf_p)| = 22.2 \text{ V/V}$. Find R_c such that $1 + R_2 / (R_1 \parallel R_c) = |a(jf_p)|$, or $1 + R_2 / R_1 + R_2 / R_c = 22.2 \Rightarrow R_c = 1.04 \text{ k}\Omega$. Then, $C_c = 5 / (\pi f_p R_c) = 4.8 \text{ mF}$.

8.38

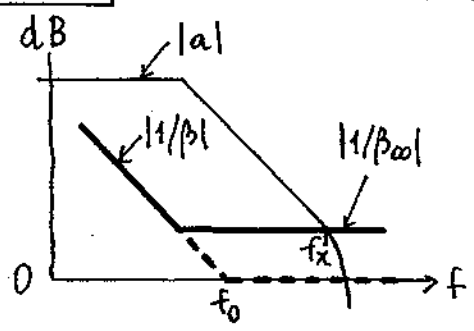

With $C_c = 0$ the $|1/\beta|$ curve (broken) would intercept the $|a|$ curve in the region of excessive phase shift:

$(1/\beta_{\infty}) = 0 \text{ dB}$. With

C_c in place, $1/\beta_{\infty} = 1 + C_c/C$; imposing $1/\beta_{\infty} = 5 \text{ V/V}$ gives $C_c = 4C = 160 \mu\text{F}$. To find f_x , impose


8.30

$$|80 \times 10^6 / j f_x| = 5 \text{ V/V} \Rightarrow f_x = 16 \text{ MHz.}$$

$$(b) f_0 = 1/2\pi RC = 1.59 \text{ MHz;}$$

$$H(jf) \cong - \frac{1}{jf/1.59 \text{ MHz}} \times \frac{1}{1+jf/16 \text{ MHz}}. \text{ Useful range is } f < 16 \text{ MHz.}$$

8.39

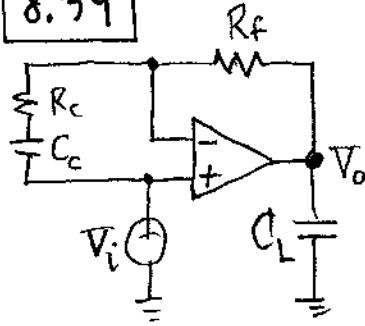

$$f_p = 1/2\pi r_o C_L = 1.06 \text{ MHz}$$

$$a_{new} \cong \frac{6 \times 10^6}{jf} \times \frac{1}{1+jf/1.06 \times 10^6}$$

$$|a_{new}(jf_p)| = 4 \text{ V/V} \Rightarrow$$

$$1 + R_f/R_c = 4 \Rightarrow R_f = 3 R_c.$$


Pick $C_c = 220 \text{ pF}$. Then, $R_c = 5/\pi C_c f_p \cong 6.8 \text{ k}$; $R_f \cong 20 \text{ k}$.

Problem 8.39


```

Vi 1 0 ac 1 pulse (0 1 0 10ns 10ns 2us 4us)
eOA 33 0 Laplace {V(1,2)}={8E6/(1+s/6.283)}
ro 33 3 30
Rf 3 2 20k
CL 3 0 5nF
Rc 2 21 6.8k
Cc 21 1 220pF
.tran 10ns 2u 0 20ns
.ac dec 50 300k 30Meg
.probe
.end


```

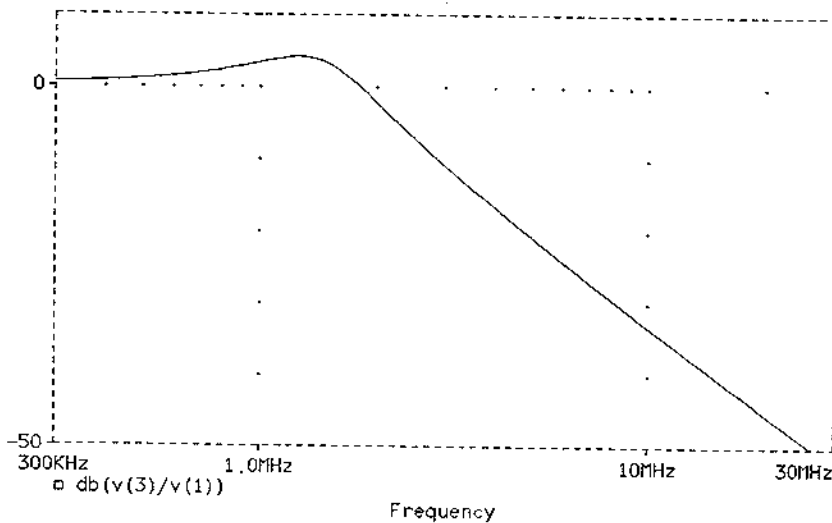

8.31

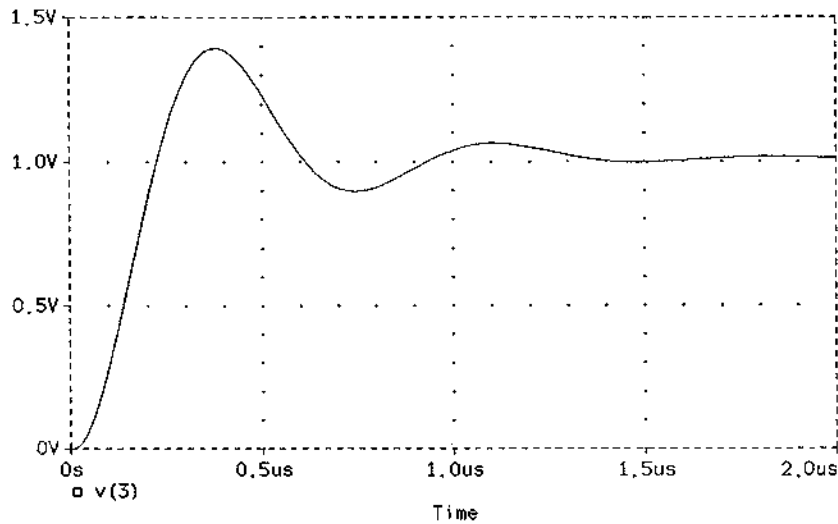

8.40

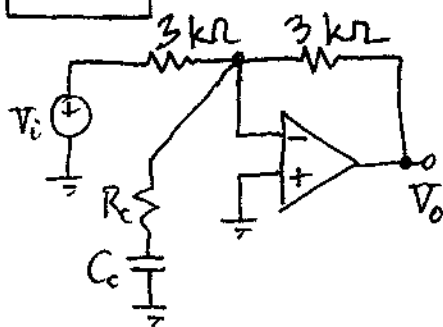

$$R_c = 3 \times 10^3 / [5 - (1+1)]$$

$$= 1 \text{ k}\Omega; f_x = \beta_{\max} \times f_t =$$

$$0.2 \times 80 = 16 \text{ MHz};$$


$$C_c = 5 / (\pi \times 1 \times 10^3 \times 16 \times 10^6)$$

$$= 100 \text{ pF}.$$

$$A(jf) \cong \frac{-1}{1 + jf/16 \times 10^6} \text{ V/V}.$$

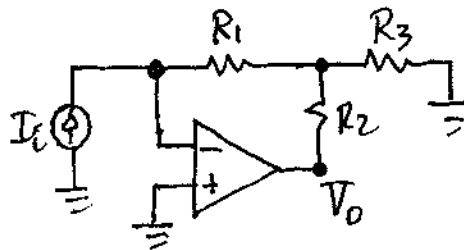8.41

$$A = -R_1 (1 + R_2/R_3 + R_2/R_1); \beta_{\infty} = R_3 / (R_2 + R_3).$$




Imposing $\beta_{\infty} = \beta_{\max} =$
 0.2 V/V gives $R_2 = 4R_3.$
 let $R_3 = 3 \text{ k}\Omega, R_2 = 12 \text{ k}\Omega.$

Imposing $A = -0.1 \text{ V}/\mu\text{A} = -100 \times 10^3 \text{ V/A}$ yields $R_1 =$
 $17.6 \text{ k}\Omega.$ We also have $f_x = 0.2 \times 20 = 4 \text{ MHz},$ so

$$A(jf) \cong [-0.1 \text{ V}/\mu\text{V}] / (1 + jf/4 \text{ MHz}).$$

8.32

8.42 (a) $|a(jf)| \approx (10^7/f)^2$; $1/\beta_0 = 21 \text{ V/V}$;

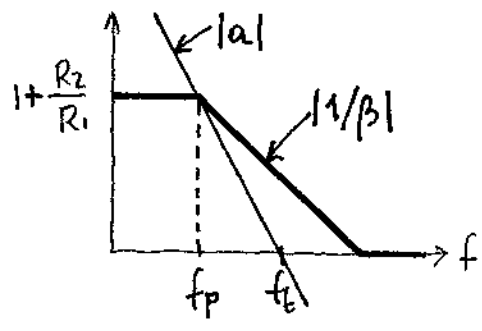

$|a(jf_p)| = 1/\beta_0 \Rightarrow f_p = 2.18 \text{ MHz} \Rightarrow C_f = 3.6 \text{ pF}$;

$A(jf) = \frac{-20 \text{ V/V}}{1 + jf/(2.18 \text{ MHz})}$

(b) ϕ_m is maximized when $f_x = (2.18 \text{ MHz} \times 10 \text{ MHz})^{1/2} = 4.67 \text{ MHz}$, or $f_p = f_x / \sqrt{21} = 1.02 \text{ MHz}$; this requires $C_f = 7.8 \text{ pF}$. $T = a\beta \approx \frac{(10^7)^2}{f} \frac{1}{21} \frac{1 + jf/(1.02 \text{ MHz})}{1 + jf/(21.4 \text{ MHz})}$; $\angle T(jf_x) = -114.6^\circ$
 $\Rightarrow \phi_m = 65.4^\circ$. Moreover, $f_{-3\text{dB}} = 1.02 \text{ MHz}$.

8.43 At high frequencies, where C_1 is virtually a short, $1/\beta \approx 1 + Z_2/R_1$, where $Z_2 = R_2 \parallel (1/j\omega C_2)$. Substituting and manipulating,

$\frac{1}{\beta} \approx \left(1 + \frac{R_2}{R_1}\right) \frac{1 + j(f/f_z)}{1 + j(f/f_p)}$, $f_z = \frac{1}{2\pi(R_1 \parallel R_2)C_2}$,

$f_p = \frac{1}{2\pi R_2 C_2}$. Numerically,

$\frac{1}{\beta} \approx 11 \frac{1 + j(f/220 \text{ kHz})}{1 + j(f/20 \text{ kHz})} \text{ V/V}$


Moreover, $a = \frac{a_0}{[1 + j(f/f_1)][1 + j(f/f_2)]}$. At

8.33

high frequencies, $a \approx \frac{1}{j[f/(a_0 f_1)][1+j(f/f_2)]}$

Numerically, $a \approx \frac{1}{j(f/10^6)[1+j(f/2\text{MHz})]}$
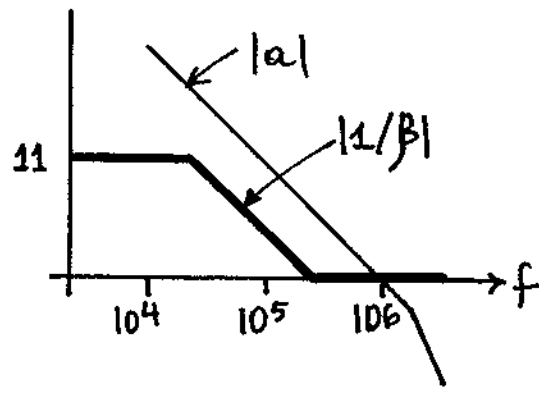
$$T = a\beta \approx \frac{(1/11)[1+j(f/20\text{kHz})]}{j(f/10^6)[1+j(f/2\text{MHz})][1+j(f/220\text{kHz})]}$$




By trial and error we find $f_x = 890$ kHz, and $\phi_m = 78.6^\circ$.

8.44 (a) Use Eq. (6.58), but with $R_1 \rightarrow R$, $R_2 \rightarrow 1/sC$, $r_m \rightarrow r_m + R_2$. The result is

$$\frac{1}{\beta} = \frac{1}{sC} + (r_m + R_2) \left(1 + \frac{1}{sRC}\right) = \frac{R + (r_m + R_2)(1 + sRC)}{sRC}$$

$$\frac{1}{\beta} = (R + r_m + R_2) \frac{1 + jf/f_1}{jf/f_0}, \quad f_0 = \frac{1}{2\pi RC}, \quad f_1 = \left[1 + \frac{R}{(r_m + R_2)}\right] f_0; \quad 1/\beta_{\infty} = r_m + R_2.$$

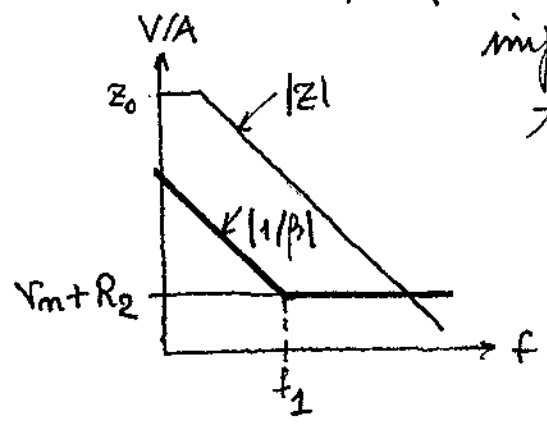As long as we impose $r_m + R_2 \geq (1/\beta)_{\min}$, the circuit will be stable.




(b) $R_2 = 10^3 - 50 = 950 \Omega$. To maximize the region of high $|T|$,

8.34

keep f_1 as low as possible, say, $R < 1 \text{ k}\Omega$.
 Choose $C = 220 \text{ pF}$, $R = 723 \Omega$.


(c) Error due to I_N flowing through R_2 .

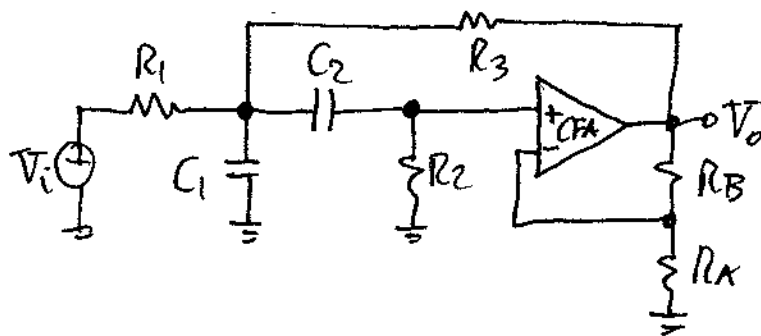8.45 You cannot use the MF configuration (Fig. 3.30) because the series C_1 - C_2 provides a direct capacitive feedback path, jeopardizing stability. Use the KRC configuration since the CFA is configured as an ordinary amplifier.



By Eq. (3.67), $K=2$, $H_{\text{OBD}} = 1 \text{ V/V}$; $R_A = R_B = 1 \text{ k}\Omega$, $C_1 = C_2 = 100 \text{ nF}$, $R_1 = R_2 = R_3 = 225 \Omega$.

8.46 (a)

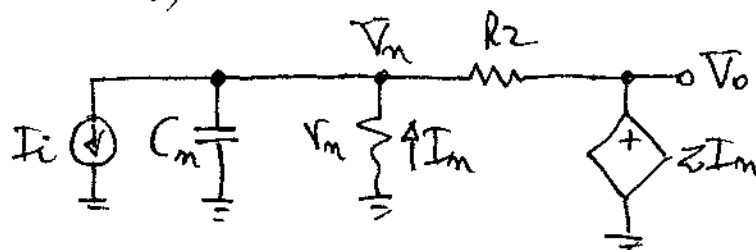

$$V_m = -V_m I_m; V_o = z I_m \Rightarrow V_m = (-V_m / z) V_o.$$

$$\text{KCL: } (V_o - V_m) / R_2 = I_i + s C_n V_m + V_m / V_m.$$

Eliminating V_m and collecting,

8.35

$$\frac{V_o}{I_i} = R_2 \frac{1}{1 + \frac{r_m + R_2}{z} [1 + s(r_m || R_2) C_m]}$$

Letting $z \rightarrow z_o f_a / jf$ and $s \rightarrow j 2\pi f$, we get

$$\frac{V_o}{I_i} = R_2 \frac{1}{1 + jf \frac{r_m + R_2}{z_o f_a} - f^2 2\pi \frac{r_m R_2}{z_o f_a} C_m} = R_2 HLP,$$

$$f_o = \sqrt{\frac{z_o f_a}{2\pi r_m R_2 C_m}}, \quad \frac{r_m + R_2}{z_o f_a} = \frac{1}{f_o Q}, \quad \text{or } Q = \frac{z_o f_a}{(r_m + R_2) f_o}$$



$$(b) f_o = \left[\frac{750 \times 10^3 \times 200 \times 10^3}{2\pi \times 50 \times 1.5 \times 10^3 \times 100 \times 10^{-12}} \right]^{1/2} = 56.4 \text{ MHz}$$

$$Q = 1.72. \text{ By Eq. (8.4), } GP = 0.127. \quad \beta = \frac{1}{2Q} = 0.291.$$

$$\text{Eq. (8.5): } OS = 38.4\%.$$

8.47

(a)

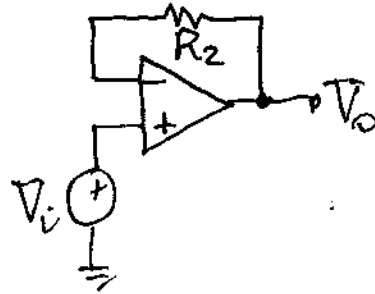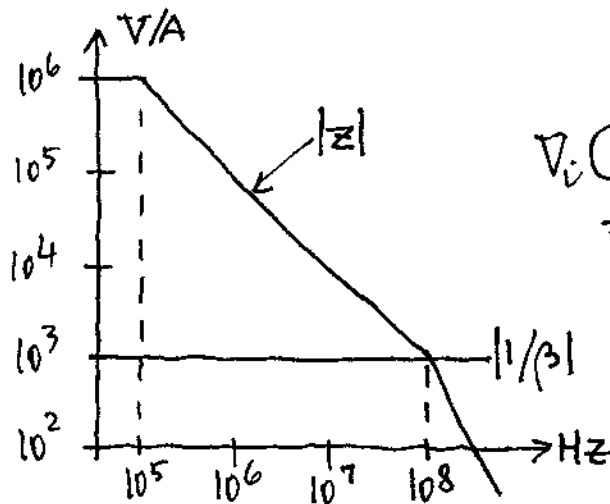

From Eq. (8.34a), $1/\beta = R_2 + r_m (1 + R_2/R_1) = R_2 + r_m$ for $R_1 = \infty$ (voltage follower).

For $\phi_m = 45^\circ$ impedance $f_x = 10^8 \text{ Hz}$, or $R_2 + r_m = 10^3 \Omega$, or $R_2 = 10^3 - 50 = 950 \Omega$; $f_{-3dB} = 10^8 \text{ Hz}$.

8.36

(b) Using the expressions

$$|z| = \frac{10^6}{\sqrt{[1+(f/10^5)^2] \times [1+(f/10^8)^2]}}$$

$$\angle z = -[\tan^{-1}(f/10^5) + \tan^{-1}(f/10^8)]$$

we find $f_{-120^\circ} = 57.8 \text{ MHz}$, where

$$|z(j57.8 \text{ MHz})| = 1498 \Omega. \text{ We now use}$$

$$R_2 = 1498 - 50 = 1448 \text{ k}\Omega, \text{ and we get}$$

$$f_{-30\text{dB}} = 57.8 \text{ MHz}.$$

8.48 (a) ϕ_m is maximized for $f_x = \sqrt{f_p f_z} =$

$$\sqrt{1 + R_2/R_1} f_p. \text{ For } f = f_x,$$

$$|a(jf_x)| = (1 + R_2/R_1)^{1/2}, \text{ or}$$

$$\frac{f_{t1} f_{t2}}{f_x^2} = (1 + R_2/R_1)^{1/2}$$

Eliminating f_x gives

$$f_p^2 = f_{t1} f_{t2} / (1 + R_2/R_1)^{3/2}; \text{ then, } C_f = 1/2\pi R_2 f_p = (1 + R_2/R_1)^{3/4} / [2\pi R_2 \sqrt{f_{t1} f_{t2}}].$$

(b) Since $\angle a(jf_x) \approx -180^\circ$, for $\phi_m \geq 45^\circ$ we need $\angle [1/\beta(jf_x)] \geq 45^\circ$, or $\tan^{-1}(f_x/f_p) - \tan^{-1}(f_x/f_z) \geq 45^\circ$, or $\tan^{-1}(1 + R_2/R_1)^{1/2} - [90^\circ - \tan^{-1}(1 + R_2/R_1)^{1/2}] \geq 45^\circ$, or $2 \tan^{-1}(1 + R_2/R_1)^{1/2} \geq 135^\circ$, or $1 + R_2/R_1 \geq \tan^2(135/2) = 5.83$.

8.37

(c) $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $C_f = 11^{3/4} / (2 \times \pi \times 10^5 \times 10^6) = 9.6 \text{ pF}$; $\phi_m = \tan^{-1}(11)^{1/2} - \tan^{-1}(11)^{-1/2} = 56.4^\circ$. $A(jf) = -10 / (1 + 1/T) \text{ V/V}$. To find T , note that $f_p = 10^6 / 11^{3/4} = 166 \text{ kHz}$, $f_z = 1.82 \text{ MHz}$, $a \cong -f_t^2 / f^2$, so

$$A = \frac{-10 \text{ V/V}}{1 + 1/T} = \frac{-10 \text{ V/V}}{1 - \frac{f^2}{f_t^2} \frac{1}{\beta_0} \frac{1 + jf/f_p}{1 + jf/f_z}}$$

$$= \frac{-10 (1 + jf/1.82 \times 10^6)}{1 + j \frac{f}{1.82 \times 10^6} - \frac{f^2}{1.1 \times 10^{13}} - \frac{jf^3}{1.8 \times 10^{18}}} \text{ V/V.}$$

8.49 (a) Composite: $A_o = (100 \text{ V/V}) / (1 + 2.5 \times 10^{-9})$; $f_B = 100 \text{ kHz}$. Cascade: $A_{o1} = A_{o2} = (10 \text{ V/V}) / (1 + 5 \times 10^{-5}) \Rightarrow A_o \cong (100 \text{ V/V}) / (1 + 10^{-4})$; $f_A = (\sqrt{2} - 1)^{1/2} \times 10^6 / 10 = 64 \text{ kHz}$.

(b) Composite: $A_o = (-100 \text{ V/V}) / (1 + 5 \times 10^{-5})$; $f_B = 100 \text{ kHz}$. Cascade: Let $A_{o1} = (+10 \text{ V/V}) / (1 + 5 \times 10^{-5})$, $A_{o2} = (-10 \text{ V/V}) / (1 + 5.5 \times 10^{-5})$; then $A_o = (-100 \text{ V/V}) / (1 + 10^{-4})$. Moreover, $f_{B1} = 100 \text{ kHz}$, $f_{B2} = 90.9 \text{ kHz}$, $f_B = 61 \text{ kHz}$.

8.50 (a) Let $\beta = 1 / (1 + R_2/R_1)$. Then,

$$T = a\beta = a_1 A_2 \beta \cong \frac{f_t}{jf} \frac{1 + R_4/R_3}{1 + jf / [f_t / (1 + R_4/R_3)]} \frac{1}{1 + R_2/R_1}$$

8.38

$$\begin{aligned} \pi &= \frac{f_t}{jf} \frac{\sqrt{(1+R_2/R_1)/2}}{1+R_2/R_1} \times \frac{1}{1+jf/[f_t/\sqrt{(1+R_2/R_1)/2}]} \\ &= \frac{f_2}{2jf} \frac{1}{1+jf/f_2}, \quad f_2 = f_t/\sqrt{(1+R_2/R_1)/2} \end{aligned}$$

$$\begin{aligned} \frac{1}{1+1/\pi} &= \frac{1}{1+\frac{2jf}{f_2}(1+jf/f_2)} = \frac{1}{1+2j\frac{f}{f_2} - 2\left(\frac{f}{f_2}\right)^2} \\ &= \text{HLP}, \quad f_0 = f_2/\sqrt{2}, \quad Q = 1/\sqrt{2} \Rightarrow \phi_m \approx 65^\circ. \end{aligned}$$

(b) $R_1 = 200 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_4/R_3 = \sqrt{51/2}$
 $-1 = 4.05$; Use $R_3 = 200 \text{ k}\Omega$, $R_4 = 8.06 \text{ k}\Omega$.
 $f_0 = (4.5 \times 10^6 / \sqrt{51/2}) / \sqrt{2} = 630 \text{ kHz}$;
 $A = \frac{-50 \text{ V/V}}{1 + (jf/630 \text{ kHz}) / (1/\sqrt{2}) - (f/630 \text{ kHz})^2}$.

8.51 $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$. $f_{b2} = f_{t2}/a_{20}$
 $= 500 \times 10^6 / (25 \times 10^3) = 20 \text{ kHz}$.

Imposing $f_1 = f_{b2}$ gives $R_3 C_1 = 1/(2\pi \times 20 \times 10^3)$.
 Use $C_1 = 1 \text{ mF}$, $R_3 = 7.96 \text{ k}\Omega$. For $f_2 = f_1/10$
 use $R_4 = 7.96 \text{ k}\Omega$, $C_2 = 10 \text{ mF}$.

The total error at OA_2 's input can be as large as $5 \text{ mV} + 7.96 \times 10^3 \times 20 \times 10^{-6} = 159 \text{ mV}$;
 reflected to OA_1 's input, it yields an error $E_I = 159 \text{ mV} / (100 \text{ V/mV}) = 1.59 \text{ }\mu\text{V}$; then, $E_o = 11 \times E_I = 17.5 \text{ }\mu\text{V}$. $f_B = f_{t2}/11 = 45.5 \text{ MHz}$.

8.39

8.52 Above $f_1 = 20 \text{ kHz}$, C_1 acts as a short and OA_1 thus contributes $e_{n01} = 2 \text{ nV}/\sqrt{\text{Hz}}$, so things go as if the voltage noise at the input of OA_2 was $e_{n2} = \sqrt{2^2 + 5^2} \cong 5.4 \text{ nV}/\sqrt{\text{Hz}}$. Most of the noise will come from the frequency spectrum near $f_B = 45.5 \text{ MHz}$, where $C_2 \cong \text{short}$.

$$E_{no} = 11 \left\{ (5.4 \times 10^{-9})^2 + [(7.96 + 10 \parallel 20) \times 10^3]^2 \times (5 \times 10^{-12})^2 + 1.65 \times 10^{-20} (7.96 + 10 \parallel 20) \times 10^3 \right\}^{1/2} \times (1.57 \times 45.5 \times 10^6)^{1/2} = 93 \times 10^3 [(5.4 \times 10^{-9})^2 + (7.3 \times 10^{-9})^2 + (15.5 \times 10^{-9})^2]^{1/2} \cong 17 \text{ mV}.$$

The main culprit is current noise, which can be reduced by scaling all resistances. The minimum output noise would be $93 \times 10^3 \times 5.4 \times 10^{-9} = 502 \mu\text{V}$. To reduce noise further, filtering must be used, with a reduction in signal bandwidth.

8.53 (a) By Eq. (8.39), $Q = 1$; by Eq. (8.6), $\phi_m \cong 52^\circ$. Using PSpice, $G_P \cong 3.3 \text{ dB}$, $OS = 34.4 \%$.

(b) $-\tan^{-1}(f/10^5)^3 = -1^\circ \Rightarrow f_{-1^\circ} \cong 26 \text{ kHz}$.
 Single op amp: $\angle A = -\tan^{-1}(f/10^5) = -1^\circ \Rightarrow f_{-1^\circ} = 1.7 \text{ kHz}$. Cascade: $f_{B1} = f_{B2} = 10^6/\sqrt{10}$

8.40

$= 316 \text{ kHz}$. Imposing $-\tan^{-1}(f/316 \text{ kHz}) = -0.50^\circ$ gives $f_{-10} = 2.76 \text{ kHz}$.

8.54 The output of OA_2 is $V_3 = \frac{1}{1+jf/\beta_2 f_{t2}} V_0$

where $\beta_2 = R_3/(R_3+R_4)$. By the superposition principle, $V_0 = A_1 \left[V_2 - \left(\frac{R_2}{R_1+R_2} V_1 + \frac{R_1}{R_1+R_2} V_3 \right) \right]$.
Substituting V_3 ,


$$V_0 \approx \frac{f_{t1}}{jf} [V_2 - (1-\beta)V_1] - \frac{\beta f_{t1}/jf}{1+jf/\beta_2 f_{t2}} V_0,$$

$\beta = R_1/(R_1+R_2)$. Collecting,


$$V_0 = \left[\frac{1}{\beta} V_2 + \left(1 - \frac{1}{\beta}\right) V_1 \right] \frac{1+jf/\beta_2 f_{t2}}{1+jf/\beta f_{t1} - f^2/\beta f_{t1} \beta_2 f_{t2}}$$

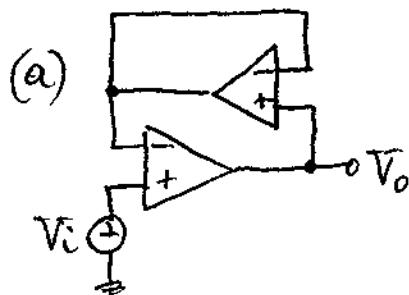8.55 Using matched op amp with $\beta_2 = \beta$, the error function becomes

$$\frac{1}{1+T} = \frac{1+jf/\beta f_t}{1-(f/\beta f_t)^2 + jf/\beta f_t} = \frac{1-j(f/\beta f_t)^3}{1-(f/\beta f_t)^2 - (f/\beta f_t)^4}$$



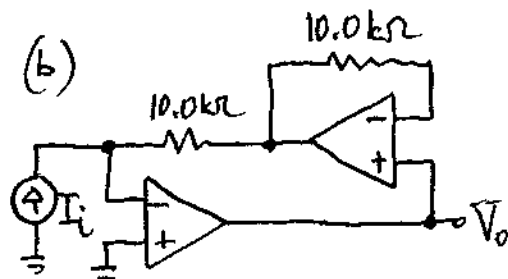
$$A = \frac{1-j(f/10^7)^3}{1-(f/10^7)^2 - (f/10^7)^4}$$



$$A = -10^4 \frac{1-j(f/10^7)^3}{1-(f/10^7)^2 - (f/10^7)^4} \frac{\text{V}}{\text{mA}}$$

8.41

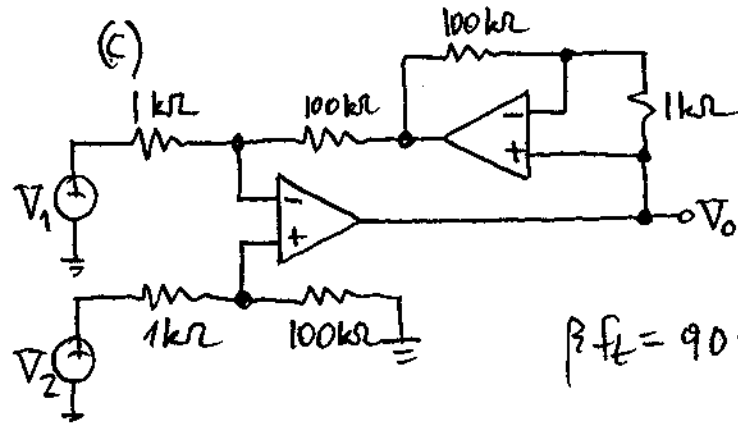

$$\beta f_t = 909 \text{ kHz}$$

$$V_0 = 100 (V_2 - V_1) \times \frac{1 - j (f/909 \text{ kHz})^3}{1 - (f/909 \text{ kHz})^2 - (f/909 \text{ kHz})^4}$$