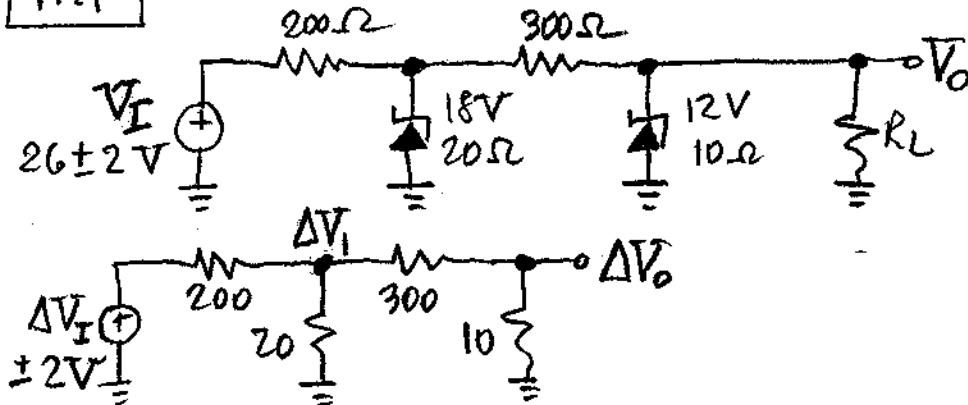


11.1

11.1



$$\Delta V_I = \frac{20 \parallel 310}{200 + 20 \parallel 310} (\pm 2) = \pm 171.7 \text{ mV}$$

$$\Delta V_o = \frac{10}{300+10} (\pm 171.7 \text{ mV}) = \pm 5.54 \text{ mV}$$


Line regulation = $2.77 \text{ mV/V} \approx 0.023\%$.

Load regulation = $-10 \parallel [300 + (200 \parallel 20)] \approx -9.7$

V/A = $-9.7 \text{ mV/mA} \approx -0.08\%/\text{mA}$.

$$R_L(\text{min}) \approx 12 / [(18-12)/300] = 600 \Omega.$$

11.2

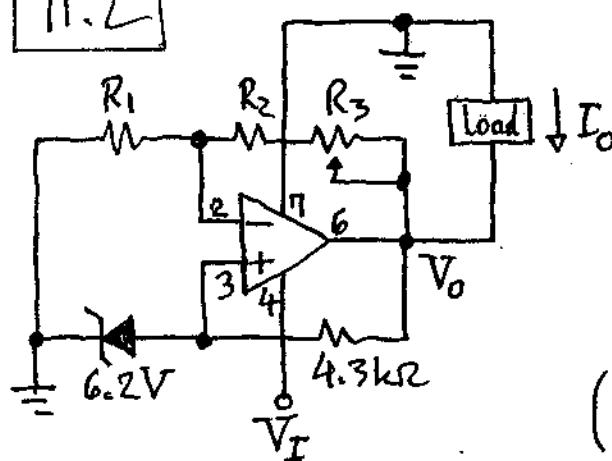

Wiper at left:

$$\left(1 + \frac{R_2}{R_1}\right) 6.2 = 10$$

$$\Rightarrow R_2 = 0.613 R_1$$

Wiper at right:


$$\left(1 + \frac{R_2 + 10}{R_1}\right) 6.2 = 15$$

$\Rightarrow R_1 = 12.4 \text{ k}\Omega, R_2 = 7.68 \text{ k}\Omega$. Allowing 2V of leeway, $-36 \text{ V} \leq V_I \leq -17 \text{ V}$.

Moreover, $|I_{O\text{max}}| \leq 25 \text{ mA}$.

11.2

11.3

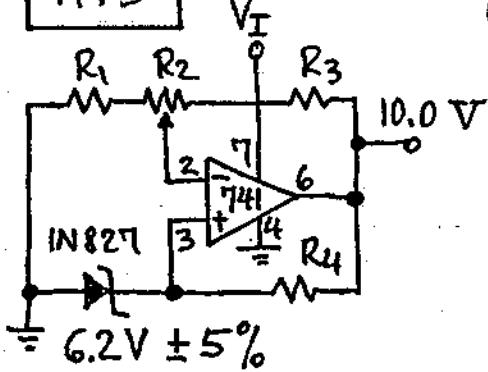


$$(a) R_4 = (10 - 6.2) / 7.5 = 50 \Omega \text{ (use } 51 \Omega\text{)}.$$

Using 1% resistors,
the wiper voltage
range must be
 $6.2V \pm (5+2)\%$,

or $5.79V \leq V_2 \leq 6.63V$. To be on the safe
side, impose $5.7V \leq V_2 \leq 6.7V$. Let R_2 be
a $10-k\Omega$ pot, so $I_{R_2} = (6.7 - 5.7) / 10 = 0.1 \text{ mA}$;
 $R_1 = 5.7 / 0.1 = 57 k\Omega$ (use $56.2 k\Omega$); $R_2 = (10 -$
 $6.7) / 0.1 = 33 k\Omega$ (use $32.4 k\Omega$).

$$(b) \Delta V_Z = 10^{-6} V_Z \times \Delta T \times TC(V_Z) = 10^{-6} \times 6.2 \\ \times 70 \times 10 = 4.34 \text{ mV}; \Delta V_{OS} = (5 \mu\text{V}/^\circ\text{C}) \times (70^\circ\text{C}) = \\ 0.35 \text{ mV}; \Delta V_O(\text{max}) = (10.0 / 6.2) \times (4.34 + 0.35) \\ \cong 7.6 \text{ mV}.$$

11.4

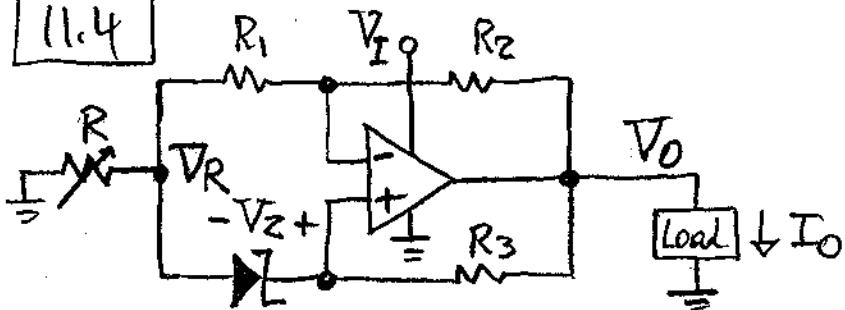


$$(a) V_O = V_R + (R_1 + R_2) V_Z / R_1, I_Z = V_{R3} / R_3 = \\ V_{R2} / R_3 = R_2 \times I_{R2} / R_3 = R_2 I_{R1} / R_3 = R_2 V_Z / R_1 R_3.$$

$$(b) V_R = R \times (I_{R1} + I_Z) = R [V_Z / R_1 + R_2 V_Z / R_1 R_3] = (R V_Z / R_1) (1 + R_2 / R_3). V_O = V_Z \times$$

11.3

$$[1 + R_2/R_1 + (R/R_1)(1 + R_2/R_3)].$$

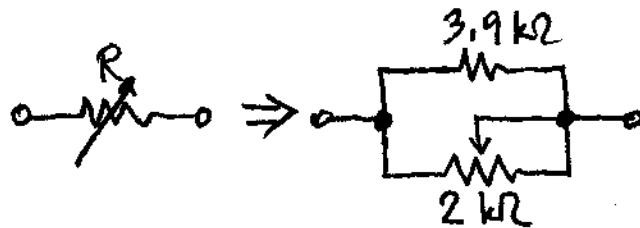(c) $R_1 = 39 \text{ k}\Omega$, $R_2 = 24 \text{ k}\Omega$, $R_3 = (10 - 6.2)/7.5 = 5.11 \Omega$. $R = 0 \Rightarrow V_0 = 10 \text{ V}$; $R = R_{\max} \Rightarrow V_0 = 20 \text{ V} \Rightarrow 6.2(R_{\max}/39)(1 + 24/0.511) = 10 \Rightarrow R_{\max} = 1.31 \text{ k}\Omega$. Use a 2-kΩ pot in parallel with a 3.9 kΩ resistor:



11.5

(a) $V_{REF} = V_{BE1} + R_1 I_{C1}$. $V_N = V_P \Rightarrow R_2 I_{C2} = R_1 I_{C1}$. Moreover, $R_2 I_{C2} = R_2 \times (V_{BE1} - V_{BE2})/R_3 = (R_2/R_3) \ln(I_{C1}/I_{C2}) V_T$. Substituting $I_{C1}/I_{C2} = R_2/R_1$ yields $V_{REF} = V_{BE1} + K V_T$, $K = (R_2/R_3) \ln(R_2/R_1)$.

(b) Recalling Eq. (11.14), $K = (V_{GO} - V_{BE1})/V_T + 3$. Let $I_{C1} = 0.2 \text{ mA}$, so that $V_{BE1} = 25.7 \ln[0.2 \times 10^{-3}/(5 \times 10^{-15})] = 0.627 \text{ V}$. Then, $K = (1.205 - 627)/25.7 + 3 = 25.5$. $R_1 = (V_{REF} - V_{BE1})/I_{C1} = (1.282 - 0.627)/0.2 = 3.27 \text{ k}\Omega$ (use 3.24 kΩ). Let $I_{C2} = (1/5)I_{C1}$. Then, $R_2 = 5R_1 = 16.35 \text{ k}\Omega$ (use 16.5 kΩ). $R_3 = (R_2/K) \ln(R_2/R_1) = (16.35/25.5) \ln 5 = 1.03 \text{ k}\Omega$ (use 1.02 kΩ). Summarizing, $R_1 = 3.24 \text{ k}\Omega$, $R_2 = 16.5 \text{ k}\Omega$, $R_3 = 1.02 \text{ k}\Omega$.


11.4

11.6

(a) $KV_T = R_2 I_{C2} = R_2 I_{R_3} = R_2 (V_{BE1} - V_{BE2}) / R_3 = (R_2 / R_3) V_T \ln (I_{C1} / I_{C2}) \Rightarrow K = (R_2 / R_3) \ln (I_{C1} / I_{C2})$.

(b) For $T C(V_{REF})=0$ we need, by Eq. (11.14), $(R_2 / R_3) \ln (I_{C1} / I_{C2}) = (V_{GO} - V_{BE3}) / V_T + 3$, or $(R_2 / R_3) \ln 5 = 1205 / 25.7 - \ln (0.2 \times 10^{-3} / 2 \times 10^{-5}) + 3$, or $R_2 / R_3 = 15.26$. But, $R_3 = V_{R_3} / I_{C2} = (V_{BE1} - V_{BE2}) / I_{C2} = V_T [\ln (I_{C1} / I_{C2}) / I_{C2}] = [(25.7 \text{ mV}) / (40 \mu\text{A})] \ln 5 = 1.03 \text{ k}\Omega$, so $R_2 = 15.8 \text{ k}\Omega$; $R_1 = (V_{REF} - V_{BE1}) / I_{C1} = (1.282 - 0.651) / 0.2 = 3.16 \text{ k}\Omega$; $R_6 = (5 - 1.282) / (0.2 + 0.2 / 5 + 0.2) = 8.45 \text{ k}\Omega$.


11.7

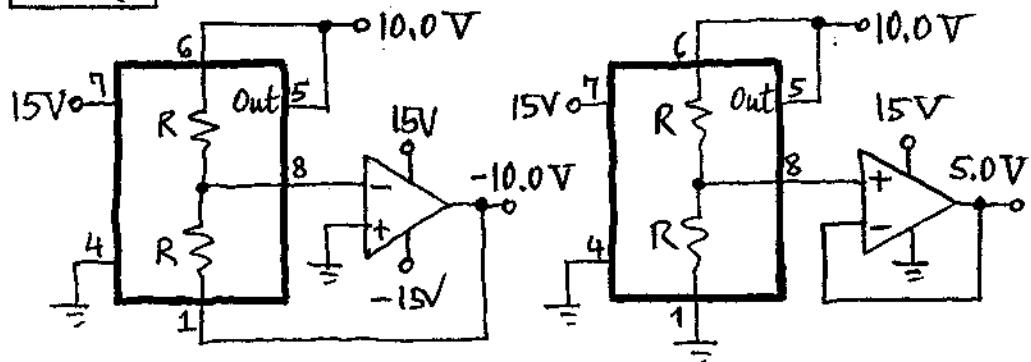


(a)

(b)


11.5

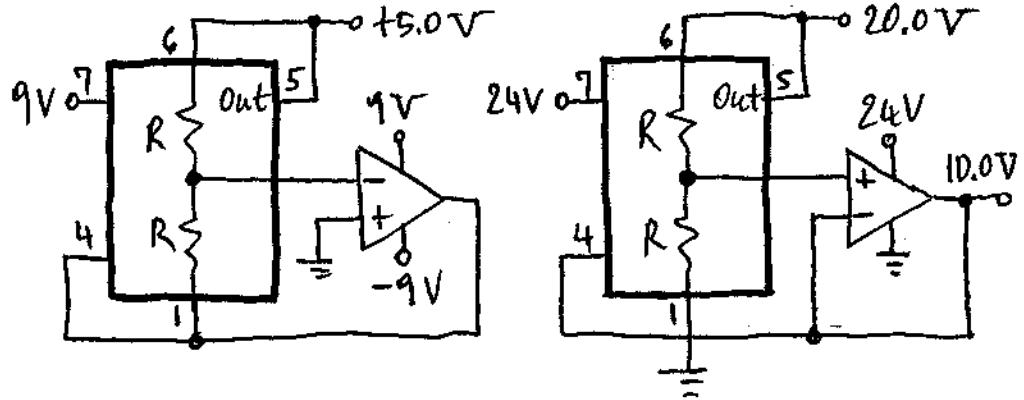

11.8

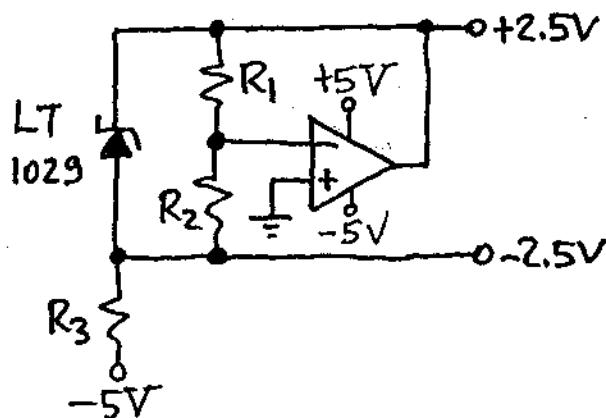
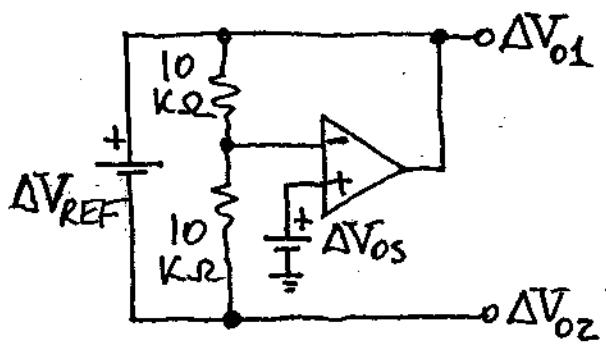
$$\text{Let } R_1 = R_2 = 10.0 \text{ k}\Omega. \text{ Impose } I_Z = 1 \text{ mA. Then, } R_3 = \frac{2.5}{1 + 2.5/10} = 2 \text{ k}\Omega.$$



To investigate thermal drift, use the model on the left. Then,


$$|\Delta V_{o1}| = \Delta V_{os} + 10 \times \Delta V_{REF} / (10 + 10) = \Delta V_{os} + \Delta V_{REF}/2$$

Likewise, $|\Delta V_{o2}| = \Delta V_{os} + \Delta V_{REF}/2$. The contribution from the op amp is about $6 \mu\text{V}/^\circ\text{C} = 10^6 \times 6 \times 10^{-6} / 2.5 \approx 2.5 \text{ ppm}$.

Thus, the outputs can drift by as much as $2.5 + 20/2 = 12.5 \text{ ppm}$.

11.6

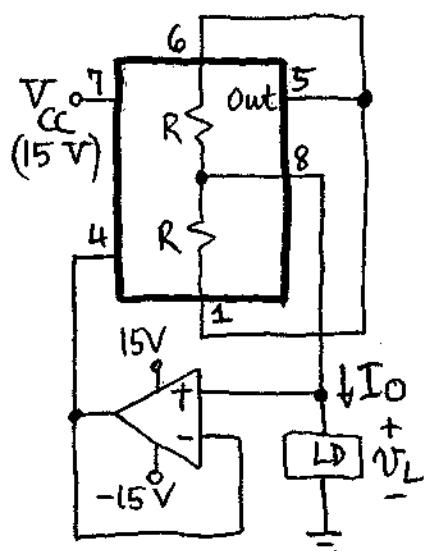11.9 (a) $i_O = (V_5 - V_4) / (R \parallel R) = (10V) / (10k\Omega) = 1 \text{ mA}$.




(b) The input voltage range of Fig. 11.7 indicates that $V_{DD} = 13.5 - 10 = 3.5V$. So, $V_L(\max) = V_{CC} - V_{REF} - V_{DD} = 15 - 10 - 3.5 = 1.5V$. If a wider compliance is desired, then V_{CC} must be raised accordingly.

Since $TC(V_{OS}) \ll TC(V_{REF}) \ll TC(R) = 50 \text{ ppm}/^\circ C$, it follows that the primary source of error is $TC(R)$, so $TC(I_O) = 50 \text{ ppm}/^\circ C$, which corresponds to $\Delta I_O = [(50/10^6) \times 10^{-3}] = 50 \text{ nA}/^\circ C$.

(c) By Fig. 11.7, the trim range is from $(-0.1V)/(10k\Omega) = -10 \mu A$ to $+0.250/10 = 25 \mu A$.


11.10

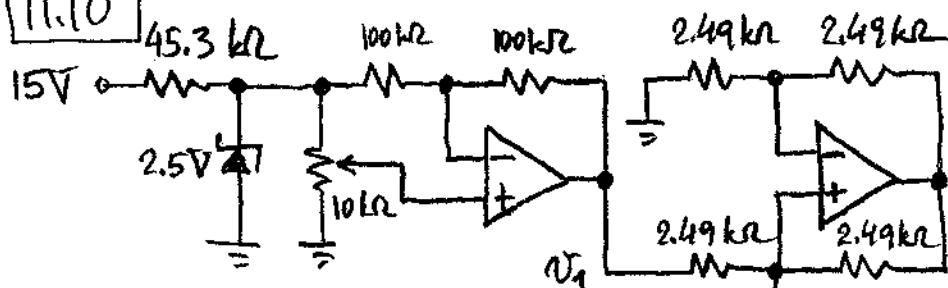

Use a variable voltage source $-2.5V \leq V_1 \leq 2.5V$, followed by a flow and current pumps.

11.7

11.11

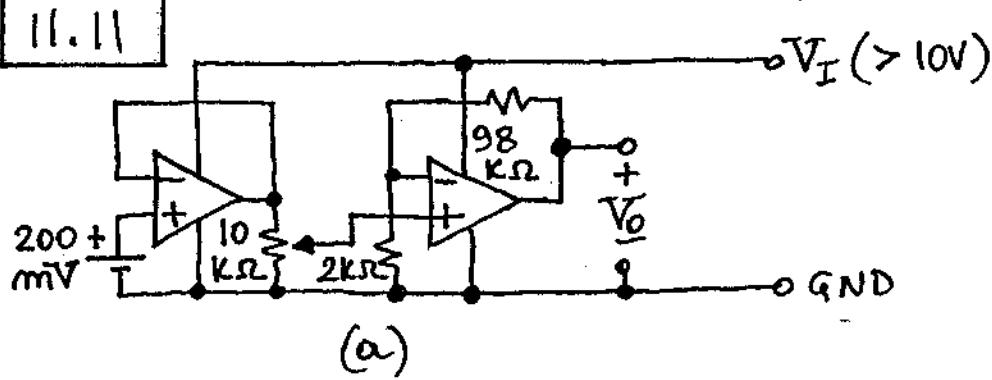


(b) The op-amps contribute a drift of $2 \times 5 = 10 \mu\text{V}/^\circ\text{C} = 100 \times 10 \times 10^{-6} / (200 \times 10^{-3}) = 0.005\% / ^\circ\text{C}$. Thus, the worst-case output drift is $0.003 + 0.005 = 0.008\% / ^\circ\text{C}$.

$90 \text{ dB} \Rightarrow 31.6 \mu\text{V/V}; 2 \times (31.6 + 31.6/2) = 95 \mu\text{V/V} = 100 \times 95 \times 10^{-6} / (200 \times 10^{-3}) = 0.047\% / \text{V}$. Thus, the worst-case line regulation is $0.001 + 0.047 = 0.048\%$.

11.12

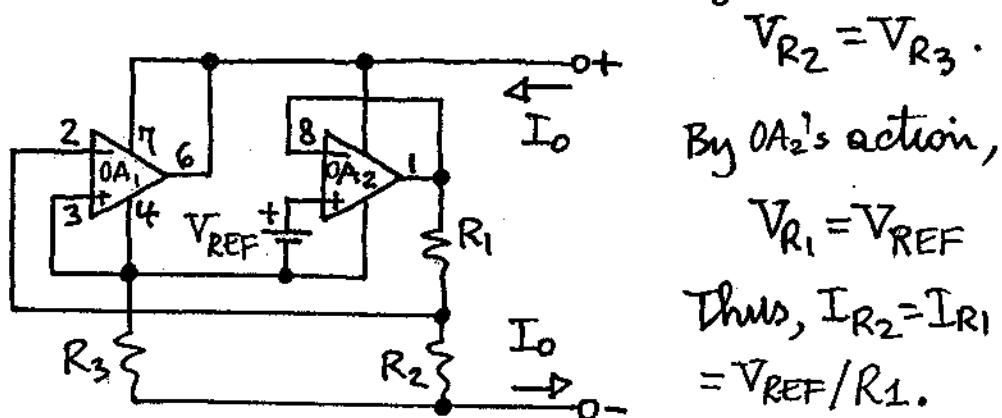(a) $I_o = I_{R_2} + I_{R_3}$. By OA₁'s action,




11.8

Moreover, $I_{R_3} = V_{R_2}/R_3 = R_2(V_{REF}/R_1)/R_3$.
 Finally, $I_o = (V_{REF}/R_1)(1 + R_2/R_3)$.

(b) R_3 must conduct at least 0.5 mA to keep the circuitry on. Impose $I_{R_3} = 1\text{mA}$. Then, $I_{R_1} = I_{R_2} = 4\text{mA}$. $R_1 = 0.2/4 = 50\Omega$ (use 49.9Ω). $1 + R_2/R_3 = 5/4 = 1.25 \Rightarrow R_2 = 0.25R_3$. Let $R_3 = 1.00\text{k}\Omega$, $R_2 = 274\Omega$.

$$(c) (V^+ - V^-)_{min} = 1.1 + V_{R_3} = 2.1\text{ V.}$$

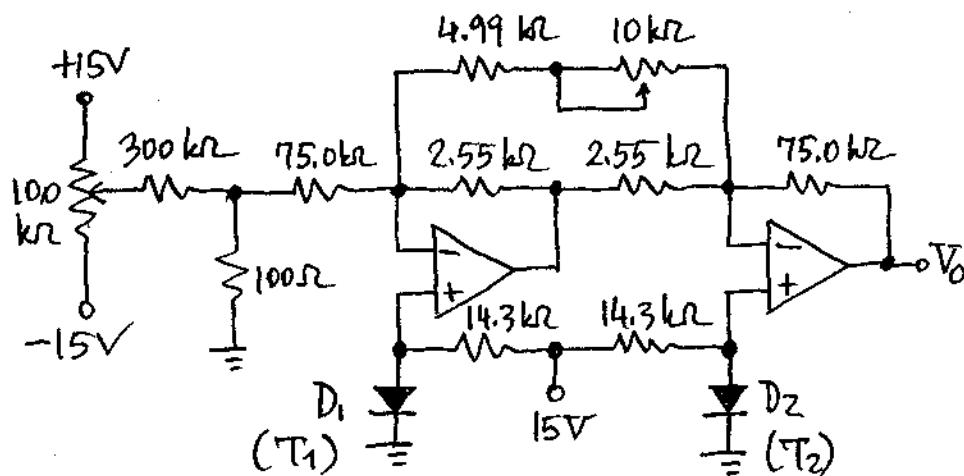11.13 Assuming diode currents of 1 mA, we have, at $T=25^\circ\text{C}$, $V_D = 25.7 \ln(10^3/2 \times 10^{15}) = 692\text{mV}$, $T\partial(V_D) = -(1.205 - 0.692 + 3 \times 25.7 \times 10^{-3})/(273.2 + 25) = -1.997\text{mV}/^\circ\text{C}$. $A = 0.1/(1.997 \times 10^{-3}) = 50.57\text{ V/V}$. Use a dual-op-amp IA with a $\pm 5\text{mV}$ offset adjustment and a $50 \pm 10\text{ V/V}$ gain adjustment



Adjust the 100-kΩ pot for $V_o = 0$ with $T_1 = T_2$.

11.9

Adjust the 10-k Ω pot for the desired sensitivity, e.g. for $V_o = 10 \text{ V}$ when $T_1 - T_2 = 100^\circ\text{C}$.

11.14 Since $1^\circ\text{C} = (9/5)^\circ\text{F}$, the sensitivity of the AD590 is $(5/9) \mu\text{A}/^\circ\text{F}$. Thus, $R_2 = (10 \text{ mV}/^\circ\text{F}) / (5/9 \mu\text{A}/^\circ\text{F}) = 18 \text{ k}\Omega$. We want $V_o(T) = 0 \text{ V}$ for $T = 0^\circ\text{F} = 273.2 - (\frac{5}{9})32 = 255.42 \text{ }^\circ\text{K}$. At this temperature, $I(T) = 255.42 \mu\text{A}$. To eliminate this offset, we need $R_1 = (10 \text{ V}) / (255.42 \mu\text{A}) = 39.15 \text{ k}\Omega$. Use $38.3 \text{ k}\Omega$ in series with a $2\text{k}\Omega$ pot. For R_2 , use $16.9 \text{ k}\Omega$ in series with another $2\text{k}\Omega$ pot.

To calibrate, adjust R_1 for $V_o = 0.0\text{V}$ with $T = 0^\circ\text{F}$. Then, adjust R_2 for $V_o = 2.120 \text{ V}$ with $T = 212^\circ\text{F}$.

11.15 Let $I_{sc} = i_o(\text{max})|_{V_o=0}$ and $I_{fb} = i_o(\text{max})|_{V_o=V_{REG}}$; let $R_{sc} = V_{BE3(\text{on})} / I_{sc}$. We need to satisfy two equations :

$$(a) @ V_o = 0 : V_{BE3(\text{on})} = \frac{R_4}{R_3 + R_4} R_{fb} I_{sc} - 0.$$

This gives

$$R_{sc} = \frac{R_4}{R_3 + R_4} R_{fb} \Rightarrow \frac{R_3}{R_4} = \frac{R_{fb}}{R_{sc}} - 1$$


$$(b) @ V_o = V_{REG} : V_{BE3(\text{on})} = \frac{R_4}{R_3 + R_4} (V_{REG} + R_{fb} I_{fb}) - V_{REG}.$$

11.10


Using $R_4/(R_3 + R_4) = R_{sc}/R_{fb}$ and $V_{BE3(on)} = R_{sc}I_{sc}$ gives, after suitable manipulations,

$$\frac{1}{R_{fb}} = \frac{1}{R_{sc}} - \frac{I_{fb} - I_{sc}}{V_{REG}}$$

11.16

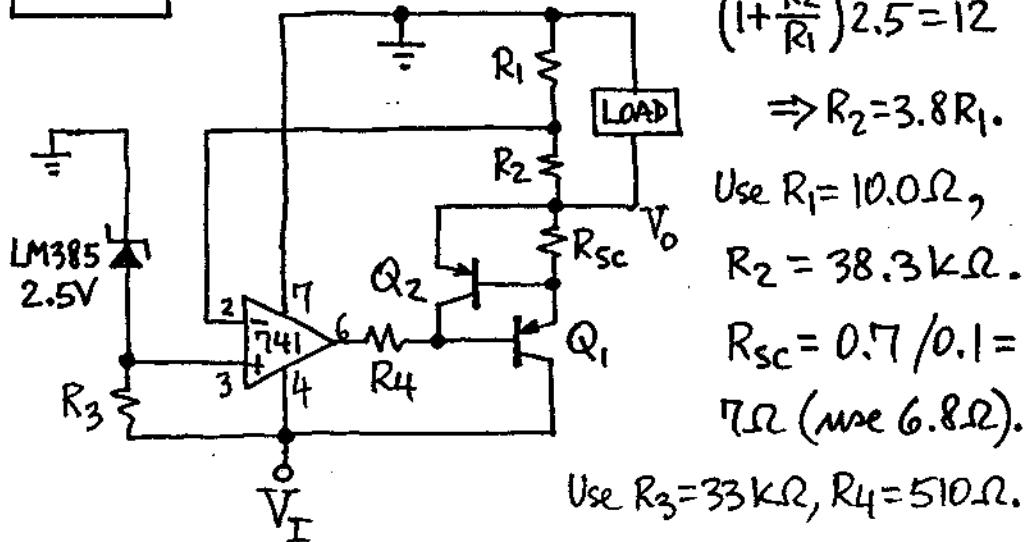

11.17

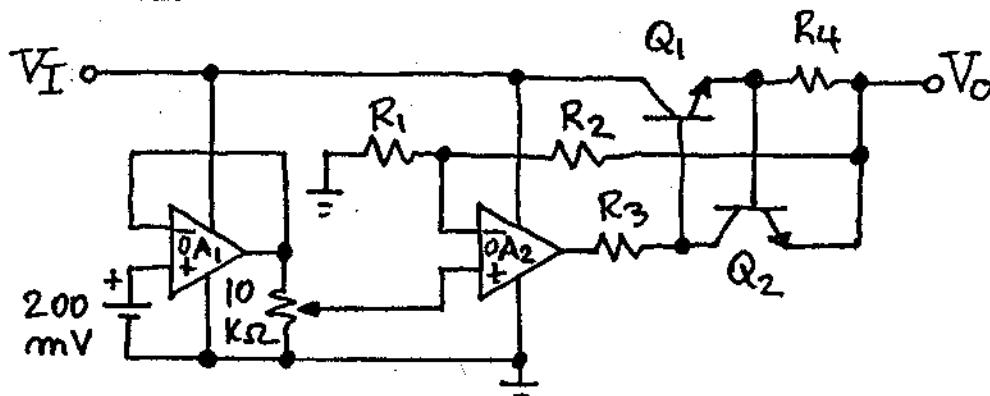

As V_{p2} is varied from 0 to 0.2 V, V_0 must vary from 0V to 15V. Thus, $(1 + R_2/R_1) = 15/0.2 = 75$. Use $R_1 = 200\Omega$, $R_2 = 15.0 k\Omega$. Note that R_2 must be derived from V_0 ! Moreover, $R_4 = 0.7 / 0.1 = 7\Omega$ (use 6.8Ω).

11.11


Let $R_3 = 1\text{ k}\Omega$. Assuming $\beta_1 = 100$ and keeping in mind that Q_{A_2} swings from rail to rail, we have $V_{I(\min)} \cong V_{OA2(\max)} = V_0(\max) + V_{BE1(on)} + V_{R_4(\max)} + R_3 I_{B1(\max)}$
 $= 15 + 0.7 + 0.7 + 1 \times 100 / 101 \cong 17.5\text{ V.}$

11.18

(a) By op amp action, $V_{pin2} = V_{pin3}$ and $V_{pin8} = V_{pin4} + V_{REF} = V_{pin3} + V_{REF}$. Thus, $V_{R_1} = V_{REF}$ and $V_o = V_{R_2} = R_2 I_{R_2} = R_2 I_{R_1}$, that is, $V_o = (R_2/R_1)V_{REF}$.

(b) Let $R_1 = 200\Omega$, $R_2 = 100\text{k}\Omega$. Assume $V_{BE1} = 1\text{V}$, $\beta_1 = 15$, $V_{BE2} = V_{BE3} = 0.7\text{V}$, $\beta_2 = \beta_3 = 100$. Then, $I_{B1} = 1/16 = 63\text{mA}$. $I_{B2} = (63 + 1/0.3)/101 = 0.65\text{mA}$. $I_{B3} = (0.65 + 0.7/3)/101 = 9\mu\text{A}$. Thus, $I_{R_5} = I_Q + I_{B2}$; $I_{R_5(\max)} \cong I_Q(\max) = 0.5\text{mA}$. Dropout voltage = $1 + 0.7 + 0.7 + 3.9 \times 0.5 \cong 4.4\text{V}$.


11.19

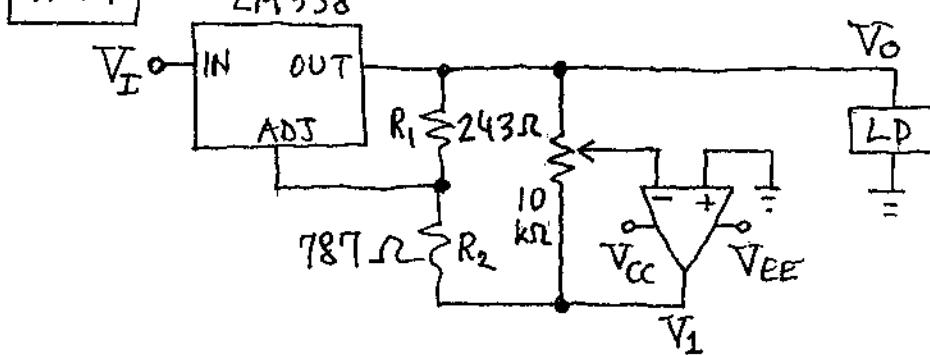

11.12

R_1 and R_2 configure the LM338 for $V_O - V_I = 5.0V$, and the op amp provides the proper drive for V_I . Wiper up $\Rightarrow V_O = 0$ and $V_I = -5V$: $V_I \leq 35V$, $V_{EE} < -5V$. Wiper down $\Rightarrow V_O = 5V$ and $V_I = 0V$: $V_I \geq 7.5V$, $V_{CC} > 0V$. Summarizing, $7.5V \leq V_I \leq 35V$, $V_{CC} > 0$, $V_{EE} < -5V$. For a 741 op amp, $V_{CC} \geq 2V$, $V_{EE} \leq -7V$.

11.20

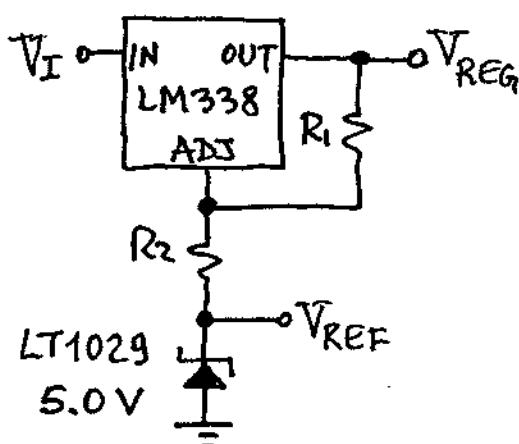


$$\text{Let } I_{R_1} = 5 \text{ mA.}$$

$$\begin{aligned} \text{Then, } R_1 &= 1.25/5 \\ &= 249 \Omega \text{ and} \\ R_2 &= (15 - 1.25 - 5)/5 \\ &= 1.69 k\Omega. \end{aligned}$$

$$17.5V < V_I < 35V.$$

11.21

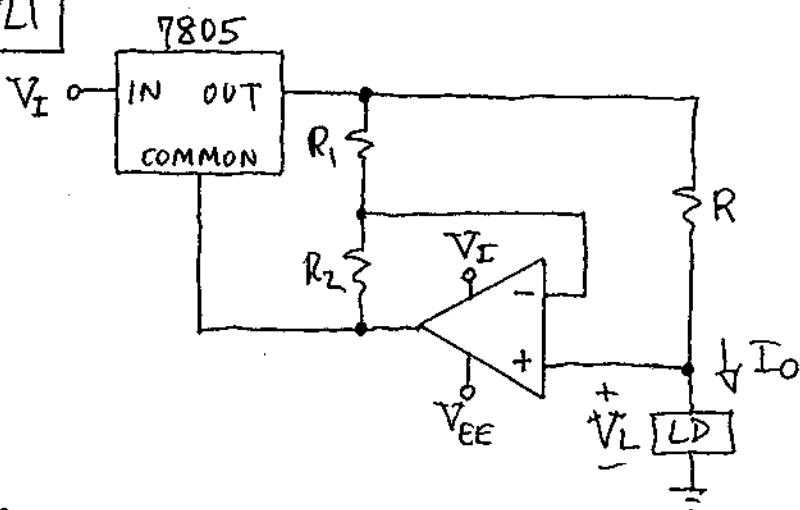


$$RI_O^2 = R \times 1 < 0.25W \Rightarrow R \leq 0.25\Omega \text{ (use } R=0.2\Omega\text{)}.$$

11.13

$V_R = 0.2 \text{ V} \Rightarrow 0.2/R_1 = 4.8/R_2$. Use $R_1 = 1.00 \text{ k}\Omega$,
 $R_2 = 24.3 \text{ k}\Omega$. $V_L \leq V_I - V_{D0} - V_R = V_I - 2.2 \text{ V}$.

11.22

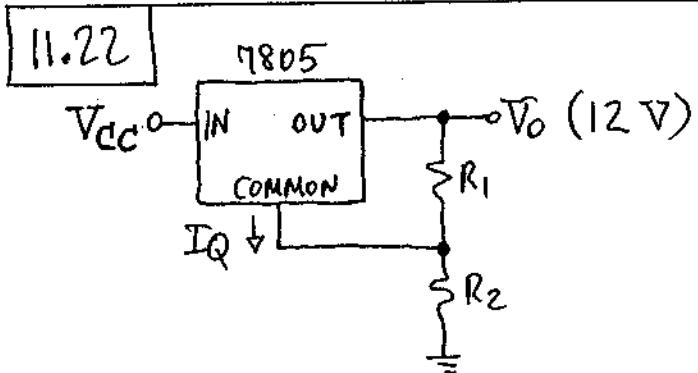



$I_Q = 4.2 \text{ mA}$ (typical). Suppose $I_{R_1} = 25 \text{ mA}$; then,
 $R_1 = 5/25 = 200 \Omega$, and $R_2 = (12-5)/(25+4.2) = 240 \Omega$ (use 237 Ω). $14 \text{ V} \leq V_{CC} \leq 47 \text{ V}$.

$$\Delta V_{R_1(\max)} = (100 \text{ mV}) / [(1.5 - 0.005) \text{ A}] \cong 67 \text{ mV/A}; \Delta I_Q(\max) = (0.5 \text{ mA}) / [(1 - 0.005) \text{ A}] = 0.5 \text{ mA/A}. \Delta V_O(\max) = (1 + R_2/R_1) \Delta V_{R_1(\max)} + R_2 \times \Delta I_Q(\max) = (1 + 237/200) 67 \times 10^{-3} + 237 \times 0.5 \times 10^{-3} = 265 \text{ mV/A} = 100 \times 265 \times 10^{-3} / 12 = 2.21\%/\text{A}.$$

$$\Delta V_{R_1(\max)} = (50 \text{ mV}) / [(25 - 7) \text{ V}] \cong 2.8 \text{ mV/V}; \Delta I_Q(\max) = (0.8 \text{ mA}) / [(25 - 8) \text{ V}] = 47 \mu\text{A/V}. \Delta V_O(\max) = (1 + 237/200) 2.8 \times 10^{-3} + 237 \times 47 \times 10^{-6} \cong 17.3 \text{ mV/V} = 100 \times 17.3 \times 10^{-3} / 12 = 0.14\%/\text{V}.$$

11.14

11.23

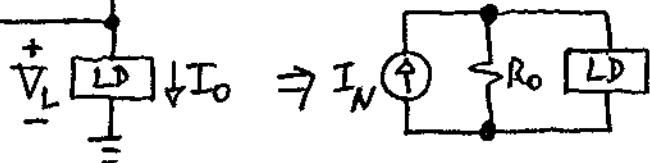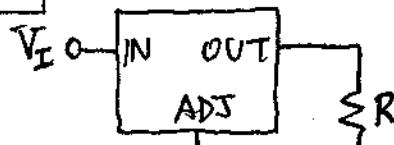


$$I_N = V_{REG}/R = 1.25/2.5 = 0.5 \text{ A. } V_L \leq V_I - V_{D0} - V_{REG} = 25 - 2 - 1.25 = 21.75 \text{ V.}$$

$$\Delta V_R(\max) = (0.07/100)1.25 = 0.875 \text{ mV/V;}$$

$$\Delta I_O(\max) = \Delta I_R(\max) + \Delta I_Q(\max) = 0.875 \times 10^{-3}/2.5 + 5 \times 10^{-6}/(40-2.5) \approx 0.35 \text{ mA/V.}$$

$$|R_0(\min)| = (1\text{V})/(0.35 \text{mA}) = 2.86 \text{ k}\Omega.$$

11.24

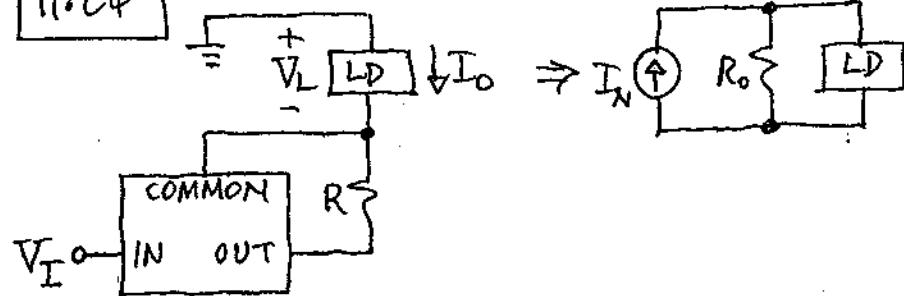


$$R = 1.25/0.5 = 2.5 \Omega \text{ (use } 2.49 \Omega, 1 \text{ W); } I_N = 0.5$$

$$\text{A. } \Delta I_O(\max) = (0.03/100) \times 1.25/2.49 + 0.135 \times 10^{-6} \approx 151 \mu\text{A/V. } R_0(\min) = (1\text{V})/(151 \mu\text{A}) = 6.6 \text{ k}\Omega.$$

11.15

11.25

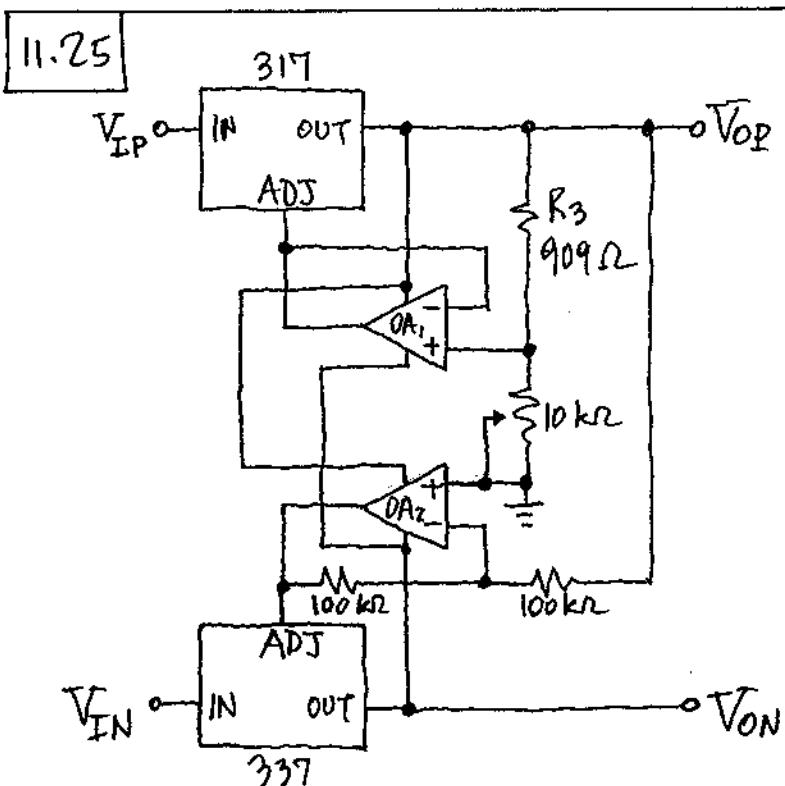

Varying the wiper from bottom to top varies V_{OP} from 1.25V to 15.0V. OA_2 , a unity-gain inverting amplifier, forces V_{ON} to vary from -1.25V to -15V. As long as they saturate within less than 1.25V of the supply rails, the op amps can be powered from V_{OP} and V_{ON} , as shown.

11.26

$$(a) T_{A(max)} = T_J(max) - \Theta_{JA} P_D(max)$$

$$= 150 - 1 \times 60 = 90^\circ C.$$


(b) $P_D \leq (10-5)I = 5W$. $\Theta_{JA(max)} = (150 - 50)/5 = 20^\circ C/W$. A μA7805 operating in free air cannot handle it. A heat sink is required.

11.16

$$11.27 \quad I_O = 5 / [(1 + 18/2)1] = 0.5 \text{ A.}$$

$P_D(\max) = (V_{IN} - V_{OUT})_{\max} \times I_O = (18 - 0.5 \times 1) 0.5 = 8.75 \text{ W.}$ $\theta_{JA} = (150 - 60) / 8.75 = 10.3^\circ\text{C/W.}$ $\theta_{CA} = \theta_{JA} - \theta_{JC} = 10.3 - 5 = 5.3^\circ\text{C/W.}$ Allowing 0.6°C/W for the mounting surface, we have $\theta_{SA} = 4.7^\circ\text{C/W.}$

11.28

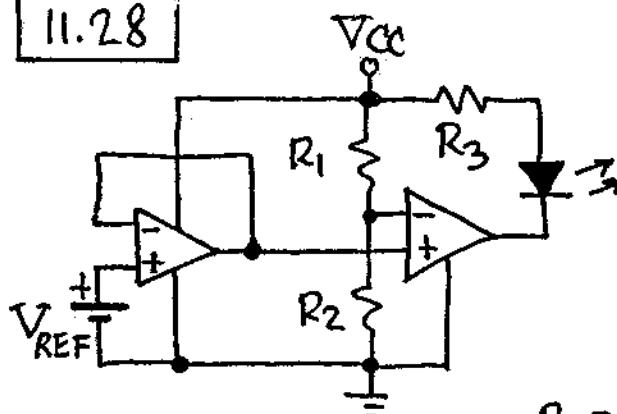

$$\frac{R_2}{R_1 + R_2} \times 4.75 =$$

$$0.2 \Rightarrow R_1 / R_2 = 22.75. \text{ Use}$$

$$R_1 = 1.02 \text{ k}\Omega \text{ and}$$

$$R_2 = 23.2 \text{ k}\Omega. \text{ Moreover,}$$

$$R_3 \cong (5 - 1.5) / 2 \cong 1.8 \text{ k}\Omega.$$

11.29 Let n be the transformer's turns ratio, so that the peak secondary voltage at 80% of the nominal line is $V_p = 0.8 \times n \times 120\sqrt{2} - V_D(m) = n 135.7 - 0.7 \text{ V.}$ Imposing $V_p \times R_3 / (R_4 + R_3) = V_{REF}$ gives $R_4 / R_3 = (135.7n - 0.7) / 2.5 - 1.$ For instance, if $n=1,$ imposing $R_3 = 10.0 \text{ k}\Omega$ gives $R_4 = 530 \text{ k}\Omega$ (use $523 \text{ k}\Omega, 1\%).$ Imposing $T_{DLY} \cong \frac{1}{2} \frac{1}{60} \cong 8 \text{ ms}$ gives $C_{UV} = 8 \times 10^{-3} / 12,500 \cong 0.68 \mu\text{F.}$ For the OV components use $R_1 = 10.0 \text{ k}\Omega, R_2 = 16.2 \text{ k}\Omega, C_{OV} = 8.2 \text{ mF.}$

11.30 (a) Both in the switched capacitor (SC) and the switched inductor (SL) the energy-storage element is used to transfer energy from one point of the circuit to another. In the SC the average current through C is zero; in the SL the average voltage across L is zero. Consequently, the polarities of V_I and V_o are opposite in the SL circuit, while the polarities of V_I and V_2 can be arbitrary in the SC circuit. This requires that the switches be bidirectional in the SC circuit; by contrast, the unidirectionality of current flow in the SL circuit allows for the second switch to be implemented with an ordinary diode, which is turned on by the kickback action of the inductor, without requiring any control signal. The duty cycle is immaterial in the SC circuit, provided C is given enough time to fully charge to V_1 and discharge to V_2 . By contrast, D and V_I and V_o are related by the last equation in Eq. (11.40) in the SL circuit.

11.18

$$(b) W_{cycle} = \frac{1}{2} L I_p^2 - \frac{1}{2} L (I_p - \Delta i_L)^2 =$$

$$\frac{1}{2} L (2 I_p \Delta i_L - \Delta i_L^2) = L (I_p - \frac{\Delta i_L}{2}) \Delta i_L = L I_L \Delta i_L.$$

$P = f_S W_{cycle} = f_S L I_L \Delta i_L.$

11.31

(a) Buck: L is in series with the load, so $I_L = I_0$. Boost: L is in series with the source, so $I_L = I_I$; but, $V_I I_I = V_0 I_0$, so $I_L = (V_0/V_I) I_0$. Buck-boost: $I_0 = I_D = [t_{OFF}/(t_{ON} + t_{OFF})] I_L$, or $I_L = (1 + t_{ON}/t_{OFF}) I_0 = (1 + N_d/V_I) \times I_0$. Moreover, in CCM, we have $I_p = I_L + \Delta i_L/2$, and $I_L(\min) = \Delta i_L/2$.

(b) $I_L = I_0 = 1A$; $I_p = 1 + 0.2/2 = 1.1A$;
 $I_0(\min) = I_L(\min) = 0.2/2 = 0.1A$.

(c) $I_L = (12/5)1 = 2.4A$; $I_p = 2.5A$;
 $I_0(\min) = (5/12)I_L(\min) = (5/12)0.1 \cong 42mA$.

(d) $I_L = (1 + 15/5)I_0 = 4A$; $I_p = 4.1A$;
 $I_0(\min) = I_L(\min)/4 = 25mA$.

11.32

By Eq. (11.39), $I_2 = \frac{D}{1-D} (V_I - 0.5) + 0.5$, $5V \leq V_I \leq 10V$. This gives $71.9\% \geq D \geq 54.8\%$.

I_I is maximum when $V_I = 5V$. Using Eq. (11.41), $I_I(\max) \cong (12/5)1 = 2.4A$. For a better estimate, include also the losses

11.19


in the diode and the transistor, $P_{\text{losses}} \approx 0.5 \times 2.4 = 1.2 \text{ W}$. Writing $\Delta I_{\text{(max)}} \times 5 = 12 \times 1 + 1.2$ gives $I_{\text{I(max)}} = 2.64 \text{ A}$.

11.33

$I_L \approx (1+15/15)I_0 = 2I_0; 0.2 \text{ A} \leq I_0 \leq 1 \text{ A}$
 $\Rightarrow 0.4 \text{ A} \leq I_L \leq 2 \text{ A} \Rightarrow \Delta I_L = 0.8 \text{ A}$. $L = [15/(1+15)] / (150 \times 10^3 \times 0.8) = 62.5 \mu\text{H}$. Letting $\Delta V_C = 1/3 V_{D(\text{max})} = 50 \text{ mV}$, we get $C = [1(1+15/15)] / (150 \times 10^3 \times 50 \times 10^{-3}) = 267 \mu\text{F}$. At full load, $\Delta i_C = \Delta i_D = I_p = I_L + \Delta i_L/2 = 2 + 0.8/2 = 2.4 \text{ A}$. So, $\text{ESR} = (100 \text{ mV}) / (2.4 \text{ A}) = 41.7 \text{ m}\Omega$. Summarizing, $L = 62.5 \mu\text{H}$, $C = 267 \mu\text{F}$, $\text{ESR} = 42 \text{ m}\Omega$.

11.34

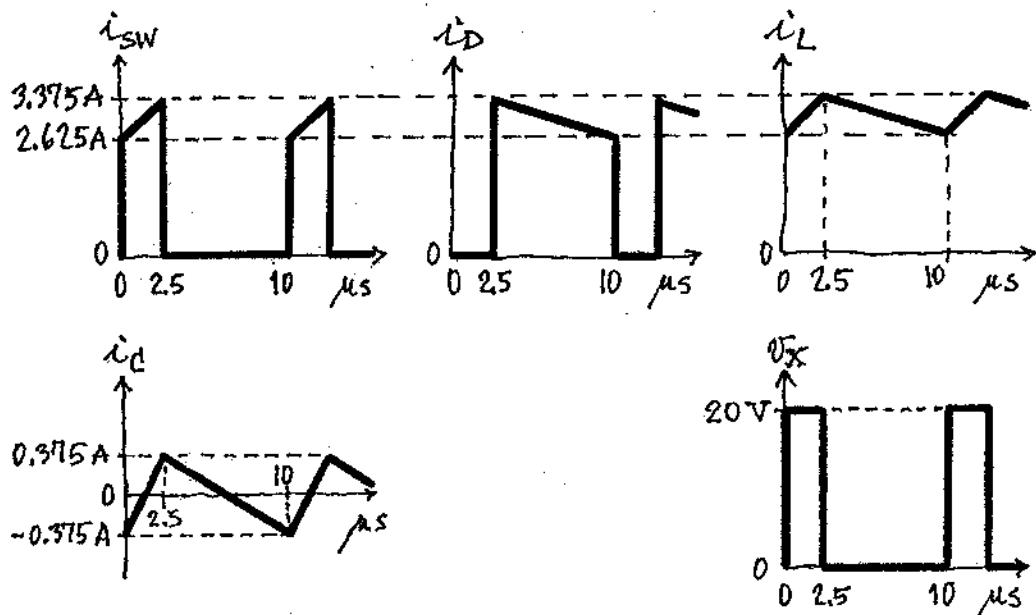(a) $T = 1/f_3 = 10 \mu\text{s}$; $D = 5/20 = 0.25$; $t_{ON} = 2.5 \mu\text{s}$. $I_L = I_0 = 3 \text{ A}$; $\Delta I_L = [5(1-5/20)] / (10^5 \times 50 \times 10^{-6}) = 0.75 \text{ A}$; $I_p = 3 + 0.75/2 = 3.375 \text{ A}$.



11.20

$$(b) \text{ During } t_{on}, \Delta i_L = \frac{20 - 5}{50 \times 10^{-6}} 2 \times 10^{-6} = 0.6 \text{ A.}$$


Consequently, $I_p = 0.6 \text{ A}$. The amount of time Δt it takes for i_L to return to zero is such that

$$0.6 \text{ A} = \frac{5}{50 \times 10^{-6}} \Delta t, \text{ or } \Delta t = 6 \mu\text{s}. \text{ During the time}$$

intervals for which $i_L = 0$, we also have $v_L = 0$. Moreover, the average currents are found as

$$I_0 = I_L = \frac{1}{10 \mu\text{s}} \int_0^{10 \mu\text{s}} i_L dt = \frac{1}{10 \mu\text{s}} \frac{(8 \mu\text{s}) \times 0.6}{2} = 0.24 \text{ A.}$$

Thus, the waveforms are as shown.

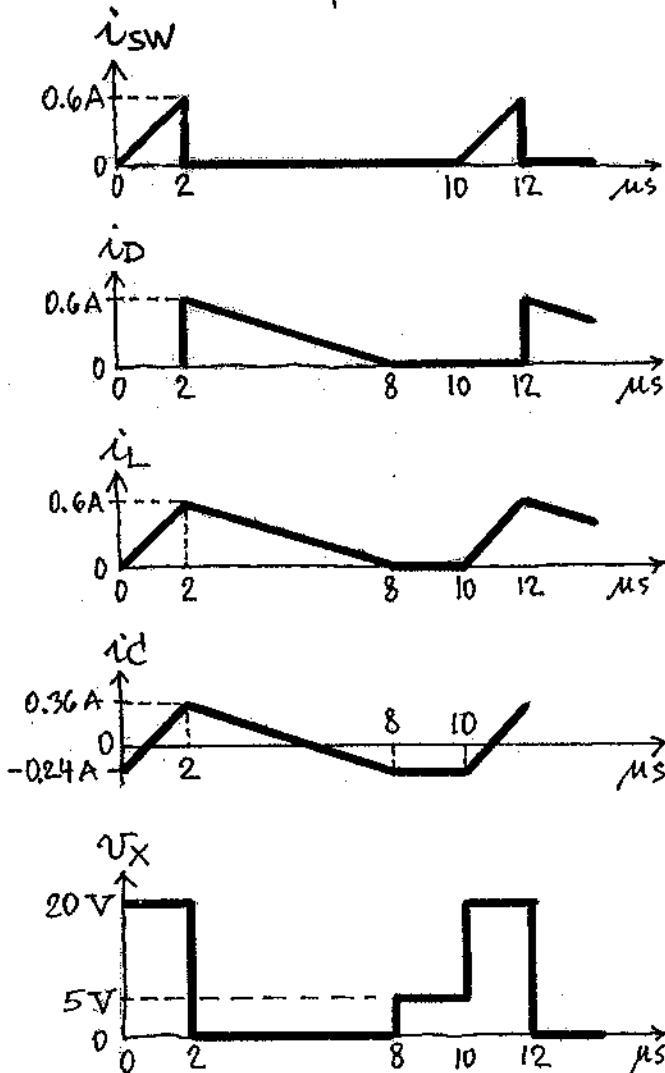

11.21

11.35 (a) $D = 19.2\%$. $P_{SW} \cong 0.58 + 0.9 = 1.48 \text{ W}$; $P_D \cong 1.72 + 0.45 = 2.17 \text{ W}$; $P_{cap} \cong 0$; $P_{coil} \cong 0.25 \text{ W}$; assuming $I_Q \cong \text{constant}$, $P_{controller} \cong 30 \times 10 = 0.3 \text{ W}$. $P_{diss} \cong 4.2 \text{ W}$; $\eta = 100 \times 15 / (15 + 4.2) = 78\%$.


(b) $D = 38.8\%$. $P_{SW} \cong 1.16 + 0.9 = 2.06 \text{ W}$; $P_D \cong 1.29 + 0.45 = 1.74 \text{ W}$; $P_{cap} \cong 0$; $P_{coil} \cong 0.5 \text{ W}$; $P_{controller} \cong 0.15 \text{ W}$; $P_{diss} = 4.45 \text{ W}$; $\eta = 77\%$.

11.36 $V_o/V_I = D = V_d/V_{sm}$; $dV_o/dV_d|_{V_I=V_I} = V_I = V_I/V_{sm}$.

$$\begin{aligned}\frac{V_o}{V_c} &= \frac{V_I}{V_{sm}} \frac{ESR + 1/sC}{R_{coil} + sL + ESR + 1/sC} \\ &= \frac{V_I}{V_{sm}} \frac{1 + s(ESR)C}{1 + s^2LC + s(R_{coil} + ESR)C} \\ &= \frac{V_I}{V_{sm}} \frac{1 + s/\omega_2}{1 + (s/\omega_0)^2 + (s/\omega_0)/Q}\end{aligned}$$

$$\omega_0 = 1/\sqrt{LC}, \omega_2 = 1/ESR \times C, Q = 1/[(R_{coil} + ESR)\sqrt{C/L}]$$

11.37

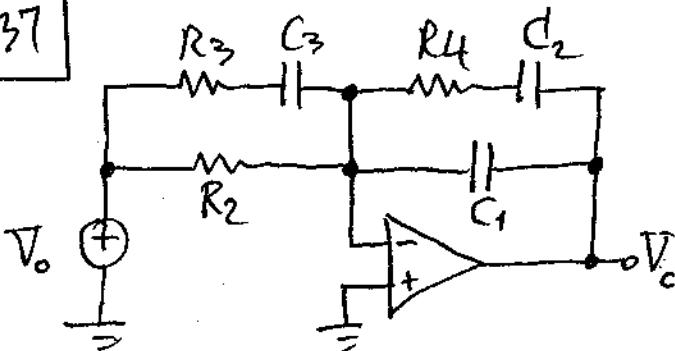

11.22

$$\frac{1}{Z_1} = \frac{1}{R_2} + \frac{1}{R_3 + 1/sC_3} = \frac{1+s(R_2+R_3)C_3}{R_2(1+sR_3C_3)}$$


$$\begin{aligned}\frac{1}{Z_2} &= sC_1 + \frac{1}{R_4 + 1/sC_2} = \frac{sC_1(1+sR_4C_2) + sC_2}{1+sR_4C_2} \\ &= \frac{s(C_1+C_2)[1+sR_4C_1C_2/(C_1+C_2)]}{1+sR_4C_2}\end{aligned}$$

$$\begin{aligned}H_{EA} &= \frac{V_c}{V_o} = -\frac{Z_2}{Z_1} \\ &= -\frac{[1+s(R_2+R_3)C_3](1+sR_4C_2)}{sR_2(C_1+C_2)[1+sR_4C_1C_2/(C_1+C_2)](1+sR_3C_3)} \\ &= -\frac{(1+jw/w_1)(1+jw/w_2)}{(jw/w_5)(1+jw/w_3)(1+jw/w_4)}\end{aligned}$$

$$w_1 = \frac{1}{R_4C_2}; w_2 = \frac{1}{(R_2+R_3)C_3} \rightarrow \frac{1}{R_2C_3}; w_3 = \frac{1}{R_3C_3};$$

$$w_4 = \frac{C_1+C_2}{R_4C_1C_2} \rightarrow \frac{1}{R_4C_1}; w_5 = \frac{1}{R_2(C_1+C_2)} \rightarrow \frac{1}{R_2C_2}.$$

11.38

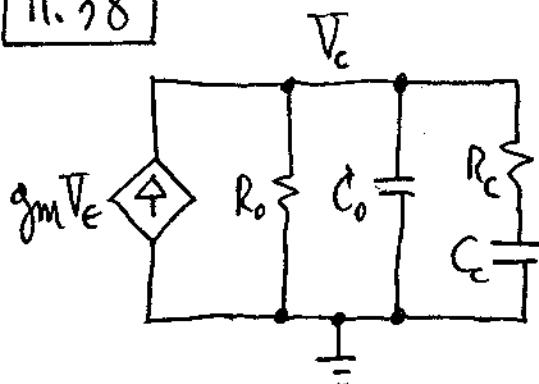

$$Z_c = R_c + 1/sC_c = (1+sR_cC_c)/sC_c;$$

$$H_{EA} = V_c/V_e = g_m \left(R_0 \parallel \frac{1}{sC_0} \parallel Z_c \right);$$

$$\begin{aligned}\frac{g_m}{H_{EA}} &= \frac{1}{R_0} + sC_0 + \frac{sC_c}{1+sR_cC_c} \\ &= \frac{1}{R_0} \frac{1+s^2R_0C_0R_cC_c + s(R_cC_c + 2R_0C_c)}{1+sR_cC_c}\end{aligned}$$

$$\cong \frac{1}{R_0} \frac{1+s^2R_0C_0R_cC_c + s2R_0C_c}{1+sR_cC_c}$$

11.23

$$H_{EA} \approx g_m R_o \frac{1+s/\omega_z}{1+(s/\omega_0)^2 + (s/\omega_0)/Q}$$

$$\omega_0 = \frac{1}{(R_o C_o R_c C_c)^{1/2}}, \quad \omega_z = \frac{1}{R_c C_c}, \quad Q = \frac{1}{2} \sqrt{R_c C_o / R_o C_c}$$

Problem 11.38
 Vepsilon 1 0 ac 1
 R 1 0 1
 gm 0 2 1 0 4.4m
 Ro 2 0 180k
 Co 2 0 3pF
 Rc 2 3 1k
 Cc 3 0 1uF
 .ac dec 10 0.1Hz 10kHz
 .probe
 .end

