

10.1

10.1

$$Z_p = R_p // [1/(j\omega C_p)] = \frac{R_p}{1 + j(f/f_p)} ;$$

$$f_p = \frac{1}{2\pi R_p C_p} ; Z_s = R_s + \frac{1}{j\omega C_s} = R_s \frac{1 + j(f/f_s)}{j(f/f_s)} ,$$

$$f_s = \frac{1}{2\pi R_s C_s} ; \frac{V_p}{V_o} = \frac{Z_p}{Z_p + Z_s} = \frac{1}{1 + Z_s/Z_p} ;$$

$$\frac{V_p}{V_o} = \frac{1}{1 + \frac{R_s}{R_p} \frac{[1 + j(f/f_s)][1 + j(f/f_p)]}{j(f/f_s)}}$$

$$\frac{1}{1 + \frac{R_s}{R_p} \frac{1 - f^2/(f_p f_s) + j f (1/f_p + 1/f_s)}{j(f/f_s)}} .$$

Let  $f_0 = 1/\sqrt{f_p f_s}$ . Then, for  $f = f_0$ , we obtain

$$\frac{V_p}{V_o} = \frac{1}{1 + \frac{R_s}{R_p} \left(1 + \frac{f_0}{f_p}\right)} = \frac{1}{1 + \frac{R_s}{R_p} + \frac{C_p}{C_s}} .$$

For a sustained sinusoid we want  $A = 1 + R_s/R_p + C_p/C_s = 1 + R_2/R_1$ . This requires  $R_2/R_1 = R_s/R_p + C_p/C_s$ .

10.2

$$T(s) = \frac{1 + R_2/R_1}{3 + s/\omega_0 + \omega_0/s} , \omega_0 = 2\pi 10^3 \text{ rad/s},$$

$1 + R_2/R_1 = 3.21, 3.00, 2.81$ . To find the poles, impose  $T(s) = 1$ . This yields

$$(s/\omega_0)^2 - (R_2/R_1 - 2)(s/\omega_0) + 1 = 0$$

$$s = \omega_0 \frac{(R_2/R_1 - 2) \pm [(R_2/R_1 - 2)^2 - 4]^{1/2}}{2} . \text{ For } R_2/R_1 =$$

2.21, 2.00, and 1.81, we get, respectively,

10.2

$$s = (+0.1050 \pm j0.9945)2\pi 10^3 \text{ Complex } \text{Np/s}$$

$$s = \pm j2\pi 10^3 \text{ rad/s}$$

$$s = (-0.0950 \pm j0.9955)2\pi 10^3 \text{ Complex } \text{Np/s.}$$

**10.3** (a) Since OA<sub>1</sub> keeps the bottom terminal of R<sub>p</sub> at virtual ground potential, we can apply the results of Problem 10.1 and write

$$B(jf_0) = \frac{V_{p2}}{V_o} = \frac{1}{1 + R_s/R_p + C_p/C_s}, \quad f_0 = \frac{1}{2\pi(R_p R_s C_p C_s)^{1/2}}$$

By the superposition principle we have  $V_o = -(R_2/R_1)(-R_3/R_p)V_{p2} + (1+R_2/R_1)V_{p2}$ , or


$$A = \frac{V_o}{V_{p2}} = 1 + \frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_p} \right). \quad \text{Imposing } AB(jf_0) \geq 1 \\ \text{gives } (R_2/R_1) \left( 1 + R_3/R_p \right) = R_s/R_p + C_p/C_s.$$

(b) Letting  $R_2/R_1 = C_p/C_s$  gives  $(R_2/R_1) \times (R_3/R_p) = R_s/R_p$ , or  $R_3 = (R_s/R_p)R_2$ .

(c)  $215 \text{ Hz} \leq f_0 \leq 21.5 \text{ kHz.}$

**10.4** Let  $C = 1 \text{ mF}$ ,  $2C = 2 \text{ mF}$ . Then,  $R = 1/(2\pi 10^4 \times 10^{-9}) = 15.915 \text{ k}\Omega$  (use  $15.8 \text{ k}\Omega, 1\%$ ). Implement the variable resistance with a  $14.7-\text{k}\Omega$  resistor in series with a  $2-\text{k}\Omega$  pot. For a peak amplitude of  $5 \text{ V}$ , impose  $5 = (R_1/R_2)(15+0.7)+0.7$ , which gives  $R_2/R_1 = 3.65$ . Use  $R_1 = 30 \text{ }\mu\Omega$ ,  $R_2 = 110 \text{ k}\Omega$ .

10.3


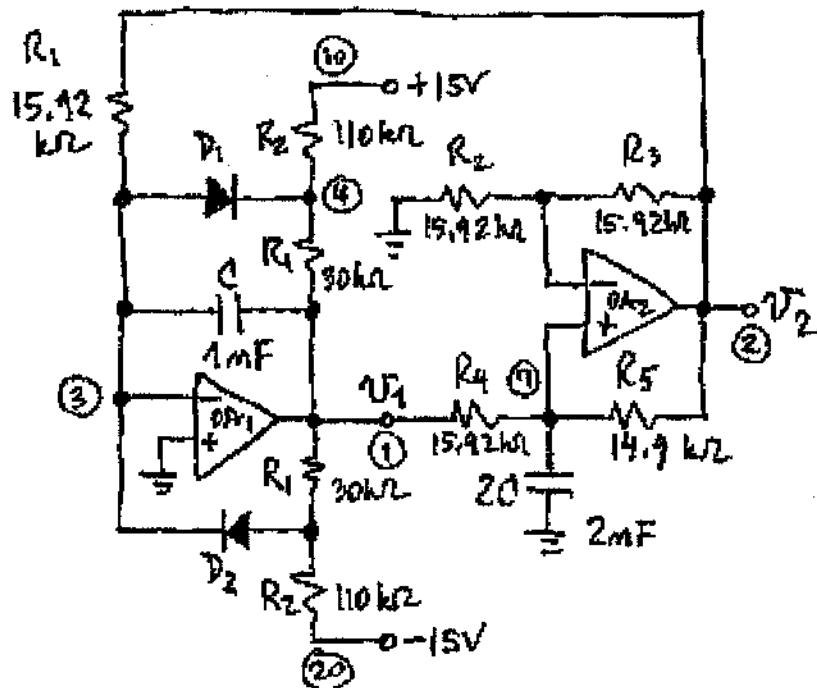


Running the accompanying PSpice program with two different sets of initial conditions gives the plots shown. Because of nonidealities, the actual frequency of oscillation is 9.74 kHz.

Problem 10.4

```
.lib eval.lib
VCC 10 0 dc 15V
VER 20 0 dc -15V
C 1 3 1mF IC=1V
D1 1 4 D6148
D2 5 9 D4149
.model D4149 D(IS=0.1p Rs=16 CJO=2p Tt=12n Bv=100 Ibv=0.1p)
R1UP G 10 110k
R1UP 4 1 30k
N1DN 1 5 30k
R2DN 5 20 110k
R1 3 2 15.92k
R2 0 6 15.92k
R3 6 2 15.92k
R4 1 7 15.92k
RS 7 2 14.9k
C+C 7 0 2mF IC=0
XQA1 0 3 10 20 1 uA741
XQA2 7 6 10 20 2 uA741
.tran 10us 2ms 0s 10us UIC
.probe
.end
```

10.4

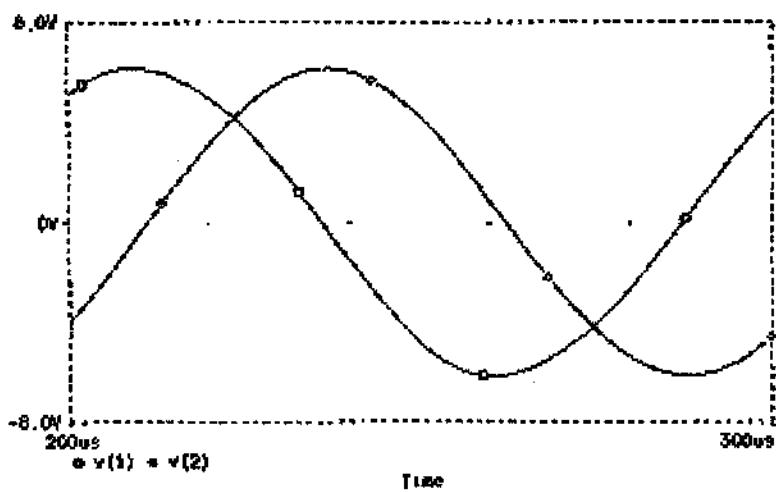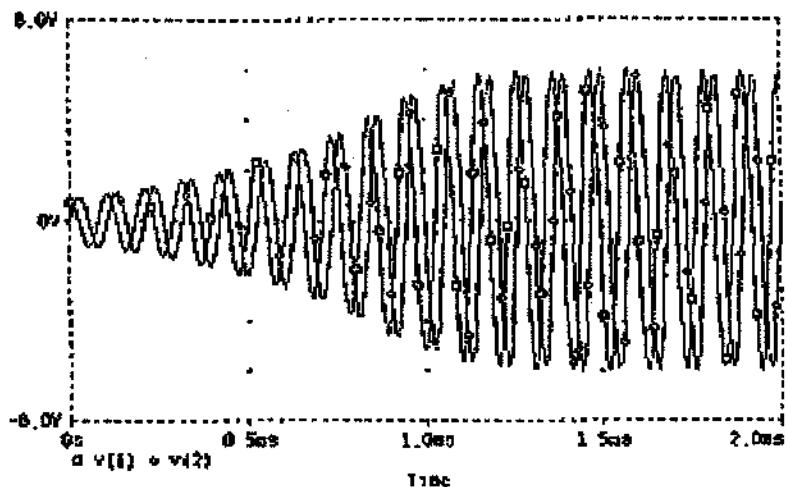

**10.5** At power turn-on, when the limiter is not yet operative, we have  $V_1 = -(1/R_0)V_2$ . According to Fig. 2.6(b), the voltage developed by the 2C capacitance is  $V_{2c} = \frac{V_1}{R} (R + \frac{1}{s2C})$ , where  $R_0 = -R/\epsilon$ , by Eq. (2.17).

Substituting, we get  $V_2 = (1 + R/R) V_{2c} = 2 \times (V_1/R) \times (-R/\epsilon) / [1 - s(R/\epsilon)2C] = -2V_1/(\epsilon - sR2C)$ .

$$T(s) = \frac{V_2}{V_1} \times \frac{V_1}{V_2} = \left( -\frac{2}{\epsilon - sR2C} \right) \times \left( -\frac{1}{sR} \right) =$$


10.5

$\frac{2}{\epsilon sRC - s^2 2(RC)^2} \cdot \text{Imposing } T(s) = 1 \text{ gives}$   
 $2(RC)^2 s^2 - \epsilon RC s + 2 = 0, \text{ whose solution are}$   
 $s = \frac{\epsilon \pm (\epsilon^2 - 16)^{1/2}}{4RC} \approx \frac{\epsilon/4 \pm j1}{RC}.$

10.6

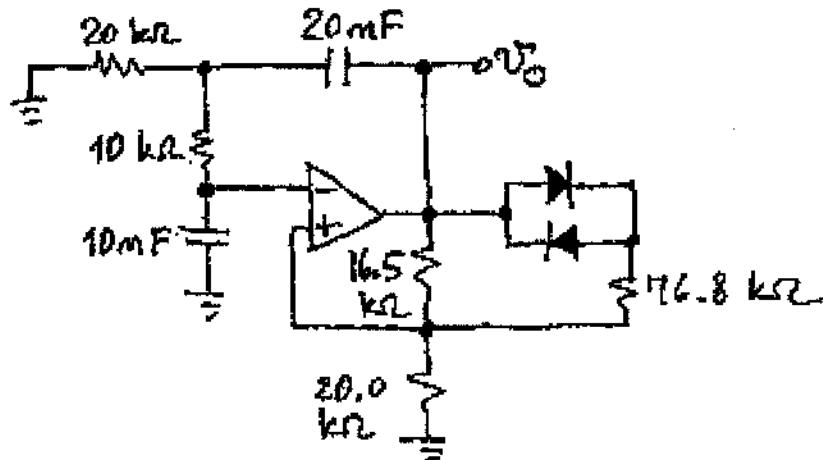(a) With the given component values we set  $\Omega = 2/(7-4K)$ . For oscillation to start, we need  $\Omega < 0$ , or  $K > 7/4 \Rightarrow R_B/R_A > 3/4$ ; for oscillation to be sustained, we need  $R_B/R_A = 3/4$ . Let  $R_A = 20.0 \text{ k}\Omega$ . Then,  $(3/4)R_A = 15 \text{ k}\Omega$ . Implement  $R_B$  with a  $16.5 \text{ k}\Omega$  resistor, and a diode limiter with a resistance of  $1/13.6 - 1/16.5 = 76.8 \text{ k}\Omega$ , as shown.

$$(b) f_0 = 1/(2\pi\sqrt{20\times 10^3 \times 20\times 10^{-18}}) \\ \approx 796 \text{ Hz.}$$



10.6

10.7

KCL when  $V_0 = +13V$ :

$$\frac{13 - V_{TH}}{20} = \frac{V_{TH}}{10} + \frac{V_{TH} - (-15)}{30} \Rightarrow V_{TH} = 0.82V.$$

KCL when  $V_0 = -13V$ :

$$\frac{0 - V_{TL}}{10} = \frac{V_{TL} + 13}{20} + \frac{V_{TL} + 15}{30} \Rightarrow V_{TL} = -6.27V.$$


$$T = 330 \times 10^3 \times 10^{-9} = 330 \mu s. \quad T_H = 330 \ln$$

$$[(13 + 6.27)/(13 - 0.82)] = 151.4 \mu s. \quad T_L =$$

$$330 \times \ln [(-13 - 0.82)/(-13 + 6.27)] = 237 \mu s.$$

$$f_0 = 1/(237 + 151) = 2.57 \text{ kHz}. \quad D = 100 \times \\ 151 / (151 + 237) = 39\%.$$

10.8

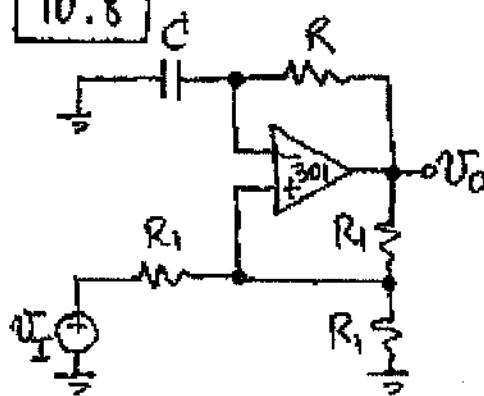

Superposition:

$$V_P = \frac{R_1 || R_1}{R_1 || R_1 + R_2} (V_I + V_0) \\ = (V_I + V_0)/3$$

$$V_0 = \pm V_{sat} = \pm 13V$$

$$\Rightarrow V_T = (V_I \pm 13V)/3.$$

During  $T_H$  we have  $V_0 = V_{TL} = (V_I - 13)/3$  V,  
 $V_{OO} = 13V$ ,  $V_1 = V_{TH} = (V_I + 13)/3$  V; by Eq. (10.3),  
 $T_H = RC \ln [(V_I - 52)/(V_I - 26)]$ .


During  $T_L$  we have  $V_0 = V_{TH}$ ,  $V_{OO} = -13V$ ,  $V_1 = V_{TL}$ , so  $T_L = RC \ln [(V_I + 52)/(V_I + 26)]$ .

$$D = 100 / (1 + T_L/T_H) = \frac{100}{1 + (\ln \frac{V_I + 52}{V_I + 26}) / (\ln \frac{V_I - 52}{V_I - 26})}$$

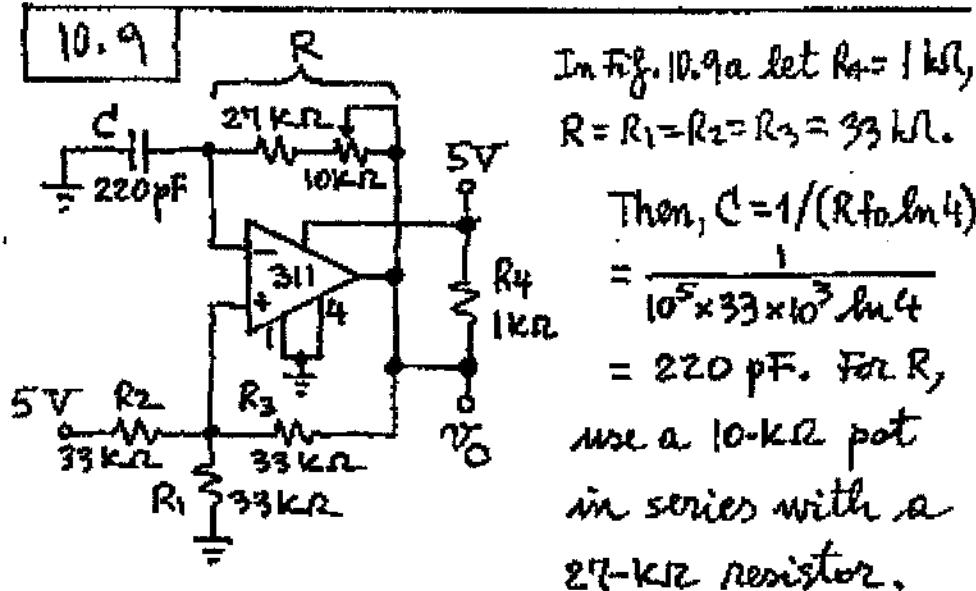10.7

$$f_0 = \frac{1}{T_L + T_H} = \frac{1}{RC \ln [(V_T^2 - 52^2)/(V_T^2 - 26^2)]}$$

To prevent the arguments of the logarithms from becoming negative, we must restrict  $V_T$  within the range  $-26 \text{ V} < V_T < 26 \text{ V}$ .



In Fig. 10.12a let  $C = 220 \text{ pF}$ . Then, for  $V_T = V_{DD}/2$ , we get  $R = 1/2.2C f_0 = 2.0 \text{ k}\Omega$ . Implement  $R$  with a 15-kΩ resistor in series with a 10-kΩ pot, and let  $10R = 200 \text{ k}\Omega$ .

10.10 (a) Use the circuit of Fig. 10.9a. Assume  $V_{OL} = 0\text{V}$  and  $V_{OH} = V_{CC}$ , and arbitrarily impose  $V_{TL} = (V_2)V_{TH}$ . Letting  $T_H/(T_L + T_H) = 0.6$  gives

$$\frac{\ln \left[ (V_{CC} - V_{TL}) / (V_{CC} - V_{TH}) \right]}{\ln 2 + \ln \left[ (V_{CC} - V_{TL}) / (V_{CC} - V_{TH}) \right]} = 0.6, \text{ or}$$

10.8

$(\ln x)/(ln 2 + \ln x) = 0.6$ ,  $x = (V_{CC} - V_{TL})/(V_{CC} - V_{TH})$ . Solving gives  $x = \exp(1.5 \ln 2)$ , or  $\exp(1.5 \ln 2) = (V_{CC} - V_{TL})/(V_{CC} - 2V_{TL})$ . Solving,  $V_{TL} = V_{CC} [\exp(1.5 \ln 2) - 1] / [2 \exp(1.5 \ln 2) - 1] = 0.3926 V_{CC}$ , and  $V_{TH} = 0.7853 V_{CC}$ . By Eq. (9.13),

$$\frac{1}{R_2} = 0.6464 \left( \frac{1}{R_1} + \frac{1}{R_3} \right), \quad \frac{1}{R_1} = 0.2735 \left( \frac{1}{R_2} + \frac{1}{R_3} \right).$$

Let  $R_4 = 2.2 \text{ k}\Omega$  and  $R_3 = 100 \text{ k}\Omega$ . Then,  $R_1 = 182.8 \text{ k}\Omega$  (use 182  $\text{k}\Omega$ ) and  $R_2 = 100 \text{ k}\Omega$ .


(b) We now get  $x = \exp[(\ln 2)/1.5]$ , which results in  $V_{TL} = 0.2701 V_{CC}$  and  $V_{TH} = 0.5402 V_{CC}$ . Use  $R_4 = 2.2 \text{ k}\Omega$ ,  $R_3 = 100 \text{ k}\Omega$ ,  $R_1 = 58.74 \text{ k}\Omega$  (use 59.0  $\text{k}\Omega$ ), and  $R_2 = 100 \text{ k}\Omega$ .

10.11 (a) Let  $C = 220 \text{ pF}$ . Then,  $R = 1/(2.2 \times 10^5 \times 220 \times 10^{-12}) = 20.7 \text{ k}\Omega$  (use 20.5  $\text{k}\Omega$ ).



(b) It is readily seen that  $f_0$  is maximized when  $V_T$  is halfway between 0 and  $V_{DD}$  ( $V_T = 2.5 \text{ V}$ ), and minimized when  $V_T$  is farthest away from 2.5 V ( $V_T = 4 \text{ V}$ ). We have  $f_0(V_T = 2.5 \text{ V}) = 100 \text{ kHz}$ , and  $f_0(V_T = 4 \text{ V}) = 84.42 \text{ kHz}$ , indicating a percentage deviation of  $100 \times [(84.42 - 100)/100] = -15.58\%$  maximum.

10.9

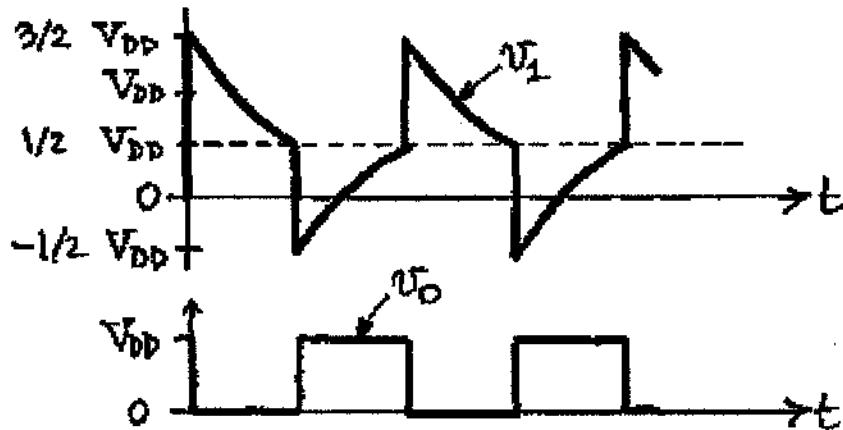**10.12** Letting  $V_1$  denote the voltage at the node common to the resistors and the capacitor, we have the accompanying waveforms.



Applying Eq. (10.11),  $f_0 = 1/2\pi RC$ .

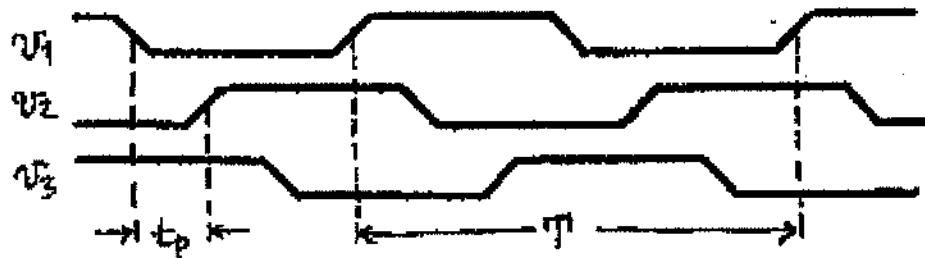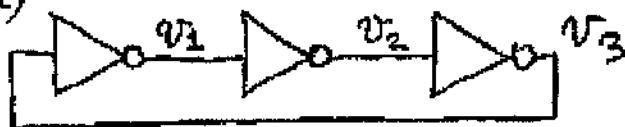**10.13 (a)**

$$T = 6t_p \Rightarrow t_p = 1/6f_0.$$



(b) To oscillate, the circuit needs an odd number of gates within the loop. With an even number, feedback is positive and the circuit will just sit in one of its two possible states permanently.

10.10

10.14 Let  $C = 330 \text{ pF}$ . Then,  $R = 10 \times 10^{-6} \times (0.69 \times 330 \times 10^{-12})^{-1} = 43.7 \text{ k}\Omega$  (use  $43.2 \text{ k}\Omega$ ).

(b)  $T_{(\text{typ})} = 0.69 \times 43.2 \times 10^3 \times 330 \times 10^{-12} = 0.69 \times 14.26 = 9.88 \mu\text{s}$ ;  $T_{(\text{min})} = 14.26 \ln [5/(5-1.1)] = 3.54 \mu\text{s}$ .  $T_{(\text{max})} = 14.26 \ln [5/(5-4)] = 22.94 \mu\text{s}$ .  $100(3.54 - 9.88)/9.88 = \sim 64\%$ ;  $100(22.94 - 9.88)/9.88 = 132\%$ . Thus,  $-64\% < \Delta T (\%) < 132\%$ .


10.15

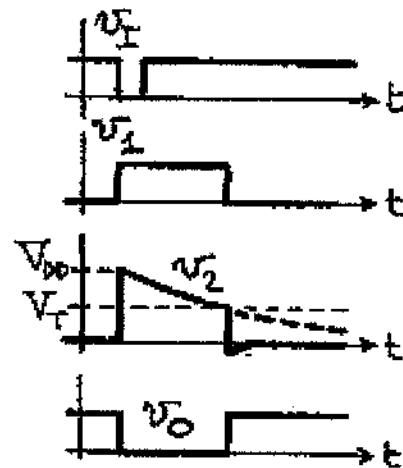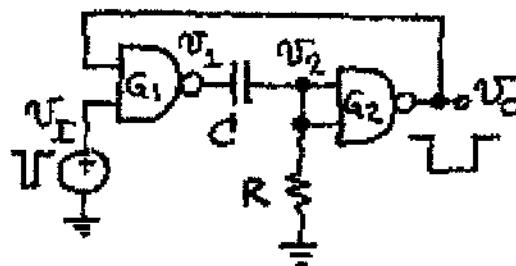

$V_1$  must be a negative-going pulse and  $R$  must be returned to ground to ensure a logic high at the upper input to  $G_1$ . Using  $V_0 = V_{DD}$ ,  $V_{DD} = 0$ ,  $V_1 = V_T$ , and  $\Delta t = T$  in Eq. (10.3) we obtain  $T = RC \ln(V_{DD}/V_T)$ .

10.11




10.16

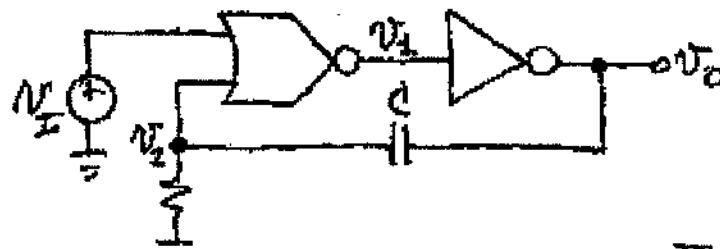

$$T = R C \ln \frac{0 - V_{DD}}{0 - V_T} = R C \ln \frac{1}{0.4}$$


$$= 10^5 \times 220 \times 10^{-12} \ln 2.5$$

$$= 20.16 \mu\text{s.}$$

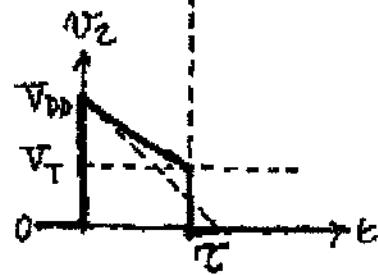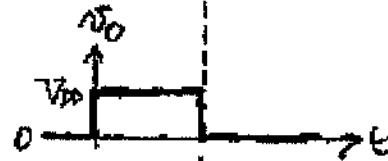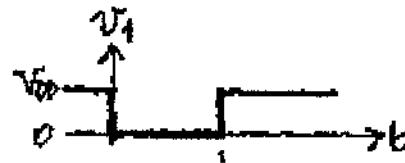

10.17

(a)

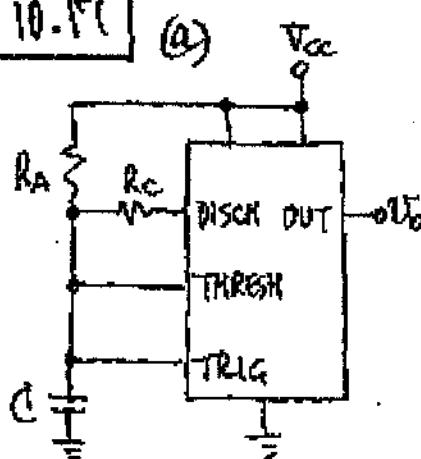

When Q inside the 555 is OFF, C charges toward  $V_{CC}$  via  $R_A$ , so  $T_H = R_A C \ln 2$ . When Q is saturated, C discharges toward  $V_{DD} = \frac{R_C}{R_A + R_C} V_{CC}$

10.12

via the parallel  $R_A \parallel R_C$ . Applying Eq. (10.3) with  $V_0 = (2/3)V_{cc}$ ,  $V_I = (1/3)V_{cc}$ ,  $V_{os} = R_C V_{cc}/(R_A + R_C)$ , and  $\Delta t = T_L$  we get, after simplification,

$$T_L = (R_A \parallel R_C) C \ln \frac{2R_A - R_C}{R_A - 2R_C}. \text{ For } D = 50\%, \text{ impose}$$


$$T_L = T_H, \text{ or } \frac{R_A R_C}{R_A + R_C} C \ln \frac{2R_A/R_C - 1}{R_A/R_C - 2} = R_A C \ln 2, \text{ or}$$

$$R_A/R_C = [\ln \frac{2R_A/R_C - 1}{R_A/R_C - 2}] / [\ln 2] - 1. \text{ Solving by iteration gives } R_A/R_C = 2.36218.$$


(b) Let  $C = 1 \mu F$ . With  $D = 50\%$ ,  $T = 2T_H \geq T_H = 1/2f_0 = 1/(2 \times 10^4) = 50 \mu s$ . Then,  $R_A = T_H/C \ln 2 = 72.13 \text{ k}\Omega$  (use  $71.5 \text{ k}\Omega$ ). Then,  $R_C = 71.5/2.36218 = 30.27 \text{ k}\Omega$  (use  $30.1 \text{ k}\Omega$ ).

10.18

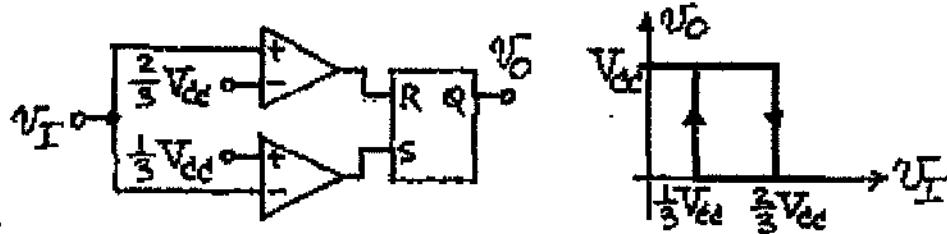(a) Since CMOS swings from rail to rail,  $V_{OH} = V_{cc}$ ,  $V_{OL} = 0V$ . Moreover,  $V_i < \frac{1}{3}V_{cc} \Rightarrow Q = \text{HIGH} \Rightarrow V_o = V_{OH}$ ;  $V_i > \frac{2}{3}V_{cc} \Rightarrow Q = \text{LOW} \Rightarrow V_o = V_{OL}$ . Thus, VTC is as shown:



10.13

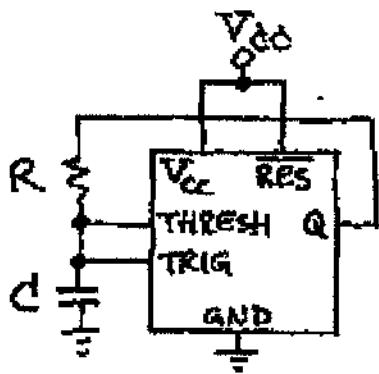

(b) Try  $C = 330 \text{ pF}$ . Then,

$$R = \frac{1}{10^5 \times 330 \times 10^{-12} \ln 4} = 22 \text{ k}\Omega.$$

Since the thresholds are symmetric, the duty cycle is 50%.

10.19

$$T = 1.1 RC, T = 1 \text{ ms} \Rightarrow 10^{-3} = 1.1 \times$$

$$(R_1 + R_2)C.$$


$$T = 1 \text{ s} \Rightarrow 1 = 1.1 \times$$

$$(10^6 + R_2)C.$$

Solving gives

$$C = 1 \mu\text{F} \text{ and}$$

$$R_1 = 1 \text{ k}\Omega.$$

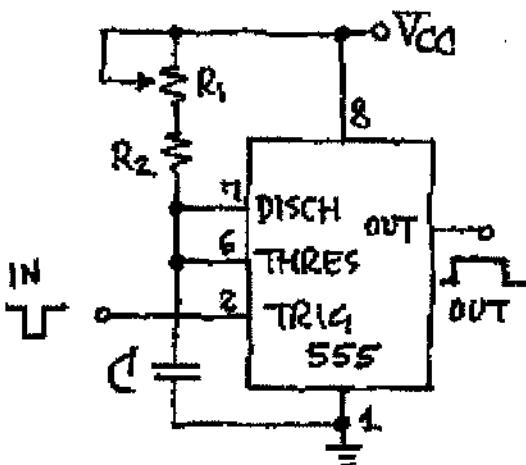

10.20

$T = RC \ln [1/(1 - V_{TH}/V_{CC})]$ , where  $RC = 10 \times 10^{-6} / \ln 3$ . Imposing  $20 \times 10^{-6} = (10^{-5} / \ln 3) \times \ln [1/(1 - V_{TH}/15)]$  gives  $V_{TH} = (8/9)15 \text{ V}$ . Likewise, imposing  $5 = (10 / \ln 3) \ln [1/(1 - V_{TH}/15)]$  gives  $V_{TH} = (1 - 1/\sqrt{3})15 = 6.34 \text{ V}$ .

10.21

$f_0 = 10 \text{ kHz} \Rightarrow T = 100 \mu\text{s}$ . Let  $T_L = 25 \mu\text{s}$ , so  $T_H = 75 \mu\text{s}$ . Following Example 10.3, we get  $C = 1 \mu\text{F}$ ,  $R_A = 72.1 \text{ k}\Omega$ ,  $R_B = 36.1 \text{ k}\Omega$ . Eq. (10.13):

10.14

$$\tau - 25\mu s = (108.2 \mu s) \ln \left[ \frac{(1-0.5V_{TH}/5)}{(1-V_{TH}/5)} \right].$$

$$f_0 = 5 \text{ kHz} \Rightarrow \tau = 200 \mu s \Rightarrow 200 - 25 = 108.2 \times$$


$$\ln \left[ \frac{(1-0.1V_{TH})}{(1-V_{TH}/5)} \right] \Rightarrow \frac{(1-0.1V_{TH})}{(1-0.2V_{TH})}$$

$$= e^{175/108.2} \Rightarrow V_{TH} = 4.45 \text{ V. } f_0 = 20 \text{ kHz} \Rightarrow$$

$$\tau = 50 \mu s \Rightarrow \frac{(1-0.1V_{TH})}{(1-0.2V_{TH})} = e^{\frac{25}{108.2}} \Rightarrow$$

$$V_{TH} = 1.71 \text{ V.}$$

10.22

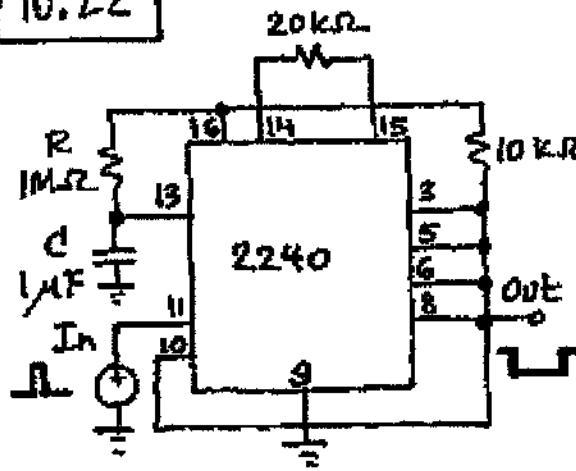


Let  $C = 1 \mu F$ . Then,

$$R = \frac{1}{10^{-6}} = 1 \text{ M}\Omega.$$

$3 \text{ min} = 180 \text{ sec} = 128 + 32 + 16 + 4$  sec. Thus, WIRE-OR pins # 3, 5, 6, and 8.

10.23

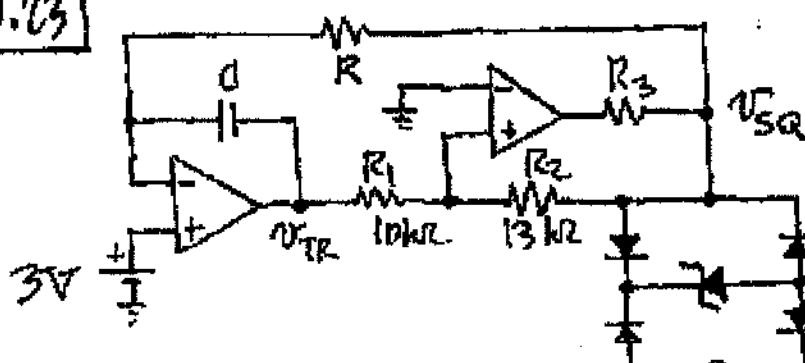


$V_{SQ}$  alternates between

$$\pm (2V_D(m) + V_Z) = \pm (1.4 + 5.1) = \pm 6.5 \text{ V.}$$

$V_{TQ}$  alternates between  $\pm (10/13) 6.5 = \pm 5 \text{ V.}$


10.15

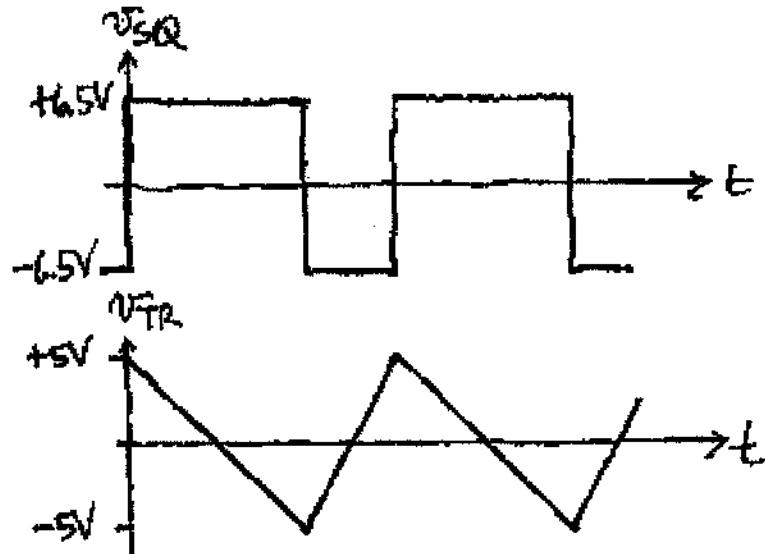

During  $T_H$ ,  $I_C = (6.5 - 3)/R = 116.6 \mu A$ , and  
 $T_H = \frac{C}{I_C} [5 - (-5)] = \frac{10^{-9}}{116.6 \times 10^{-6}} 10 = 85.7 \mu s$

During  $T_L$ ,  $I_C = (6.5 + 3)/R = 316.6 \mu A$ , and  
 $T_L = 10^{-8}/(316.6 \times 10^{-6}) = 31.6 \mu s$ .  $f_0 = 1/(T_L + T_H)$   
 $= 8.526 \text{ kHz}$ ,  $D(\%) = 73\%$

10.24

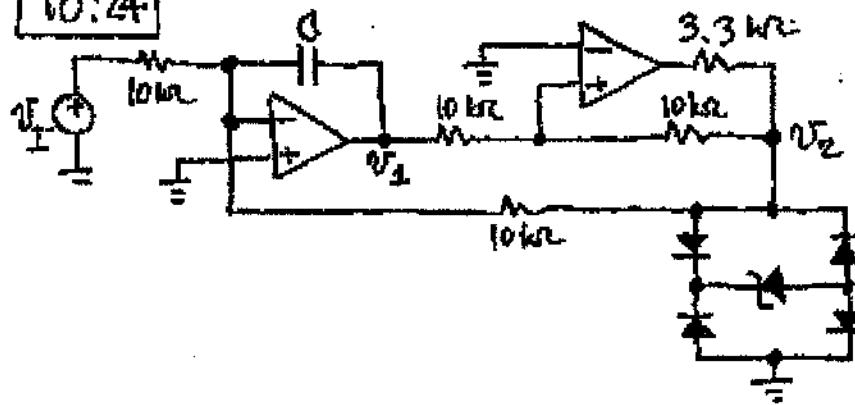

$V_2 = \pm (V_{25} + 2V_{D(on)}) = \pm 5V$ ;  $V_T = \pm 5V$ .

 $V_2 = 5V \Rightarrow i_C(\rightarrow) = (5 + V_I)/10^4 \Rightarrow CA = I_A t$ 
 $\Rightarrow T_H = 10RC/(5 + V_I)$ .  $V_2 = -5V \Rightarrow i_C(\leftarrow) = (5 - V_I)/10^4 \Rightarrow T_L = 10RC/(5 - V_I)$ .



10.16

$D = 100T_H / (T_L + T_H) = 10(5 - V_C); f_0 = 1 / (T_L + T_H)$   
 $= 1/4RC - V_E^2/100RC$ . The permissible range  
is  $-5V < V_E < +5V$ .

10.25

To ensure  $V_{clamp} = 5V$ , use a 3.6 V zener diode and a CA3039 diode array. Let  $R_1 = 10\text{ k}\Omega$ . Then,  $R_2 = [(5 - 0.7)/5]10 = 8.66\text{ k}\Omega$ . Use two 2.5 M $\Omega$  pots. Then,  $R_3 = 2.5\text{ k}\Omega$  and  $R_4 = 1.5\text{ k}\Omega$ . To find C, impose  $50 \times 10^{-6} = 2C(10/8.66)2.5 \times 10^3$ . Solving,  $C = 8.66\text{ nF}$ .

10.26

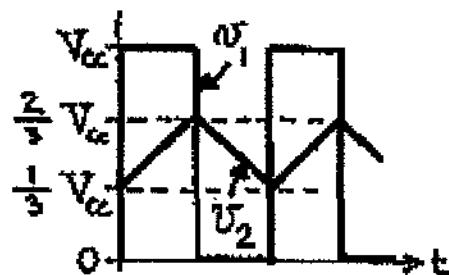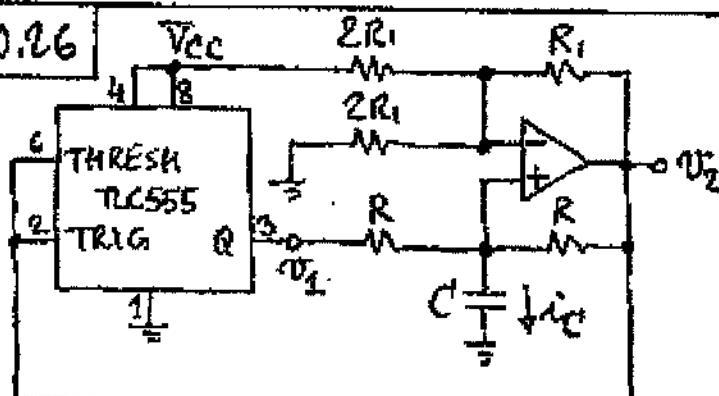


$V_1$  alternates between 0 and  $V_{cc}$ . To make  $i_C$  alternate between two symmetric values about zero, we must offset the integrator, as shown. Then,  $i_C = (V_1 - V_{cc}/2)/R = \pm V_{cc}/2R$ . We observe that as  $V_2$  alternates between  $(1/3)V_{cc}$  and  $(2/3)V_{cc}$ ,

offset the integrator, as shown. Then,  $i_C = (V_1 - V_{cc}/2)/R = \pm V_{cc}/2R$ . We observe that as  $V_2$  alternates between  $(1/3)V_{cc}$  and  $(2/3)V_{cc}$ ,

10.17

or  $\Delta V_2 = (1/3)V_{CC}$ , the voltage change across the capacitor is half as large, or  $\Delta V = (1/6)V_{CC}$ . Thus,  $C(1/6)V_{CC} = (V_{CC}/2R)T/2$  gives  $f_0 = 1/T = 3/2RC$ .

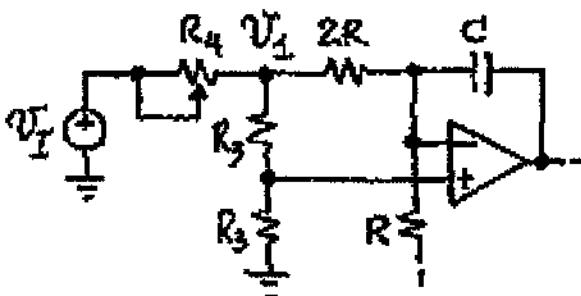10.27 Modify the circuit by adding  $R_4$ , as shown. When the wiper is on the right, we want



$$f_0 = \left(1.25 \frac{\text{kHz}}{V}\right) V_1$$

$$\text{Let } R = 10 \text{ k}\Omega$$


$$\text{Eq. (10.20)} \Rightarrow$$

$$1.25 \times 10^3 = \frac{1}{8 \times 10^4 \times C \times 10}, \text{ that is, } C = 1 \text{ mF.}$$

When the wiper is at the left, we want  $f_0 = (0.75 \frac{\text{kHz}}{V}) V_I = (1.25 \frac{\text{kHz}}{V_1}) V_1$ . This yields  $V_1 = 0.6 V_I$ , indicating that  $R_4$  must drop  $0.4 V_I$  volts (max). Since  $V_{NM} = V_{P1} = \frac{1}{2} V_1 = 0.3 V_I$ , we have, by KCL,  $0.4 V_I / R_4 = 0.3 V_I / R_3 + 0.3 V_I / (2R)$ . Let  $R_4 = 10 \text{ k}\Omega$  pot. Then,  $0.4 / 10 = 0.3 / R_3 + 0.3 / 20$ , that is,  $R_3 = 12 \text{ k}\Omega$ . Summarizing,  $R = 10.0 \text{ k}\Omega$ ,  $2R = 20.0 \text{ k}\Omega$ ,  $C = 1 \text{ mF}$ ,  $R_3 = 12.1 \text{ k}\Omega$ ,  $R_4 = 10 \text{ k}\Omega$  pot.

10.18


10.18 | CMP forms an inverting Schmitt trigger with  $V_{TL} = 0\text{V}$  and  $V_{TH} = 10\text{ V}$ . Depending on whether M is open or closed, the gain of  $OA_1$  is  $+1/V_I$  or  $-1/V_I$ , respectively. So,  $V_I = \pm V_{SQ}$ , thus providing a square wave of controllable amplitude for  $OA_2$  to integrate. Using  $CV = IAt$  with

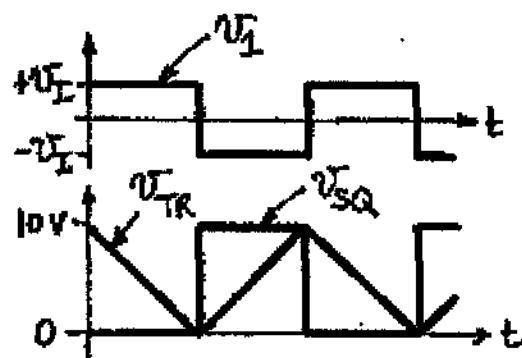

$$\begin{aligned} AV &= 10\text{V}, I = V_I/R, \\ \text{and } At &= T/2, \text{ we} \\ \text{get } T &= 20RC/V_I, \\ \text{or} \\ f_0 &= \frac{V_I}{20RC}. \end{aligned}$$

10.19

10.29

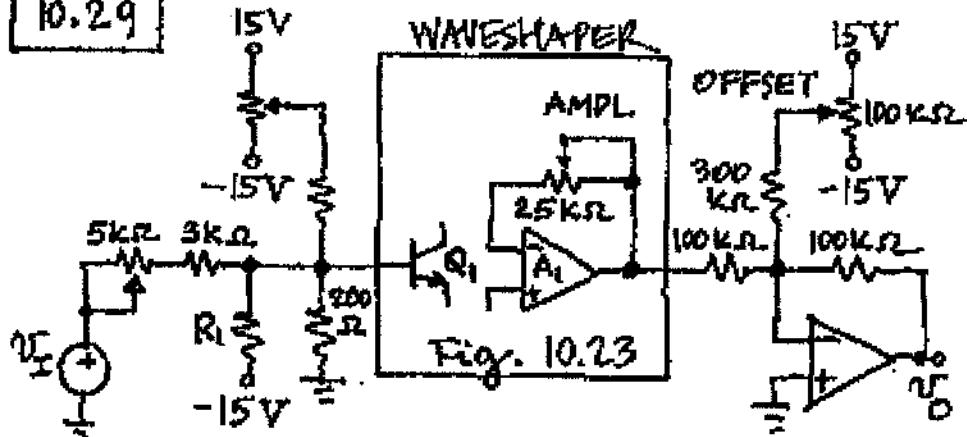

Since the triangular wave output of the circuit of Fig. 10.21 has a 5V dc component, we use offsetting resistor  $R_1$  to ensure that the input to  $Q_1$  is centered around OV. Since we want  $V_{B1}$  to vary from  $-172\text{ mV}$  to  $+172\text{ mV}$ , we find  $R_1$  by imposing  $V_{B1} = -172\text{ mV}$  when  $V_I = 0\text{V}$ . Thus,  $-15 \times 200 / (200 + R_1) \approx -0.172 \Rightarrow R_1 = 17.4\text{ k}\Omega$ . Output amplitude control is offered by the AMPL pot. Output offset control is offered by the OFFSET pot and corresponding network.

10.20

10.30

$V_{SIN} = 0.7 \sin 2\pi ft$ ;  $\frac{dV_{SIN}}{dt}|_{t=0} = 0.7 \times 2\pi f$ . The slope of a triangular wave of peak amplitude  $V_p$  and period  $T$  is  $2V_p/(T/2) = 4V_p f$ . Equating the slopes gives  $V_p = 0.7 \times 2\pi / 4 = 1.0996$  V. We have two conditions to meet:  $[R_1/(R_1+R_2)]5 = 1.0996$ , and  $(1.0996 - 0.7)/(R_1/R_2) = 1$  mA. Solving gives  $R_1 = 512.2$   $\Omega$  and  $R_2 = 1.817$  k $\Omega$ .

For a diode to develop 0.7 V at 1 mA we need  $I_S = 2 \times 10^{-15}$  A.


## Problem 10.30

```

vi 1 0 pulse(-5V 5V -0.25ms 0.5ms 0.5ms 1us 1ms)
R2 1 2 1.817k
R1 2 0 512.2
D1 2 10 Diode
D2 10 2 Diode
Vs 10 0 dc 0
.model Diode D(Is=2fA n=1)
.tran 10us 2ms 0ms 10ns
.probe
.end

```

10.21

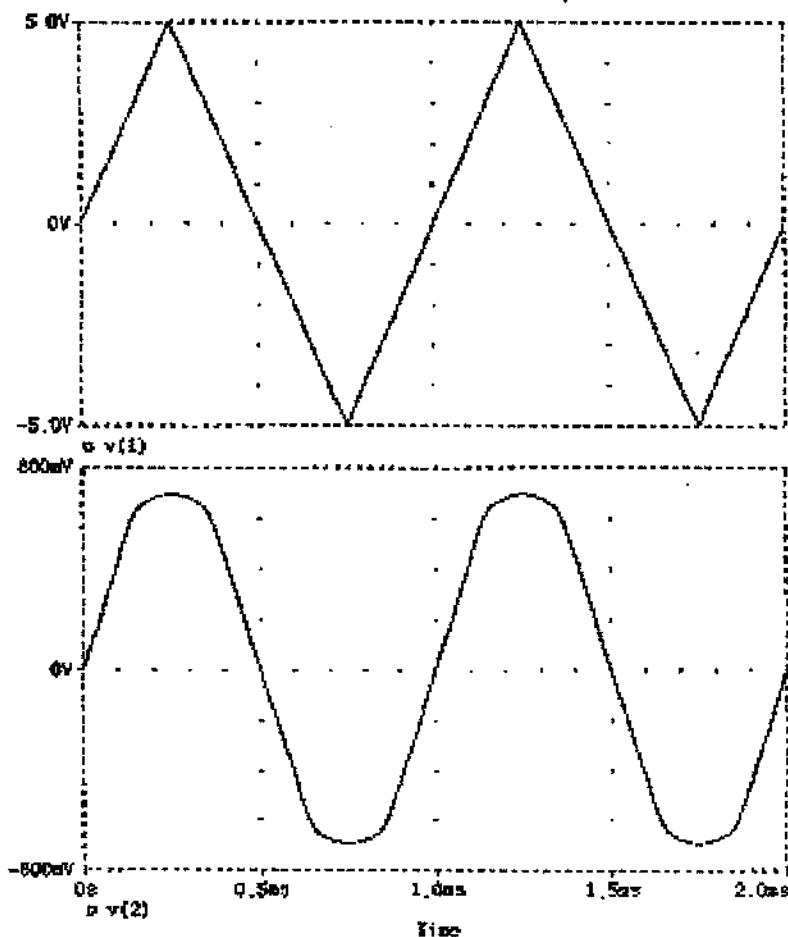

10.31

(a) By the superposition principle,

$$V_T = \frac{R_3 || R_4}{R_3 || R_4 + R_2} V_{CC} + \frac{R_2 || R_3}{R_2 || R_3 + R_4} V_I = V_{T0} - k|V_I|,$$

$$V_{T0} = V_{CC} / (1 + R_2/R_3 + R_2/R_4), \quad k = 1 / (1 + R_4/R_2 + R_4/R_3), \quad V_I < 0.$$

(b) By Eq.(10.21),

$$f_0 = \frac{1}{RC(V_{T0} - k|V_I|)/|V_I| + T_D}$$

Making  $RCk = T_D$  cancels out  $T_D$ , yielding

10.22

$$f_0 = |V_{IF}| / R_C T_0 \quad k = (1 + R_4/R_2 + R_4/R_3)^{-1} = \\ T_0/R_C \Rightarrow R_4 = (R_2||R_3)(R_C/T_0 - 1).$$

(c) For a sensitivity of  $2 \text{ Hz/V}$ , we use  $C = 2.2 \text{ nF}$  and  $R = 45.3 \text{ k}\Omega$ . For a low-frequency amplitude of  $5 \text{ V}$  we need

$$V_{TO} = \frac{R_3||R_4}{R_3||R_4 + R_2} 15 = 5 \Rightarrow R_2 = 2(R_3||R_4).$$

To cancel out the error due to  $T_0$ , we need

$$\frac{R_2||R_3}{R_2||R_3 + R_4} = \frac{T_0}{RC} = \frac{10^{-6}}{45.3 \times 10^3 \times 2.2 \times 10^{-9}} \cong 0.01.$$

Thus,  $R_4 \cong 99(R_2||R_3)$ . Use  $R_3 = 10.0 \text{ k}\Omega$ .


$R_2 = 19.6 \text{ k}\Omega$ ,  $R_4 = 649 \text{ k}\Omega$ , all 1%.

10.32

$$\text{Use } CAV = IAT, \text{ with } \Delta V = \left(\frac{2}{3} - \frac{1}{3}\right)V_{cc} \\ = \frac{1}{3}V_{cc}, I_H = I_A = V_I/R_A, I_L = 2I_B - I_A = 2V_I/R_B - V_I/R_A = V_I(2/R_B - 1/R_A), \Delta t = T_H \text{ or } \Delta t \\ = T_L. \text{ Thus, } T_H = CAV/I_H = \frac{1}{3}R_ACV_{cc}/V_I; \\ T_L = CAV/I_L = \frac{1}{3}R_AC(V_{cc}/V_I)R_B/(2R_A - R_B). \\ T = T_L + T_H = [2R_A/(2R_A - R_B)] \frac{1}{3}R_ACV_{cc}/V_I. \\ f_0 = \frac{1}{T} = 3[1 - R_B/(2R_A)][1/(R_ACV_{cc})]V_I; \\ D\% = 100T_H/T = 100[1 - R_B/(2R_A)].$$

10.23

10.33

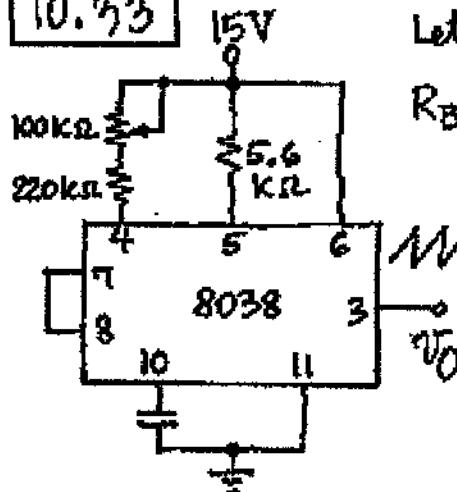Let  $I_B = 0.5 \text{ mA}$  so that

$$R_B = (15/5)/0.5 = 6 \text{ k}\Omega \text{ (use } 5.6 \text{ k}\Omega\text{). Eq. (10.23):}$$

$$99 = 100 \left(1 - \frac{5.6}{2R_A}\right) \Rightarrow$$

$R_A = 280 \text{ k}\Omega$ . For a  $\pm 20\%$  adjustment range, use a 220-kΩ resistor in series with a 100-kΩ pot.

$$\text{Eq. (10.23): } 10^3 = 3 \left(1 - \frac{5.6}{560}\right) \frac{15/5}{280 \times 10^3 \times C \times 15} \\ \Rightarrow C \approx 2.2 \text{ nF.}$$

10.34  $V_I = 10V \Rightarrow I_I = 10/5 = 2 \text{ mA} \Rightarrow I_A =$ 


$I_B = 1 \text{ mA} \Rightarrow I_C = 1 \text{ mA}$ . During half-period  $T/2$  we have  $C = (I_C T/2) / (\frac{1}{3} V_{cd}) = 10^3 \times \frac{1}{2} \times [1/(20 \times 10^3)] / 5 = 5 \text{ mF.}$

10.35


$T_H = R_1 C, T_L = R_2 C$ . Thus,  $f_0 = 1/(T_L + T_H) = 1/[(R_1 + R_2)C]$ . Moreover,  $D(\%) = 100 R_1 / (R_1 + R_2) = 99\% \Rightarrow R_1 = 99 R_2$ . Use  $R_2 = 1 \text{ k}\Omega, R_1 = 100 \text{ k}\Omega$ . Then,  $C = 1/(10^3 \times 101 \times 10^3) \approx 10 \text{ mF}$ . Since the dc offset is 7.5 V, use two 5.1-kΩ resistors. Since the peak amplitude is 2.5 V, the resistance seen by

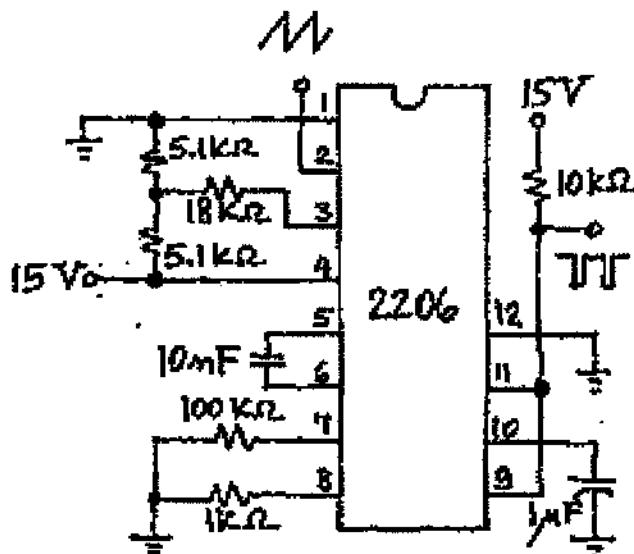10.24

pin 3 must be  $2.5/0.120 = 20.8 \text{ k}\Omega$ . Use a series resistance of value  $20.8 - (5.1/(5.1) \approx 18 \text{ k}\Omega$ , as shown.




10.36 (a)

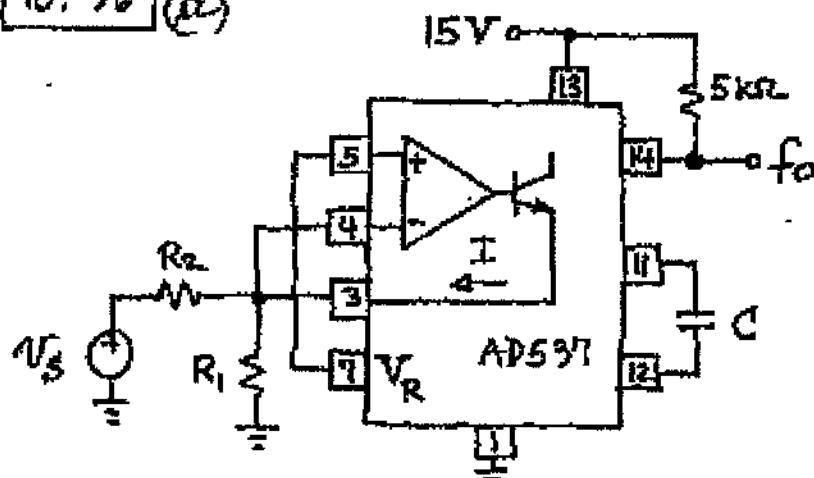

$V_N = V_P = V_R = 1.00 \text{ V}$ . With  $V_I = +10 \text{ V}$ , impose  $I = 0$ . This requires  $R_2 = 9 R_1$ . With  $V_I = -10 \text{ V}$ , impose  $I = 1 \text{ mA}$ . This requires  $1/V_2 + 1/R_1 = 1$ . Combining & solving,  $R_2 = 20.0 \text{ k}\Omega$ ,  $R_1 = 2.22 \text{ k}\Omega$ ;  $20 \times 10^3 = 10^{-3} / (10C) \Rightarrow C = 5 \text{ mF}$ .

10.25

(b)

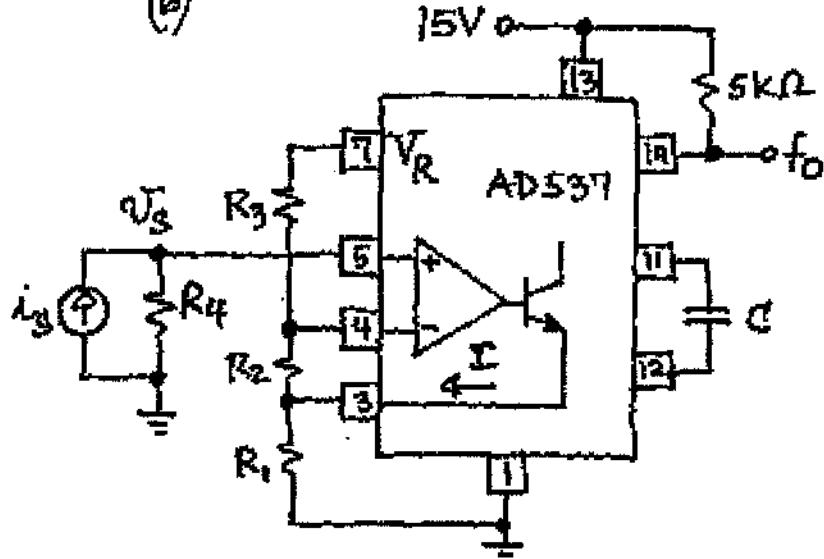

Use  $R_4 = 50\Omega$  to convert  $i_S$  to a 0.2 V to 1.0 V voltage  $V_S$ . Impose  $I = 0$  with  $V_S = 0.2\text{V}$ . Thus,  $(V_R - 0.2)/R_3 = 0.2/(R_1 + R_2)$ . Letting  $V_R = 1.00\text{V}$  yields  $R_3 = 4(R_1 + R_2)$ . With  $V_S = 1.0\text{V}$ , impose  $I = 1\text{mA}$  and  $V_S = 1.0\text{V}$ . Then,  $I_{R_2} = I_{R_3} = 0$  and  $R_1 = 1/1 = 1\text{k}\Omega$ . Substituting yields  $R_3 = 4(R_2 + 1)$ . Use, for instance,  $R_3 = 40.2\text{k}\Omega$  and  $R_2 = 9.09\text{k}\Omega$ . Finally,  $C = 1\text{mF}$ .

10.37

$0^{\circ}\text{F} = -(5/9)32^{\circ}\text{C} = -17.78^{\circ}\text{C} = 273.2 - 17.78 = 255.4^{\circ}\text{K}$ . We want  $R_3/(0.2554) = R_2/(1-0.2554)$ , that is,  $R_2 = 2.91R_3$ . For a sensitivity of  $10\text{ Hz}/^{\circ}\text{F} = (9/5)10 = 18\text{ Hz}/^{\circ}\text{K}$ , we want  $18 = 1/(10^4 RC)$ . Let  $C = 2.2\text{ mF}$ . Then,  $R = 2.525\text{ k}\Omega$ . Let  $R_3 = 2.55\text{ k}\Omega$ , 1%. Then,  $R_2 = 2.91 \times 2.55 = 7.42\text{ k}\Omega$  (use  $6.49\text{ k}\Omega$  in series with a  $2\text{-k}\Omega$  pot). Finally,  $R_1 = 2.525 - 2.55/7.42 = 627\Omega$  (use  $374\Omega$  in series with a  $500-\Omega$  pot).

10.38

(a)  $V_I > 0 \Rightarrow D_1 = \text{ON} \& D_2 = \text{OFF}$ . Thus,  $V_{P2} = 0$ ,  $I_{R4} = 0$ , and  $i_{R1} = (1 + R_2/R_1) \times V_I/R_3 = V_I/R_p$ ,  $R_p = R_3/(1 + R_2/R_1)$ .  $V_I < 0 \Rightarrow D_1 = \text{OFF} \& D_2 = \text{ON}$ . This implies

$$V_{P1} = V_{N1} = \left(1 + \frac{R_2 + R_3}{R_1}\right)V_I < 0. \text{ Consequently, } i_{R1} = i_{R3} + i_{R4} = i_{R1} + i_{R4} = \frac{0 - V_I}{R_1} + \frac{0 - V_{P1}}{R_4} = -V_I/R_m, \quad R_m = \frac{R_1 R_4}{R_1 + R_2 + R_3 + R_4}. \text{ Imposing}$$


$R_m = R_p$  yields, after little algebra,

$$R_4 = R_3 \frac{R_1 + R_2 + R_3}{R_1 + R_2 - R_3}.$$

10.27

(b) Let  $(1+R_2/R_1)=10$ , so that a 1V input voltage is mapped into a 10V voltage at the output of  $A_2$ . Use  $R_1 = 11.0\text{ k}\Omega$ ,  $R_2 = 100\text{ k}\Omega$ . For  $i_{C_1(\max)} = 0.25\text{ mA}$ , use  $R_3 = 10/0.25 = 40\text{ k}\Omega$  (use 40.2 k $\Omega$ ). Then,  $R_4 = 85\text{ k}\Omega$  (use 84.5 k $\Omega$ ). Finally,  $C_1 = 1\text{ mF}$ ,  $C = 330\text{ pF}$  (NPO).

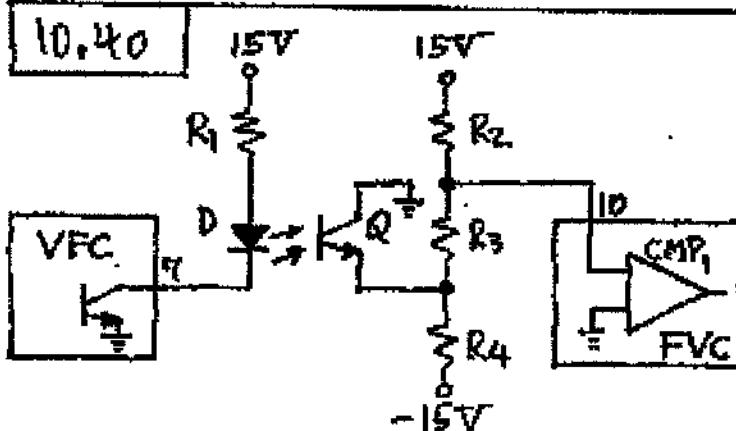**10.39** Following Example 10.8,  $C = 330\text{ pF}$ ,  $R = 34.8\text{ k}\Omega$  in series with a 10 k $\Omega$  pot. By Eq. (10.34),  $C_1 = 330 \times 10^{-12} \times 7.5 / 0.01 = 0.247\mu\text{F}$  (use  $0.33\mu\text{F}$ ). Then,  $\tau = RC_1 = 40.4 \times 10^3 \times 0.33 \times 10^{-6} = 13.3\text{ ms}$ . Since  $\ln(0.1/100) \approx -7$ , the delay is approximately  $7 \times 13.3 \approx 100\text{ ms}$ .



To ensure  $I_F \approx 10\text{ mA}$ , use  $R_1 = 1.3\text{ k}\Omega$ . Impose a  $\pm 3\text{ V}$  swing at pin 10 of the FVC. Then, when Q is off, we want

10.28

$V_{10} = -3V$ , that is,  $18/R_2 = 12/(R_3+R_4)$ .

When Q is on (saturation), we want

$12/R_2 = 3/R_3$ . This yields  $R_2 = 4R_3$ .

We have two equations in three un-

knowns. Let  $R_4 = 10k\Omega$ . Then,  $R_3 = 6.2$

$k\Omega$  and  $R_2 = 24 k\Omega$ , all 5%.