

(3.1)

$$3.1 \quad H(s) = \frac{s - 10^3}{[s - (-10^3 + j10^3)][s - (-10^3 - j10^3)]}$$

$$H(s) = \frac{s - 10^3}{(s + 10^3 - j10^3)(s + 10^3 + j10^3)} = \frac{s - 10^3}{s^2 + 2 \times 10^3 s + 2 \times 10^6}$$

$$(a) A_1 = H(s) \times (s + 10^3 - j10^3) \Big|_{s = -10^3 + j10^3}$$

$$= \frac{-10^3 + j10^3 - 10^3}{-10^3 + j10^3 + 10^3 + j10^3} = 0.5 + j1$$

$$= 1.118 \angle 26.57^\circ.$$

$$h(t) = 2.236 e^{-10^3 t} \cos(10^3 t + 26.57^\circ) u(t)$$

$$(b) H(j10^3) = \frac{j10^3 - 10^3}{-10^6 + 2 \times 10^3 j10^3 + 2 \times 10^6} = \frac{j1-1}{10^3 (1+2j)}$$

$$= 6.32 \times 10^{-4} \angle 71.57^\circ.$$

$$x_o(t) = 6.32 \times 10^{-4} \cos(10^3 t + 71.57^\circ).$$

$$3.2 \quad (a) V_m = V_o / 2 = V_p. \text{ KCL:}$$

$$\frac{V_i - V_p}{1/j\omega C} = \frac{V_p}{R} + \frac{V_p - V_o}{1/j\omega C}. \text{ Eliminating } V_p$$

$$\text{and collecting terms, } H = \frac{V_o}{V_i} = j(f/f_0),$$

$$f_0 = 1/(4\pi RC).$$

$$(b) \text{ Let } C = 10 \text{ mF. Then, } R = 1/(4\pi \times 100 \times 10 \times 10^{-9}) = 79.6 \text{ k}\Omega \text{ (use } 80.6 \text{ k}\Omega\text{).}$$

$$\text{Use } R_1 = 100 \text{ k}\Omega.$$

3.2

3.3

$$(a) V_p = \frac{1}{1+j(f/f_0)} V_i, V_m = \frac{j(f/f_0)}{1+j(f/f_0)} V_0.$$


$$V_m = V_p \Rightarrow V_0 = \frac{1}{j(f/f_0)} V_i, f_0 = \frac{1}{2\pi R_1 C_1}.$$

(b) 20 dB gain at $f = 100\text{Hz} \Rightarrow f_0 = 1\text{kHz}$. Let $C_1 = C_2 = 10\text{nF}$. Then, $R_1 = R_2 = 1/(2\pi \times 10^3 \times 10^{-8}) = 15.8\text{ k}\Omega$.

3.4

(a) Let $2C = 10\text{nF}$. Then $R = 1/2\pi f_0 C = 1/(2\pi \times 10^3 \times 5 \times 10^{-9}) = 31.8\text{ k}\Omega$ (use $31.6\text{ k}\Omega, 1\%$).

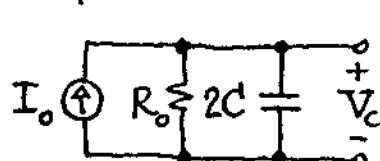(b) Because of mismatches, $2C$ sees a Norton equivalent with $I_o = V_i/R$ and $R_o = 31.8/[31.8/31.8 - 31.8(1-0.01)/31.8] = 3.180\text{ M}\Omega$, as per Eq.(2.8). By Ohm's law,




$$V_c = \left(R_o \parallel \frac{1}{s2C}\right) I_o = \frac{R_o / R}{1 + j f / f_1} V_i,$$

$$f_1 = \frac{1}{2\pi R_o 2C} = 5\text{ Hz}. \text{ Since}$$

$$V_o = \left(1 + \frac{31.8(0.99)}{31.8}\right) V_c \approx 2 V_c,$$

it follows that
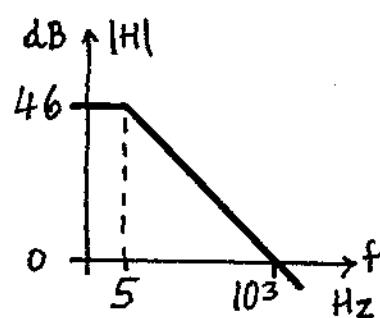
$$H \approx \frac{2 R_o / R}{1 + j f / f_1} = \frac{200}{1 + j f / 5}.$$




3.5

(a) Let $f_0 = 1/(2\pi R_2 C_2)$. Then,
 $1/(2\pi R_1 C_1) = 1/[2\pi R_2 C_2 (1-\varepsilon)] \cong (1+\varepsilon)/(2\pi \times R_2 C_2) = f_0(1+\varepsilon) \cong f_1$; $V_p = [1/(1+jf/f_1)] V_i$;
 $V_m = [(jf/f_0)/(1+jf/f_0)] V_0$. Letting $V_m = V_p$ gives

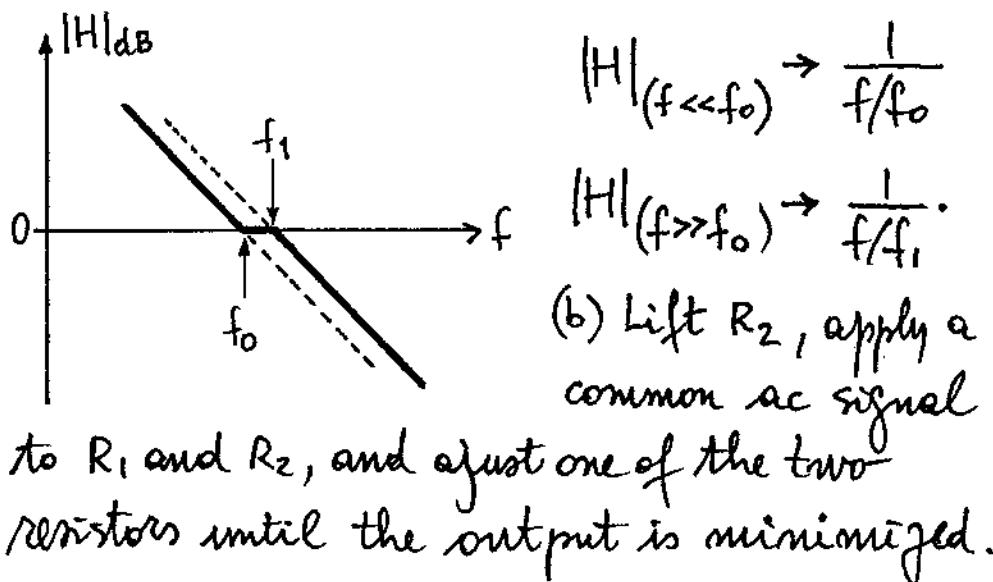
(3.3)

$$H = \frac{V_o}{V_i} = -\frac{1}{j(f/f_0)} \times \frac{1+jf/f_0}{1+jf/f_1}$$



3.6

(a)

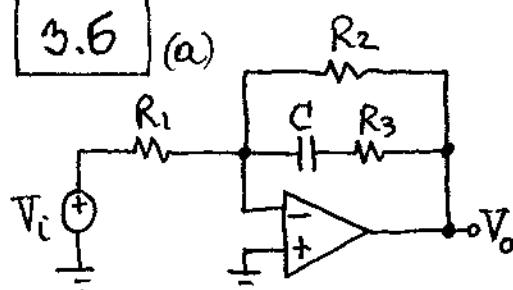

$$\text{Let } Z_s = 1/sC + R_3 = (1 + sR_3C)/sC$$

$$\text{Let } \frac{1}{Z_p} = \frac{1}{Z_s} + \frac{1}{R_2}$$

$$\text{Eliminating } Z_s \text{ gives } \frac{1}{Z_p} = \frac{1 + s(R_2 + R_3)C}{R_2(1 + sR_3C)}, \text{ so}$$


$$H = -\frac{Z_p}{R_1} = -\frac{R_2}{R_1} \frac{1+jf/f_z}{1+jf/f_p}, f_z = \frac{1}{2\pi R_3 C}, f_p = \frac{1}{2\pi(R_2 + R_3)C}$$

(b) Let $C = 1 \mu F$. Then, $R_3 = 1/(2\pi \times 10^4 \times 10^{-9})$

$$= 15.9 \text{ k}\Omega \text{ (use } 15.8 \text{ k}\Omega,$$

$$1\%); R_1 = R_2 = 159 - 15.9$$


$$= 143 \text{ k}\Omega, 1\%.$$

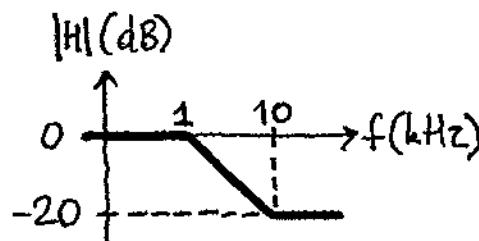

3.4

3.7

1

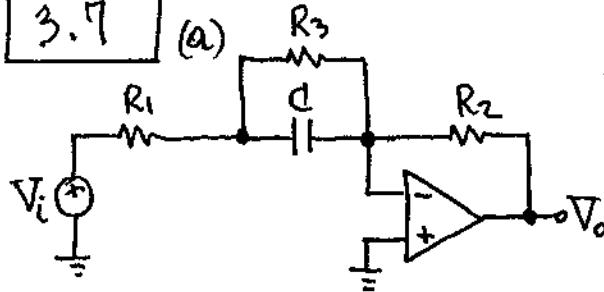

$$\text{Let } Z_p = R_3 \parallel \frac{1}{sc}$$


$$= \frac{R_3}{1+sR_3C}.$$

Let $Z_s = R_1 + Z_p$.

Eliminating Z_p gives $Z_s = (R_1 + R_3) \frac{1 + s(R_1 || R_3)C}{1 + sR_3C}$, so


$$H = -\frac{R_2}{Z_s} = -\frac{R_2}{R_1+R_3} \frac{1+jf/f_z}{1+jf/f_p}, f_z = \frac{1}{2\pi R_3 C}, f_p = \frac{1}{2\pi (R_1//R_3) C}.$$

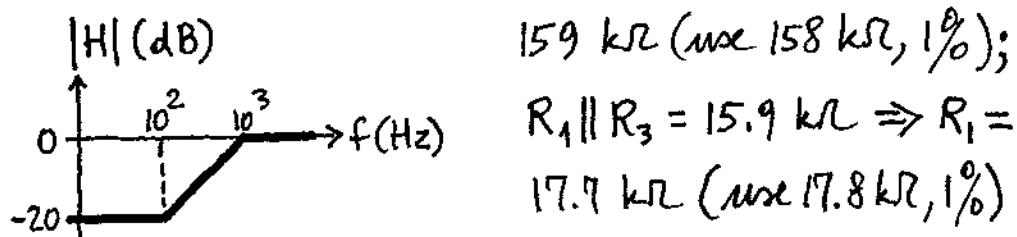(b) Let $C = 10 \text{ mF}$. Then, $R_3 = 1/(2\pi \times 100 \times 10^{-8}) =$



$$H(f \rightarrow \infty) = -\frac{R_2}{R_1 + R_3} \frac{f_p}{f_z} = -\frac{R_2}{R_1} = -1 \Rightarrow R_2 = 17.8 \text{ k}\Omega.$$

3,8


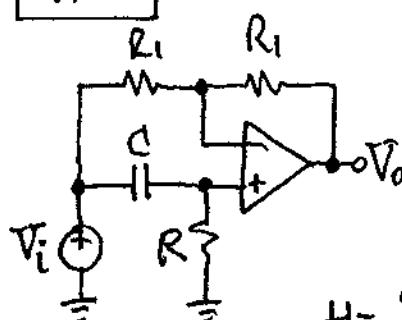


$$V_p = \frac{if/f_0}{1+if/f_0}, \quad f_0 = \frac{1}{2\pi RC}.$$

Superposition: $V_o = 2V_p - V_i$.

Eliminating V_p gives


$$H = \frac{if/f_0 - 1}{if/f_0 + 1} = 1 \quad |180^\circ - 2\tan^{-1}(f/f_0)|.$$

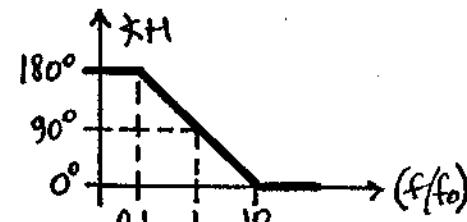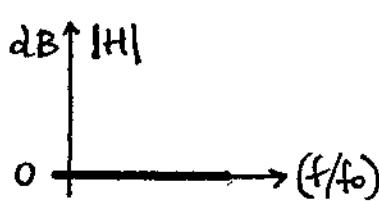


Difference: $\chi H(f/f_0 = 1) = +90^\circ$ instead of -90° ; disadvantage: C passes high-frequency noise to output.

3.5

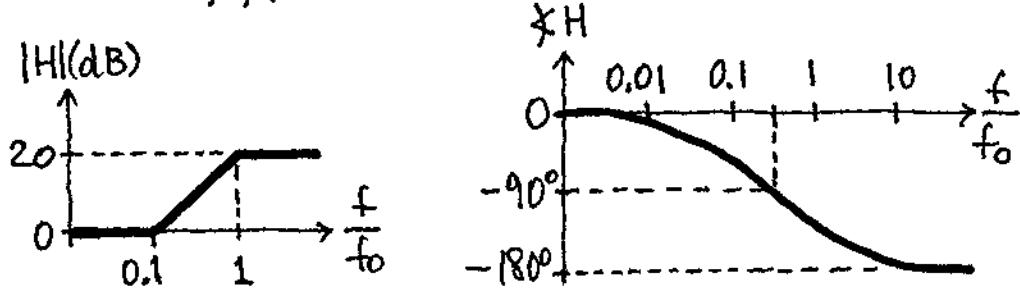
3.9 (a) Superposition: $V_o = -10V_i + 11V_p$, $V_p/V_i = 1/(1+jf/f_0)$, $f_0 = 1/2\pi RC$. Eliminating V_p gives $H = \frac{1-jf/(f_0/10)}{1+jf/f_0}$, whose Bode plots are:



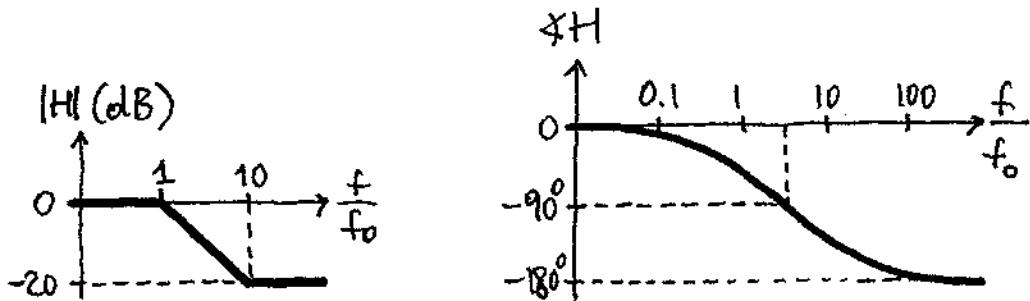(b) We now have $V_o = -0.1V_i + 1.1V_p$, so $H = \frac{1-jf/10f_0}{1+jf/f_0}$, whose Bode plots are:



3.10

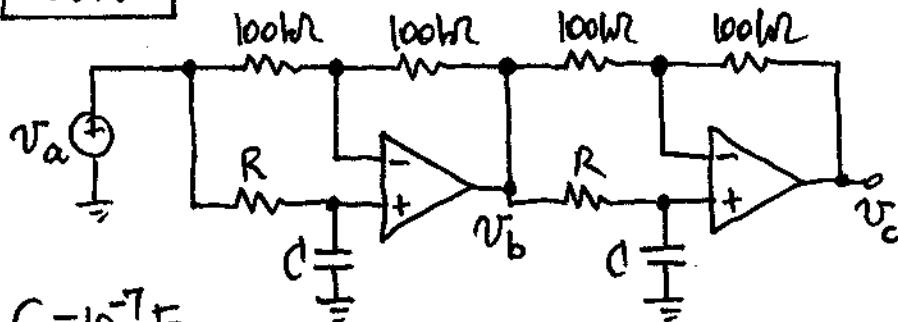


$$C = 10^{-7} F$$

$$\begin{aligned}\phi &= -2 \tan^{-1}(f/f_0) \Rightarrow -120^\circ = -2 \tan^{-1}(2\pi 60R \times 10^{-7}) \\ &\Rightarrow R = 45.9 \text{ k}\Omega.\end{aligned}$$

3.6

3.11

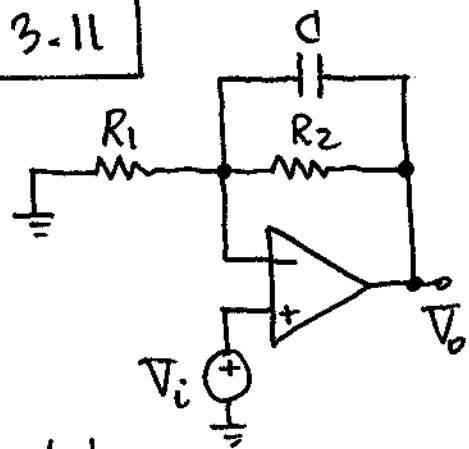


$$\text{Let } Z_2 = R_2 \parallel \frac{1}{j\omega C}, \text{ or}$$

$$Z_2 = \frac{R_2}{1+j\omega R_2 C} = \frac{R_2}{1+jf/f_0}$$


$$f_0 = \frac{1}{2\pi R_2 C} = 884.2 \text{ Hz}$$

Let $Z_1 = R_1$. Then,

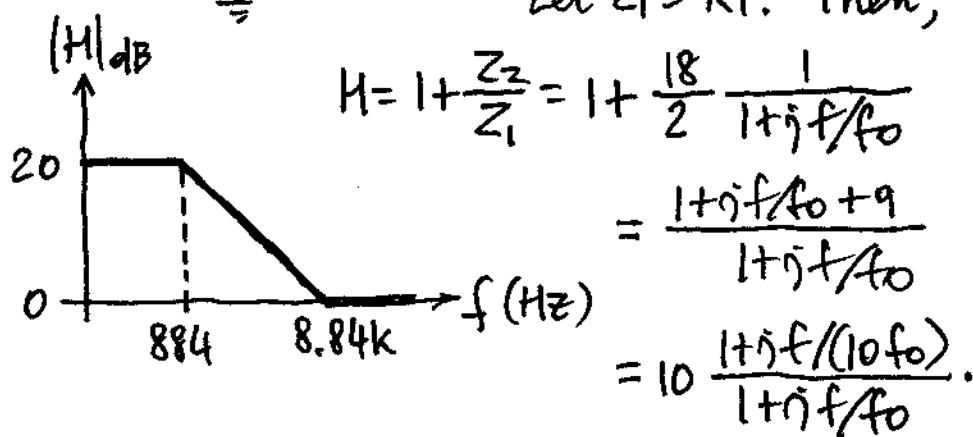

$$\begin{aligned} H &= 1 + \frac{Z_2}{Z_1} = 1 + \frac{1}{2} \frac{1}{1+jf/f_0} \\ &= \frac{1+jf/f_0 + 1}{1+jf/f_0} \\ &= 10 \frac{1+jf/(10f_0)}{1+jf/f_0}. \end{aligned}$$

3.12

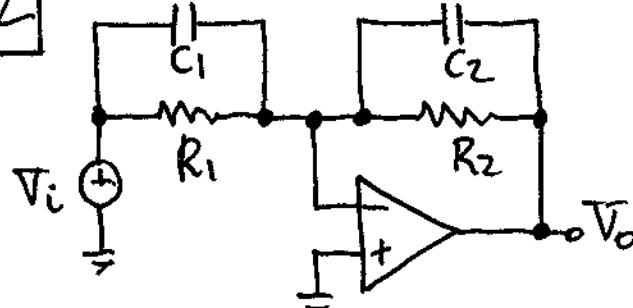

$$R \parallel (1/j2\pi f C) = \frac{R}{1+jf/f_0}, \quad f_0 = \frac{1}{2\pi RC}$$

$$H = -\frac{Z_2}{Z_1} = -\frac{R_2}{1+jf/f_2} \times \frac{1+jf/f_1}{R_1} = -\frac{R_2}{R_1} \frac{1+jf/f_1}{1+jf/f_2}$$

$$f_1 = 1/2\pi R_1 C_1, \quad f_2 = 1/2\pi R_2 C_2, \quad H_0 = -R_2/R_1,$$

$$H_{\infty} = -(R_2/R_1) \times (f_2/f_1) = C_1/C_2. \quad H_0 = 20 \text{ dB} \Rightarrow R_2 = 100R_1.$$

$$H_{\infty} = 0 \text{ dB} \Rightarrow C_1 = C_2. \quad (f_1 f_2)^{1/2} = 10^3 \Rightarrow 20\pi R_1 C_1 = 10^3.$$

$$\text{Let } C_1 = C_2 = 10 \mu\text{F}. \text{ Then, } R_1 = 1.591 \text{ k}\Omega, R_2 = 159.1 \text{ }\Omega.$$

3.7

3.13

$$V_o = \left(1 + \frac{1}{j\omega R_2 C_2}\right) \frac{1}{1 + j\omega R_1 C_1} V_i, \text{ so}$$


$$H = \frac{1}{j\omega R_2 C_2} \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1}$$

(a) $R_1 C_1 = 0.1 \text{ ms}$, $R_2 C_2 = 1 \text{ ms}$,

$$H = \frac{1}{j\omega/10^3} \frac{1 + j\omega/10^3}{1 + j\omega/10^4}$$

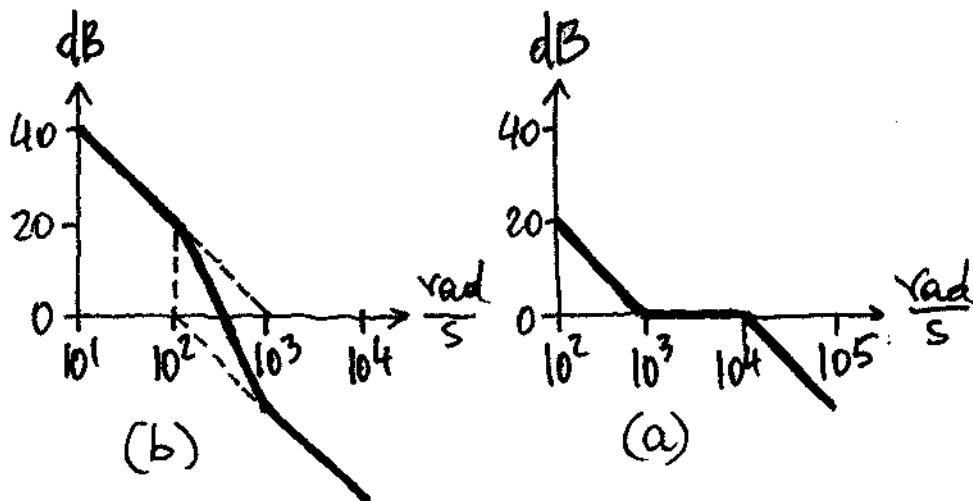(b) $R_1 C_1 = 10 \text{ ms}$, $R_2 C_2 = 1 \text{ ms}$,

$$H = \frac{1}{j\omega/10^3} \frac{1 + j\omega/10^3}{1 + j\omega/10^2}$$



3.14

With equal component values, we get

$$H = -\frac{j\omega RC}{(1 + j\omega RC)^2}$$

(a) $\omega = 1/RC \Rightarrow \omega RC = 1 \Rightarrow H = \frac{-j1}{(1 + j1)^2} = -j1/(1 - 1 + j2) = -0.5 = 0.5 \angle -180^\circ$. Thus,
 $V_o(t) = 0.5 \cos(t/RC - 180^\circ) \text{ V.}$

(38)

$$(b) \omega = 1/2RC \Rightarrow j\omega RC = j0.5 \Rightarrow H = \frac{-j0.5}{(1+j0.5)^2} = 0.4 \angle -90^\circ - 2\tan^{-1} 0.5 = 0.4 \angle -143^\circ$$

$$\Rightarrow V_o(t) = 0.4 \cos(t/2RC - 143^\circ) V.$$

$$(c) \omega = 2/RC \Rightarrow j\omega RC = 2 \Rightarrow H = 0.4 \angle +143^\circ$$

$$\Rightarrow V_o(t) = 0.4 \cos(2t/RC + 143^\circ) V.$$

3.15 (a) Let V_1 and V_2 be the outputs of OA₁ and OA₂. Applying a test voltage V at the input gives $V_1 = V$, and $V_2 = (-R_2/R_1)V$. The current out of the test source is $I = (V - V_2)/(1/sC) = sC(1 + R_2/R_1)V$. Then, $Z_{eq} = V/I = 1/sC_{eq}$, $C_{eq} = (1 + R_2/R_1)C$.

(b) $C = 0.1 \mu F$, $R_1 = 1 k\Omega$, $R_2 = 1 M\Omega$ pot connected as a variable resistance from 0 to $1 M\Omega$.

3.16 (a) Applying a test voltage V at the input gives $V_{m2} = V_{p2} = V_{p1} = V_{m1} = V$; moreover, $V_{o2} = (1 + R_3/R_4)V$, $(V_{o1} - V)/R_2 = (V - V_{o2})/(1/sC)$, and $I = (V - V_{o1})/R_1$, where I is the current out of the test source. Eliminating V_{o1} and V_{o2} gives $I = sC_{eq}V$, $C_{eq} = (R_2R_3/R_1R_4)C$.

(b) $C = 1 \mu F$, $R_1 = R_4 = 1 k\Omega$, $R_2 = R_3 = 1 M\Omega$. C_{eq} could be used to create very long time constants without using excessively large R 's.

3.9

3.17 Let $Z_2 = R_2 // (1/j\omega C_2) = R_2 / (1 + j\omega R_2 C_2)$, and $Z_3 = R_3 // (1/j\omega C_3) = R_3 / (1 + j\omega R_3 C_3)$. Then, $H = 1 + (Z_2 + Z_3)/R_1$, that is,

$$H = 1 + \frac{1}{R_1} \frac{R_2 (1 + j\omega R_3 C_3) + R_3 (1 + j\omega R_2 C_2)}{(1 + j\omega R_2 C_2) \times (1 + j\omega R_3 C_3)} =$$

$$1 + \frac{1}{R_1} \frac{(R_2 + R_3) + j\omega R_2 R_3 (C_2 + C_3)}{(1 + j\omega R_2 C_2) \times (1 + j\omega R_3 C_3)} =$$

$$1 + \frac{1}{R_1} \frac{1 + j\omega (R_2 // R_3) (C_2 + C_3)}{(1 + j\omega R_2 C_2) \times (1 + j\omega R_3 C_3)} =$$

$$1 + \frac{R_2 + R_3}{R_1} \frac{1 + j(f/f_1)}{[1 + j(f/f_2)][1 + j(f/f_3)]},$$

$$f_1 = \frac{1}{2\pi(R_2 // R_3)(C_2 + C_3)}, f_2 = \frac{1}{2\pi R_2 C_2}, f_3 = \frac{1}{2\pi R_3 C_3}.$$

3.18(a) Let $Z_2 = R_2 + 1/j\omega C_2$, that is,

$$Z_2 = R_2 + \frac{1 + j\omega R_2 C_2}{j\omega R_2 C_2}. \text{ Let } Z_F = R_3 // Z_2, \text{ that is,}$$

$$Z_F = \frac{R_3 \times R_2 \frac{1 + j\omega R_2 C_2}{j\omega R_2 C_2}}{R_3 + R_2 \frac{1 + j\omega R_2 C_2}{j\omega R_2 C_2}} =$$

$$R_3 \frac{R_2 (1 + j\omega R_2 C_2)}{j\omega R_2 R_3 C_2 + R_2 (1 + j\omega R_2 C_2)}. \text{ Then,}$$


$$H = 1 + \frac{Z_F}{R_1} = 1 + \frac{R_3}{R_1} \frac{1 + j\omega R_2 C_2}{1 + j\omega (R_2 + R_3) C_2} =$$

$$1 + \frac{R_3}{R_1} \frac{1 + j(f/f_1)}{1 + j(f/f_2)}, f_1 = \frac{1}{2\pi R_2 C_2}, f_2 = \frac{1}{2\pi (R_2 + R_3) C_2}.$$

3.10

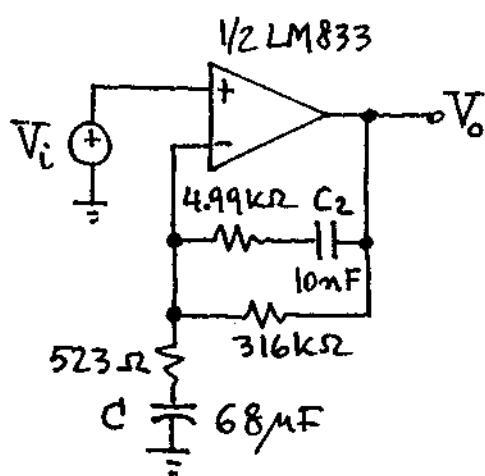(b) Let $C_2 = 10\text{nF}$. Then,

$$R_2 = \frac{1}{2\pi \times 3,183 \times 10^{-8}} = 5\text{k}\Omega.$$



$$R_3 = \frac{1}{2\pi \times 50 \times 10^{-8}} - 5\text{k} = 313\text{k}\Omega.$$

For $f = 1\text{kHz}$,

$$|H| \approx \frac{R_3}{R_1} \sqrt{\frac{1 + (10^3/3183)^2}{1 + (10^3/50)^2}} \\ = \frac{R_3}{R_1} \times 5.23 \times 10^{-2}.$$

$$R_1 = \frac{5.23 \times 10^{-2}}{10^{30/20}} \times 313 = 518\Omega \text{ (use } 523\Omega\text{).}$$

$$C \approx 10 \frac{1}{2\pi \times 50 \times 518} = 61\mu\text{F} \text{ (use } 68\mu\text{F).}$$

3.19

Using $R_1 = 10\text{k}\Omega$, $R_2 = 100\text{k}\Omega$, and $R_3 = 1\text{M}\Omega$, we obtain $C_2 = (2 + 100/10)^{1/2} / (20\pi \times 10^5 f_0) = (0.551 \times 10^{-6})/f_0$. Moreover, $C_1 = 10C_2$. Using the above equations repeatedly, we obtain:

$$32\text{Hz} : C_2 = 18\text{nF}, C_1 = 180\text{nF};$$

$$64\text{Hz} : C_2 = 9.1\text{nF}, C_1 = 91\text{nF};$$

$$125\text{Hz} : C_2 = 4.7\text{nF}, C_1 = 47\text{nF};$$

$$250\text{Hz} : C_2 = 2.2\text{nF}, C_1 = 22\text{nF};$$

$$500\text{Hz} : C_2 = 1\text{nF}, C_1 = 10\text{nF};$$

$$1\text{kHz} : C_2 = 560\text{pF}, C_1 = 5.6\text{nF};$$

$$2\text{kHz} : C_2 = 270\text{pF}, C_1 = 2.7\text{nF};$$

(3.11)

4kHz: $C_2 = 130\text{ pF}$, $C_1 = 1.3\text{ nF}$;

8kHz: $C_2 = 68\text{ pF}$, $C_1 = 680\text{ pF}$

16kHz: $C_2 = 33\text{ pF}$, $C_1 = 330\text{ pF}$.

3.20

$$(a) H = H_0 \frac{j\omega/\omega_L}{1 - \omega^2/\omega_L\omega_H + j\omega(1/\omega_L + 1/\omega_H)} =$$

$$H_{OBP} \frac{(j\omega/\omega_0)/Q}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}, \text{ where } \omega_0^2 = \omega_L\omega_H$$

$$\frac{1}{Q\omega_0} = \frac{1}{\omega_L} + \frac{1}{\omega_H} = \frac{\omega_L + \omega_H}{\omega_L\omega_H} = \frac{\omega_L + \omega_H}{\omega_0^2}. \text{ Thus, } Q = \frac{\omega_0}{\omega_L + \omega_H}.$$

(b) Let $\omega_H = m\omega_L$. Then, $Q = \sqrt{m}/(m+1)$. This reaches its maximum when $m=1$, where $Q=0.5$. Thus, no matter how we choose ω_L and ω_H , we always have $Q \leq 0.5$.

3.21

(a) Low-pass: $\angle H_{LP}(\omega/\omega_0 \ll 1) \approx \angle 1 = 0^\circ$;

$$\angle H_{LP}(\omega/\omega_0 = 1) = \angle \frac{1}{\omega + (j/Q)\omega_0} = -90^\circ;$$

$$\angle H_{LP}(\omega/\omega_0 \gg 1) \approx \angle 1 / -(\omega/\omega_0)^2 = -180^\circ.$$

The phase at other frequencies is found as

$$\angle H_{LP} = -\tan^{-1} \frac{(\omega/\omega_0)/Q}{1 - (\omega/\omega_0)^2}. \text{ For instance,}$$

$$\angle H_{LP}(\omega/\omega_0 = 0.5) = -\tan^{-1} \frac{0.5/Q}{1 - 0.25} = -\tan^{-1} \frac{2/3}{Q},$$

(3.12)

indicating that the higher the value of Q , the closer the phase to 0° at $(w/w_0) = 0.5$. This is readily generalized by saying that the higher the value of Q , the narrower the transition region from 0° to -180° (see Fig. 1).

(b) $\Im H_{HP} = \Im [-(w/w_0)^2] + \Im H_{LP} = 180^\circ + \Im H_{LP}$, indicating that the plot of $\Im H_{HP}$ can be obtained by shifting that of $\Im H_{LP}$ upward by 180° (see Fig. 2).

(c) $\Im H_{BP} = \Im [(i/Q)(w/w_0)] + \Im H_{LP} = 90^\circ + \Im H_{LP}$, indicating that the plot of $\Im H_{BP}$ can be obtained by shifting that of $\Im H_{LP}$ upward by 90° (see Fig. 3).

(d) By inspection, $\Im H_N = \Im H_{LP}$ for $w/w_0 < 1$, $\Im H_N = \Im H_{HP}$ for $w/w_0 > 1$. Thus, the plot of $\Im H_N$ is as in Fig. 4. Note the phase discontinuity at $w/w_0 = 1$.

3.13

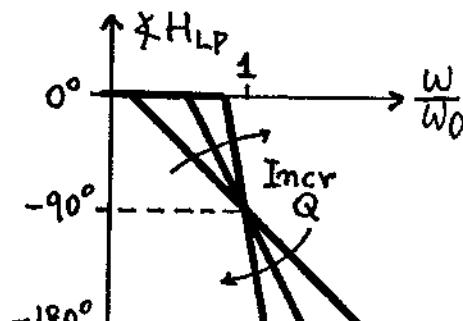


Fig. 1

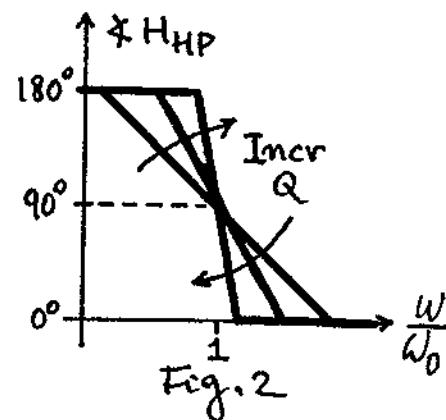


Fig. 2

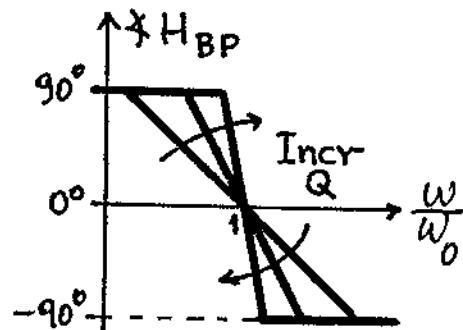


Fig. 3

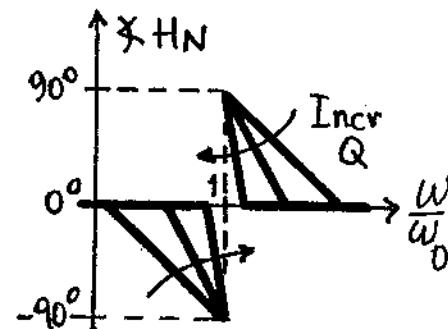


Fig. 4

3.22

(a) With $R_A = R_B$, Eq. (3.60a) gives $H_{OLP} = K = 2 V/V$. With $R_2/R_1 = C_1/C_2 = Q$, Eq. (3.60b) gives $w_0 = 1/R_1 C_1$, so the design equation is $R_1 = 1/w_0 C_1$.

(b) Let $C_1 = 10 \text{ mF}$, so that $C_2 = C_1/Q = 2 \text{ mF}$. Then, $R_1 = 1/(2\pi 10^3 \times 10^{-8}) = 15.9 \text{ k}\Omega$ (use $15.8 \text{ k}\Omega, 1\%$), and $R_2 = QR_1 = 78.7 \text{ k}\Omega, 1\%$. Use also $R_A = R_B = 15.8 \text{ k}\Omega, 1\%$.

3.23

(a) With $C_1 = C_2 = C$, Eq. (3.60b) gives $R_1 = 1/w_0^2 C^2 R_2$, and Eq. (3.60c) gives $1/Q = (2-K) \times \sqrt{R_1/R_2} + \sqrt{R_2/R_1} = (2-K)/w_0 C R_2 + w_0 C R_2$, or

(3.14)

$\omega_0 (R_2^2 - (1/Q)R_2 + (2-K)/\omega_0 C = 0$, whose physically acceptable solution, for $K = H_{OLP} > 2$, is

$$R_2 = [1 + \sqrt{1 + 4Q^2(H_{OLP}-2)}] / 2\omega_0 Q C.$$


(b) Let $C_1 = C_2 = 10 \text{ mF}$. Then,

$$R_2 = \frac{1 + \sqrt{1 + 4 \times 5^2 (10-2)}}{2 \times 2\pi \times 10^3 \times 5 \times 10^{-8}} = 46.6 \text{ k}\Omega \text{ (use } 46.4 \text{ k}\Omega)$$

$$R_1 = \frac{1}{(2\pi 10^3)^2 \times 46.6 \times 10^3 \times (10^{-8})^2} = 5.43 \text{ k}\Omega \text{ (use } 5.49 \text{ k}\Omega)$$

Moreover, for $K = 1 + R_B/R_A = 10$, use $R_A = 10.0 \text{ k}\Omega$ and $R_B = 90.9 \text{ k}\Omega$, all 1%.

3.24 (a)

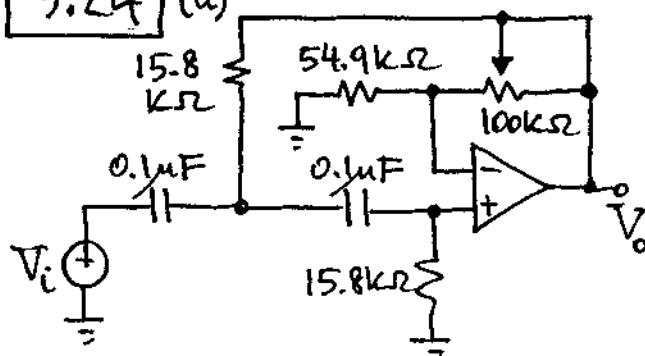

Let $C = 0.1 \mu\text{F}$.

Then,

$$R = \frac{1}{2\pi \times 100 \times 10^{-7}} = 15.9 \text{ k}\Omega.$$

Use 15.8 kΩ.

$$R_B/R_A = K-1 = 3-1/Q-1 = 2-1/Q.$$

$$(Q=0.5) \Rightarrow R_B/R_A = 2-1/0.2 = 0$$

$$(Q=5) \Rightarrow R_B/R_A = 2-1/5 = 1.8. \text{ Thus,}$$

$$R_A = 100/1.8 = 55.5 \text{ k}\Omega \text{ (use } 54.9 \text{ k}\Omega).$$

(b) The DC component is blocked out, and since $\omega/\omega_0 = 60/100 = 0.6$, the ac component is magnified by

$$H = \frac{-(3-1/Q)0.6^2}{1-0.6^2+j0.6/Q} = \frac{0.5625(1/Q-3)}{1+j0.9375/Q}.$$

(3.15)

For $Q=0.5$, $H = \frac{-0.5625}{1+j1.875}$, so that $|H| =$

$$\frac{0.5625}{\sqrt{1+1.875^2}} = 0.265, \angle H = 180^\circ - \tan^{-1} 1.875 =$$

118° . Thus, $V_{om} = 0.265 \times 5 \times \sqrt{2} = 1.874 \text{ V}$, so that
 $v_o(t) = 1.874 \cos(2\pi 60t + 118^\circ) \text{ V}$.

Likewise, for $Q=5$, it is found that

$$v_o(t) = 10.95 \cos(2\pi 60t + 169^\circ) \text{ V}$$

3.25 (a) With $C_1=C_2=C$, Eq. (3.65a) gives
 $R_2 = 1/w_0^2 C^2 R_1$, and Eq. (3.65b) gives $1/Q =$
 $= (1-K)\sqrt{R_2/R_1} + 2\sqrt{R_1/R_2} = (1-K)/w_0 R_1 C + 2 w_0 R_1 C$,
or $(2w_0 C)R_1^2 - (1/Q)R_1 + (1-K)/w_0 C = 0$. Solving
and letting $K \rightarrow H_{OHP}$ gives, for $K > 1$, $R_1 =$
 $[1 + \sqrt{1 + 8Q^2 (H_{OHP} - 1)}]/4w_0 Q C$.

(b) Let $C_1=C_2=10 \text{ nF}$. Then,

$$R_1 = \frac{1 + \sqrt{1 + 8 \times 0.5 (10 - 1)}}{4 \times 2\pi 10^3 \times 10^{-8}/\sqrt{2}} = 39.9 \text{ k}\Omega \text{ (use } 40.2 \text{ k}\Omega)$$

$$R_2 = \frac{1}{(2\pi 10^3 \times 10^{-8})^2 \times 39.9 \times 10^3} = 6.35 \text{ k}\Omega \text{ (use } 6.34 \text{ k}\Omega)$$

Moreover, for $H_{OHP} = 10 \text{ V/V}$ use $R_A = 10.0 \text{ k}\Omega$ and $R_B = 90.9 \text{ k}\Omega$, all 1%.

3.26 With $C_1=C_2=C$ and $K=2$, Eqs. (3.66)
give $H_{OBP} = 2/(1 + 2R_1/R_2 - R_1/R_3)$.

$$\frac{w_0}{Q} = \frac{1}{C} \left(\frac{1}{R_1} - \frac{2}{R_2} - \frac{1}{R_3} \right) \text{ and } w_0^2 = \frac{1}{R_2 C^2} \left(\frac{1}{R_1} + \frac{1}{R_3} \right)$$

3.16

To simplify our calculations, let us first design for $\omega_0 = 1 \text{ rad/s}$ with $C = 1 \text{ F}$ and $R_1 = 1 \Omega$; then we suitably rescale all components. Our equations are now $1/Q = (1 - 2/R_2 - 1/R_3)$, $1 = (1 + 1/R_3)/R_2$. Letting $1/R_2 \rightarrow G_2$ and $1/R_3 \rightarrow G_3$ gives $1/5 = 1 + 2G_2 - G_3$, $1 = G_2(1 + G_3)$. Eliminating G_2 gives $G_3^2 + 0.2G_3 - 2.8 = 0$, $G_2 = 1/(1 + G_3)$.


$$G_3 = \frac{-0.2 + \sqrt{0.2^2 + 4 \times 2.8}}{2} = 1.5763 \Rightarrow R_3 = 0.6344 \Omega,$$

$$R_2 = 2.5763 \Omega, H_{OBP} = 10 \text{ V/V}.$$

Use $C = 10 \text{ mF}$, indicating that all resistances must be increased by $(1 \text{ F})/(10 \text{ mF}) = 10^8$, and then decreased by $\omega_0/(1 \text{ rad/s}) = 2\pi/10^3$, for a total of $10^8/2\pi/10^3 = 10^5/2\pi$. Thus, $R_1 = 1 \times 10^5/2\pi = 15.9 \text{ k}\Omega$ (use $15.8 \text{ k}\Omega$), $R_2 = 41.0 \text{ k}\Omega$ (use $41.2 \text{ k}\Omega$), and $R_3 = 10.1 \text{ k}\Omega$ ($10.0 \text{ k}\Omega$). Finally, to ensure $H_{OBP} = 0 \text{ dB}$, replace R_1 with a voltage divider as in Eq. (3.63) to get $R_{1A} = 158 \text{ k}\Omega$ and $R_{1B} = 17.8 \text{ k}\Omega$, all 1% . The circuit checks with PSpice.

3.17

3.27

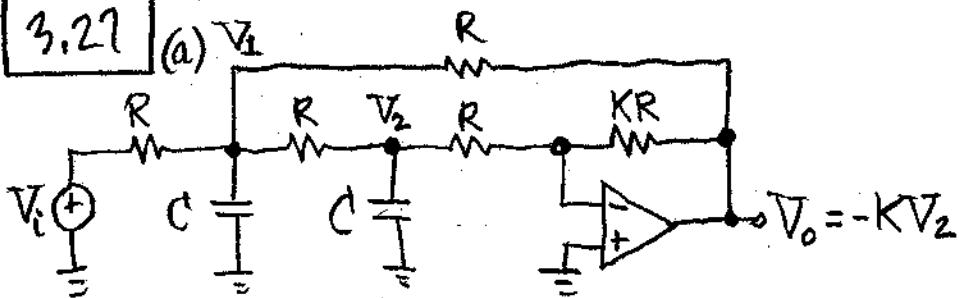

Summing currents at V_1 and V_2 :

$$\frac{V_i - V_1}{R} - sCV_1 + \frac{V_2 - V_1}{R} + \frac{V_o - V_1}{R} = 0$$


$$\frac{V_1 - V_2}{R} - sCV_2 - \frac{V_2}{R} = 0. \text{ Eliminating } V_1 \text{ and } V_2 \text{ gives}$$

$H = V_o / V_i = H_{OLP} \times H_{LP}$, where $H_{OLP} = -K$, $\omega_0 = \sqrt{K+5}/RC$, and $Q = \sqrt{K+5}/5$.

(b) $K = 25Q^2 - 5 = 620$. Let $C = 0.5\mu F$; then $R = \sqrt{620+5} / (0.5 \times 10^{-6} \times 2\pi \times 2 \times 10^3) = 3.98 k\Omega$, and $KR = 2.47 M\Omega$ (use $2.49 M\Omega$, 1%). For 0-dB dc gain, replace R_i with a voltage divider as per Eq. (3.63). This gives $R_{IA} = 2.49 M\Omega$ and $R_{IB} = 4.02 k\Omega$.

3.28

(a)

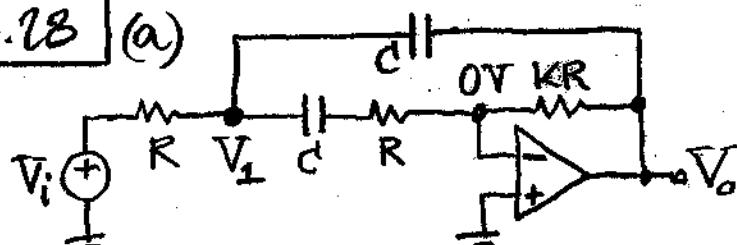


$$V_o = -\frac{KR}{R+1/sC} V_1; \frac{V_o - V_1}{R} + \frac{V_o - V_1}{1/sC} - \frac{V_1}{R+1/sC} = 0$$

Eliminating V_1 gives $H = V_o / V_i = H_{OBP} \times H_{BP}$, $\omega_0 = 1/(RC\sqrt{K+1})$, $Q = \sqrt{K+1}/3$, $H_{OBP} = -K/3$.

(3.18)

(b) $K = 9Q^2 - 1 = 899$; let $C = 3.3 \text{ mF}$; then
 $R = 1 / (\sqrt{900} \times 2\pi \times 10^3 \times 3.3 \times 10^{-9}) = 1.607 \text{ k}\Omega$, and
 $KR = 1.445 \text{ M}\Omega$ (inc $1.43 \text{ M}\Omega$, 1%). To
lower the resonance gain from $-899/3 \text{ V/V}$
to -1 V/V , replace R_1 with a voltage divider
consisting of $R_{1A} = 1.43 \text{ M}\Omega$ and $R_{1B} = 1.43 \text{ k}\Omega$.

(3.29) (a)

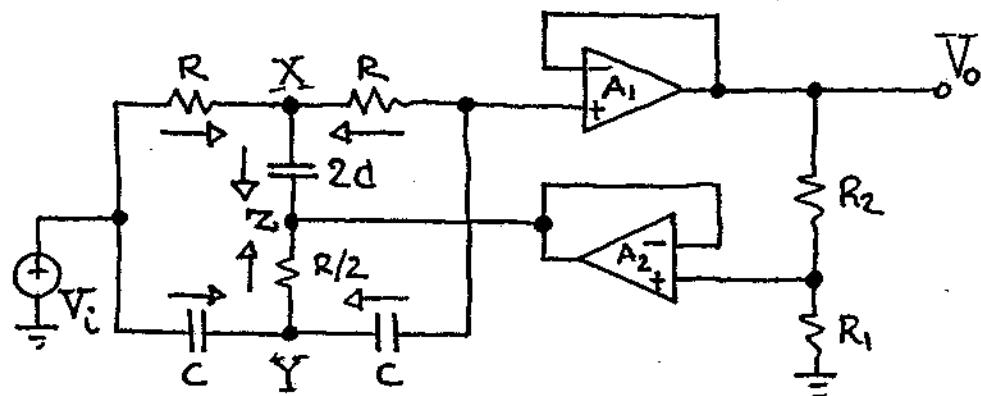

$$V_{p1} = V_{M1} = V_o. \quad V_z = V_{p2} = KV_o, \quad K = R_1 / (R_1 + R_2).$$

KCL at X:

$$(V_i - V_x)/R + (V_o - V_x)/R = j\omega 2C(V_x - KV_o).$$

Solving for V_x :

$$V_x = \frac{V_i + (1 + 2j\omega KR) V_o}{2(1 + j\omega RC)}.$$

KCL at Y:

$$j\omega C(V_i - V_y) + j\omega C(V_o - V_y) = (V_y - KV_o)/(R/2).$$

Solving for V_y :

$$V_y = \frac{j\omega R C V_i + (2K + j\omega RC) V_o}{2(1 + j\omega RC)}.$$

3.19

Superposition principle at A₁'s noninverting input:

$$V_o = V_{p1} = \frac{1}{1+j\omega RC} V_x + \frac{j\omega RC}{1+j\omega RC} V_y.$$

Substituting V_x and V_y and collecting:

$$V_i(1-\omega^2 R^2 C^2) = [1-\omega^2 R^2 C^2 + j4(1-k)\omega RC] V_o.$$

Letting $\omega^2 R^2 C^2 = (\omega/\omega_0)^2$, so that $\omega_0 = 1/RC$ and $Q = 1/[4(1-k)] = (1+R_1/R_2)/4$, we have

$$H = \frac{V_o}{V_i} = \frac{1 - (f/f_0)^2}{1 - (f/f_0)^2 + (j/Q)(f/f_0)} = H_N.$$

(b) Let $C = 0.1 \mu F$; then $R = 1/(2\pi 60 \times 10^{-7}) = 26.5 \text{ k}\Omega$ (use $26.7 \text{ k}\Omega, 1\%$); $25 = (1+R_1/R_2)/4$
 $\Rightarrow R_1/R_2 = 99$. Pick $R_1 = 100 \text{ k}\Omega$, $R_2 = 1.00 \text{ k}\Omega$.

3.30 With $R_1 = R_2 = R_3 = R$, Eq. (3.74) gives $H_{OLP} = -1 \text{ V/V}$, $\omega_0 = 1/(R\sqrt{C_1 C_2})$, $Q = \sqrt{C_1/C_2}/3$. Pick C_2 ; then $C_1 = Q^2 C_2$, $R = 1/3\omega_0 Q C_2$.

3.31 (a) $V_o = -KV_i - K(-2H_{BP}V_i) = -K(1-2H_{BP})V_i$
 $\times V_i = -KH_{AP}V_i$.

(b) $C_1 = C_2 = 10 \text{ mF}$, $R_2 = 158 \text{ k}\Omega$, $R_{1A} = 40.2 \text{ k}\Omega$, $R_{1B} = 3.32 \text{ k}\Omega$, $R_3 = R_4 = 10.0 \text{ k}\Omega$, $R_5 = 100 \text{ k}\Omega$, all 1%.

3.32

$V_m = V_p = V_i/3$. Let V_1 be the voltage at the left plates of the capacitors. KVL:

$$V_1 = \frac{V_i}{3} + \frac{1}{sC} \frac{V_i/3 - V_o}{R}; \text{ KCL:}$$

$$\frac{V_i - V_1}{0.5R} + sC(V_i/3 - V_1) + sC(V_o - V_1) = 0.$$

Eliminating V_1 , collecting, and letting $s = j\omega$,

$$\frac{V_o}{V_i} = \frac{1}{3} \frac{1 - \omega^2 R^2 C^2 / 2 + j\omega R C}{1 - \omega^2 R^2 C^2 / 2 + j\omega R C} = \frac{1}{3} \text{HAP},$$

$$\omega_0 = \frac{\sqrt{2}}{RC}, Q = \frac{1}{\sqrt{2}}.$$

3.33

(a) Denoting the output of OA₁ as V_1 , we have $V_o = H_{OBP} H_{BP} V_1 = H_{OBP} H_{BP} [(-R_5/R_3)V_i - (R_5/R_4)V_o]$, where $H_{OBP} = -2Q^2 R_{IB}/(R_{IA} + R_{IB})$, and $Q = 0.5\sqrt{R_2/(R_{IA}\parallel R_{IB})}$. Collecting gives

$$-\frac{V_o}{V_i} = H_{OBP(\text{comp})} \times \frac{(j\omega/\omega_0)/Q_{\text{comp}}}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q_{\text{comp}}},$$


$$\omega_0 = \frac{1}{[R_2(R_{IA}\parallel R_{IB})]^{1/2}C}, Q_{\text{comp}} = \frac{Q}{1 - (R_5/R_4)|H_{OBP}|}$$

$$H_{OBP(\text{comp})} = \frac{R_5}{R_3} \frac{Q_{\text{comp}}}{Q} |H_{OBP}|.$$

(b) For simplicity, design the band-pass stage for $|H_{OBP}| = 1 \text{ V/V}$. A component set is $C = 10 \text{ nF}$, $R_2 = 88.7 \text{ k}\Omega$, $R_{IA} = 44.2 \text{ k}\Omega$, $R_{IB} = 221 \Omega$. To achieve $G_0 = 10/(1 - R_5/R_4)$ and $2 = (R_5/R_3) \times G_0/10$ use $R_5 = 100 \text{ k}\Omega$, $R_4 = 121 \text{ k}\Omega$, $R_3 = 301 \text{ k}\Omega$.


3.21

3.34

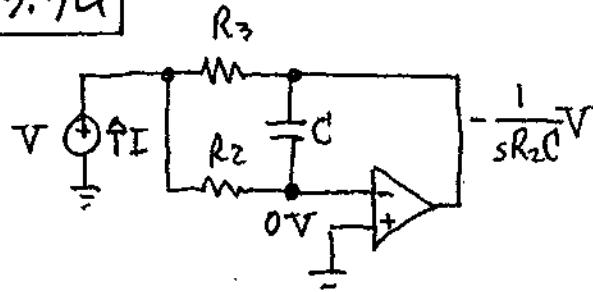

$$I = \frac{V}{R_2} + \frac{V - (-V/sR_2C)}{R_3} = V \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{sR_2R_3C} \right);$$

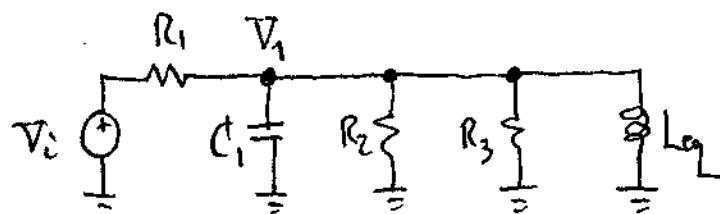
$$Z_{eq} = \frac{V}{I} = R_2 \parallel R_3 \parallel sL_{eq}, L_{eq} = R_2R_3C.$$



$\omega \rightarrow 0 \Rightarrow V_1 \rightarrow 0$ because of L_{eq}
 $\omega \rightarrow \infty \Rightarrow V_1 \rightarrow 0$ because of $C_1 \}$ $\Rightarrow V_1 = \text{band-pass.}$

The op amp integrates V_1 , indicating that the pole at the origin due to integration cancels out the zero at the origin due to the band-pass response V_1 . Consequently, the op amp output is a low-pass response.

3.35

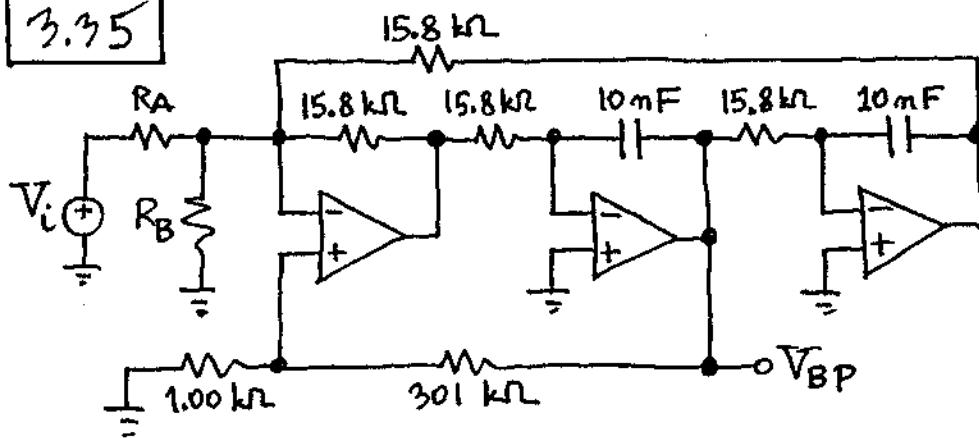

(3.22)

Impose $R_A // R_B = \frac{R_A R_B}{R_A + R_B} = 15.8 \text{ k}\Omega$ and

$\frac{R_B}{R_A + R_B} = \frac{1}{Q} = \frac{1}{100}$. Solving, we obtain

$R_A = 1.58 \text{ M}\Omega$ and $R_B = 15.8 \text{ k}\Omega$.

3.36 (a) By the superposition principle,
 $V_{HP} = KV_i + KV_{BP} - V_{LP}$, where

$$K = 2 \frac{R_1 // R_2}{R_1 // R_2 + R_2} = \frac{2R_1}{2R_1 + R_2}. \text{ Expanding,}$$

$$V_{HP} = KV_i - K \frac{1}{j\omega/\omega_0} V_{HP} + \frac{1}{j\omega/\omega_0} V_{HP}.$$

Expanding and collecting,

$$[1 - (\omega/\omega_0)^2 + jK(\omega/\omega_0)]V_{HP} = -K(\omega/\omega_0)^2 V_i.$$

Letting $Q = 1/K = 1 + (1/2)R_2/R_1$, we have

$$\frac{V_{HP}}{V_i} = \frac{1}{Q} H_{HP}. \text{ Likewise, } \frac{V_{BP}}{V_i} = -H_{BP}, \text{ and}$$

$$\frac{V_{LP}}{V_i} = \frac{1}{Q} H_{LP}, \quad \omega_0 = 1/RC.$$

(b) $f_0 = (594 \times 606)^{1/2} = 600 \text{ Hz}$. $Q = 600/(606 - 594) = 50$. Let $C = 10 \text{ mF}$. Then,

$$R = 1/(2\pi \times 600 \times 10^{-8}) = 26.5 \text{ k}\Omega \text{ (use } 26.7 \text{ k}\Omega\text{).}$$

$R_2/R_1 = 2(Q-1) = 98$. Use $R_1 = 1.02 \text{ k}\Omega$, $R_2 = R_3 = 100 \text{ k}\Omega$, all 1%.

(c) $H_{OLP} = 1/Q = 1/50 = 0.02 \text{ V/V}$.

3.23

3.37 (a) $V_{m1} = V_{p1} = V_{LP}$. Integrator:

$$V_{LP} = -\frac{1}{j\omega m RC} V_{BP} \Rightarrow V_{BP} = -j\omega m R C V_{LP}.$$

KCL:

$$\frac{V_i - V_{LP}}{R} = \frac{V_{LP}}{mR} + j\omega C (V_{LP} - V_{BP})$$

Eliminating V_{BP} and collecting,

$$\frac{V_{LP}}{V_i} = \frac{m}{m+1} \frac{1}{1 - \omega^2 R^2 C^2 \frac{mm}{m+1} + j\omega R C \frac{m}{m+1}}.$$

Letting $\omega^2 R^2 C^2 mm/(m+1) = (\omega/\omega_0)^2$,
 $\omega R C m/(m+1) = (\omega/\omega_0)/Q$, and $H_{LP} = m/(m+1)$ yields

$$H = H_{LP} H_{LP}, \quad \omega_0 = \frac{1}{\sqrt{mm/(m+1)} RC} \quad \text{and} \\ Q = \sqrt{m(m+1)/m}.$$

$$\frac{V_{BP}}{V_i} = -j\omega m R C \frac{V_{LP}}{V_i} = -\frac{j\omega m R C m / (m+1)}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}.$$

Letting $\omega m R C m / (m+1) = H_{OBP} (\omega/\omega_0)/Q$
yields $H_{OBP} = -m$.

(b) Let $m = \infty$ (mR absent). Then,
 $Q = 10 \Rightarrow m = 100$. Let $C = 1 \mu F$. Then, $R = 7.957 \text{ k}\Omega$
(use 8.06 k Ω) and $mR = 806 \text{ k}\Omega$. $H_{OBP} = 100 \text{ V/V}$.

(c) $H_{OBP} \propto Q^2$, increases quadratically
with Q .

3.24

3.38

(a) $V_N = \alpha V_{LP} + \beta V_{HP}$ implies

$$\frac{V_N}{V_i} = \alpha \frac{V_{LP}}{V_i} + \beta \frac{V_{HP}}{V_i} = \alpha H_{OLP} H_{LP} + \beta H_{OHP} H_{HP}$$

$$H_N = \frac{\alpha H_{OLP} - \beta H_{OHP} (f/f_0)^2}{1 - (f/f_0)^2 + (j/Q)(f/f_0)}$$


$$H_N = \alpha H_{OLP} \frac{1 - (f/f_z)^2}{1 - (f/f_0)^2 + (j/Q)(f/f_0)},$$

$$f_z = f_0 \left[\frac{\alpha}{\beta} \frac{H_{OLP}}{H_{OHP}} \right]^{1/2}.$$


(b) Let $C = 10 \mu F$. Then, $R = 15.8 k\Omega$.

$R_2/R_1 = 2(Q-1) = 18$. Let $R_1 = 10 k\Omega$, $R_2 = 180 k\Omega$. Since $H_{OLP}/H_{OHP} = 1$ for the noninverting state-variable filter, it follows that $\alpha/\beta = (f_z/f_0)^2 = 2^2$. Moreover, since the dc gain of the notch response is $\alpha H_{OLP} = \alpha/Q$, it follows that to achieve unity dc gain we need $\alpha = 10$. Thus, we need a summing amplifier such that $V_N = -(10V_{LP} + 2.5V_{HP})$. This is shown below.

3.25

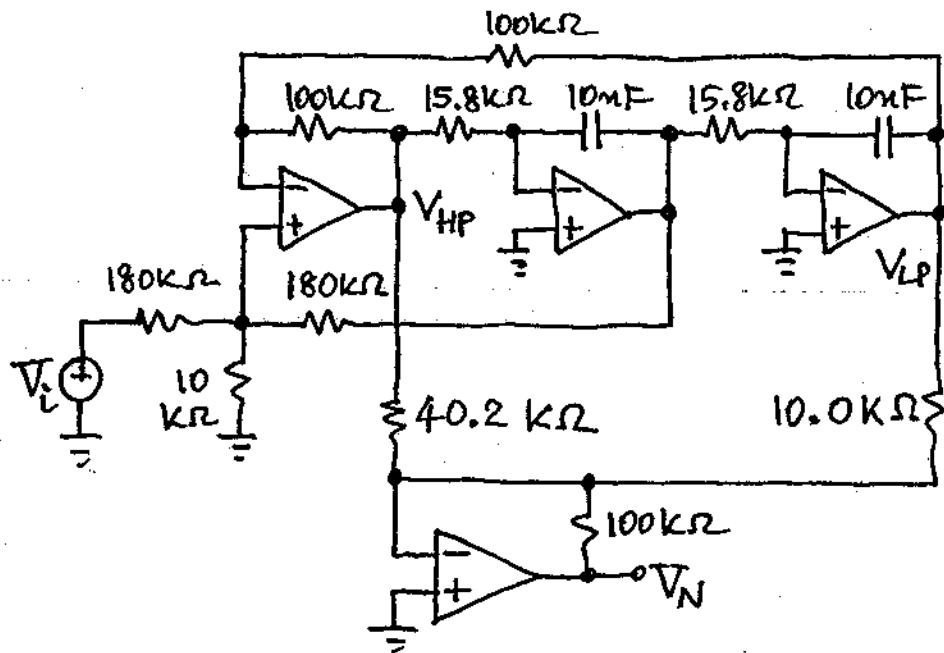

3.39

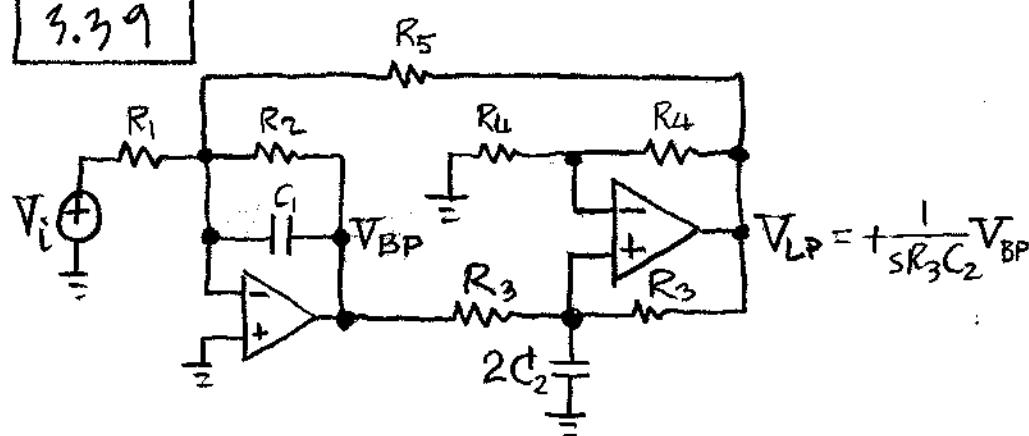

$$V_{BP} = -\frac{1}{sR_1C_1}V_i - \frac{1}{sR_2C_1}V_{BP} - \frac{1}{sR_5C_1} \left(+\frac{1}{sR_3C_2}V_{BP} \right)$$

$$\frac{V_{BP}}{V_i} = -\frac{(R_2/R_1) \times sR_3R_5C_1C_2/R_2C_1}{1 + s^2R_3R_5C_1C_2 + sR_3R_5C_1C_2/R_2C_1}$$


$$\omega_0 = 1/\sqrt{R_3R_5C_1C_2}, Q = R_2\sqrt{C_1}/\sqrt{R_3R_5C_2}, H_{0BP} = -\frac{R_2}{R_1}$$

$$H_{0LP} = -R_5/R_1.$$

$$\text{Let } C_1 = C_2 = 1 \text{ nF}, R_3 = R_5 = \frac{1}{2\pi \times 10^4 \times 10^{-9}} = 15.8 \text{ k}\Omega, R_2 = 80.6 \text{ k}\Omega, R_1 = 15.8 \text{ k}\Omega = R_4.$$

3.26

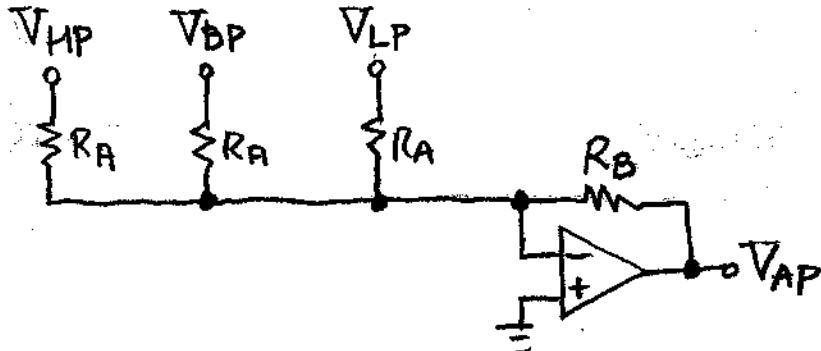3.40 Use the filter of Fig. 3.34 with $C_1 = C_2 = 10 \text{ mF}$, $R_6 = R_7 = 1/(2\pi 10^3 \times 10^{-8}) = 15.8 \text{ k}\Omega$, $R_1 = 10.0 \text{ k}\Omega$, $R_2 = 20.0 \text{ k}\Omega$, $R_3 = R_4 = R_5 = 10.0 \text{ k}\Omega$. Then the circuit gives $V_{HP} = -1H_{HP}V_i$, $V_{BP} = 1H_{BP}V_i$, and $V_{LP} = -1H_{LP}V_i$, which we combine as:



$$\frac{V_{AP}}{V_i} = -\frac{R_B}{R_A} \left(-H_{HP} + H_{BP} - H_{LP} \right) = \frac{R_B}{R_A} H_{AP}.$$

Use $R_A = R_B = 10.0 \text{ k}\Omega$.

3.41 (3.92a):

$$S_{1/x}^y = \frac{\partial y}{\partial (1/x)} \frac{1/x}{y} = \frac{\partial y}{\partial x} \frac{\partial x}{\partial (1/x)} \frac{1/x}{y} = -\frac{\partial y}{\partial x} \frac{x}{y} = -S_x^y$$

Likewise, $S_x^{1/y} = -S_x^y$.

(3.92b):

$$\begin{aligned} S_x^{y_1, y_2} &= \frac{\partial(y_1 y_2)}{\partial x} \frac{x}{y_1 y_2} = \left(y_2 \frac{\partial y_1}{\partial x} + y_1 \frac{\partial y_2}{\partial x} \right) \frac{x}{y_1 y_2} \\ &= \frac{\partial y_1}{\partial x} \frac{x}{y_1} + \frac{\partial y_2}{\partial x} \frac{x}{y_2} = S_x^{y_1} + S_x^{y_2} \end{aligned}$$

(3.92c):

$$S_x^{y_1/y_2} = S_x^{y_1 y_2^{-1}} = S_x^{y_1} + S_x^{y_2^{-1}} = S_x^{y_1} - S_x^{y_2}.$$

(3.92d):

(3.27)

$$S_x^{x^n} = \frac{x}{x^n} \frac{\partial x^n}{\partial x} = \frac{1}{x^{n-1}} n x^{n-1} = n.$$

(3.92e):

$$S_{x_1}^y = \frac{x_1}{y} \frac{\partial y}{\partial x_1} = \frac{x_2}{y} \frac{\partial y}{\partial x_2} \frac{x_1}{x_2} \frac{\partial x_2}{\partial x_1} = S_{x_2}^y S_{x_1}^{x_2}.$$

3.42

The denominator of $H(s)$ can be expressed as

$$D(s) = (s+a)(s+b) - Kcs$$

where $c > 0$ is a suitable constant, and $-a$ and $-b$ are the zeros of D (poles of H) in the limit $K \rightarrow 0$. Rearranging as

$$D(s) = s^2 + s(a+b-Kc) + ab \text{ indicates}$$

$$\omega_0 = 1/\sqrt{ab} \text{ and } Q = \sqrt{ab}/(a+b-Kc). \text{ Then,}$$

$$S_K^Q = -\frac{-Kc}{a+b-Kc} = Q \left(\sqrt{\frac{a}{b}} + \sqrt{\frac{b}{a}} \right) - 1. \text{ It is readily seen that the expression within parentheses is always } \geq 2, \text{ so } S_K^Q \geq 2Q-1.$$

3.43

$$(a) \omega_0 = 1/R\sqrt{C_1 C_2}, Q = \sqrt{C_1/C_2}/3.$$

$$(b) S_{R_2}^{w_0} = S_{R_3}^{w_0} = S_{C_1}^{w_0} = S_{C_2}^{w_0} = -1/2;$$

$$S_{R_1}^{w_0} = 0; S_{R_2}^Q = S_{R_3}^Q = -1/6; S_{R_1}^Q = 1/3; S_{C_1}^Q = -S_{C_2}^Q = 1/2.$$

3.44

$$\text{From Eq. (3.79), } S_{K_4}^{w_0} = S_{R_6}^{w_0} = S_{R_7}^{w_0} = -S_{K_5}^{w_0} = S_{C_1}^{w_0} = S_{C_2}^{w_0} = 1/2.$$

3.28

Writing $Q = A(1 + R_2/R_1)$ gives

$$S_{R_2}^Q = -S_{R_1}^Q = \frac{R_2}{Q} \frac{\partial Q}{\partial R_2} = \frac{R_2}{Q} \frac{A}{R_1} = \frac{1}{1+R_1/R_2} = \frac{1}{1+1/299} \cong +1.$$

Writing $\frac{1}{Q} = B \left(1 + \frac{R_5}{R_3} + \frac{R_5}{R_4} \right)$ gives

$$S_{R_3}^Q = -S_{R_3}^{1/Q} = -QR_3 \frac{\partial(1/Q)}{\partial R_3} = \frac{1}{1+R_3/R_4+R_3/R_5} = +\frac{1}{3}.$$

Writing $Q = D \sqrt{R_6 C_1 / R_7 C_2}$ gives

$$S_{R_6}^Q = S_{R_7}^Q = -S_{R_7}^Q = -S_{C_2}^Q = 1/2.$$

Writing $Q = E \frac{R_5^{1/2}}{1+R_5/R_3+R_5/R_4}$ gives

$$S_{R_5}^Q = \frac{1}{2} \frac{1-R_5/R_3-R_5/R_4}{1+R_5/R_3+R_5/R_4} = -\frac{1}{6}$$

Writing $\frac{1}{Q} = F \left(1 + \frac{R_5}{R_3} + \frac{R_5}{R_4} \right) \sqrt{R_4}$ gives

$$S_{R_4}^Q = -S_{R_4}^{1/Q} = -\frac{1}{2} \frac{1+R_5/R_3-R_5/R_4}{1+R_5/R_3+R_5/R_4} = -\frac{1}{6}$$