

12.1

**12.1** Ideally,  $1 \text{ LSB} = 3.2/2^3 = 0.4 \text{ V}$ . The offset error is  $V_o(000) = 0.2 \text{ V} = +1/2 \text{ LSB}$ . To eliminate the offset error, we decrease each output value by 0.2. This gives  $V_o(111) = 2.9 - 0.2 = 2.7 \text{ V}$ . Ideally, we want  $V_o(111) = V_{FSV} = 3.2 - 0.4 = 2.8 \text{ V}$ , indicating a gain error of  $-0.1 \text{ V} = -1/4 \text{ LSB}$ . To eliminate the gain error, multiply all new values of  $V_o$  by  $2.8/2.7$ . The result is  $V_o(000) = (0.2 - 0.2)28/27 = 0$ ,  $V_o(001) = (0.5 - 0.2)28/27 = 0.3\bar{7}$ ,  $V_o(010) = (1.1 - 0.2)28/27 = 0.9\bar{3}$ ,  $1.2\bar{4}$ ,  $1.\bar{5}$ ,  $1.8\bar{6}$ ,  $2.4\bar{8}$ , and  $2.8$ , all in volts. The ideal values are 0, 0.4, 0.8, 1.2, 1.6, 2.0, 2.4, and 2.8, all in volts. We have:

$$\begin{aligned} \text{INL}_k &= 0, -0.0\bar{8}, 0.1\bar{3}, 0.0\bar{4}, -0.0\bar{4}, -0.1\bar{3}, 0.0\bar{8}, 0, \text{ in V} \\ \text{DNL}_k &= -0.0\bar{8}, 0.\bar{2}, -0.0\bar{8}, -0.0\bar{8}, -0.0\bar{8}, 0.\bar{2}, -0.0\bar{8}, \text{ in V.} \end{aligned}$$

Thus,  $\text{INL} = 0.1\bar{3} \text{ V} = 4/3 \text{ LSB}$ ;  $\text{DNL} = 0.\bar{2} \text{ V} = 5/9 \text{ LSB}$ .

**12.2**  $\text{SNR} = 10 \log_{10} [(1 \text{ W}) / (0.6 \mu\text{W})] = 62.22 \text{ dB}$ . But,  $\text{SNR} = 6.02m + 1.76 = 62.22$ , so,  $m = 10.04$  effective bits. Since  $1/100 = -40 \text{ dB}$ , we have  $\text{SNR} = 62.22 - 40 = 22.22 \text{ dB}$ .

12.2

12.3

$$1 \text{ LSB} = 1.600 / 2^6 = 25 \text{ mV.}$$

To find the offset error, set all bits to zero.

$$\text{Then, } V_o = V_{os} = \pm 5 \text{ mV} = \pm \sqrt{5} \text{ LSB.}$$

To find the gain error, assume the offset error has been nulled, and set all bits to 1. Then,  $V_o = -(R_f/R_{eq})V_{ref}/(1 + 1/T)$ , where

$$R_{eq} = (2R) \parallel (4R) \parallel (8R) \parallel \dots \parallel (64R) = (64/63)R,$$

$$\beta = R_{eq}/(R_{eq} + R_f) = (64/63)/[(64/63) + 0.99] = 0.506, T = \alpha\beta = 200 \times 0.506 = 101.3. \text{ Substituting, } V_o = -\frac{0.99}{64/63} 1.6 \frac{1}{1 + 1/101.3} = -1.544 \text{ V.}$$

$$\text{Ideally, } V_o = -1.600(1 - 2^{-6}) = -1.575 \text{ V.}$$

The gain error is thus +30.3 mV, or +1.2 LSB.

The worst-case value of  $V_o$  occurs when  $V_{bs} = +5 \text{ mV}$ . Then,

$$V_o = \left[ -\frac{R_f}{R_{eq}} V_{REF} + \frac{1}{\beta} V_{os} \right] \frac{1}{1 + 1/T} = -1.535 \text{ V,}$$

which differs from the ideal value of -1.575 V by +40 mV, or 1.6 LSB.

12.3

12.4

$1 \text{ LSB} = 3.200/2^4 = 0.20 \text{ V}$ . Ideally, we have  $V_o(1111) = 3.2 - 0.2 = 3.00 \text{ V}$ . In practice,  $V_o(1111) = \left(\frac{1}{22} + \frac{1}{35} + \frac{1}{50} + \frac{1}{250}\right)V_{REF} = 2.823 \text{ V}$ , indicating a gain error of  $-0.88 \text{ LSB}$ . To null this error, change  $R_f$  to  $9 \times 3 / 2.823 = 9.564 \text{ k}\Omega$ .

CODE	$V_o(\text{ideal})$	$V_o(\text{actual})$	$\text{INL}_k$	$\text{DNL}_k$
0000	0	0	0	0
0001	0.2	0.1224	-0.39	-0.39
0010	0.4	0.6121	1.06	1.45
0011	0.6	0.7345	0.67	-0.39
0100	0.8	0.8744	0.37	-0.30
0101	1.0	0.9968	-0.02	-0.39
0110	1.2	1.4865	1.43	1.45
0111	1.4	1.6089	1.04	-0.39
1000	1.6	1.3911	-1.04	-2.08
1001	1.8	1.5135	-1.43	0.39
1010	2.0	2.0032	0.02	1.45
1011	2.2	2.1256	-0.37	0.39
1100	2.4	2.2655	-0.67	-0.30
1101	2.6	2.3879	-1.06	-0.39
1110	2.8	2.8996	0.39	1.45
1111	3.0	3.0000	0	-0.39


$$\text{INL} = 1.43 \text{ LSB}$$

$\text{DNL} = -2.08 \text{ LSB} \Rightarrow \text{Nonmonotonic}$

12.4

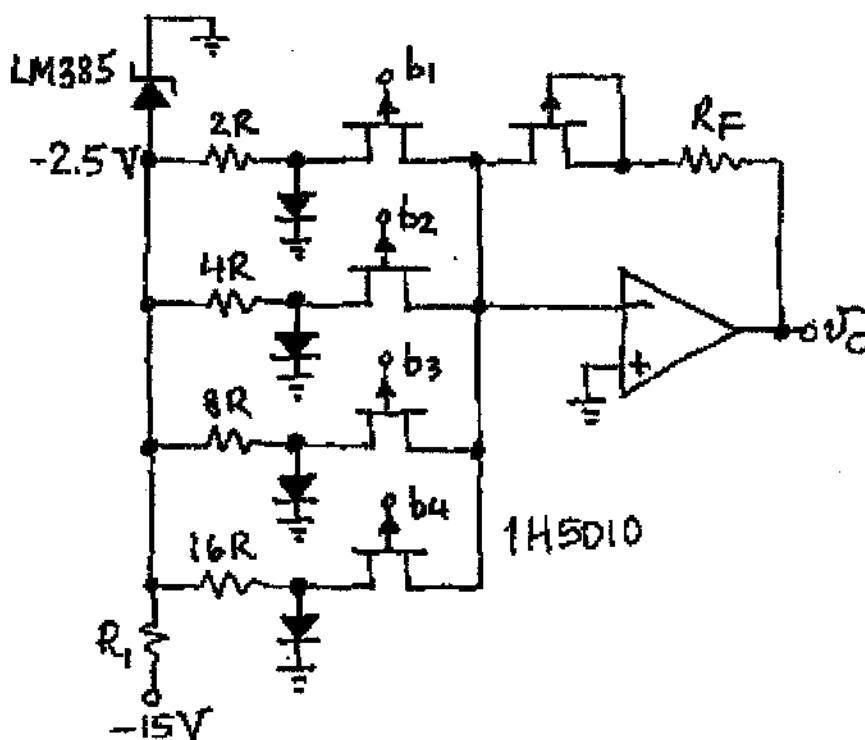12.5

$$(a) V_{PSV} = V_{PSR} (1 - 2^{-4}) = 9.375 \text{ V.}$$



$$V_o(1111) = (-R_F/R)(2^{-1} + 2^{-2} + 2^{-3} + 2^{-4})(-2.5) = 9.375 \text{ V.}$$

Let  $2R = 10 \text{ k}\Omega$ ,  $4R = 20 \text{ k}\Omega$ ,  $8R = 40 \text{ k}\Omega$ ,  $16R = 80 \text{ k}\Omega$ . Then,  $R_F = 20 \text{ k}\Omega$ . The maximum current through the weighted-resistor network is  $9.375/20 = 0.47 \text{ mA}$ . Imposing a minimum reference-diode current of  $1 \text{ mA}$ , we get  $R_1 = (15 - 2.5)/(1 + 0.47) \approx 8.2 \text{ k}\Omega$ .

(b) Taking  $r_{ds(on)} \approx 0.1 \text{ k}\Omega$  into consideration, we have

$$V_o = 2.5 \times 20.1 \left( \frac{b_1}{10.1} + \frac{b_2}{20.1} + \frac{b_3}{40.1} + \frac{b_4}{80.1} \right)$$

As  $b_1, b_2, b_3, b_4$  is varied from 0000 to 1111,  $V_o$

12.5

takes on the following values, in volts:

0, 0.629, 1.253, 1.880, 2.500, 3.127, 3.753,  
4.380, 4.975, 5.603, 6.228, 6.856, 7.475,  
8.103, 8.728, 9.356 V.

(c) We now have


$$V_o = 1 \text{ mV} + 2.501 \times 20.1 \left( \frac{b_1}{10.1} + \frac{b_2}{20.1} + \frac{b_3}{40.1} + \frac{b_4}{80.1} \right).$$

$V_o$  (Volts) = 0.001, 0.629, 1.254, 1.882, 2.502, ... 8.733, 9.360. The offset error is 1 mV. After offset error nulling,  $V_o$  (III) = 9.359 V, which differs from the ideal value of 9.375 V by -0.016 V. Thus, the gain error is -16 mV, or -1/40 LSB.

12.6

As shown in the accompanying figure, the 8-bit DAC consists of two 4-bit DACs with  $V_{FSR} = 10.0$  V. The output of the LS 4-bit DAC is inverted and then scaled by  $R_5$  to a current that is fed into OA<sub>3</sub>'s summing junction along with the four MS bits.  $R_1$  is chosen on the basis of allowing a current of about 1 mA through the reference diode. Due to the presence of the dummy FET in the feedback path of OA<sub>3</sub>, no dummy FET is used in the feedback

12.6

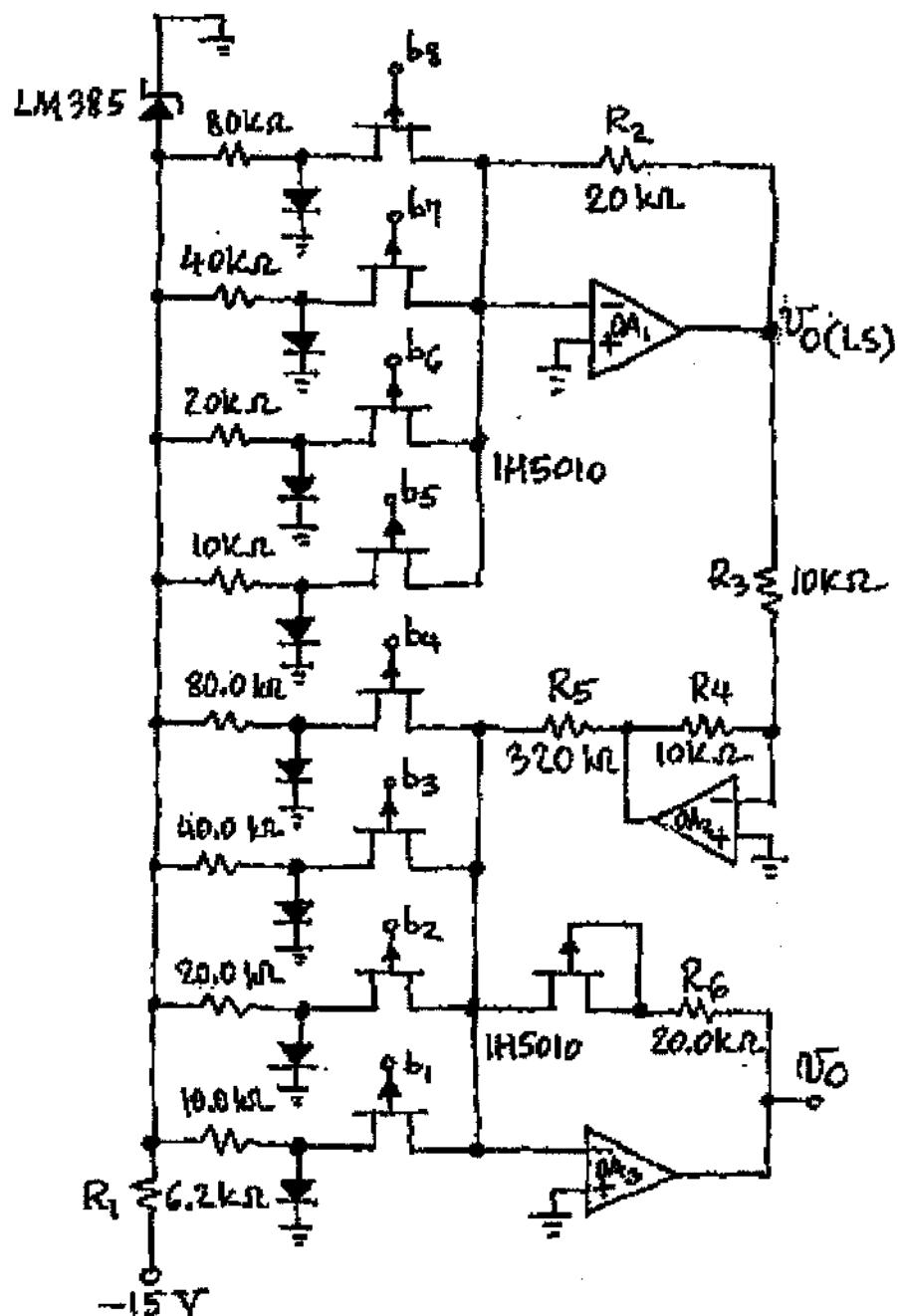
path of  $OA_1$ .

12.7 (a) With reference to the accompanying figure, we set the offsetting resistor  $R_3$  to  $\infty$  ( $R_3$  is absent). Then, the condition

12.7

$10 = (1 + R_2/R_1)2.5$  gives  $R_2/R_1 = 3$ . Use  $R_1 = 10.0$  k $\Omega$  and  $R_2 = 30.0$  k $\Omega$ . Clearly,  $V_{PSV} = 10(1 - 2^{-8}) = 9.961$  V.

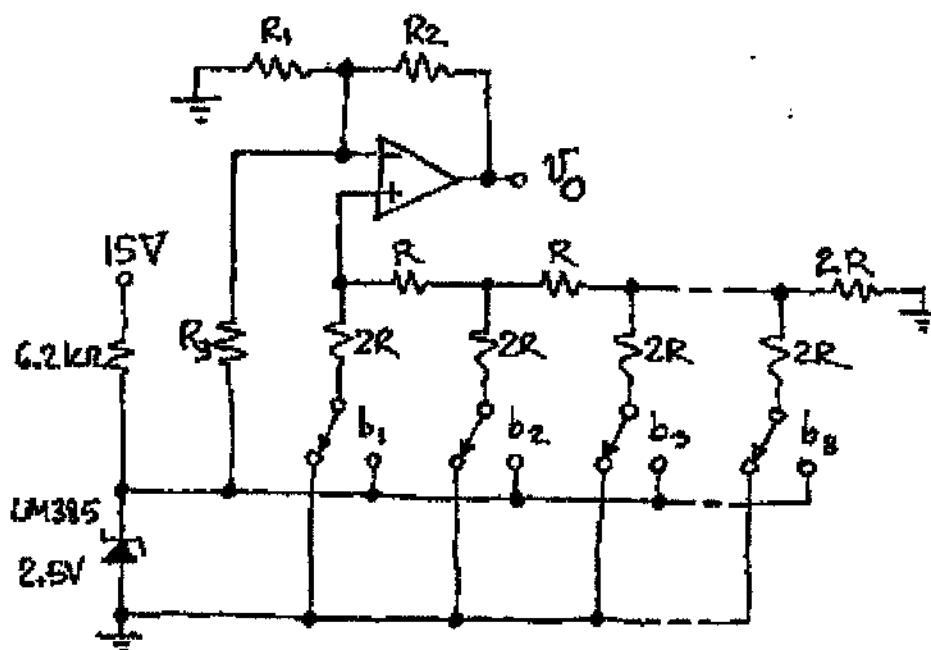(b) With all switches flipped to the left we have  $V_p = 0$ , and we want  $V_o = -5$  V. This requires  $-5 = (-R_2/R_3)2.5$ , or  $R_2/R_3 = 2$ . With all switches flipped to the right we have  $V_p = 2.5(1 - 2^{-8})$ , and we want  $V_o = -5 + 10(1 - 2^{-8}) = 5(1 - 2^{-7})$ . Using the superposition principle, we find that this requires  $5(1 - 2^{-7}) = (-R_2/R_3)2.5 + [1 + R_2/(R_1 \parallel R_3)]2.5(1 - 2^{-8})$ , or  $5(1 - 2^{-7}) = -5 + [1 + R_2/R_1 + 2]2.5(1 - 2^{-8})$ , or  $R_2/R_1 = 1$ . Use  $R_3 = 10.0$  k $\Omega$ ,  $R_1 = R_2 = 20.0$  k $\Omega$ .



12.8

(a) All BJTs conduct the same current  $I = V_{REF}/R_F$ . By R-2R ladder properties,  $R_o = R$ . With  $SW_1$  flipped to the left,  $V_O = RI$ ; With  $SW_2$  flipped to the left,  $V_O = (RI)/2$ ; Generalizing and using the superposition principle, we can write

$$V_O = \frac{V_O}{R} = b_1 I + b_2 \frac{I}{2} + b_3 \frac{I}{4} + b_4 \frac{I}{8}$$

$$= 2 \frac{V_{REF}}{R_F} \left( b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + b_4 2^{-4} \right).$$

(b)  $V_{FSR} = R_F I_{FSR} = (1 k\Omega)(2 \mu A) = 2 V$ ;  
 $1/2 \text{ LSB} = V_{FSR}/2^{m+1} = 2/2^5 = 2^{-4} V = 62.5 \text{ mV}$ .

$$V_O = \frac{1}{2} \text{ LSB} + (V_{FSR} \times D_I) \frac{D_I(\text{max}) - \frac{1}{2} \text{ LSB}}{D_I(\text{max})}$$


$$= 62.5 \text{ mV} + 2 D_I \left[ (-2^{-4} - 2^{-5}) / (1 - 2^{-4}) \right] V$$

$$= [0.0625 + (29/15) D_I] V.$$

The requested actual (ideal) values of  $V_O$  are:  $V_O(0000) = 0.0625 \text{ V (0 V)}$ ;  $V_O(0100) = 0.5458 \text{ V (0.5 V)}$ ;  $V_O(1000) = 1.0292 \text{ V (1 V)}$ ;  $V_O(1100) = 1.5125 \text{ V (1.5 V)}$ ;  $V_O(1111) = 1.8750 \text{ V (1.875 V)}$ .

(c)  $\beta = R_o/(R_o + R_F) = 1/2$ ;  $f_{-3dB} = 25 \text{ MHz}$ .


12.9

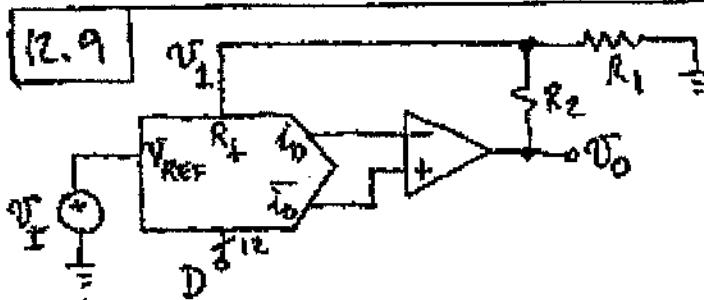

$$V_I = -DV_T; \quad \frac{0-V_I}{R_f} + \frac{0-V_I}{R_1} = \frac{V_I-V_O}{R_2}$$

$V_O = -(1 + R_2/R_1 + R_2/R_f)DV_T$ . To desensitize the circuit to process variations in the value of  $R_f$ , impose  $R_1 \ll R_f$ , e.g. let  $R_1 = R_f/100 = 100 \Omega$ . Then, imposing  $(1 + R_2/0.1 + R_2/10)(1 - 2^{-12}) = 64$  gives  $R_2 = 6.24 \text{ k}\Omega$  (use  $6.19 \text{ k}\Omega, 1\%$ ).

12.10

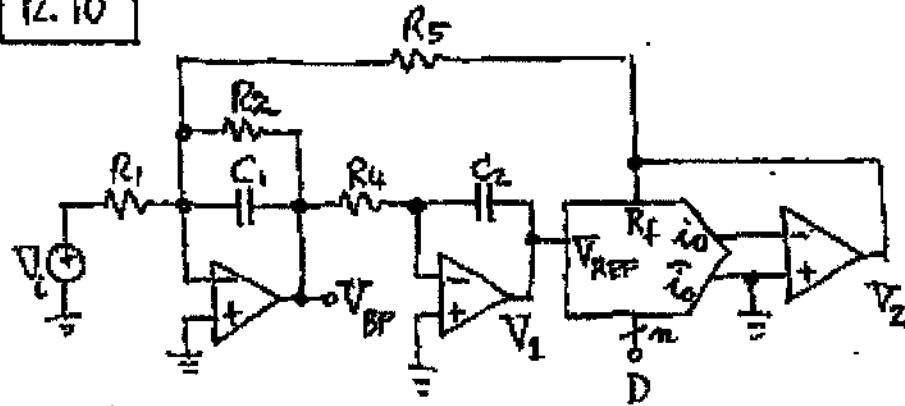

$$V_2 = -DV_1 = -\frac{-D}{5R_4C_2}V_{BP} = \frac{1}{5(R_4/D)C_2} \Rightarrow R_4 \rightarrow \frac{R_4}{D};$$


$$f_{OBP} = -\frac{R_2}{R_4}; \quad f_0 = \frac{1}{2\pi[(R_4/D)R_5C_1C_2]^{1/2}} = \frac{\sqrt{D}}{2\pi\sqrt{R_4R_5C_1C_2}}$$

$$Q = [R_2^2C_1/(R_4/D)R_5C_2]^{1/2} = \sqrt{D} \sqrt{\frac{R_2^2C_1}{R_4R_5C_2}}. \text{ Thus,}$$

$$f_0 \propto \sqrt{D}, \quad Q \propto \sqrt{D}, \text{ and } BW = f_0/Q = 1/2\pi R_2 C_1.$$

12.10

12.11 (a)

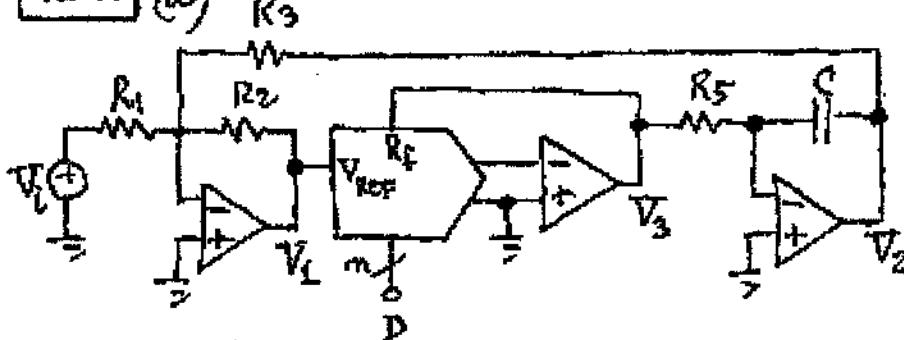

$$V_1 = -\frac{R_2}{R_1} V_i - \frac{R_2}{R_3} V_2; V_2 = -\frac{1}{sR_5C} V_3 = \frac{D}{sR_5C} V_1$$

$$V_1 \left(1 + \frac{DR_2/R_3}{sR_5C}\right) = -\frac{R_2}{R_1} V_i. \text{ Manipulating,}$$

$$\frac{V_1}{V_i} = -\frac{R_2}{R_1} \frac{j\omega/\omega_0}{1+j\omega/\omega_0}, \quad \frac{V_2}{V_i} = -\frac{R_3}{R_2} \frac{1}{1+j\omega/\omega_0},$$


$$\omega_0 = D \frac{R_2/R_3}{R_5C}.$$

$$(b) R_1 = 10.0 \text{ k}\Omega, R_2 = 10.0 \text{ k}\Omega, R_3 = 100 \text{ k}\Omega$$

The full-scale frequency is  $2\pi \times (2^{10}-1)5 = 2\pi \times 5,115 \text{ rad/s. Imposing } 2\pi 5,115 = (1-2^{-10}) \times (10/100)/R_5C \text{ gives } R_5C = 3.1085 \mu\text{s. Use } C = 1 \text{ mF. Then, } R_5 = 3.11 \text{ k}\Omega \text{ (use } 3.09 \text{ k}\Omega, 1\%).$

12.12  $f_{0(\max)} = 10(2^{10}-1) = 10,230 \text{ kHz} = D_{\max}/(2\pi RC) = (1-2^{-10})/RC \Rightarrow RC = 1/10240 \text{ s. Let } C = 10 \text{ nF, } 2C = 20 \text{ nF, } R = 9.96 \text{ k}\Omega; \text{ variable } R: 8.66 \text{ k}\Omega \text{ in series with a } 2-\text{k}\Omega \text{ potentiometer connected as a variable resistance. Imposing } 5 = 0.7 + (R_1/R_2)(15+0.7) \text{ gives } R_2 = 3.65 R_1; \text{ use } R_1 = 10 \text{ k}\Omega, R_2 = 36 \text{ k}\Omega.$


12.11

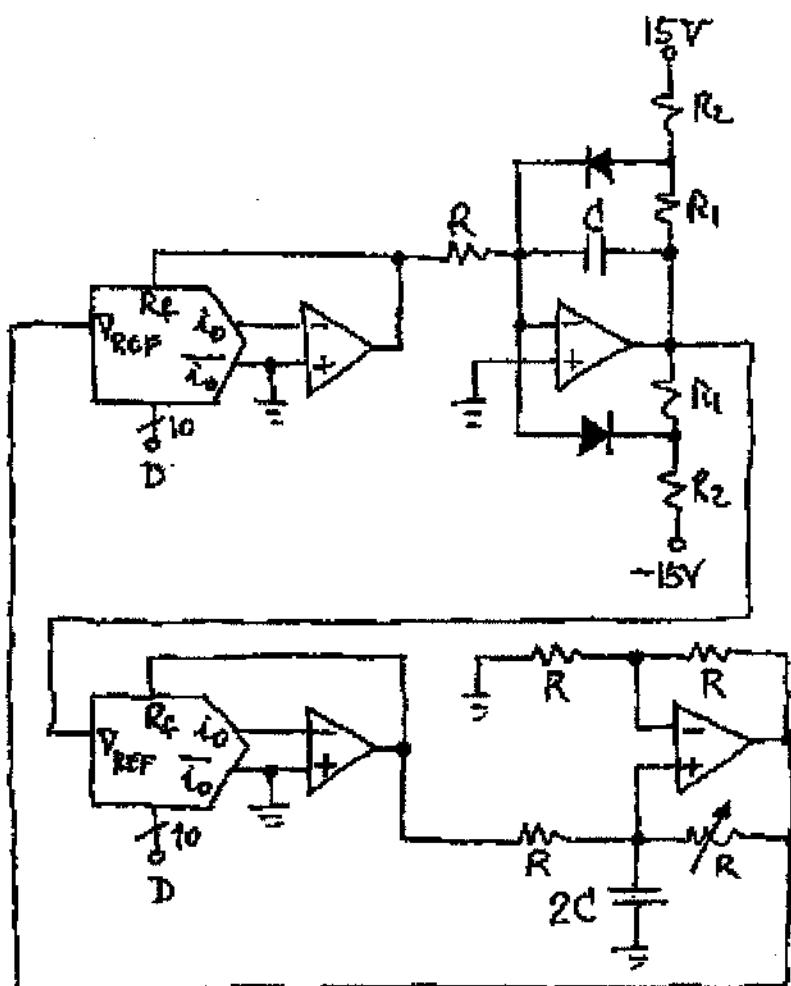

Use of amps with adequately fast dynamic characteristics.

12.13 As shown in the accompanying figure, the DAC is operated in the voltage mode to interpolate between 0 V and  $V_R (1 - 2^{-12})$ . By Eq. (10.28),  $f_0 = DV_R/10RC$ ;  $f_{0(\max)} = (2^{12}-1)10 = 40,950 \text{ Hz} = (1 - 2^{-12}) \times 1/RC \Rightarrow RC = 24.414 \mu\text{s}$ . Use  $C = 20 \text{ mF}$ , and  $R = 1.00 \text{ k}\Omega$  in series with a  $500-\Omega$  potentiometer connected as a variable resistance. Buffer and am-


12.12

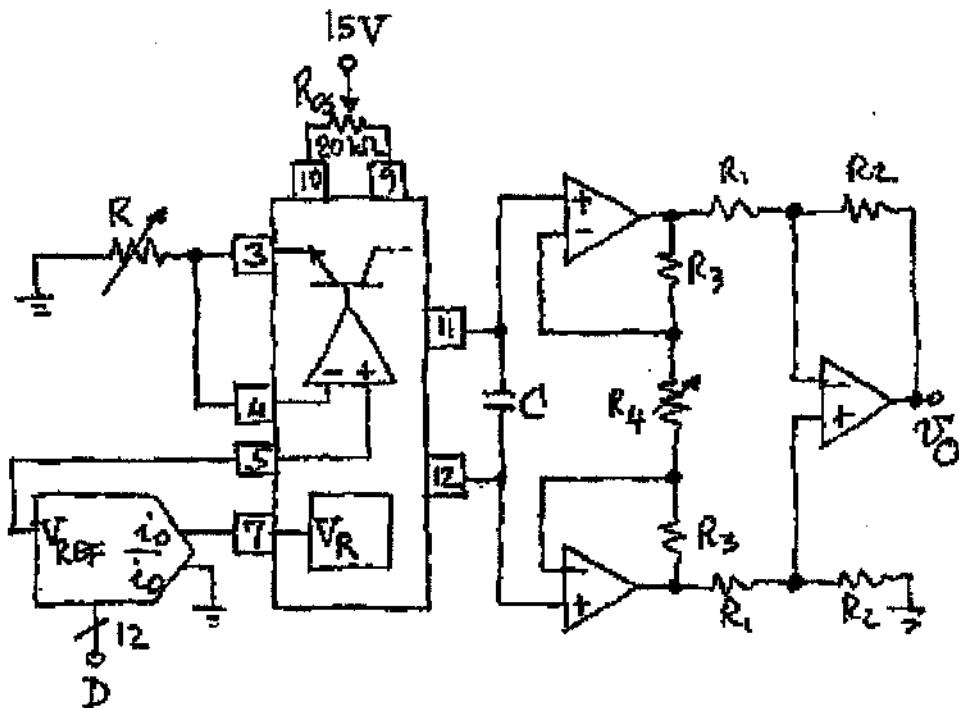

amplify the triangular wave across  $C$  with an IA having gain  $A = 10/(5/3) = 6 \text{ V/V}$ . Use  $R_1 = 10.0 \text{ k}\Omega$ ,  $R_2 = 20.0 \text{ k}\Omega$ ,  $R_3 = 20.0 \text{ k}\Omega$ ,  $R_4 = 15.0 \text{ k}\Omega$  in series with a  $10\text{-k}\Omega$  pot connected as a variable resistance. To calibrate, set  $D = 0\dots 0$  and adjust  $R_{03}$  so that the circuit is barely oscillating. Set  $D = 1\dots 1$  and adjust  $R$  for  $f_0 = 40,950 \text{ Hz}$ . With  $D = 10\dots 0$ , adjust  $R_4$  for a peak-to-peak amplitude of  $10 \text{ V}$  at the output. Implement the IA with JFET-input opamps.

12.13

12.14

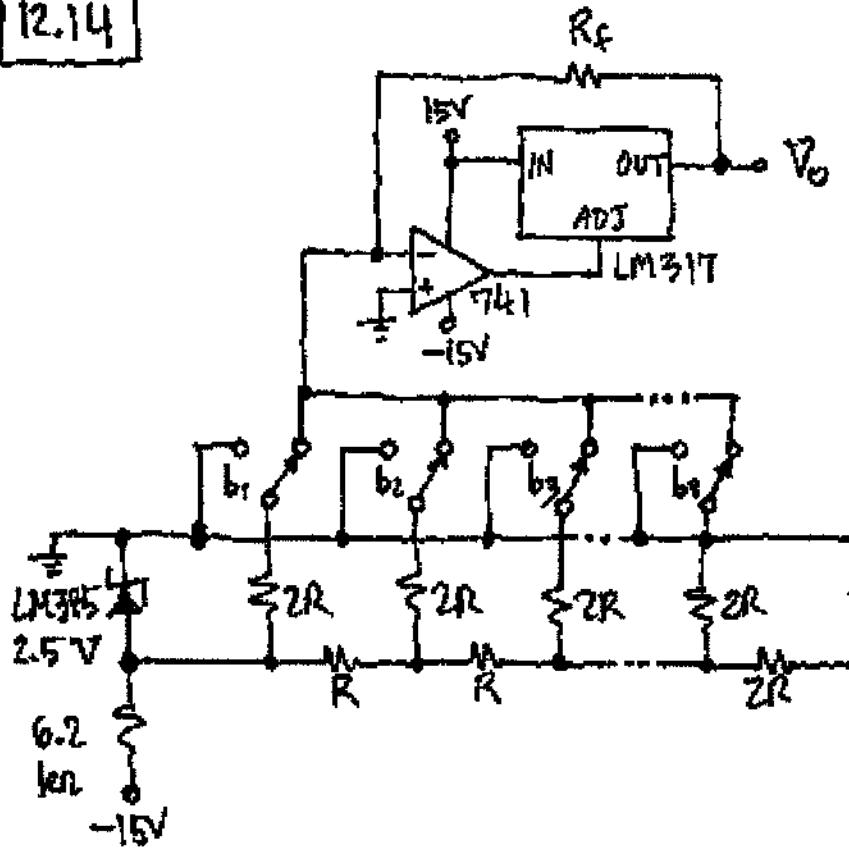

Use the LM 311 to boost the output current capability of the op amp. Assume  $R = 10\text{ k}\Omega$ , and use a  $6.2\text{ k}\Omega$  resistor to bias the reference diode and ladder. To find  $R_f$ , impose

$$I_2 = -\frac{R_f}{R} (1 - 2^{-8}) (-2.5)$$

This gives  $R_f = 48.19\text{ k}\Omega$  (use  $48.7\text{ k}\Omega$ ).

12.14

**12.15** (a) Let  $V_I(t) = (V_{FSR}/2) \sin 2\pi f t$ . Then,  $|dV_I/dt|_{max} = 2\pi f V_{FSR}/2 = \pi f V_{FSR}$ . Impairing  $|dV_I/dt|_{max} \leq (1 \text{ LSB})/t_{SAC}$  gives  $\pi f V_{FSR} \leq V_{FSR}/2^{n-1} t_{SAC}$ , or  $f_{max} = 1/2^n \pi t_{SAC}$ .

(b)  $t_{SAC} = 1/10^6 = 1 \mu\text{s}$ ;  $f_{max} = 1/(2^8 \times \pi \times 10^{-6}) = 1.243 \text{ kHz}$ . With an ideal S/H preceding the ADC, we have; by the sampling theorem,  $f_{max} = (1/2)10^6 = 500 \text{ kHz}$ .

**12.16** Require an accuracy of  $\pm 1/2 \text{ LSB}$ , or  $\pm V_{FSR}/2^{8+1} = \pm 10/2^9 = \pm 19.5 \text{ mV}$ . Thus, the reference must be  $10.00 \text{ V} \pm 19.5 \text{ mV}$ , and its temperature coefficient must be less than  $(19.5 \text{ mV})/(50^\circ) = 390 \mu\text{V}/^\circ\text{C} = 39 \text{ ppm}/^\circ\text{C}$ .

The comparator's hysteresis must be less than  $19.5 \text{ mV}$ , and its gain must be greater than  $(V_{ref} - V_{OL})/(1/2 \text{ LSB}) = 5/(19.5 \times 10^{-3}) = 256 \text{ V/V}$ .

Allowing 1 clock cycle/bit plus an additional clock cycle for overhead operations (initialization and I/O commands), we have  $T_{cycle} = (1 \mu\text{s})/9 = 111 \text{ ns}$ . The combined settling time of the DAC and comparator, plus the delays of the digital control cir-

12.15

entry must thus be less than 11 ns.

[12.17]  $C_t = C + C/2 + C/4 + C/8 + C/8 = 2C = 16 \text{ pF}; C_p = 4 \text{ pF}.$

(1) Sample cycle:  $V_p = 0$ ;  $C_p$  is discharged, while all remaining capacitances are pre-charged to  $V_I = 1.00 \text{ V}$ .

(2) Hold cycle:  $SW_1$  through  $SW_4$  are connected to ground;  $C_t$  and  $C_p$  form a voltage divider to give

$$V_p = \frac{C_t}{C_t + C_p} (-V_I) = -\frac{16}{16+4} 1 = -0.800 \text{ V}.$$

(3) 1<sup>st</sup> bit cycle:  $SW_1$  is connected to  $V_{REF}$  to give

$$V_p = -0.800 + \frac{8}{20} 3 = +0.4 \text{ V}$$

Since  $V_p > 0$ ,  $SW_1$  is flipped back to ground, returning  $V_p$  back to  $-0.800$ ;  $b_1 = 0$ .

(4) 2<sup>d</sup> bit cycle:  $SW_2$  is connected to  $V_{REF}$ ,

$$V_p = -0.800 + \frac{4}{20} 3 = -0.200 \text{ V}$$

Since  $V_p < 0$ , leave  $SW_2$  as is;  $b_2 = 1$ .

(5) 3<sup>d</sup> bit cycle:  $SW_3$  is connected to  $V_{REF}$ ,

$$V_p = -0.200 + \frac{2}{20} 3 = +0.1$$

flip  $SW_3$  back to ground;  $b_3 = 0$ .

(6) 4<sup>th</sup> bit cycle:  $SW_4$  is connected to  $V_{REF}$ ,

12.16

$$V_p = -0.200 + \frac{1}{20} \cdot 3 = -0.05 \text{ V} \Rightarrow b_4 = 1.$$

Final result is  $b_1 b_2 b_3 b_4 = 0101$ , which ideally corresponds to  $DV_{FSR} = (0/2 + 1/4 + 0/8 + 1/16) \cdot 3 = 0.9375$  V; the quantization error is  $0.9375 - 1.00 = -0.0625$ . Since  $1 \text{ LSB} = 3/2^4 = 0.1875$  V, this represents an error of  $-1/3$  LSB, i.e. within  $\pm 1/2$  LSB, as expected.

**12.18** (a) We have  $1 \text{ LSB} = 2.560 / 2^8 = 10 \text{ mV}$ . The coarse flash ADC consists of 16 equal-valued resistors to establish 15 reference levels for the corresponding 15 comparators at  $kV_{FSR}/2^4 = k \cdot 0.16 \text{ V}$ ,  $k=1, 2, \dots, 15$ . These levels are thus 0.16 V, 0.32 V, 0.48 V, ... 2.24 V, 2.40 V. Each level must be accurate within  $\pm 1/2 \text{ LSB} = \pm 5 \text{ mV}$ .

The fine flash ADC consists of 15 comparators with levels at 0.08 V, 0.24 V, 0.40 V, 0.56 V, ... 2.00 V, 2.16 V, and 2.32 V; each level must be accurate within  $\pm 1/2 (2.56/24) = \pm 80 \text{ mV}$ . Total # of comparators: 30.

(b)  $V_I = 0.5 \text{ V}$  falls within the 3<sup>rd</sup> and 4<sup>th</sup> level (0.48 V and 0.64 V) of the coarse DAC, so  $b_1 b_2 b_3 b_4 = 0011$ ;  $V_{RES} = 0.5 - 0.48 = 0.02 \text{ V}$ ;  $2^4 V_{RES} = 0.32 \text{ V}$ , which

12.19

falls between the 2<sup>d</sup> and 3<sup>d</sup> level of the fine DAC; so,  $b_5b_6b_7b_8 = 0010$ . The code 00110010 corresponds, ideally, to  $D \times V_{FSR} = (1/8 + 1/16 + 1/28) \times 2.560 = 0.500$  V, indicating zero quantization error.

$V_I = 1.054$  V falls between the 6th and 7th of the coarse DAC. So,  $b_1b_2b_3b_4 = 0110$ ;  $V_{RES} = 1.054 - 6 \times 0.16 = 0.094$  V;  $2^4 V_{RES} = 1.504$ , which falls between the 9th and 10th level of the fine DAC. So,  $b_5b_6b_7b_8 = 1001$ .  $D \times V_{FSR} = (1/4 + 1/8 + 1/32 + 1/256) \times 2.560 = 1.050$  V; the quantization error is  $-4\text{mV}$ , or  $-0.4$  LSB.

$V_I = 2.543$  V  $\Rightarrow b_1b_2b_3b_4 = 1111$ ;  $V_{RES} = 0.143$  V;  $2^4 V_{RES} = 2.288$  V  $\Rightarrow b_5b_6b_7b_8 = 1110$ ; quantization error =  $3\text{mV}$ , or  $\frac{1}{3}$  LSB

12.19


Let  $v_i = V_m \cos(\omega t + \theta)$ , and  $T = 2^m T_{ck}$ . Define  $V_i(\omega) \triangleq \frac{1}{RC} \int_0^T v_i(t) dt$ . Then

$$V_i(\omega) = \frac{1}{RC} \int_0^T V_m \cos(\omega t + \theta) dt = \frac{V_m}{\omega RC} [\sin(\omega T + \theta) - \sin \theta]. \text{ For } \theta = 0, \text{ this reduces to } V_i(\omega) =$$

12.18

$\frac{V_m T}{RC} \frac{\sin wT}{wT} = \frac{V_m T}{RC} \text{Sa}(wT)$ . The plot of  $|\text{Sa}(wT)|_{\text{dB}}$  versus  $wT$  rolls off at a rate of  $-20 \text{ dB/dec}$  and has zeros at  $\pi, 2\pi, 3\pi, 4\pi, \dots$

$|\text{Sa}(wT)|_{\text{dB}}$

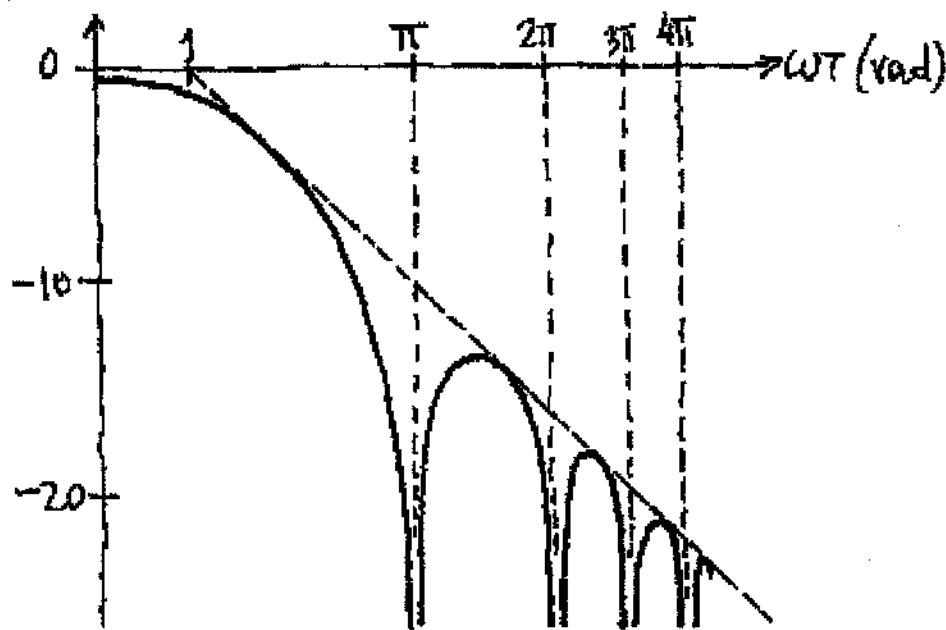

On the other hand, if we let  $\theta = -90^\circ$ , so that  $V_i(t) = V_m \sin w t$ , then we obtain  $V_i(w) = \frac{V_m T}{RC} \frac{1 - \cos wT}{wT}$ , which again rolls off at a rate of  $-20 \text{ dB/dec}$ , but with zeros at  $0, 2\pi, 4\pi, 6\pi, \dots$ . The zeros of  $\text{Sa}(wT)$  at the odd multiples of  $\pi$  are due to the even-symmetry of the  $\cos$  function. In the most general case of arbitrary symmetry of  $V_i$ , we consider only the zeros at even multiples of  $\pi$ , or  $wT = 2\pi, 4\pi, 6\pi, \dots$ , i.e.  $f = 1/T, 2/T, 3/T, \dots$

12.19

12.20

$$(a) V_0(0) = 0; V_0(\infty) = -\alpha V_E = -10^3 \text{ V};$$

$$R = R_{eq} C = (1+\alpha)RC \approx 10^3 RC;$$

$$V_0(t) = V_0(\infty) + [V_0(0) - V_0(\infty)] e^{-t/(RC)}, \text{ or}$$

$$V_0(t) \approx 10^3 [e^{-t/(10^3 RC)} - 1] \text{ V.}$$

$$(b) \text{ Ideally, } V_0(t) = V_0(0) - \frac{1}{RC} \int_0^t V_E dt,$$

$$\text{or } V_0(\text{ideal})(t) = -\frac{1}{RC} t. \text{ Impose}$$

$$V_0(100 \text{ ms}) - V_0(\text{ideal})(100 \text{ ms}) \leq 1 \text{ mV}, \text{ or}$$

$$10^3 [e^{-0.1/(10^3 RC)} - 1] + \frac{0.1}{RC} \leq 10^{-3}. \text{ Expanding,}$$

$$10^3 [1 - \frac{1}{10^4 RC} + \frac{1}{2} \left( \frac{1}{10^4 RC} \right)^2 + \dots - 1] + \frac{1}{10^4 RC} \leq 10^{-3},$$

$$\text{or } \frac{10^3}{2} \left( \frac{1}{10^4 RC} \right)^2 \leq 10^{-3}, \text{ or } RC \geq \frac{1}{14.14 \text{ s}}.$$

$$\text{We also have } V_0(\text{ideal})(100 \text{ ms}) = \frac{-1}{14.14} \times 0.1 = -0.141 \text{ V.}$$

12.21

$$(a) f_{ck} = 60 \times 2^{14} = 983.040 \text{ kHz}; T = 2 \times 2^{14} \text{ cycles, or } T = 2^{15} / f_{ck} = 33.3 \text{ ms.}$$

$$(b) 5 / (2^{14} T_{ck}) = 2.5 / RC \Rightarrow RC = 8.3 \text{ ms.}$$

$$(c) T_{new} = R (1+0.05) C (1-0.02) = 1.029 RC = 1.029 T_{old}. \text{ The new value of } \Delta V_2 \text{ is thus } \Delta V_2 = 5 / 1.029 = 4.859 \text{ V, and accuracy is unaffected.}$$

12.20


12.22 (a) 1<sup>st</sup> Order Σ-Δ:

$$|e_{q,1}| = 2 \left( \sin \frac{\pi f}{kfs} \right) |e_{q,2}| \approx 2 \frac{\pi f}{kfs} \frac{q}{(kfs/2)^{1/2}} = \frac{2\sqrt{2}\pi q}{(kfs)^{1/2}} f.$$

2<sup>nd</sup> Order Σ-Δ:

$$|e_{q,1}| = \left( 2 \sin \frac{\pi f}{kfs} \right)^2 |e_{q,2}| \approx 4 \left( \frac{\pi f}{kfs} \right)^2 \frac{q}{(kfs/2)^{1/2}} = \frac{4\sqrt{2}\pi^2 q}{(kfs)^{1/2}} f^2.$$

These curves can be plotted using Pspice.

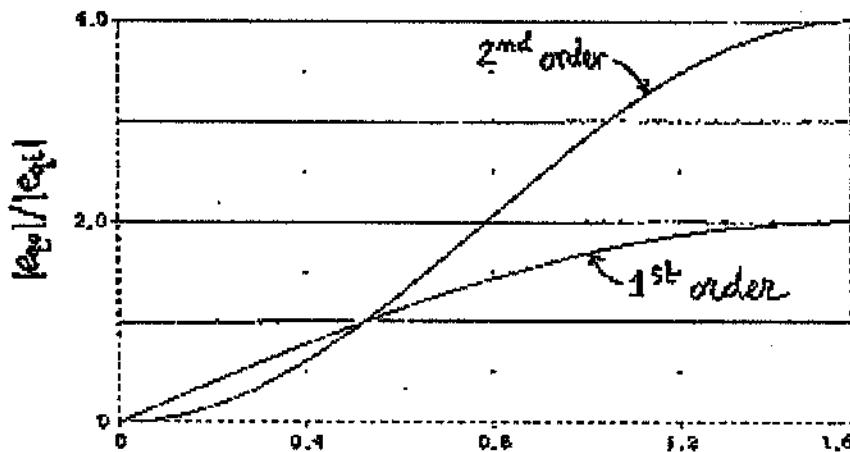(b) 1<sup>st</sup> order Σ-Δ before filtering:

$$\begin{aligned} E_q^2 &= \int_0^{kfs/2} |e_{q,1}|^2 df = \int_0^{kfs/2} 2^2 \sin^2 \left( \frac{\pi f}{kfs} \right) \times \frac{q^2}{kfs/2} df \\ &= \frac{(2q)^2}{kfs/2} \int_0^{kfs/2} \sin^2(\alpha f) df, \quad \alpha = \pi/kfs. \end{aligned}$$

Using

the integral tables,

$$E_q = \frac{2q}{(kfs/2)^{1/2}} \left[ \frac{kfs/2}{2} - 0 \right]^{1/2} = \sqrt{2} q, \text{ indicating}$$

that noise shaping increases the total noise at the quantizer's output by  $\sqrt{2}$ , or 3 dB.

(12.21)

2nd order  $\Sigma-\Delta$  before filtering:

$$E_q^2 = \int_0^{kfs/2} 4^2 \sin^4\left(\frac{\pi f}{kfs}\right) \times \frac{q^2}{kfs/2} df = 8q^2, \text{ or}$$

$E_q = \sqrt{8} q$ , indicating that noise shaping now increases the total output noise by  $\sqrt{8}$ , or 9dB.

(c) 1st order  $\Sigma-\Delta$  after filter/decimator:

$$E_t^2 \approx \frac{8\pi^2 q^2}{(kfs)^3} \int_0^{fs/2} f^2 df = \frac{8\pi^2 q^2}{(kfs)^3} \frac{1}{3} \left(\frac{f_s}{2}\right)^3, \text{ or}$$

$$E_t = (\pi q / \sqrt{3}) / k^{3/2}.$$

2nd order  $\Sigma-\Delta$  after filter/decimator:

$$E_t^2 \approx \frac{32\pi^4 q^2}{(kfs)^5} \int_0^{fs/2} f^4 df, \text{ or } E_t = \frac{\pi^2 q}{\sqrt{6}} \frac{1}{k^{5/2}}.$$

(d) 1st order:

$$100 \frac{\sqrt{2} q - \pi q / (3k^3)^{1/2}}{\sqrt{2} q} = 100 \left(1 - \frac{\pi}{(6k^3)^{1/2}}\right)$$

For  $k=16$ , this is 97.996%, indicating that only 2% of noise is left.

2nd order:

$$100 \frac{\sqrt{8} q - \pi^2 q / (5k^5)^{1/2}}{\sqrt{8} q} = 100 \left(1 - \frac{\pi^2}{(40k^5)^{1/2}}\right)$$

For  $k=16$  this is 99.8476%, indicating that only 0.152% of noise is left.

12.22

12.23

(a) By Eq. (12.21), the required SNR for a 16-bit ADC is  $\text{SNR} = 6.02 \times 16 + 1.76 = 98.08 \text{ dB}$ . With a 1-bit quantizer ( $n=1$ ), Eq. (12.25) indicates that we need  $98.08 = 6.02(1+0.5m) + 1.76$ , or  $m = 30$ . Thus,  $f_s = 2^{30} \times 44.1 \text{ kHz} = 47.352 \text{ GHz}$ !

(b) By Eq. (12.31),  $98.08 = 6.02 \times (1+1.5m) - 3.41$ , or  $m = 10.57$ , so now  $f_s = 2^{10.57} \times 44.1 \text{ kHz} = 67.16 \text{ MHz}$ .

(c) Eq. (12.33) finds  $m = 6.857$ , so  $f_s = 2^{6.857} \times 44.1 \text{ kHz} = 5.113 \text{ MHz}$ .

12.24

(a) Since doubling the oversampling rate improves accuracy by 0.5 bits, for a 4-bit improvement we need  $k = 2^{4/0.5} = 256$ . So,  $f_s = 2 \times 10^5 \times 256 = 51.2 \text{ MHz}$ .

(b) For a 4-bit improvement, using a 1st-order  $\Sigma-\Delta$  we need, by Eqs (12.21) and (12.31),  $6.02 \times 12 + 1.76 = 6.02 \times 8 + 6.02 \times 1.5m - 3.41$ , or  $m = 3.239$ , or  $k = 2^m = 9.44$ .  $f_s = 2 \times 10^5 \times 9.44 = 1.888 \text{ MHz}$ .

(c) By Eq. (12.33),  $74 = 6.02 \times 8 + 6.02 \times 2.5m - 11.4$ , or  $m = 2.549$ , or  $k = 2^m = 5.49$ .  $f_s = 2 \times 10^5 \times 5.49 = 1.09825 \text{ MHz}$ .

12.23

12.25 (a) Imposing

$$20 \log_{10} \frac{1}{\sqrt{1 + [20 \times 10^3 \times 2\pi RC]^2}} = -0.1 \text{ dB}$$

gives  $RC = 1.21 \times 10^{-6}$ . To allow for component tolerances, impose  $RC = 1 \mu\text{s}$ ; use  $R = 1 \text{k}\Omega$ ,  $C = 1 \text{nF}$ .

$$(b) 1/2 \text{ LSB} = (2 \text{ V})/2^{17} = 15.26 \text{ }\mu\text{V.}$$

The first image band is  $kfs \pm 20 \text{ kHz}$ , or  $3.052 \text{ MHz} \leq f \leq 3.092 \text{ MHz}$ . The attenuation of the RC filter over this band is approximately  $\sqrt{1 + (3.072 \times 10^6 \times 2\pi \times 10^{-6})^2} = 0.0517$ , or 25.7 dB. The rms noise of the first band is  $E_n = e_{\text{mw}} \sqrt{(3.092 - 3.052) \times 10^6} = 200 e_{\text{mw}}$ . Imposing  $0.0517 \times 200 e_{\text{mw}} \leq 15.26 \mu\text{V}$  gives  $e_{\text{mw}} \leq 1.48 \mu\text{V}/\sqrt{\text{Hz}}$ .