

13.1

13.1 $1/\beta_{00} = 1 + 20/100 = 1.2 \text{ V/V} = 1.584 \text{ dB}$, regardless of v_I .

$v_I = 10 \text{ V}$: $r_e = 26 \Omega$, $r_o = 100 \text{ k}\Omega$, $R_1 = (10 \text{ k}\Omega) \parallel (100 \text{ k}\Omega) \parallel (2 \text{ M}\Omega) = 9.05 \text{ k}\Omega$, $R_2 = 26 + 4.3 \text{ k}\Omega = 4.33 \text{ k}\Omega$; $1/\beta_0 = R_2/R_1 = 0.478 \text{ V/V} = -6.40 \text{ dB}$; $f_z = 1/(2\pi \times 9.05 \times 10^{-3} \times 120 \times 10^{-12}) = 147 \text{ kHz}$; $f_p = 367 \text{ kHz}$.

$v_I = 10 \text{ mV}$: $r_e = 26 \text{ k}\Omega$, $r_o = 100 \text{ M}\Omega$, $R_1 \approx 10 \text{ k}\Omega$, $R_2 = 30.3 \text{ k}\Omega$; $1/\beta_0 = 9.7 \text{ dB}$; $f_z = 133 \text{ kHz}$; $f_p = 52.5 \text{ kHz}$.

$v_I = 1 \text{ mV}$: $r_e = 260 \text{ k}\Omega$, $R_2 = 264.3 \text{ k}\Omega$; $1/\beta_0 = 28.4 \text{ dB}$; $f_z = 133 \text{ kHz}$; $f_p = 6.0 \text{ kHz}$.

13.2 Worst case is $v_I = 10 \text{ V}$, when $R_1 = 9.05 \text{ k}\Omega$, $R_2 = 4.33 \text{ k}\Omega$, $f_z = 147 \text{ kHz}$, $f_p = 367 \text{ kHz}$;

$$T = a\beta \approx \frac{10^6}{jf} \frac{9.05}{4.33} \frac{1 + jf/367 \times 10^3}{1 + jf/147 \times 10^3}$$

Using trial and error we find that $|T| = 1$ for $f = f_x = 893 \text{ kHz}$, where $\angle T = -103^\circ$.

Thus, $\phi_m = -103 + 180 = 77^\circ$.

13.3 $-2.303(1 + R_2/R_1)0.026 = -2 \Rightarrow R_2 = 32.4 R_1$. Use $R_1 = 1 \text{ k}\Omega$ Q81 type, $R_2 = 32.4 \text{ k}\Omega$, 1%. For optimum logging range,

13.2

leave $R = 10.0 \text{ k}\Omega$. Then,

$$\frac{i_I}{I_C} = \frac{V_E/R}{V_{REF}/R_x} = \frac{V_E}{1V} \Rightarrow \frac{R}{R_x} V_{REF} = 1V \Rightarrow$$

$$R_x = R V_{REF}/(1V) = 10^4 \times 6.95 = 69.8 \text{ k}\Omega, 1\%.$$

All remaining components remain the same.

13.4 (a) $i_{C1}/i_{C2} = (I_{S1}/I_{S2}) e^{v_{B1}/V_T}$. Using $e^x = 10^{x/2.303}$ and letting $i_{C2} = i_o$, we get $i_o = I_o \times 10^{v_E/V_i}$, where

$$I_o = \frac{I_{S2}}{I_{S1}} i_{C1} = \frac{I_{S2}}{I_{S1}} \frac{V_{REF}}{R_x}, \text{ and}$$

$$V_i = -2.303 \frac{R_1 + R_2}{R_1} V_T.$$

(b) $I_o = 10 \mu\text{A} \Rightarrow R_x = 6.95/0.01 = 698 \text{ k}\Omega$, 1%. Using $10^x = 2^{3.322x}$ and imposing

$$-1V = -\frac{2.303}{3.322} \left(1 + \frac{R_2}{R_1}\right) 26 \text{ mV} \text{ gives } R_2 =$$

$54.49 R_1$. Use $R_1 = 1 \text{ k}\Omega$ Q81 type, and $R_2 = 54.6 \text{ k}\Omega$, 1%.

(c) Assuming the $-15V$ supply is well regulated and clean, connect a resistor R_3 between the base of Q_1 and $-15V$ to down-shift v_{B1} . In part (a) v_{B1} varied over the range $-90.11 \text{ mV} \leq v_{B1} \leq +90.11 \text{ mV}$. To ensure the same range of variability, we now need, for $v_E = 0$,

13.3

$$\frac{0 - (-0.09011)}{R_2} + \frac{0 - (-0.09011)}{R_1} = \frac{-0.09011 - (-15)}{R_3}$$

and, for $v_I = +10\text{ V}$,


$$\frac{10 - 0.09011}{R_2} = \frac{0.09011}{R_1} + \frac{0.09011 + 15}{R_3}$$

Letting $R_1 = 1\text{ k}\Omega$ Q81 type and solving, we get $R_2 = 54.15\text{ k}\Omega$ (use $53.6\text{ k}\Omega$, 1%), and $R_3 = 162.46\text{ k}\Omega$ (use $162\text{ k}\Omega$, 1%).

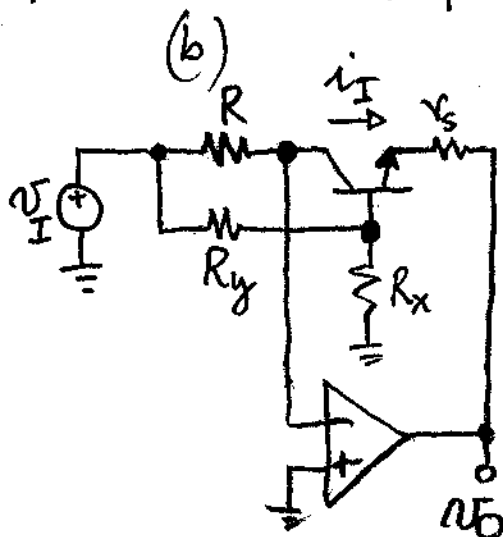13.5 (a) By Eq. (13.5) and KVL,

$$v_O = -v_{BE} - v_{v_s} = -V_T \ln \frac{v_I}{R I_s} - \frac{v_s}{R} v_I, \text{ or also}$$

$v_O = -V_T \ln \frac{i_I}{I_s} - v_s i_I$. For $i_I = 1\text{ mA}$, $v_s i_I = 1\text{ mV}$; for $i_I = 0.1\text{ mA}$, $v_s i_I = 0.1\text{ mV}$. The percentage input error p is such that $v_s i_I = (26\text{ mV}) \ln(1+p)$. Substituting, we find $p(1\text{ mA}) = 3.92\%$, $p(0.1\text{ mA}) = 0.385\%$.



$$v_O = v_B - v_{BE} - v_s i_I$$

$$= \frac{R_x}{R_x + R_y} v_I - \left[V_T \times \right.$$

$$\left. \ln \frac{v_I}{R I_s} + \frac{v_s}{R} v_I \right]$$


$$\text{Imposing } \frac{R_x}{R_x + R_y} = \frac{v_s}{R},$$

$$\text{or } R_y/R_x = R/v_s - 1$$

gives $v_O = -V_T \ln(v_I/R I_s)$, regardless of v_s .

13.4

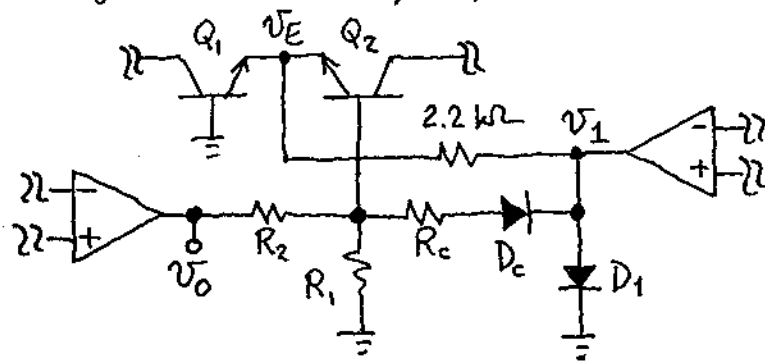13.6 The compensation network for the case of the logarithmic amplifier becomes:



The voltages across R_c and the 2.2-k Ω resistance are

$$V_{R_c} = V_{B2} - V_{D_c} - V_1$$


$$V_{2.2\text{ k}\Omega} = V_{B2} - V_{BE2} - V_1$$

As long as $V_{D_c} \cong V_{BE2}$ we have $V_{R_c} \cong V_{2.2\text{ k}\Omega}$, so $i_{R_c} = V_{R_c}/R_c \cong V_{2.2\text{ k}\Omega}/R_c = [(2.2\text{ k}\Omega)/R_c] \times (i_I + I_{REF})$. The current i_{R_c} shifts V_{B2} and, hence, V_E , by the amount $\Delta V_E = \Delta V_{B2} = -(R_1//R_2)i_{R_c} = -(R_1//R_2) \frac{2.2\text{ k}\Omega}{R_c} (i_I + I_{REF})$; the bulk resistance r_s of Q_1 causes the shift $\Delta V_E = -r_s i_I$. Imposing $-(R_1//R_2) \frac{2.2\text{ k}\Omega}{R_c} i_I = -r_s i_I$ will compensate for the error due to r_s . This requires using $R_c = (R_1//R_2)(2.2\text{ k}\Omega)/r_s$, and also recalibrating R_2 and R_r slightly.

For the circuit shown, use $R_c = (1//15.7) \times 10^3 \times 2.2 \times 10^3 / 0.5 = 4.12\text{ M}\Omega$.

13.5

13.7 (a)

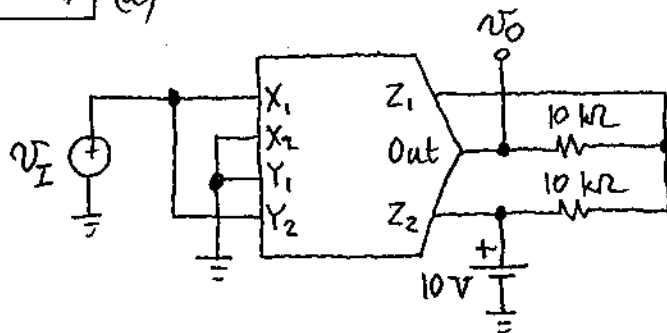


$$v_{Z_1} = \frac{1}{2}(v_O + 10\text{ V}); \quad v_{Z_2} = 10\text{ V}; \quad v_{Z_1} - v_{Z_2} = \frac{1}{2}v_O - 5\text{ V}.$$

By Eq. (13.21) with $k = 1/10$,

$$\frac{1}{2}v_O - 5 = \frac{1}{10}(10 \cos \omega t - 0)(0 - 10 \cos \omega t) = -10 \cos^2 \omega t$$

$$\Rightarrow v_O = 10 - 20 \frac{1 + \cos 2\omega t}{2} = 10 \cos 2\omega t \text{ V}.$$

(b) Connect as follows:

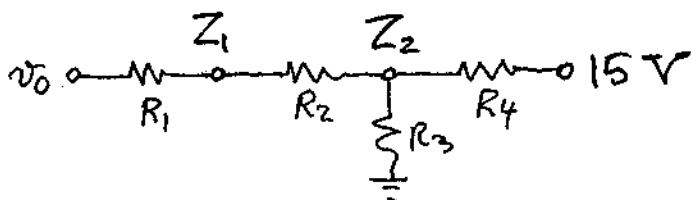


We want $v_{Z_1} - v_{Z_2} = \frac{1}{2}v_O - 5\text{ V}$. The Thévenin equivalent of the circuit to the right of R_2 is a source $15R_3/(R_3 + R_4)$ with a series resistance $R_3 \parallel R_4$, so

$$v_{Z_1} - v_{Z_2} = R_2 \frac{v_O - 15R_3/(R_3 + R_4)}{R_1 + R_2 + (R_3 \parallel R_4)} = \frac{1}{2}v_O - 5\text{ V}.$$

Use $R_3 = 20.0\text{ k}\Omega$, $R_4 = 10.0\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_1 = 3.32\text{ k}\Omega$, all 1%.

13.6

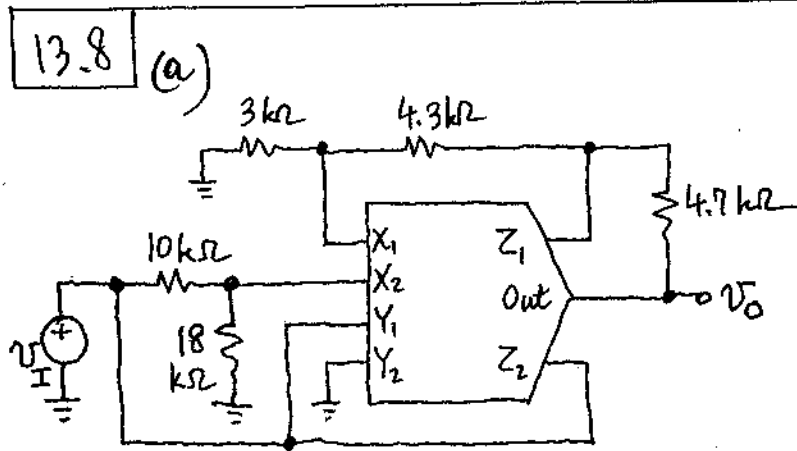

By Eq. (13.21),


$$10 \left(\frac{7.3}{12} V_O - V_I \right) = \left(\frac{3}{12} V_O - \frac{18}{28} V_I \right) \times (V_I - V_O), \text{ or}$$

$$V_O = \frac{840 V_I - 54 V_I^2}{511 - 21 V_I} \approx 10 \sin \left(\frac{V_I}{10} 90^\circ \right) = 10 \sin 9 V_I.$$


V_I (V)	V_I ($^\circ$)	V_O (actual)	V_O (ideal)	% error
10	90	9.967	10	-0.330
5	45	7.020	7.071	-0.725
0	0	0	0	0
10/3	30	4.989	5	-0.227
20/3	60	8.625	8.660	-0.400
5/3	15	2.626	2.588	+1.470
25/3	75	9.673	9.659	+0.141

(b) As shown in the accompanying diagram, we use an absolute-value circuit to map the ± 5 V range of V_{TR} to the range of 0 to 10 V needed by the sine converter, and then we use a programmable amplifier with a gain of $+0.5$ V/V when $V_I > 0$, and a gain of -0.5 V/V when $V_I < 0$.


13.9

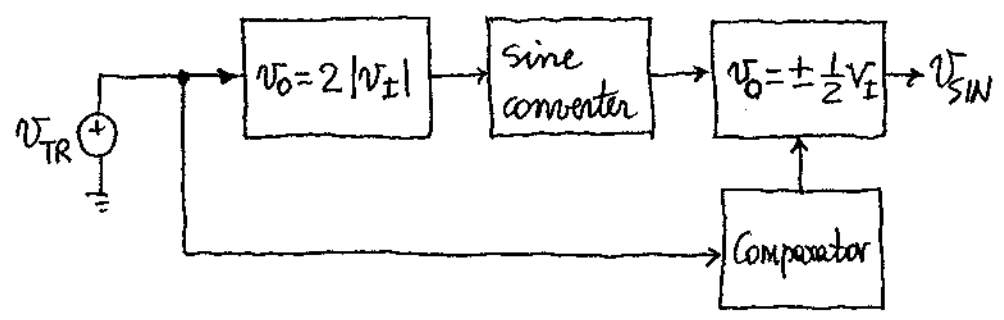

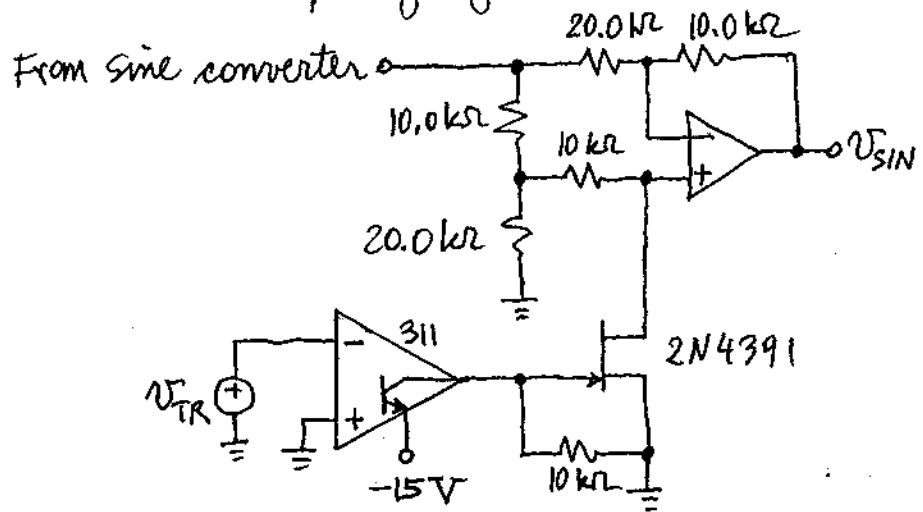For the absolute-value circuit use Fig. (9.30) with $R_1 = R_2 = 2R_3 = R_4 = R_5/2 = 10.0 \text{ k}\Omega$. For the sine converter use part (a) above. For the polarity detector and programmable gain amplifier use the accompanying circuit.



13.9

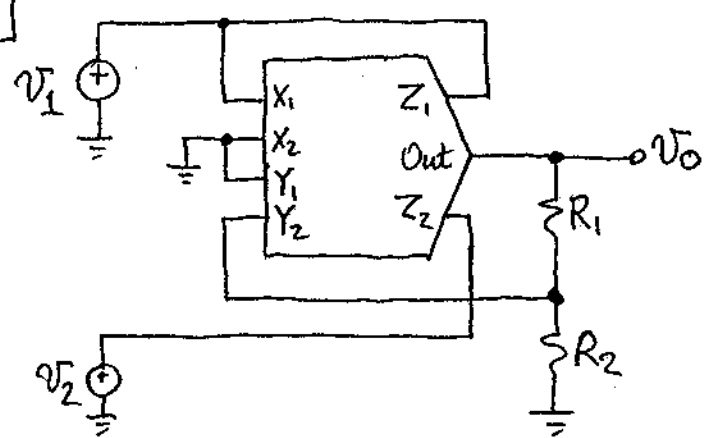


$$V_1 - V_2 = \frac{1}{10} (V_1 - 0) \times \left(0 - \frac{R_2}{R_1 + R_2} V_0 \right) \Rightarrow V_0 = \left(1 + \frac{R_1}{R_2} \right) 10 \frac{V_2 - V_1}{V_1}$$

Use $R_1 = 18 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$.

13.8

13.10 $v_{x_1} = v_{z_2} = 10 - R20/[R+R(1+\delta)] = 10\delta/(2+\delta)$, indicating a nonlinear dependence on δ , as we know. Now, since $v_{x_2} = v_{y_2} = 0$ and $v_{y_1} = v_{z_1} = v_0$, Eq. (13.21) gives: $v_0 - v_{x_1} = (1/10)(v_{x_1} - 0)(v_0 - 0)$, that is, $v_0 = 10x_1/(10 - v_{x_1})$. Substituting the above expression for v_{x_1} yields $v_0 = 5\delta$, a linear dependence on δ .

13.11

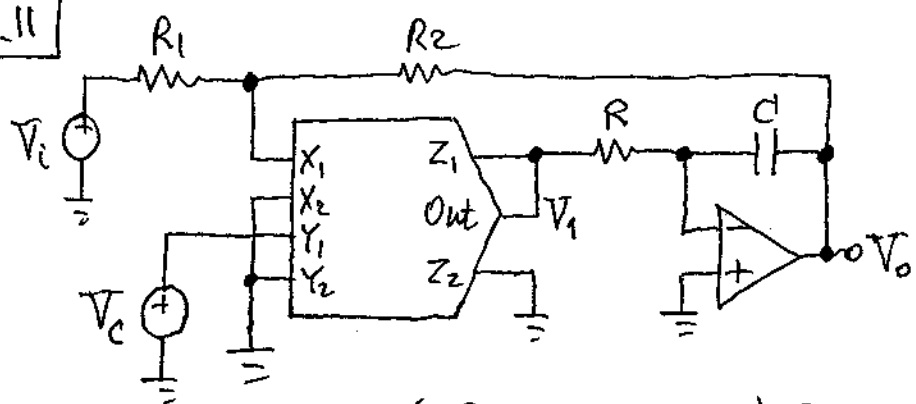

$$V_0 = -[1/(sRC)]V_1, \quad V_1 = \left(\frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_0 \right) \frac{V_c}{10}$$

$$H = \frac{V_0}{V_i} = -\frac{R_2}{R_1} \frac{1}{1 + jf/f_0}, \quad f_0 = \frac{V_c}{2\pi(1 + R_2/R_1)10RC}$$

For a dc gain of 20 dB use $R_1 = 10\text{ k}\Omega$, $R_2 = 100\text{ k}\Omega$.

$$V_c = 10\text{ V} \Rightarrow f_0 = 10 \times 100 = 1\text{ kHz} = \frac{10}{2\pi \times 11 \times 10^3 RC}$$

Use $C = 1\text{ }\mu\text{F}$, $R = 14.3\text{ k}\Omega$.

13.12

Let V_1 be the output of g_{m1} , and let I_1 and I_2 be the outputs of g_{m1} and g_{m2} . We then have

13.9

$$V_o = V_i + \frac{1}{sC_1} I_2 = V_i + \frac{g_{m2}}{sC_1} (V_i - V_o)$$


$$V_i = \frac{1}{sC_2} I_1 = \frac{g_{m1}}{sC_2} (V_i - V_o). \text{ Eliminating } V_i,$$

$$\left(1 + s^2 \frac{C_1 C_2}{g_{m1} g_{m2}}\right) V_i = \left(s^2 \frac{C_1 C_2}{g_{m1} g_{m2}} + s \frac{C_2}{g_{m1}} + 1\right) V_o$$

$$\frac{V_o}{V_i} = \frac{1 - (\omega/\omega_0)^2}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)Q}, \quad \omega_0 = \sqrt{C_1 C_2 / g_{m1} g_{m2}}$$

$$Q = \sqrt{(C_1/C_2)(g_{m1}/g_{m2})}. \text{ Notch response.}$$

13.13

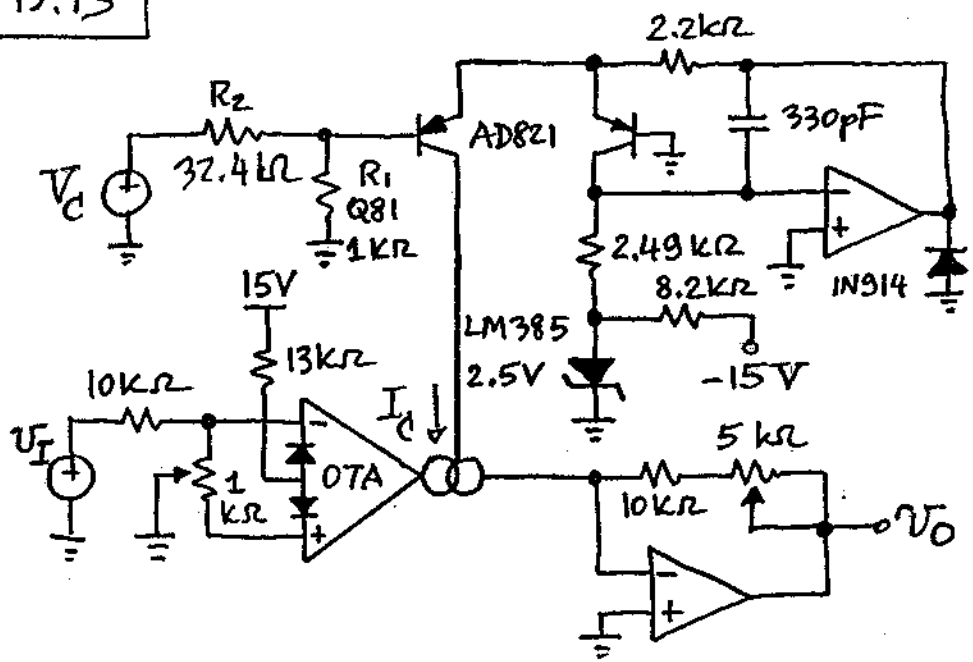


For a sensitivity of 1 oct/V we need $2.303(1 + R_2/R_1)0.026 = 2$, that is, $R_2 = 32.4R_1$. Use $R_1 = 1\text{ k}\Omega$ Q81 type, and $R_2 = 32.4\text{ k}\Omega$, 1%. To calibrate, set $v_I = 0$, $V_C = 0$, and adjust the 1-k Ω pot for $v_o = 0$. Then, set v_I to a 1-kHz, 5-V amplitude sine wave, and adjust the 5-k Ω pot so that v_o has a 5-V amplitude.

13.10

13.14 Use the circuit of Fig. 13.19 with the exponential V-I converter of Fig. 13.17. For a sensitivity of 1 octave/volt, use $R_2 = 32.4 \text{ k}\Omega$, 1% in Fig. 13.17. Since for $V_C = 0$ the V-I converter gives $I_C = 1 \text{ mA}$, which is then split in half by the AD821 pair of Fig. 13.19, we must have, by Eq. (13.30), $20 \text{ kHz} = 0.5 \text{ mA} / (2 \times \pi \times 12.2 \text{ C})$ or $C = 326 \text{ pF}$. Use two 330-pF capacitors, and make the 2.49-k Ω resistor of Fig. 13.17 adjustable until $f_0 = 20 \text{ kHz}$ with $V_C = 0$.

13.15

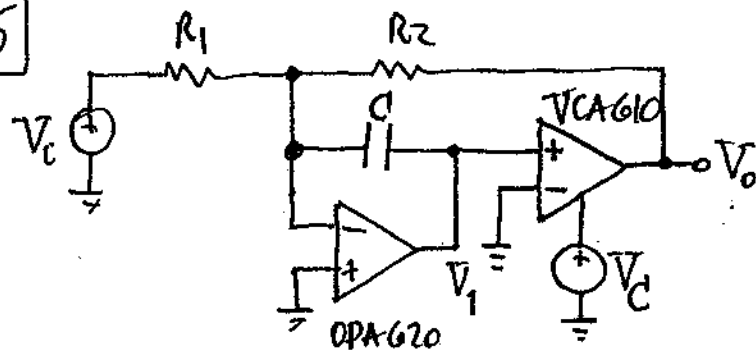

$$V_1 = -\frac{1}{sR_1C} V_i - \frac{1}{sR_2C} V_0; \quad V_0 = 0.01 \times 10^{-2} V_C \times V_1.$$


Substituting,

$$\frac{V_0}{V_C} = -\frac{R_2}{R_1} \frac{1}{1 + jfA_0}, \quad f_0 = \frac{10^{-2} V_C}{200\pi R_2 C}.$$

Unity dc gain $\Rightarrow R_1 = R_2$. For $V_C = -2 \text{ V}$ we want $f_0 = 1 \text{ MHz}$, or $10^6 = 10^4 / (200\pi R_2 C)$. Let $C = 10 \text{ nF}$. Then $R_1 = R_2 = 1.58 \text{ k}\Omega$, 1%.

13.11

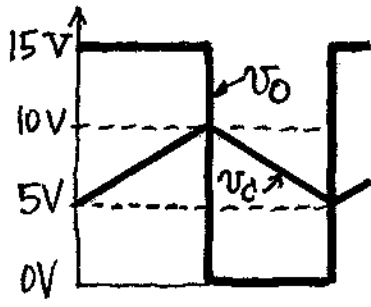13.16 (a) $v_o = 5\text{ V} \Rightarrow$ DISCH pin floating \Rightarrow



OTA inputs are $v_p = 2.5\text{ V}$ and $v_n = 1.36\text{ V} \Rightarrow$ OTA's input stage saturates such that OTA sources

the control current I_c to the capacitor.

$v_o = 0\text{ V} \Rightarrow$ DISCH pin shorted to ground $\Rightarrow v_p \approx 0\text{ V}$ and $v_n = 1.36\text{ V} \Rightarrow$ OTA now sinks I_c from capacitor. Thus, v_c is a triangular wave alternating between $1/3 V_{cc}$ and $2/3 V_{cc}$.

$CAV = I\Delta t \Rightarrow C(10-5) = I_c T/2 \Rightarrow f_o = 1/T = I_c/10C.$

(b) $C = I_c/10f_o = 10^{-3}/(10 \times 10^5) = 1\text{ nF}.$

Generate I_c with the exponential V-I converter of Fig. 13.17, where $R_2 = 32.4\text{ k}\Omega$ in order to achieve the desired sensitivity.

To calibrate, make the $2.49\text{ k}\Omega$ resistor in Fig. 13.17 adjustable, and set it so that $f_o = 100\text{ kHz}$ with $v_c = 0\text{ V}.$

13.12

13.17 With $F(s) = 1$ we have $v_e(s) = K_d K_a \theta_d(s) = (10^4/\pi 10^4) \theta_d(s) = \theta_d(s)/\pi$, or $\theta_d(s) = \pi v_e(s)$.

$$(a) \theta_d(t) = \pi \times 0.2 [1 - e^{-t/(100 \mu s)}] u(t) \\ = 36^\circ [1 - e^{-t/(100 \mu s)}] u(t).$$

$$(b) \theta_d(t) = 19.33^\circ \cos(2\pi 2500t - 57.52^\circ).$$

13.18 (a) With $R_2 = 0$ we get $F(s) = 1/(1 + s/\omega_p)$, $\omega_p = 1/R_1 C = 100$ rad/s. Then, $T(j\omega) = 1/[(j\omega/10^4)(1 + j\omega/100)]$. Using trial and error, we find that $|T| = 1$ for $\omega_x = 997.5$ rad/s, where $\angle T = -174.3^\circ$, so $\phi_m = 5.7^\circ$, an inadequate margin.

(b) For $\phi_m = 45^\circ$ impose $\omega_p = K_v = 10^4$ rad/s. The actual crossover frequency and phase margin are then $\omega_x = 7,860$ rad/s, and $\phi_m = 51.8^\circ$.

13.19 $R_1 C = 1/100$, $R_2 C = 1/10^3$. Let $C = 0.1 \mu\text{F}$. Then, $R_1 = 100 \text{ k}\Omega$, and $R_2 = 10 \text{ k}\Omega$. $T(j\omega) = [1 + j\omega/10^3]/[(j\omega/10^4)(j\omega/10^2)]$. $|T| = 1$ for $\omega_x = 1272$ rad/s, and $\phi_m = 51.8^\circ$.

13.13

13.20 Passive filter:

$$\begin{aligned}
 H(s) &= \frac{K_v F(s)}{s + K_v F(s)} = \frac{K_v (1 + s/w_z) / (1 + s/w_p)}{s + K_v (1 + s/w_z) / (1 + s/w_p)} \\
 &= \frac{K_v + K_v s/w_z}{s + s^2/w_p + K_v + K_v s/w_z} = \frac{1 + s/w_z}{s^2/K_v w_p + s(1/K_v + 1/w_z) + 1} \\
 &= \frac{N(s)}{(s/w_m)^2 + 2\zeta(s/w_m) + 1}, \quad \omega_m = \sqrt{K_v w_p};
 \end{aligned}$$

$$2\zeta s/w_m = s(1/K_v + 1/w_z) \Rightarrow \zeta = \frac{\omega_m}{2w_z} \left(1 + \frac{w_z}{K_v}\right);$$

$$N(s) = 1 + \frac{2\zeta s}{w_m} - \frac{s}{K_v} = 1 + \frac{s}{w_m} \left(2\zeta - \frac{\omega_m}{K_v}\right).$$


Active filter:

$$\begin{aligned}
 H(s) &= \frac{k_v (1 + s/w_z) / (s/w_p)}{s + K_v (1 + s/w_z) / (s/w_p)} = \frac{K_v + K_v s/w_z}{s^2/w_p + K_v + s k_v/w_z} \\
 &= \frac{1 + s/w_z}{s^2/K_v w_p + s/w_z + 1} = \frac{1 + 2\zeta(s/w_m)}{(s/w_p)^2 + 2\zeta(s/w_m) + 1}
 \end{aligned}$$

$$\omega_m = \sqrt{K_v w_p}, \quad \zeta = \frac{\omega_m}{2w_z}.$$

13.21 $K_v = 0.2 \times 1 \times 2\pi 10^6 = 2\pi 10^5 \text{ s}^{-1}$; $\omega_m \cong \omega_0/100 = 2\pi 10^4 \text{ rad/s}$. $R_1 C = 1/w_p = K_v/\omega_m^2 = 1/2\pi 10^3 \text{ s}$; $R_2 C = 1/w_z = 2\zeta/\omega_m = 1/Q\omega_m = 1/\pi 10^4 \text{ s}$. Let $C = 10 \text{ nF}$. Then, $R_1 = 15.8 \text{ k}\Omega$ and $R_2 = 3.16 \text{ k}\Omega$.

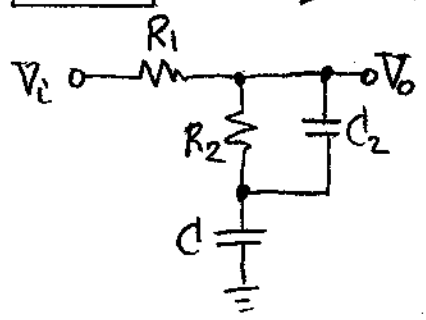13.22 Let $Z_2 = R_2 \parallel (1/sC_2) = R_2 / (1 + sR_2C_2)$. Then,



$$\begin{aligned}
 F(s) &= \frac{V_o}{V_i} = \frac{Z_2 + 1/sC}{R_1 + Z_2 + 1/sC} \\
 &= \frac{1 + sR_2(C_1 + C_2)}{s^2 R_1 R_2 C C_2 + s(R_1 C + R_2 C + R_2 C_2) + 1}
 \end{aligned}$$

13.14


Substituting $C_2 = C_1/10$, $R_2 = 1/366C$, and $R_1 = 1/25C - 1/366C$ we get

$$F(s) = \frac{1 + s/332.7}{1 + s^2/98208 + s/24.83} \text{ . Consequently,}$$


$$T(j\omega) = K_v \frac{F(j\omega)}{j\omega} = \frac{10^4 (1 + j\omega/332.7)}{j\omega [1 - \omega^2/98208 + j\omega/24.83]}$$

By trial and error we find $\omega_x = 797 \text{ rad/s}$, and $\phi_m = 57.7^\circ$; ω_x increases by 40 rad/s , and ϕ_m decreases by 8.3° .

13.23 Case $D_I = D_O = 1/2$:

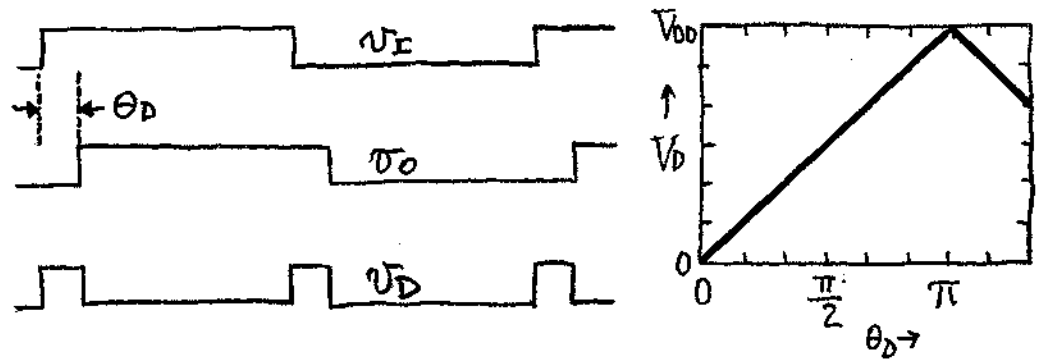


Case $D_I = 1/2, D_O = 1/3$:

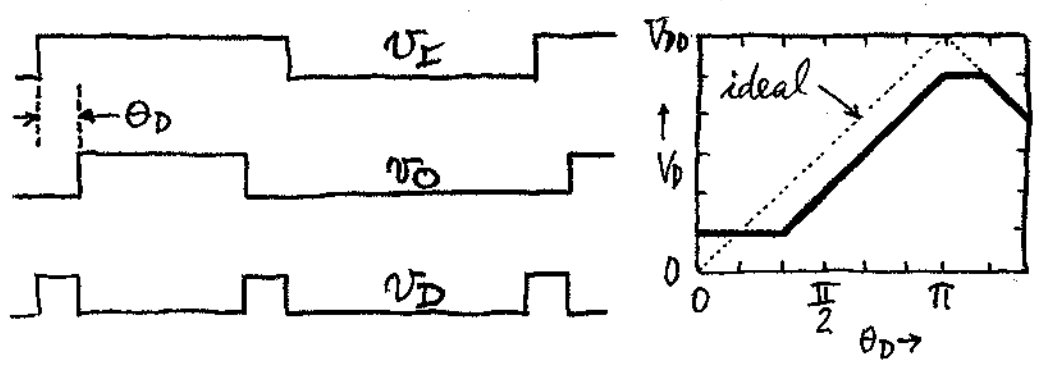


13.15

Case $D_I = 1/3, D_O = 1/2$:

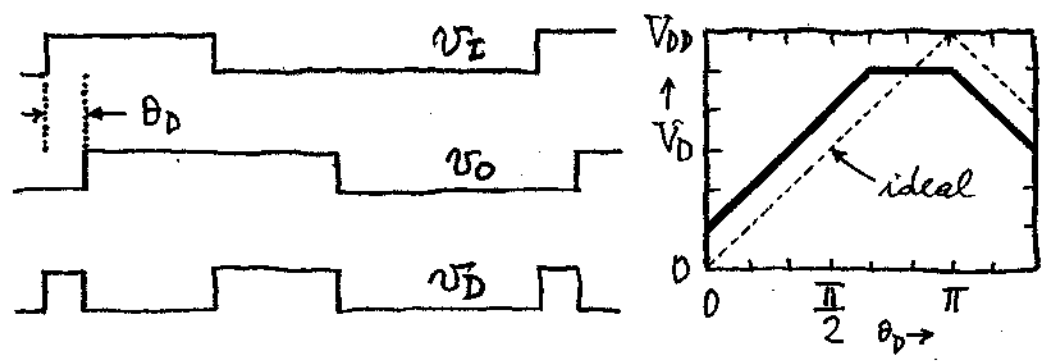


13.24


(a) ω_I slightly higher than ω_O :

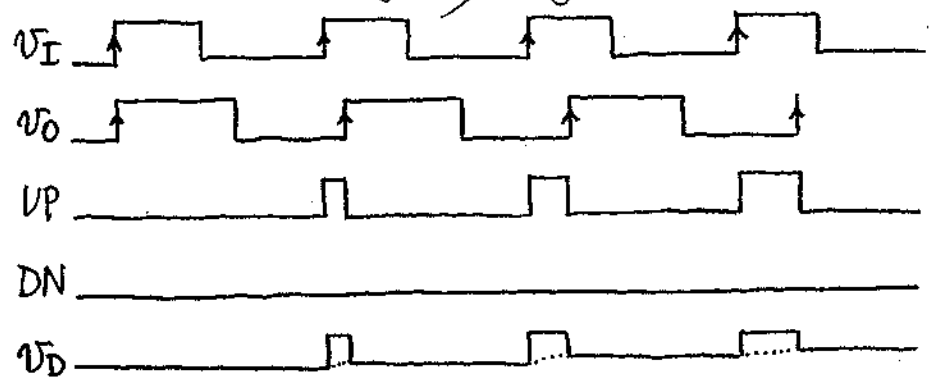

(b) ω_I slightly lower than ω_O :

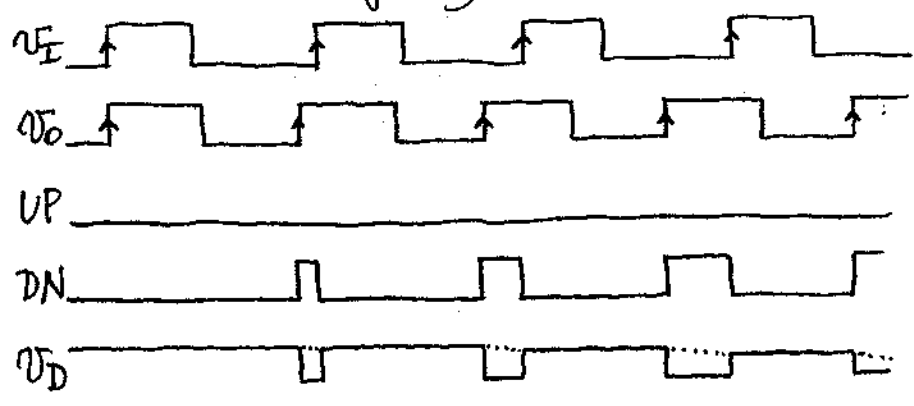


(c) $\omega_I \gg \omega_O$:

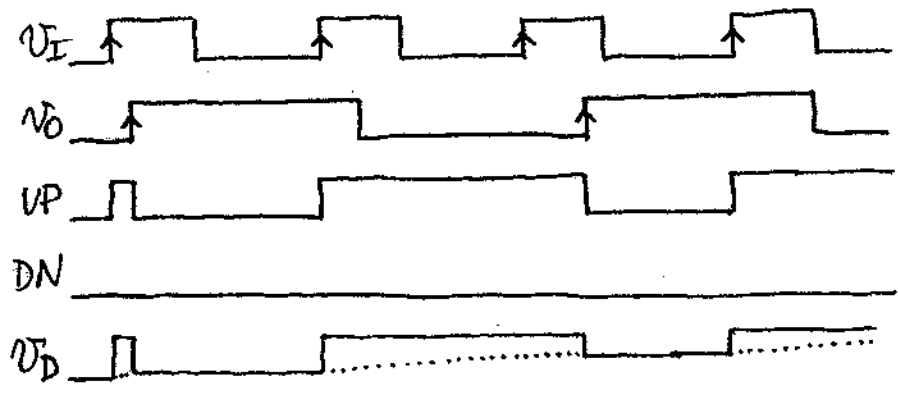

13.16

(d) $\omega_I \ll \omega_0$

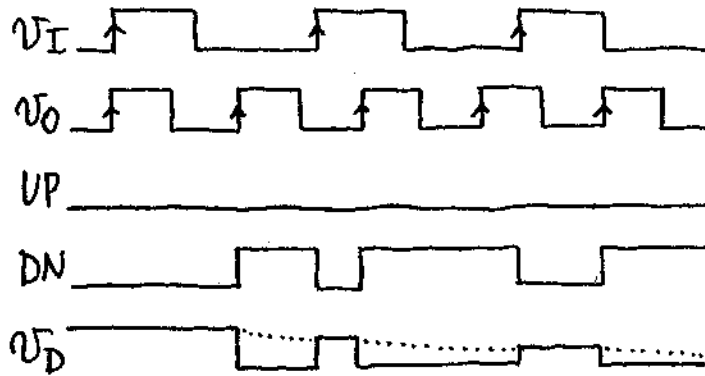

13.25

(a) $K_d = 5/\pi$; $K_a = 1$; $K_o = 2\pi \times 5 \times 10^6 = \pi 10^7$;

$K_v = (5/\pi) \times 1 \times \pi 10^7 = 5 \times 10^7 \text{ s}^{-1}$.

$\omega_m = \pi 10^4 \text{ rad/s}$. Using Eqs. (13.46),

$\omega_p = \omega_m^2 / K_v = (\pi 10^4)^2 / (5 \times 10^7) = 19.74 \text{ rad/s}$

$\Rightarrow (R_1 + R_2)C = 1/19.74$

$3 = 1/2Q = 1/(2 \times 0.5) = 1 = \pi 10^4 \left(\frac{1}{2\omega_c} + \frac{1}{2 \times 5 \times 10^7} \right)$

$\approx \pi 10^4 / (2\omega_c) \Rightarrow \omega_c = \frac{\pi}{2} 10^4 = 15,708 \text{ rad/s}$

$\Rightarrow R_2 C = 1/15,708$. Pick $C = 100 \text{ nF}$. Then,

$R_2 = 637 \Omega$ (use 634Ω , 1%), and $R_1 = 507 \text{ k}\Omega$

(use $511 \text{ k}\Omega$, 1%). Use $C_2 = 10 \text{ nF}$.


(b) $f_0 = 10^7 + (V_E - 2.5) 5 \times 10^6$; $f_0 = 7.5$

$\text{MHz} \Rightarrow V_E = 2 \text{ V}$.

$\theta_I - \theta_O = V_E / K_d = 2 / (5/\pi) = 1.25\pi \text{ radians}$.

The waveforms are as follows:

13.17

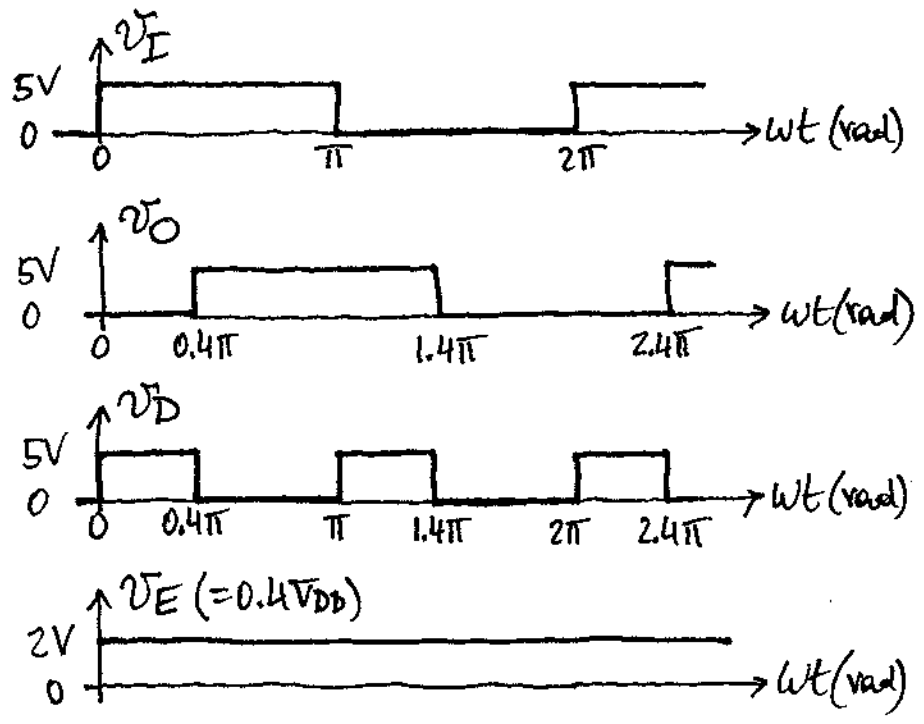

13.26 $\omega_p = 553 \text{ rad/s}$, $\omega_z = 22.5 \times 10^3 \text{ rad/s}$,
 $\zeta = 1/\sqrt{2}$, $K_0 = 1.122 \times 10^6 \text{ rad/s}$, $K_v = 1.786 \times 10^6$
 s^{-1} , $\omega_m = \sqrt{\omega_p K_v} = 3.143 \times 10^4 \text{ rad/s}$; $2\zeta - \omega_m/K_v$
 $= 1.397$. Substituting into Eq. (13.46a),

$$H(s) = \frac{s/(2.25 \times 10^4) + 1}{[s/(3.143 \times 10^4)]^2 + s/(2.22 \times 10^4) + 1}$$


Computing at $s = j\omega_m = j2\pi \times 10^3$ we get
 $H(j2\pi \times 10^3) = 1.0373 \angle -0.82^\circ$. Then,

$$v_e(t) = \frac{|w_i|}{K_0} 6.0373 \cos(2\pi \times 10^3 t - 0.82^\circ).$$

Substituting $|w_i| = 2\pi \times 10 \times 10^3 \text{ rad/s}$ and $K_0 = 1.122 \times 10^6 \text{ rad/s}$ we finally get

$$v_e(t) = (58.09 \text{ mV}) \cos(2\pi \times 10^3 t - 0.82^\circ).$$

13.18

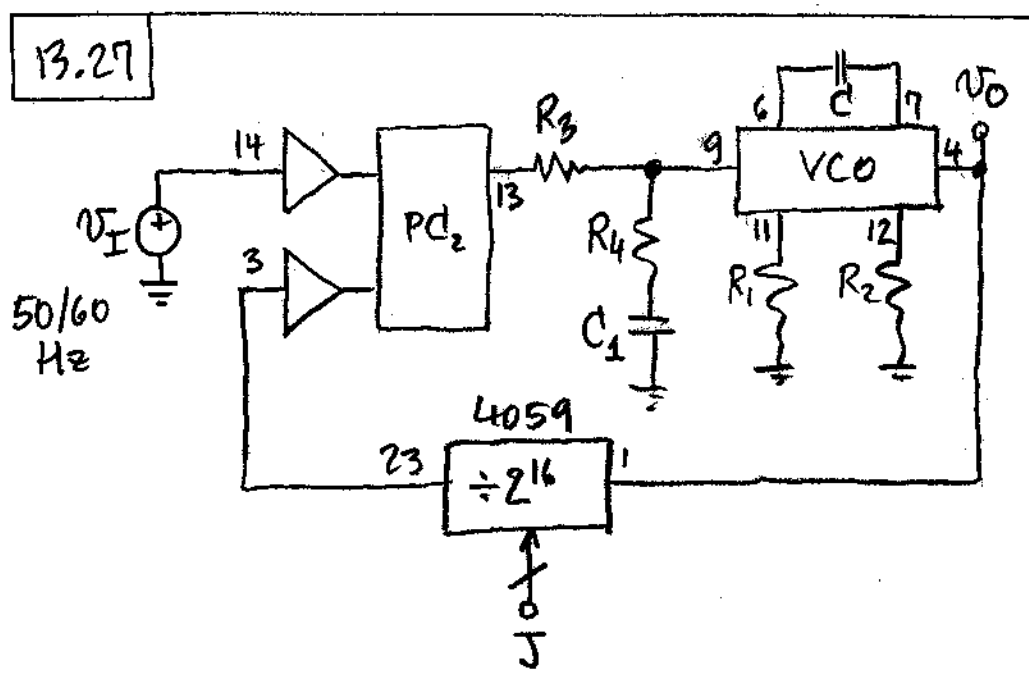


Design for $f_I = 55$ Hz. Then, $f_o = 55 \times 216 = 3.60$ MHz. Arbitrarily impose $2f_r = 2$ MHz, so that $K_o = 2\pi \times 2 \times 10^6 / (3.9 - 1.1) = 4.49$ (Mrad/s)/V. To meet these specifications, the PLL Design Program suggests using $R_1 = 22$ k Ω , $R_2 = 39$ k Ω , and $C = 100$ pF.

Using PC2, we get $K_d = 5/4\pi$. Then, $K_v = (5/4\pi) \times 4.49 \times 10^6 / 216 = 27.2$ s $^{-1}$.

Choose $\omega_m = \omega_I / 20 = 2\pi 55 / 20 = 17$ rad/s, and $\zeta = 1/\sqrt{2}$. Then, $\omega_p = \omega_m^2 / K_v = 11$ rad/s, and $\omega_z = 21.5$ rad/s. Let $C_1 = 1$ μ F. Then, $R_4 = 1/\omega_z C_1 \approx 47$ k Ω , and $R_3 = 1/\omega_p C - R_4 = 91$ k Ω .

13.19

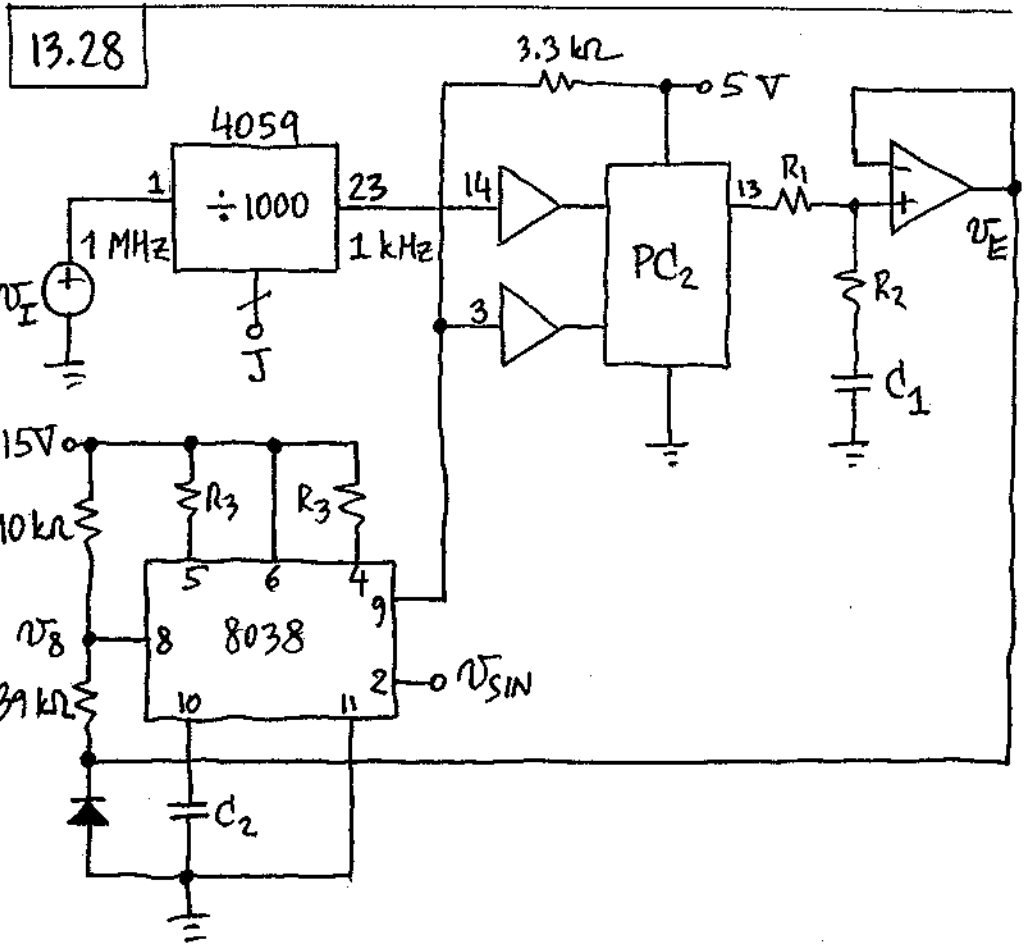


Use a 4059 counter configured as a modulo-1000 counter to divide the 1-MHz input down to a 1-kHz reference signal for the phase comparator. The other input to the phase comparator is obtained from the 8038's open-collector output using the 3.3-k Ω pullup resistor. Buffer the filter with a FET-input op amp to avoid loading. $0V \leq v_E \leq 5V \Rightarrow 12V \leq v_8 \leq 13V$. Let $f_0 = 1\text{ kHz}$ for $v_E = 2.5V$, i.e. for $v_8 = 12.5V$. Impose $i_{R_3} = 0.1\text{ mA}$, so $R_3 = (15 - 12.5)/0.1 = 24.9\text{ k}\Omega$. Using $C_2 \Delta V = I \Delta t$ with $\Delta V = 2 \times$

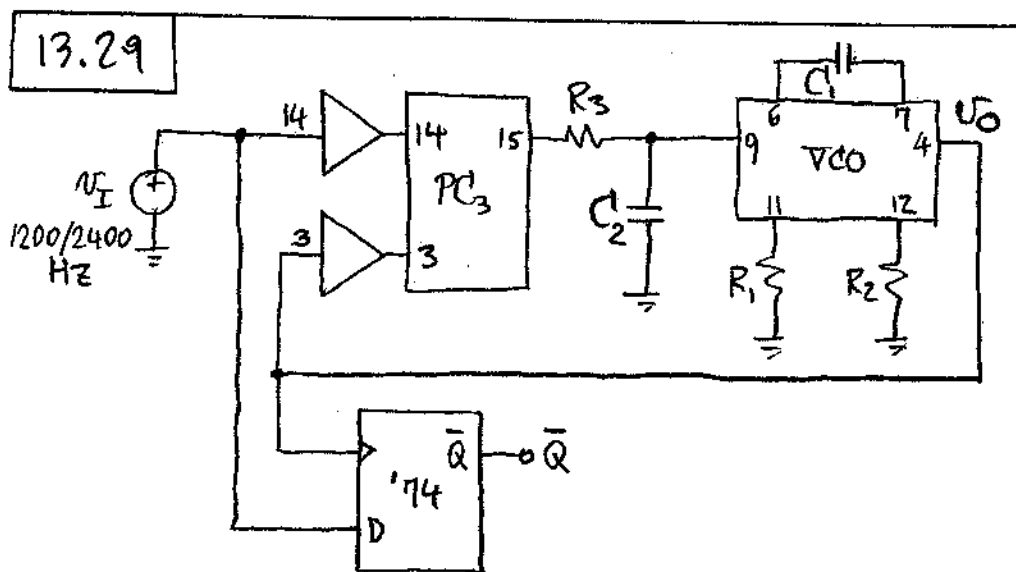13.20

$(15/3) = 10 \text{ V}$, $I = 0.1 \text{ mA}$, $\Delta t = 1/f_0 = 1 \text{ ms}$ gives $C_2 = 10 \text{ nF}$. The purpose of the diode is to protect the 8038 against possible excessively negative swings of V_E at power turn-on.

To design the filter, observe that $K_d = 5/4\pi \text{ V/rad}$. Moreover, $\Delta V_E = 5 \text{ V} \Rightarrow \Delta V_{R_3} = 1 \text{ V} \Rightarrow \Delta i_{R_3} = 1/(25 \text{ k}\Omega) = 40 \mu\text{A} \Rightarrow \Delta f_0 = (40 \mu\text{A}) / (10 \text{ V} \times 10 \times 10^{-9} \text{ F}) = 400 \text{ Hz}$. So, $K_0 = \Delta f_0 / \Delta V_E = 400/5 = 80 \text{ Hz/V} = 160\pi \text{ (rad/s)/V}$. Consequently, $K_V = (5/4\pi) 160\pi = 200 \text{ s}^{-1}$. Arbitrarily impose $\omega_m = 2\pi \text{ rad/s}$, so $\omega_p = \omega_m^2 / K_V = 0.2 \text{ rad/s}$; and $\zeta = 1/\sqrt{2}$, so $\omega_z = (2\zeta/\omega_m - 1/K_V)^{-1} = 4.54 \text{ rad/s}$. Let $C = 3.3 \mu\text{F}$. Then, $R_2 = 68 \text{ k}\Omega$, $R_1 = 1.5 \text{ M}\Omega$.




PLL Design program $\Rightarrow C_1 = 33 \text{ nF}$, $R_1 = 91 \text{ k}\Omega$, $R_2 = 1.3 \text{ M}\Omega$. $R_3 C_2 = 1/2\pi f_H \Rightarrow C_2 = 33 \text{ nF}$, $R_3 = 2 \text{ k}\Omega$.


13.21

With reference to Fig. 13.26 we can write $f_o = A V_E + B$; substituting $f_o (V_E = 1.1) = 1800 - 1000$ and $f_o (V_E = 3.9) = 1800 + 1000$, we get $f_o = (5000 V_E + 100) / 7$. The control voltages required to make the VCO oscillate at $f_o = 1200$ Hz and $f_o = 2400$ Hz are, respectively, $V_{EL} = 83/50 = 1.66$ V, and $V_{EH} = 83/25 = 3.32$ V. According to Fig. 13.29b, the corresponding phase differences are $\theta_{DL} \cong 120^\circ$ and $\theta_{DH} \cong 240^\circ = -120^\circ$.

Case $f_I = 1200$ Hz ($V_E = 1.66$ V):

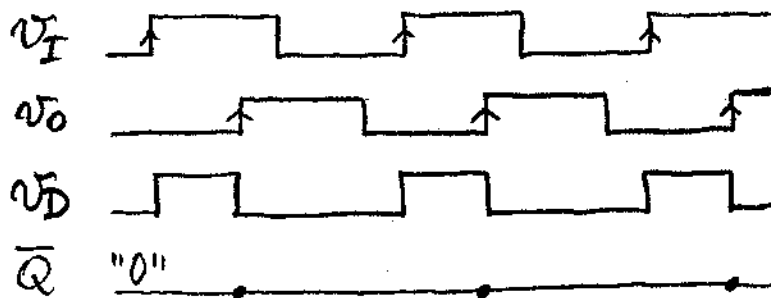

Case $f_I = 2400$ Hz ($V_E = 3.32$ V):

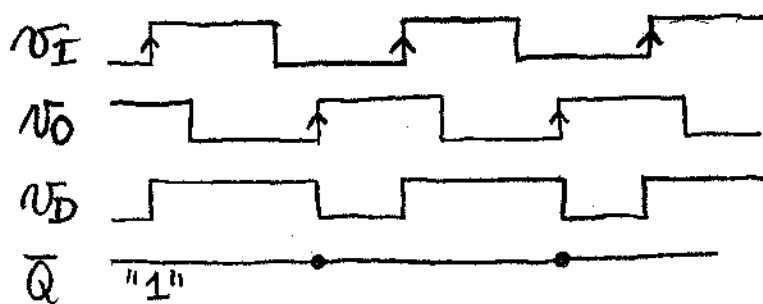

The use of PC_3 simplifies the D-flip-flop timing considerably.