

7.1

$$7.1 \quad e_{nw} = 6 \mu\text{V}/\sqrt{\text{Hz}}; \quad 20^2 = 6^2 (f_{ce}/10 + 1) \Rightarrow \\ f_{ce} \cong 100 \text{ Hz}. \quad E_n = 6 \times 10^{-9} [100 \ln(10^6/10^3) + 106]^{1/2} \\ = 6 \mu\text{V (rms)}.$$

$$7.2 \quad A_{total} = \frac{A_0^2}{(1+jf/f_B)^2}; \quad |A_{total}| = \frac{A_0^2}{1+(f/f_B)^2} \\ NEB = \frac{1}{A_0^4} \int_0^{\infty} \frac{A_0^4}{[1+(f/f_B)^2]^2} df = f_B \int_0^{\infty} \frac{dx}{(1+x^2)^2} = \frac{\pi}{4} f_B.$$

7.3 For this problem see also IEEE Transactions on Circuit Theory, Vol CT-20, NO. 5, September 1973, pp. 524-532. We have

$$\int_0^{\infty} |H_{LP}|^2 df = f_0 \int_0^{\infty} \frac{d(f/f_0)}{[1-(f/f_0)^2]^2 + (f/f_0)^2/Q^2}$$

$$\int_0^{\infty} |H_{BP}|^2 df = \frac{f_0}{Q^2} \int_0^{\infty} \frac{(f/f_0)^2}{[1-(f/f_0)^2]^2 + (f/f_0)^2/Q^2} d(f/f_0).$$

Using integral tables (see, for instance, Gradshteyn and Ryzhik, "Table of Integrals, Series, and Products," Academic Press, New York, 1965) it is found that

$$\int_0^{\infty} |H_{LP}|^2 df = Q^2 \int_0^{\infty} |H_{BP}|^2 = Q \frac{\pi}{2} f_0.$$

Since $|H_{BP}|_{max} = 1$, it follows that $NEB_{BP} = (\frac{\pi}{2} f_0)/Q$. The higher the Q , the narrower the $|H_{BP}|$ curve, so it makes sense that NEB_{BP} decreases with Q .

7.2

For $Q < 1/\sqrt{2}$, $|H_{LP}|_{\max} = 1$, so $NEB_{LP} = Q \frac{\pi}{2} f_0$. For higher values of Q , we can either retain this expression, or we can rigorously comply with the definition of Eq. (7.13). In the former case we observe that NEB increases with Q due to the additional area available in the frequency region where peaking occurs. In the latter we must use $NEB_{LP} = |H_{LP}|_{\max}^{-1} \times Q \frac{\pi}{2} f_0$. For large Q s (say $Q \geq 5$), $|H_{LP}|_{\max} \cong Q$, so $NEB_{LP} \cong (1/Q^2) Q \frac{\pi}{2} f_0 = (\frac{\pi}{2} f_0)/Q = NEB_{BP}$, indicating that for high Q s the NEB s of the two functions tend to be the same. Indeed, in this case, most of the noise comes from the frequency region of peaking, where the two functions are virtually indistinguishable.

7.4 (a) $H = 1/(1+jf/f_0)^2$, $f_0 = 1/2\pi RC$; $|H|^2 = 1/[1+(f/f_0)^2]^2$; $NEB = \int_0^{\infty} df/[1+(f/f_0)^2]^2 = f_0 \int_0^{\infty} \frac{dx}{(1+x^2)^2}$. Using the integral tables, or also applying the results of Problem 7.2 with $Q=0.5$, we get $NEB = (\pi/4)f_0 = 0.785f_0$.

(b) $H = (jf/f_0)/[1+jf/f_0]^2$; $|H|^2 = (f/f_0)^2/[1+(f/f_0)^2]^2$; $|H|_{\max}^2 = (1/2)^2 = 1/4$;

7.3

$$NEB = 4f_0 \int_0^{\infty} \frac{x^2}{(1+x^2)^2} dx = \pi f_0.$$

(c) The order in which the stages are cascaded is mathematically irrelevant, so $NEB = \pi f_0$.

(d) (a) is the best since it has the lowest

7.4

$$\begin{aligned}
 NEB &= \frac{1}{50^2} \int_0^{\infty} |A_m|^2 df = \frac{1}{50^2} \int_0^{\infty} (1 + 50 \text{HBP})^2 \frac{df}{1 + (f/10^6)^2} \\
 &\cong \frac{1}{50^2} \left[\int_0^{\infty} |50 \text{HBP}|^2 df + \int_0^{\infty} \frac{df}{1 + (f/10^6)^2} \right] \\
 &= \frac{1}{50^2} \left[50^2 \frac{\pi f_0}{2Q} + 1.57 f_t \right] \cong 500 + 628 = 1.3 \text{ kHz.}
 \end{aligned}$$

7.6 The noise gain, normalized to unity at dc, can be expressed as

$$|A_m(jf)|^2 = \frac{1 + (f/f_1)^2}{[1 + (f/f_2)^2][1 + (f/f_3)^2]}$$

At low frequencies ($f < f_1 < f_3$) we can write

$$|A_m(jf)|^2 \cong \frac{1}{1 + (f/f_2)^2},$$

whose integral from 0 to f_1 can be approximated with the integral from 0 to ∞ to yield a contribution of $1.57 f_2 = 1.57 \times 50 = 78.5 \text{ Hz}$. At high frequencies ($f > f_1 > f_2$) we can write

$$|A_m(jf)|^2 \cong \left(\frac{f_2}{f_1}\right)^2 \frac{1}{1 + (f/f_3)^2},$$

whose integral from f_1 to ∞ yields a contribution of $(f_2/f_1)^2 (1.57 f_3 - f_1) = (50/500)^2 (1.57 \times 2,122 - 500) = 28.3 \text{ Hz}$.

Thus, $NEB \cong 78.5 + 28.3 \cong 110 \text{ Hz}$. This is confirmed by PSpice:


7.5

Problem 7.6:

```

Vi 1 0 ac 1
R1 1 0 1
E2 2 0 Laplace {V(1,0)}={1+s/3142}
R2 2 0 1
E3 3 0 Laplace {V(2,0)}={1/((1+s/314.2)*(1+s/13333))}
R3 3 0 1
.ac dec 10 0.1 1Meg
.probe
.end

```

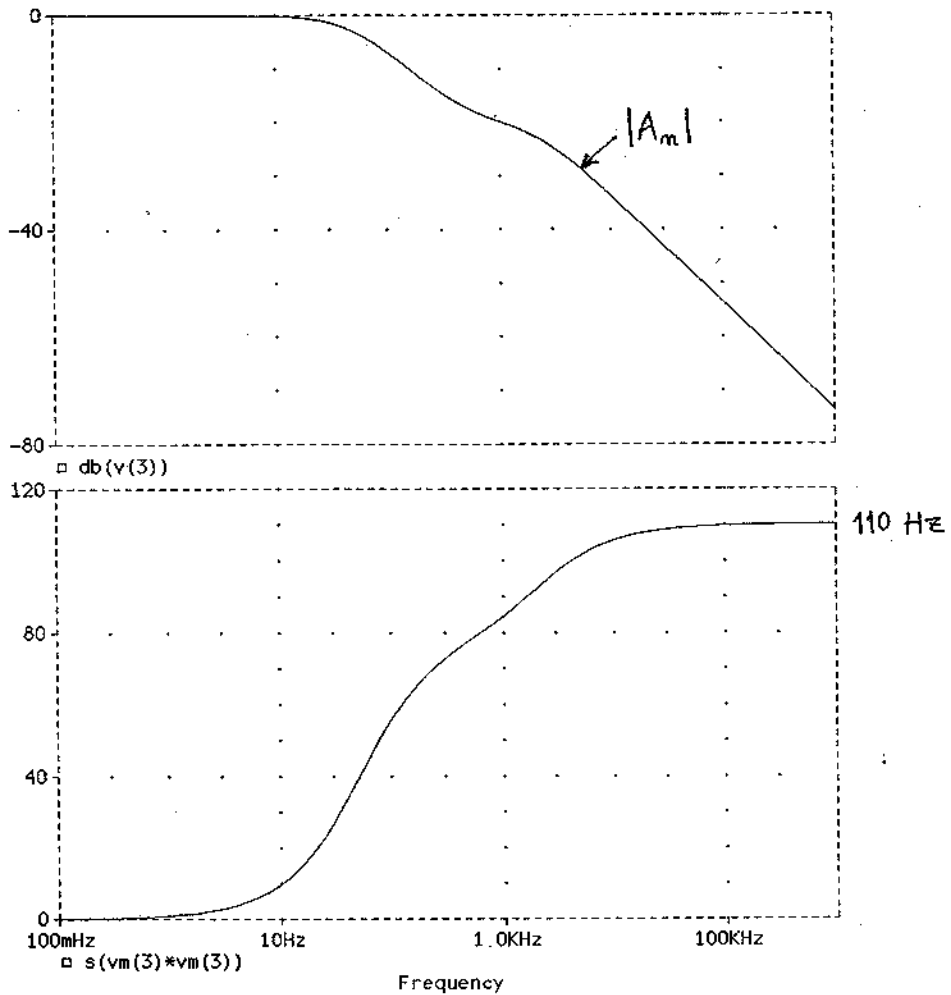

7.7

PROBLEM 7.7


```

Vi 1 0 AC 1
R1 1 0 1
E2 2 0 Laplace {V(1,0)}=((1+s/62.83)*(1+s/6283))
R2 2 0 1
E3 3 0 Laplace {V(2,0)}=(1/((1+s/628.3)*(1+s/1257)))
R3 3 0 1
E4 4 0 Laplace {V(3,0)}={1/((1+s/62832)*(1+s/62832))}
R4 3 0 1
.ac dec 10 0.1 1Meg1
.probe
.end


```

7.6

From the plots, $|A_m|_{max} = 6.72 \text{ V/V}$, $NEB = 1.12 \text{ kHz}$.

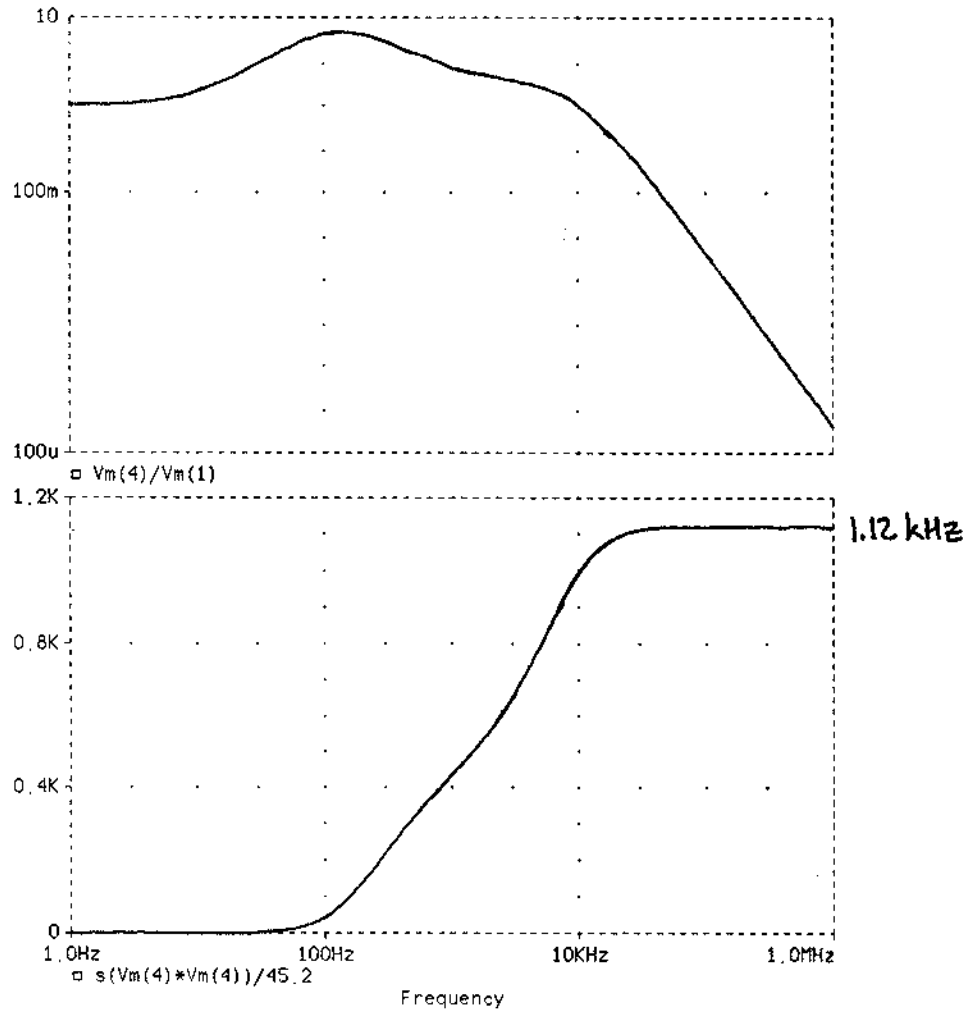

7.8

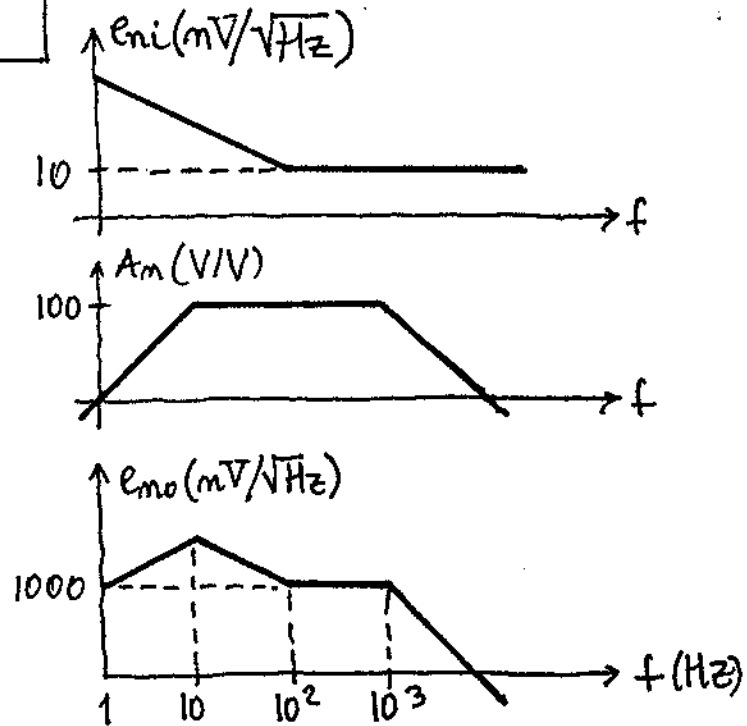

7.7

$$\text{For } f \leq 1 \text{ Hz, } e_{m0}^2 = (1000 \times 10^{-9} \sqrt{f})^2 = 10^{-12} f;$$

$$E_{m01}^2 = 10^{-12} \int_0^{10} f df = \frac{1}{2} 10^{-12} f^2 \Big|_0^{10} = 5 \times 10^{-11} \text{ V}^2.$$

$$\text{For } 10 \text{ Hz} \leq f \leq 100 \text{ Hz we have } e_{m0}^2 = 10^{-10}/f;$$

$$E_{m02}^2 = 10^{-10} \int_{10}^{100} \frac{df}{f} = 10^{-10} \ln\left(\frac{100}{10}\right) = 2.3 \times 10^{-10} \text{ V}^2.$$


For $f \geq 100 \text{ Hz}$ we have white noise going through a low-pass filter with $f_0 = 1 \text{ kHz}$;

$$E_{m03}^2 = (1000 \times 10^{-9})^2 \times (1.57 \times 10^3 - 100) = 1.47 \times 10^{-9} \text{ V}^2.$$

$$E_{m0} = \sqrt{5 \times 10^{-11} + 2.3 \times 10^{-10} + 1.47 \times 10^{-9}} = 41.83 \mu\text{V}.$$

Pink noise tangent gives $E_{m0} \approx 10^3 \text{ mV} \sqrt{1.57 \times 10^3} = 39.6 \text{ V}$, close enough to $41.83 \mu\text{V}$.

7.9

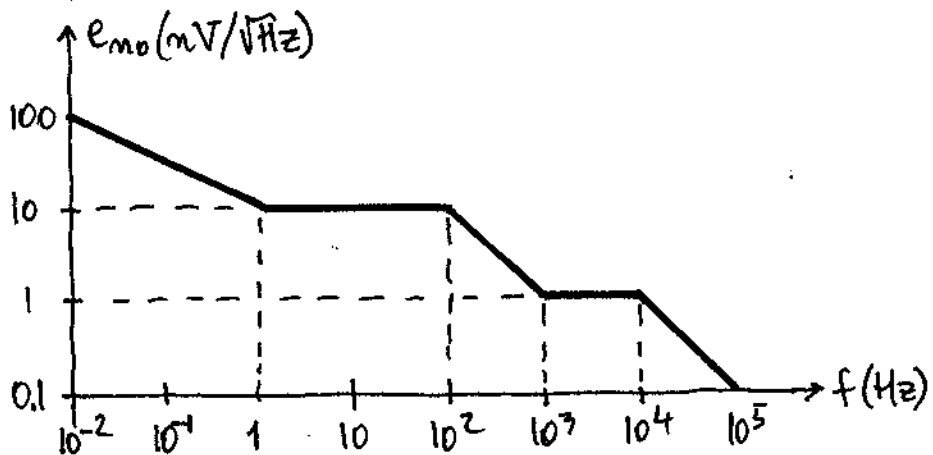

$$10^{-2} \text{ Hz} \leq f \leq 1 \text{ Hz: } e_{m01}^2 = 10^{-6}/f \text{ V}^2/\text{Hz};$$

$$E_{m01}^2 = \int_{10^{-2}}^1 e_{m01}^2 df = 4.6 \times 10^{-16} \text{ V}^2.$$

$$1 \text{ Hz} \leq f \leq 10^2 \text{ Hz: } e_{m02}^2 = 10^{-16} \text{ V}^2/\text{Hz};$$

$$E_{m02}^2 = 10^{-16} (100 - 1) = 99 \times 10^{-16} \text{ V}^2.$$

9.8

$$10^2 \text{ Hz} \leq f \leq 10^3 \text{ Hz}: e_{n03}^2 = 10^{-12} / f^2 \text{ V}^2/\text{Hz};$$

$$E_{n03}^2 = 10^{-12} \int_{10^2}^{10^3} \frac{df}{f^2} = 10^{-12} \left(-\frac{1}{f} \right)_{10^2}^{10^3} = 90 \times 10^{-16} \text{ V}^2.$$

$$f \geq 10^3 \text{ Hz}: E_{n04}^2 = 10^{-18} \left(\frac{\pi}{2} 10^4 - 10^3 \right) = 147 \times 10^{-16} \text{ V}^2.$$

$$E_{n0}^2 = (4.6 + 99 + 90 + 147) \times 10^{-16} = (0.185 \mu\text{V})^2.$$

The pink noise line touches e_{n0} at $f = 100$ Hz as well as $f = 10^4$ Hz. We can thus approximate as

$$\begin{aligned} E_{n0}^2 &\approx (10 \text{ mV})^2 \times \frac{\pi}{2} \times 100 + (1 \text{ mV})^2 \times \frac{\pi}{2} \times 10^4 \\ &= (0.177 \mu\text{V})^2. \end{aligned}$$

9.10 We have $f_L = 1/60$ and $f_0 = 1/2\pi RC = 16$ Hz. Moreover, $e_m^2 = (118 \text{ mV}/\sqrt{\text{Hz}})^2 (30/f + 1)$ and $e_{10 \text{ k}\Omega}^2 = 4kTR = (12.8 \text{ mV}/\sqrt{\text{Hz}})^2$. Consequently, $e_{mi}^2 = e_m^2 + e_{10 \text{ k}\Omega}^2 = 118.7^2 + 118^2 \times 30/f \text{ mV}^2/\text{Hz}$
 $= 118.7^2 (29.65/f + 1) \text{ mV}^2/\sqrt{\text{Hz}}.$

$$e_{n0}^2 = (118.7 \times 10^{-9})^2 (29.65/f + 1) \frac{1}{1 + (f/16)^2}.$$

Piecewise integration:

$$\begin{aligned} 1/60 < f < 16 \text{ Hz}: e_{n0}^2 &\approx (118.7 \times 10^{-9})^2 \times \\ &30.36/f; E_{n01} = 118.7 \times 10^{-9} \left[\int_{1/60}^{16} (29.65/f) df \right]^{1/2} \approx \end{aligned}$$

7.9

1.7 μV .

$$16 \text{ Hz} < f < 29.65 \text{ Hz}: e_{mo}^2 \cong (118.7 \times 10^{-9})^2 \times (29.65/f) \times (16/f)^2 = (10.34 \times 10^{-6})^2 / f^3. \text{ Now}$$

$$\int_{16}^{29.65} df/f^3 = -\frac{1}{2} \frac{1}{f^2} \Big|_{16}^{29.65} = 1/122, \text{ so } E_{mo2} \cong$$

0.38 μV .

$$f > 29.65 \text{ Hz}: e_{mo}^2 \cong (118.7 \times 10^{-9})^2 \times (16/f)^2 = (1.9 \times 10^{-6})^2 / f^2. \text{ Now } \int_{29.65}^{\infty} df/f^2 = 1/29.65,$$


$$\text{so } E_{mo3} = 1.9 \times 10^{-6} / \sqrt{29.65} = 0.35 \mu\text{V}.$$

Finally, $E_{mo} = (1.7^2 + .38^2 + .35^2) = 1.78 \mu\text{V}$ (rms), or 11.7 μV peak-to-peak.

7.11 $R = \frac{4kT}{i_R^2} = \frac{4kT}{i_D^2} = \frac{4kT}{2qI_D} = \frac{51.5 \times 10^{-3}}{I_D}$


For $I_D = 50 \mu\text{A}$, $R = 1.03 \text{ k}\Omega$; for $I_D = 1 \text{ pA}$, $R = 51.5 \text{ G}\Omega$.

7.12 (a) $e_{mo}^2 = |R \parallel \frac{1}{sC}|^2 i_R^2 = \frac{R^2}{|1+sRC|^2} \frac{4kT}{R}$

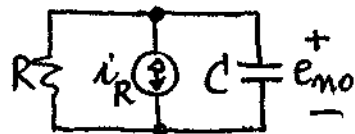

$$= \frac{4kTR}{1+(f/f_0)^2}, \quad f_0 = \frac{1}{2\pi RC}$$
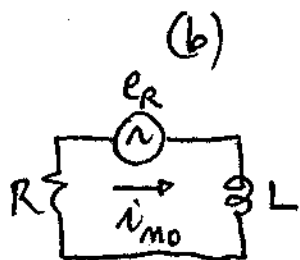
$$E_m = \sqrt{4kTR \times (\pi/2) f_0} = \sqrt{kT/C}$$



$$i_{mo}^2 = e_R^2 / |R+sL|^2$$

$$= \frac{4kTR}{|R(1+sL/R)|^2} =$$

$$= (4kT/R) / [1+(f/f_0)^2],$$


7.10

$$f_0 = 1/(2\pi L/R); I_m = \sqrt{(4kT/R)(\pi/2)f_0} = \sqrt{kT/L}.$$

7.13 (a) $R(k\Omega) \approx (e_{nw}/4)^2 = (20/4)^2 \Rightarrow R \approx 25 k\Omega.$

(b) $I = (0.5 \times 10^{-12})^2 / 2q = 780 \text{ nA}.$ This is much larger than the input bias current I_B (80 nA typical), indicating the presence of other noise sources besides shot noise due to I_B alone.

7.14

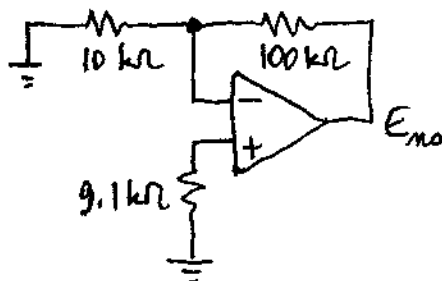

(a) 741: $f_B = \beta f_t = 10^6 / 11 = 91 \text{ kHz}; E_{noe} = 11 \times 20 \times 10^{-9} [200 \ln(91 \times 10^3 / 0.1) + 1.57 \times 91 \times 10^3]^{1/2} \approx 84.0 \mu\text{V}; E_{noi} = 11 \times 91 \times 10^3 \sqrt{2} \times 0.5 \times 10^{-12} \times [2 \times 10^3 \ln(91 \times 10^3 / 0.1) + 1.57 \times 91 \times 10^3]^{1/2} \approx 292 \mu\text{V}; E_{noR} = 11 \times [1.65 \times 10^{-20} \times 2 \times 91 \times 10^3 \times 1.57 \times 91 \times 10^3]^{1/2} \approx 228 \mu\text{V}; E_{no} = (84^2 + 292^2 + 228^2)^{1/2} \approx 380 \mu\text{V}.$


(b) OP-27: $f_B = 8 \times 10^6 / 11 = 727 \text{ kHz}; E_{noe} = 11 \times 3 \times 10^{-9} [2.7 \ln(727 \times 10^3 / 0.1) + 1.57 \times 727 \times 10^3]^{1/2} \approx 35.3 \mu\text{V}; E_{noi} = 11 \times 91 \times 10^3 \sqrt{2} \times 0.4 \times 10^{-12} \times [140 \ln(727 \times 10^3 / 0.1) + 1.57 \times 727 \times 10^3]^{1/2} = 605 \mu\text{V}; E_{noR} = 11 \times [1.65 \times 10^{-20} \times 2 \times 91 \times 10^3 \times 1.57 \times 727 \times 10^3]^{1/2} \approx 644 \mu\text{V}; E_{no} \approx 885 \mu\text{V}; \text{all rms}.$

In both circuits current and thermal

7.11

noise far exceed voltage noise, indicating that the resistances ought to be suitably reduced. Moreover, under the given conditions, the OP-27 circuit is noisier because of the higher f_t .

7.15

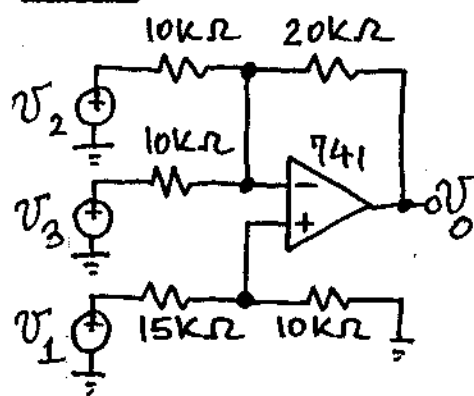

$$R_p = 15 // 10 = 6 \text{ k}\Omega,$$

$$R_m = 10 // 10 // 20 = 4 \text{ k}\Omega,$$

$$\beta = 5/25 = 0.2 \text{ V/V.}$$

$$f_B = 0.2 \times 10^6 = 200 \text{ kHz};$$

$$NEB = 1.57 f_B = 314 \text{ kHz};$$

$$A_m = 1/\beta = 5 \text{ V/V.}$$

$$E_{mo} = 5 \left[(20 \times 10^{-9})^2 (200 \ln 200,000 + 314,000) + (6,000^2 + 4,000^2) (0.5 \times 10^{-12})^2 (2,000 \times \ln 200,000 + 314,000) + 1.65 \times 10^{-20} \times 10,000 \times 314,000 \right]^{1/2} = 69.7 \mu\text{V rms.}$$

7.16


$$0A_1: (A-1)R = 100 \text{ k}\Omega; R_p = 0; R_m = 100 // 100 = 50 \text{ k}\Omega; \beta = 0.5; A_m = 2; f_B = 500 \text{ kHz}; NEB = 1.57 \times 500 = 785 \text{ kHz.}$$

$$E_{mo1} = 2 \left[(20 \times 10^{-9})^2 (200 \ln 500,000 + 785,000) + (50,000 \times 0.5 \times 10^{-12})^2 (2,000 \times \ln 500,000 + 785,000) + 1.65 \times 10^{-20} \times 50,000 \times 785,000 \right]^{1/2} = 76.7 \mu\text{V rms}$$

7.12

$0A_2: AR = 200 \text{ k}\Omega; R_p = 0; R_m = 200 // 100 = 67 \text{ k}\Omega; b = 1/3; A_m = 3; f_B = 333 \text{ kHz}; NEB = 523 \text{ k}\Omega. E_{mo2} = 112.4 \mu\text{V rms}.$
 $E_{no} = (76.7^2 + 112.4^2)^{1/2} = 136 \mu\text{V rms}.$

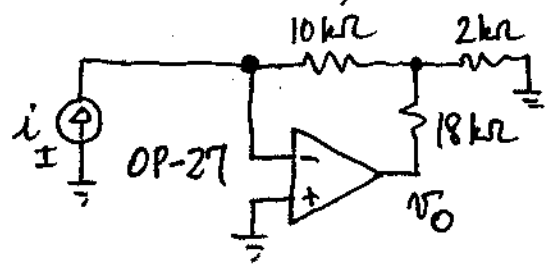7.17 (a) $R_p = 0, R_m = 10 + 2 // 18 = 11.8 \text{ k}\Omega; \beta =$



$2 / (2 + 18) = 0.1 \text{ V/V};$
 $f_B = 0.1 \times 8 = 800 \text{ kHz};$
 $A_{no} = 1 / \beta = 10 \text{ V/V}.$

$E_{noe} = 10 \times 3 \times 10^{-9} [2.7 \ln(8 \times 10^5 / 0.1) + 1.57 \times 8 \times 10^5]^{1/2}$
 $= 34 \mu\text{V}; E_{noi} = 10 \times 11.8 \times 10^3 \times 0.4 \times 10^{-12} \times$
 $[140 \times \ln(8 \times 10^6) + 1.57 \times 8 \times 10^5]^{1/2} = 53 \mu\text{V};$
 $E_{nor} = 10 \sqrt{1.65 \times 10^{-20} \times 11.8 \times 10^3 \times 1.57 \times 8 \times 10^5} =$
 $156 \mu\text{V}; E_{no} = (34^2 + 53^2 + 156^2)^{1/2} \approx 168 \mu\text{V}.$

(b) $V_{i(rms)} = (10 \mu\text{A}) / \sqrt{3} = 5.77 \mu\text{A}; I_{ni} =$
 $E_{no} / R_{eq} = (168 \mu\text{V}) / [10^4 (1 + 18/2 + 18/10)] =$
 $1.34 \text{ nA}; \text{SNR} = 20 \log_{10} [5.77 \times 10^{-6} / (1.34 \times 10^{-9})]$
 $= 72.7 \text{ dB}.$

7.18 (a) $A_{ideal} = -8 \text{ V/V}; \beta = 1/13 \text{ V/V}; f_B =$


$\beta f_t \approx 77 \text{ kHz}; R_m = 10 // \{ 10 + 10 // [10 + (10 // 10)] \} =$
 $6.15 \text{ k}\Omega. E_{noe} = 13 \times 20 \times 10^{-9} [200 \ln(77 \times 10^3 / 0.1)$
 $+ 1.57 \times 77 \times 10^3]^{1/2} = 91.4 \mu\text{V}; E_{noi} = 13 \times 6.15 \times$
 $10^3 \times 0.5 \times 10^{-12} [2 \times 10^3 \ln(77 \times 10^3 / 0.1) + 1.57 \times 77 \times$
 $10^3]^{1/2} = 15.4 \mu\text{V}; E_{nor} = 13 (1.65 \times 10^{-20} \times 6.15 \times$

7.13

$$10^3 \times 1.57 \times 177 \times 10^3]^{1/2} = 45.5 \mu V. E_{no} = (91.4^2 + 15.4^2 + 45.5^2)^{1/2} \approx 103 \mu V.$$

(b) $V_{i(rms)} = (0.5^2 + 0.25^2)^{1/2} = 0.56 V;$
 $E_{ni} = 103/13 = 7.92 \mu V; SNR = 20 \log_{10}(0.5 / 7.92 \times 10^{-6}) = 97 \text{ dB}.$

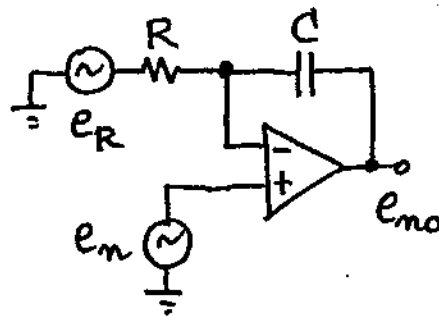7.19 Ignore i_n . Noise model is as follows:



$$\frac{1}{\beta} = 1 + \frac{1/j\omega C}{R} = \frac{1+j(f/f_0)}{j(f/f_0)},$$




$$f_0 = \frac{1}{2\pi RC} = 1 \text{ kHz}.$$

The contribution from e_n to e_{mo} is

$$e_{mo1} = |A_m| e_n.$$

The pink noise tangent principle shows that most noise comes from below f_{ce} and from near f_t .

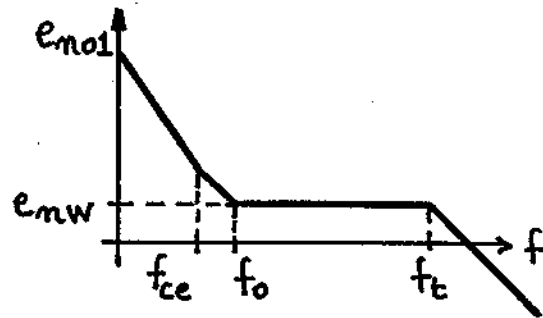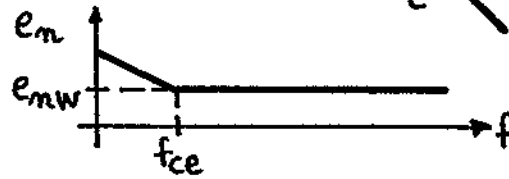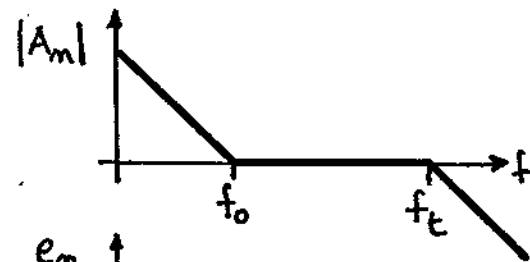Thus, for $f_L < f < f_{ce}$ we can write



$$e_{mo1} \approx 18 \times 10^{-9} \left(\frac{200}{f}\right)^{1/2} \times \frac{1}{f/10^3} = 2.55 \times 10^{-4} / f^{3/2}.$$

7.14

$$\text{Hence, } E_{no1} \approx 2.55 \times 10^{-4} \left[\int_1^{200} \frac{1}{f^3} df \right]^{1/2} = \\ 2.55 \times 10^{-4} \left[\frac{1}{2} \left(\frac{1}{12} - \frac{1}{2002} \right) \right]^{1/2} = 180 \mu\text{V.}$$

$$\text{For } f > f_0 \text{ we have } E_{no2} \approx 18 \times 10^{-9} \times \\ (1.57 \times 3 \times 10^6)^{1/2} = 39 \mu\text{V.}$$


The contribution from e_R to e_{no} is, up to f_t , $e_{no2} = (kTR)^{1/2} \times 1/(1/f_0) = (1.65 \times 10^{-20} \times 158 \times 10^3)^{1/2} \times 10^3/f = 5.1 \times 10^{-5}/f$. Past f_t the contribution rolls off quadratically and can therefore be ignored. Thus, $E_{no3} \approx 5.1 \times 10^{-5} \left[\int_1^{3 \times 10^6} \frac{1}{f^2} df \right]^{1/2} \approx 51 \mu\text{V}$.

$$\text{Finally, } E_{no} = (E_{no1}^2 + E_{no2}^2 + E_{no3}^2)^{1/2} = \\ (180^2 + 39^2 + 51^2)^{1/2} = 191 \mu\text{V rms.}$$

7.20 In the single-op-amp realization, e_n is magnified by 10^3 with $NEB = 1.57 \times 1 \text{ kHz}$. In the two-op-amp cascade realization, the first-stage e_n is magnified by 10^3 with $NEB = 1.11 \times 20.35 \text{ kHz}$, as seen in Example 6.2, and additional noise is produced by the second stage. Thus, the two-op-amp realization is at least $[(1.11 \times 20.35)/(1.57 \times 1)]^{1/2} = 3.8$ times as noisy as the single-op-amp realization.

7.15

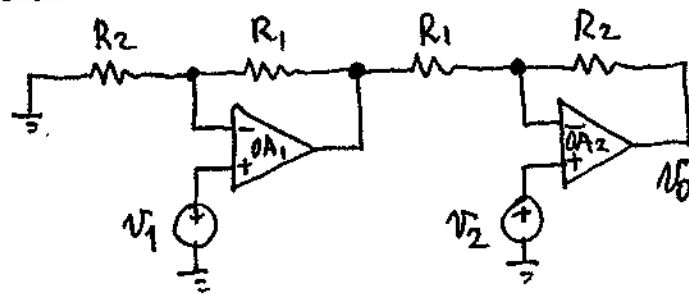7.21 $A_0 = 10^3 \text{ V/V} \Rightarrow R_2 = (10^3 - 1)R_1 \approx 10^3 R_1; R_n =$



$R_1 || R_2 \approx R_1$

$\beta_1 \approx 1 \text{ V/V}$

$\beta_2 \approx 10^{-3} \text{ V/V}$

$f_{B1} \approx f_t =$

8 MHz; $f_{B2} = \beta_2 f_t = 8 \text{ kHz}$. Since $f_{B1} \gg f_{B2}$, we can write

$$e_{moe}^2 \approx \left[\left(1 + \frac{R_2}{R_1}\right)^2 e_{m2}^2 + \frac{R_2^2}{R_1^2} \left(1 + \frac{R_1}{R_2}\right)^2 e_{m1}^2 \right] \frac{1}{1 + (f/f_{B2})^2}$$

$$\approx 2e_m^2 \frac{(10^3)^2}{1 + (f/8 \times 10^3)^2}$$

$$\Rightarrow E_{moe} = 10^3 \sqrt{2} \times 3 \times 10^{-9} \left[2.7 \ln \frac{8 \times 10^3}{0.1} + 1.57 \times 8 \times 10^3 \right]^{1/2} = 476 \mu\text{V}$$

Likewise, the contributions from current and resistor noise are

$$E_{noi}^2 + E_{nor}^2 = 2 \times 10^6 \left\{ R_1^2 \times (0.4 \times 10^{-12})^2 [140 \ln(8 \times 10^4) + 1.57 \times 8 \times 10^3] + R_1 [1.65 \times 10^{-20} + 1.57 \times 8 \times 10^3] \right\}$$


$$= 4.52 \times 10^{-15} R_1^2 + 4.14 \times 10^{-10} R_1$$

Imposing $E_{noi}^2 + E_{nor}^2 \leq E_{moe}^2 / 3$ gives $R_1 \leq 180 \Omega$. Use

$R_1 = 178 \Omega, R_2 = 178 \text{ k}\Omega$. Then, $E_{mo} \approx 550 \mu\text{V}$.

7.16

7.22 (a)

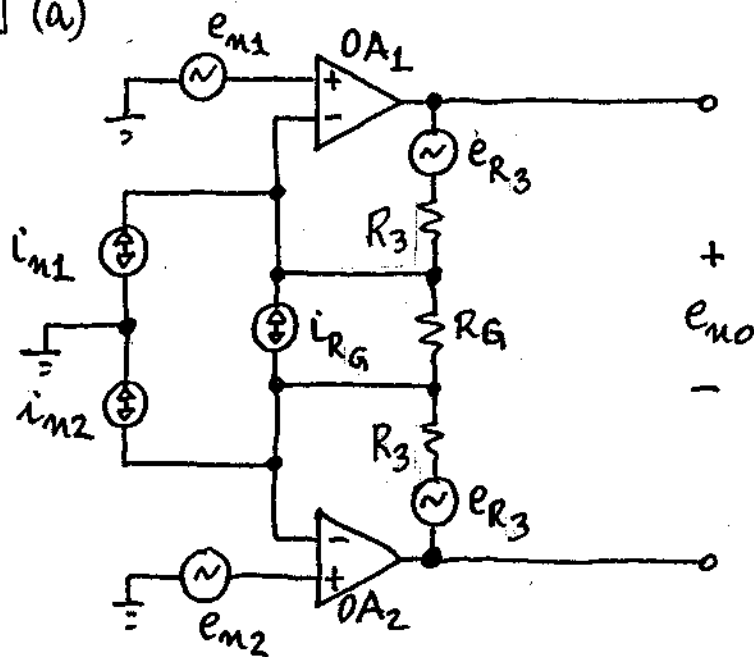

Let $A_{\pm} = 1 + 2R_3/R_G$. The contribution to e_{no}^2 from e_{n1} and e_{n2} is $A_{\pm}^2 (e_{n1}^2 + e_{n2}^2) = 2A_{\pm}^2 e_n^2$. The contribution from i_{n1} and i_{n2} is $R_3^2 i_{n1}^2 + R_3^2 i_{n2}^2 = 2R_3^2 i_n^2 = (2R_3)^2 (i_n^2/2) = A_{\pm}^2 [(2R_3)^2/A_{\pm}^2] i_n^2/2 = A_{\pm}^2 [R_G \parallel (2R_3)]^2 i_n^2/2$. The contribution from i_{R_G} , e_{R_3} , and e_{R_3} is $(R_3 + R_3)^2 i_{R_G}^2 + e_{R_3}^2 + e_{R_3}^2 = (2R_3)^2 \frac{4kT}{R_G} + 2 \times 4kTR_3 = 4kT(2R_3) (1 + 2R_3/R_G) = A_{\pm} \times 4kT(2R_3) = A_{\pm}^2 \times 4kT(2R_3/A_{\pm}) = A_{\pm}^2 \times 4kT [R_G \parallel (2R_3)]$. So, $e_{ni}^2 = e_{no}^2/A_{\pm}^2 = 2e_n^2 + [R_G \parallel (2R_3)]^2 i_n^2/2 + 4kT [R_G \parallel (2R_3)]$.

(b) $f_{BI} = \beta f_c = 8 \times 10^6 / 10^3 = 8 \text{ kHz}$;
 $R_G \parallel (2R_3) \cong R_G = 100 \Omega$. $E_{noe} = 10^3 \times \sqrt{2} \times 3 \times 10^{-9} \times$


7.17

$$\begin{aligned} & [2.7 \ln(8 \times 10^3 / 0.1) + 1.57 \times 8 \times 10^3]^{1/2} = 476 \mu\text{V}; \\ E_{noi} &= 10^3 \times 10^2 \times (0.4 \times 10^{-12} / \sqrt{2}) \times [140 \ln(8 \times 10^4) + \\ & 1.57 \times 8 \times 10^3]^{1/2} = 3.4 \mu\text{V}; E_{nor} = 10^3 [1.65 \times \\ & 10^{-20} \times 10^2 \times 1.57 \times 8 \times 10^3]^{1/2} = 144 \mu\text{V}. E_{no} = \\ & (476^2 + 3.4^2 + 144^2)^{1/2} = 497 \mu\text{V}. \end{aligned}$$

7.23 (a) $\beta_I = 1/2000 \text{ V/V}$, $\beta_{II} = 2/3 \text{ V/V}$;
 $f_{BI} = \beta_I f_t = 8 \times 10^6 / 2000 = 4 \text{ kHz}$; $f_{BII} = 5.33 \text{ MHz}$.
Since $f_{BII} \gg f_{BI}$, the total output noise of the first stage is transmitted to the output with a gain of 0.5 V/V , thus contributing the rms noise $0.5 \times 2000 \left\{ 2 (3 \times 10^{-9})^2 [2.7 \ln(4 \times 10^3 / 0.1) + 1.57 \times 4 \times 10^3] + [(50 \times 0.4 \times 10^{-12})^2 / 2] \times [140 \ln(4 \times 10^4) + 1.57 \times 4 \times 10^3] + 1.65 \times 10^{-20} \times 50 \times 1.57 \times 4 \times 10^3 \right\}^{1/2} = 345 \mu\text{V}$. The second stage contributes the rms noise $1.5 \left\{ (3 \times 10^{-9})^2 [2.7 \ln(5.33 \times 10^6 / 0.1) + 1.57 \times 5.33 \times 10^6] + [(50 \parallel 100)^2 \times (10^3)^2 \times (0.4 \times 10^{-12})^2 \times [140 \ln(5.33 \times 10^7) + 1.57 \times 5.33 \times 10^6] + 1.65 \times 10^{-20} \times 2 \times (50 \parallel 100) \times 10^3 \times 1.57 \times 5.33 \times 10^6] \right\}^{1/2} = 166 \mu\text{V}$. Finally, $E_{no} = (345^2 + 166^2)^{1/2} = 383 \mu\text{V}$.
(b) $E_{mi} = (383 \mu\text{V}) / 10^3 = 383 \text{ nV}$; $\text{SNR} = 20 \log_{10} [(10 \times 10^{-3} / \sqrt{2}) / (383 \times 10^{-9})] = 85.3 \text{ dB}$.

7.18


7.24

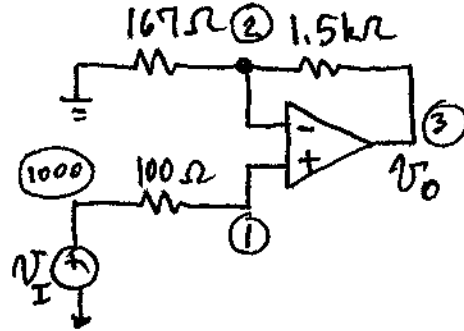

Problem 7.24:

```
.subckt noisyCFA vP vN vO
*Input noise sources:
IDe 0 11 dc 3.12uA
De 11 0 De
*fce = 50kHz
.model De D (KF=1.6E-14,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
*enw = 2.4 nV/sqrt(Hz)
he 1 vP vse 2.4k
IDp 0 21 dc 3.12uA
Dp 21 0 Dp
*fcip = 100kHz
.model Dp D (KF=3.2E-14,AF=1)
Cp 21 22 1GF
vsp 22 0 dc 0V
*inpw = 3.8 pA/sqrt(Hz)
fp 0 1 vsp 3.8
IDn 0 31 dc 3.12uA
Dn 31 0 Dn
*fcin = 100 kHz
.model Dn D (KF=3.2E-14,AF=1)
Cn 31 32 1GF
vsn 32 0 dc 0V
*inw = 20 pA/sqrt(Hz)
fn 0 vN vsn 20
*Noiseless CFA:
*z0 = 710 k, fb = 350 kHz, rn = 50 Ohm
ein 100 0 vp 0 1 ;input buffer
rn 100 200 50 ;buffer's output resistance
vs 200 vN dc 0 ;0-V source to sense iN
fCFA 0 300 vs 1 ;CCCS
Req 300 0 710k ;dc gain
Ceq 300 0 0.641pF ;fa=350kHz
eout vO 0 300 0 1 ;output buffer
.ends noisyCFA
*Main circuit:
Vi 1000 0 ac 1V
Rs 1000 1 100
R1 0 2 166.7
R2 2 3 1.5k
XCFA 1 2 3 noisyCFA
.ac dec 10 10KHz 10GHz
.noise v(3) vi 10
.probe
.end
```

7.19

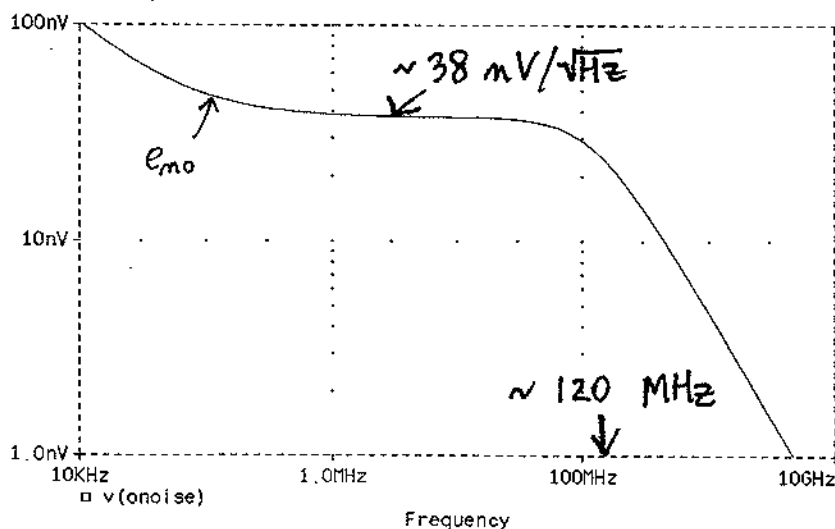

$$E_{mo} \approx 38 \times 10^{-9} \times (1.57 \times 120 \times 10^6)^{1/2} \approx 522 \mu V.$$

7.25 $1/\beta = 10^3 \text{ V/V}$; $R_m \approx R_p = 10 \Omega \approx 0$.

$$0.120 \times 10^{-3} = 10^3 e_m \sqrt{100} \Rightarrow e_m = 12 \text{ nV}/\sqrt{\text{Hz}}.$$

With the 500-k Ω resistors in place, $R_p \approx R_m = 500 \text{ k}\Omega$;

$$2.25 \times 10^{-3} = 10^3 \left\{ (12 \times 10^{-9})^2 \times 100 + 2 \times (500 \times 10^3 i_m)^2 \times 100 + 4kT (2 \times 500 \times 10^3) 100 \right\}^{1/2} \Rightarrow i_m =$$

$$2.6 \text{ pA}/\sqrt{\text{Hz}}.$$

7.26 (a) Denoting the voltage at the opamp output pin as V_1 , we have, by KVL at V_m and V_o ,

$$\frac{V_o - V_i}{mR} = I_i + \frac{V_i - V_1}{1/smC}, \quad \frac{V_1 - V_o}{R} = \frac{V_o}{1/sC} + \frac{V_o - V_i}{mR}.$$


Eliminating V_1 gives

$$V_o = \frac{mRI_i + [1 + s(m+1)mRC]V_i}{1 + s(m+1)mRC + s^2 m m R^2 C^2}$$

$$= \text{HLP } mRI_i + (\text{HLP} + \text{HBP})V_i.$$

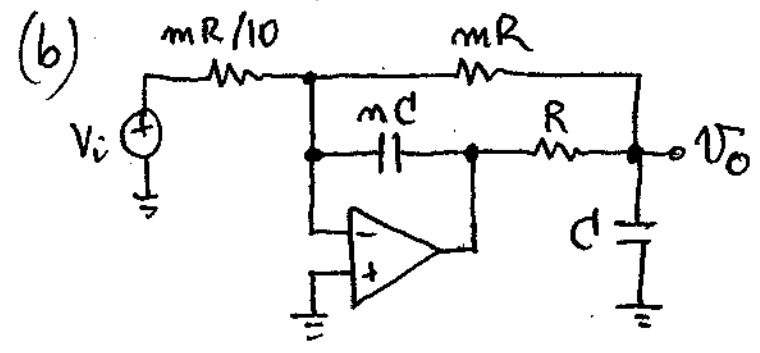7.20

$$f_0 = 1/[2\pi\sqrt{mR}RC], \quad Q = \sqrt{m/m}/(m+1).$$





7.29 $m=1; Q=1/2 \Rightarrow m=1; R=1/(2\pi \times 100 \times 0.1 \times 10^{-6}) = 15.9 \text{ k}\Omega.$

```


Problem 7.27:
.subckt noisyOA vP vN vO
*enw = 20 nV/sqrt(Hz), fce = 200 Hz:
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=6.41E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 20k
*inpw = 0.5 pA/sqrt(Hz), fcip = 2 kHz:
IDp 0 21 dc 3.12uA
Dp 21 0 Dp
.model Dp D (KF=6.41E-16,AF=1)
Cp 21 22 1GF
vsp 22 0 dc 0V
fp 0 1 vsp 0.5
*innw = 0.5 pA/sqrt(Hz), fcin = 2 kHz:
IDn 0 31 dc 3.12uA
Dn 31 0 Dn
.model Dn D (KF=6.41E-16,AF=1)
Cn 31 32 1GF
vsn 32 0 dc 0V
fn 0 vN vsn 0.5
*Noiseless op amp (a0 = 200V/mV, fb = 5 Hz):
ea0 5 0 1 vN 200k
Req 5 6 1
Ceq 6 0 31.83mF
ebuf vO 0 6 0 1
.ends noisyOA
*Main circuit:
Vi 1 0 ac 1V
Ri 1 0 1
RF 2 4 15.9k
CF 2 3 0.1uF
R 3 4 15.9k
C 4 0 0.1uF
XOA 1 2 3 noisyOA
.ac dec 10 0.01Hz 1MegHz
.noise v(4) vi 10
.probe
.end

```

7.21

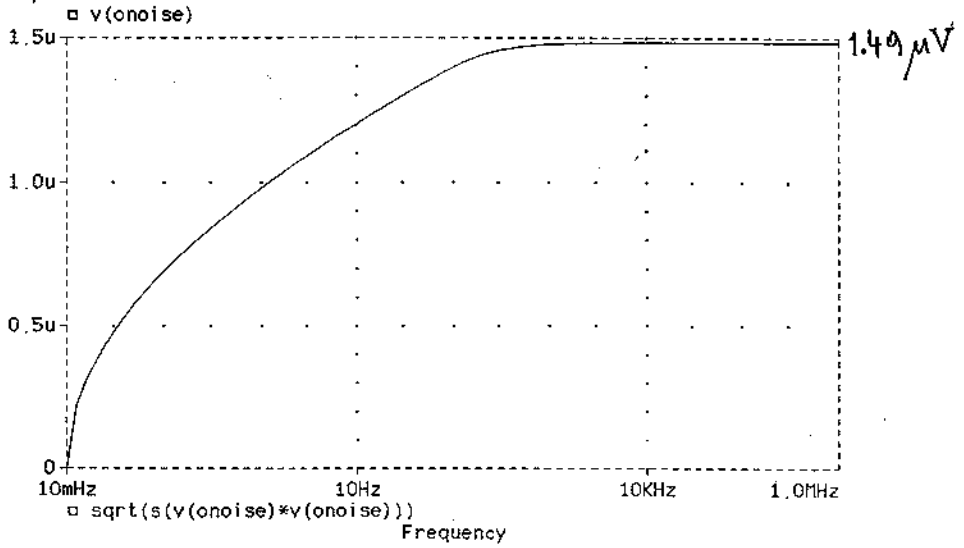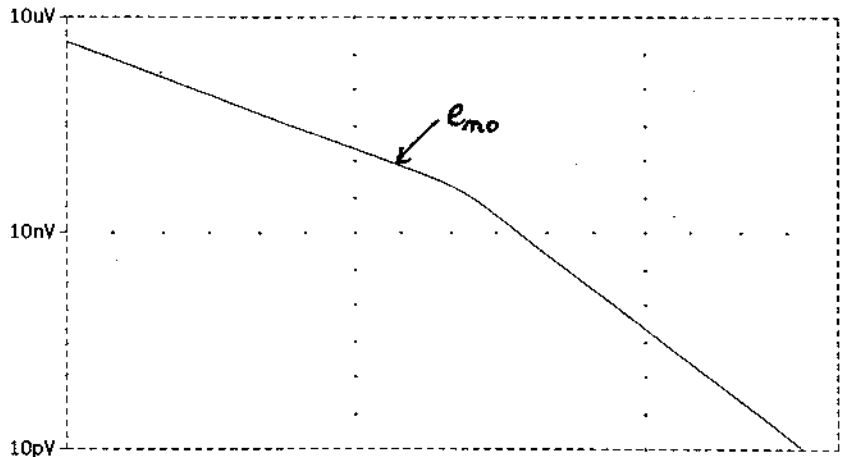

7.28

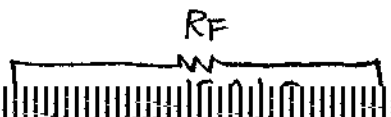


7.22


Problem 7.28:

```
.subckt noisyOA vP vN vO
*enw = 3 nV/sqrt(Hz), fce = 2.7 Hz:
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=8.6E-19,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 3k
*inpw = 0.4 pA/sqrt(Hz), fcip = 140 Hz:
IDp 0 21 dc 3.12uA
Dp 21 0 Dp
.model Dp D (KF=4.5E-17,AF=1)
Cp 21 22 1GF
vsp 22 0 dc 0V
fp 0 1 vsp 0.4
*innw = 0.4 pA/sqrt(Hz), fcin = 140 Hz:
IDn 0 31 dc 3.12uA
Dn 31 0 Dn
.model Dn D (KF=4.5E-17,AF=1)
Cn 31 32 1GF
vsn 32 0 dc 0V
fn 0 vN vsn 0.4
*Noiseless op amp (a0 = 8V/uV, fb = 1 Hz):
ea0 5 0 1 vN 8Meg
Req 5 6 1
Ceq 6 0 159mF
ebuf vO 0 6 0 1
.ends noisyOA
*Main circuit:
*LT009 noise model
*enw = 118 nV/sqrt(Hz), fce = 30 Hz:
IDz 0 41 dc 3.12uA
Dz 41 0 Dz
.model Dz D (KF=4.8E-18,AF=1)
Cz 41 42 1GF
vsz 42 0 dc 0V
hz 100 0 vsz 118k
Rz 100 0 1
R3 100 200 15.9k
C3 200 0 10uF
Vi 1 200 ac 1V
Ri 1 200 1
RF 2 4 15.9k
CF 2 3 1uF
R 3 4 15.9k
C 4 0 1uF
XOA 1 2 3 noisyOA
.ac dec 10 0.01Hz 1MegHz
.noise v(4) vi 10
.probe
.end
```

7.23

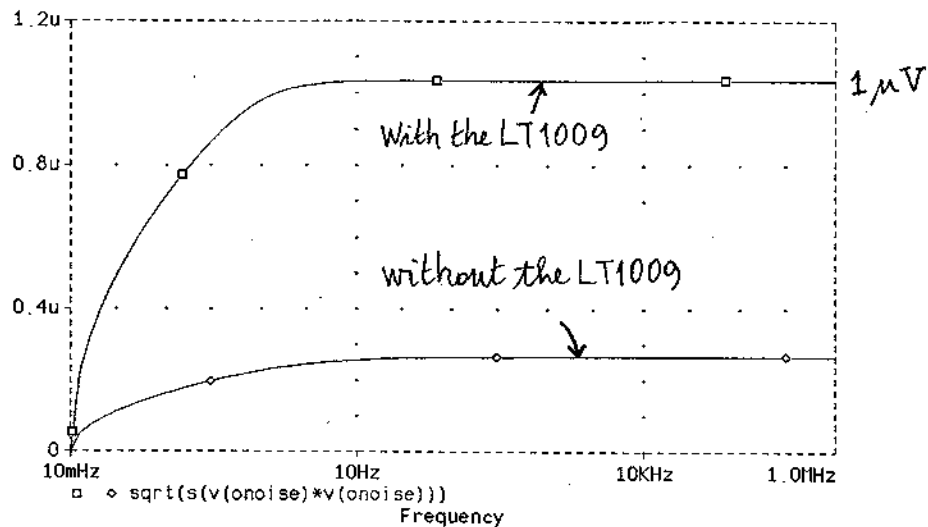

7.29

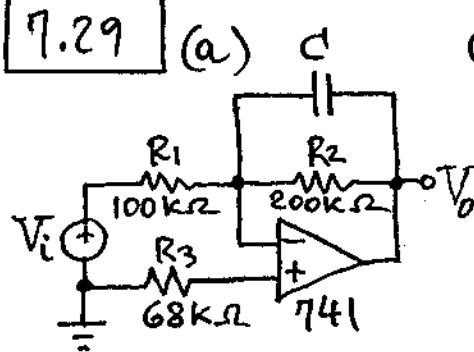

$$C = 1 / (2\pi \times 10^3 \times 200 \times 10^3) = 795 \text{ pF. It is easily seen that}$$

$$\frac{1}{\beta} = \frac{1}{\beta_0} \frac{1 + j(f/f_z)}{1 + j(f/f_p)}$$

$$\frac{1}{\beta_0} = 1 + \frac{R_2}{R_1} = 3, f_p = \frac{1}{2\pi R_2 C} = 1 \text{ kHz}, f_z = \frac{1}{2\pi R_1 / R_2 C} = 3 \text{ kHz}; \beta_{\infty} = 1 \text{ V/V}; \beta_{\infty} f_c = 1 \text{ MHz.}$$

We identify two types of noise:

1. Noninverting input noise,

consisting of e_n , e_{R_3} , and $R_3 i_n$. This noise is amplified by A_n , where $A_n \approx 1/\beta$ for $f < 1 \text{ MHz}$, and $A_n \approx a$ for $f > 1 \text{ MHz}$. The pink noise tangent indicates that most noise comes from the vicinity of 1 MHz , where $|A_n| \approx 1 \text{ V/V}$. Thus,

$$E_{\text{no1}} = [(e_{nw}^2 + R_3^2 i_{nw}^2 + 4kTR_3) \times 1.57 \times 10^6]^{1/2} =$$

9.24

$$[(20 \times 10^{-9})^2 + (68 \times 10^3 \times 0.5 \times 10^{-12})^2 + 1.65 \times 10^{-20} \times 68 \times 10^3]^{1/2} \times (1.57 \times 10^6)^{1/2} = 64.8 \mu\text{V}.$$

2. Inverting-input noise, consisting of i_{R_1} , i_{R_2} , and i_m flowing through

$$Z_2 = \frac{R_2}{1 + j(f/f_p)} = \frac{200 \text{ k}\Omega}{1 + j(f/10^3)}.$$

Denoting the density of this noise as i_2 ,

$$\text{we have } i_2^2 = i_m^2 + i_{R_1}^2 + i_{R_2}^2 = i_m^2 +$$

$$4kT/(R_1 \parallel R_2), \text{ where } R_1 \parallel R_2 = 100 \parallel 200 = 67 \text{ k}\Omega. \text{ Thus,}$$

$$i_2^2 = (0.5 \times 10^{-12})^2 \left(\frac{2000}{f} + 1 \right) + \frac{1.65 \times 10^{-20}}{67 \times 10^3}$$

$$\approx (0.7 \times 10^{-12})^2 \left(\frac{10^3}{f} + 1 \right).$$

The corresponding output power density is

$$e_{\text{no2}}^2 = |Z_2|^2 i_2^2 = (200 \times 10^3 \times 0.7 \times 10^{-12})^2 \times$$

$$\left(\frac{10^3}{f} + 1 \right) \frac{1}{1 + (f/10^3)^2}$$

$$= (140 \text{ mV})^2 \left(\frac{10^3}{f} + 1 \right) \frac{1}{1 + (f/10^3)^2}.$$

For $f < 10^3 \text{ Hz}$, $e_{\text{no2}}^2 \approx (140 \text{ mV})^2 \frac{10^3}{f}$, so

$$\text{that } E_{\text{no2}}(1) = (140 \text{ mV}) \times [10^3 \ln(10^3/0.01)]^{1/2} = 15 \mu\text{V}.$$

For $f > 10^3 \text{ Hz}$, $e_{\text{no2}}^2 \approx (140 \text{ mV})^2 \left(\frac{10^3}{f} \right)^2$, so that

7.25


$$E_{no2}(2) = (140 \text{ mV}) \times \left[\int_{10^3}^{\infty} \frac{10^6}{f^2} df \right]^{1/2} = 140 \times \left\{ 10^6 \left[-\frac{1}{f} \right]_{10^3}^{\infty} \right\}^{1/2} = 4.43 \mu\text{V}. \text{ Thus, } E_{no2} =$$

$$(15^2 + 4.43^2)^{1/2} \approx 16 \mu\text{V}. \text{ Finally, } E_{no} = (E_{no1}^2 + E_{no2}^2)^{1/2} = (64.8^2 + 16^2)^{1/2} = 67 \mu\text{V}.$$

Using the capacitor reduces E_{no} from $154 \mu\text{V}$ to $67 \mu\text{V}$; however, it also reduces the signal gain bandwidth from 333 kHz to 1 kHz .

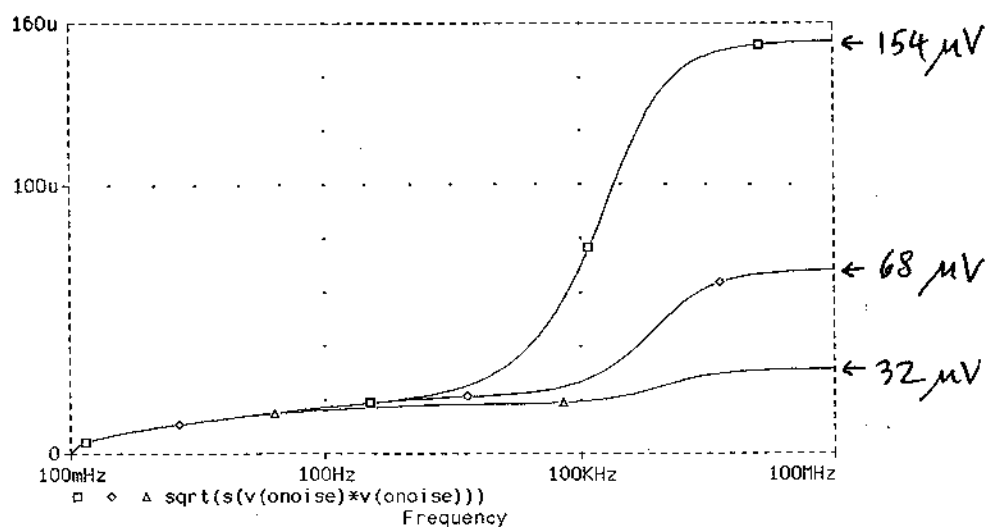(b) Let $f_3 = 1/(2\pi \times 68 \times 10^3 \times 0.1 \times 10^{-6}) = 23 \text{ Hz}$. Such a low corner frequency renders the effect of i_{mp} and i_{R_3} insignificant, so that we now have $E_{no1} \approx e_n \sqrt{1.57 f_c} = 20 \text{ mV} \sqrt{1.57 \times 10^6} = 25 \mu\text{V}$. Then, $E_{no} = (25^2 + 16^2)^{1/2} = 29.7 \mu\text{V}$, which is less than half the noise without the $0.1 \mu\text{F}$ cap.

The above results are confirmed by PSpice:



7.26

7.30


```
Problem 7.30 (enoe)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G ;avoids floating nodes
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1u;***zero innw
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
G2 2 3 2 3 1E-7;***noiseless R2
C2 2 3 0.5pF
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.30 (enoi)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 1u;***zero enw
Rhe 1 vP 1G ;avoids floating nodes
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
```

7.27


```
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
G2 2 3 2 3 1E-7;***noiseless R2
C2 2 3 0.5pF
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.30 (enoR)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 1u;***zero enw
rhe 1 vP 1G ;avoids floating nodes
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1u;***zero innw
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
R2 2 3 10Meg
C2 2 3 0.5pF
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.30 (eno)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
```

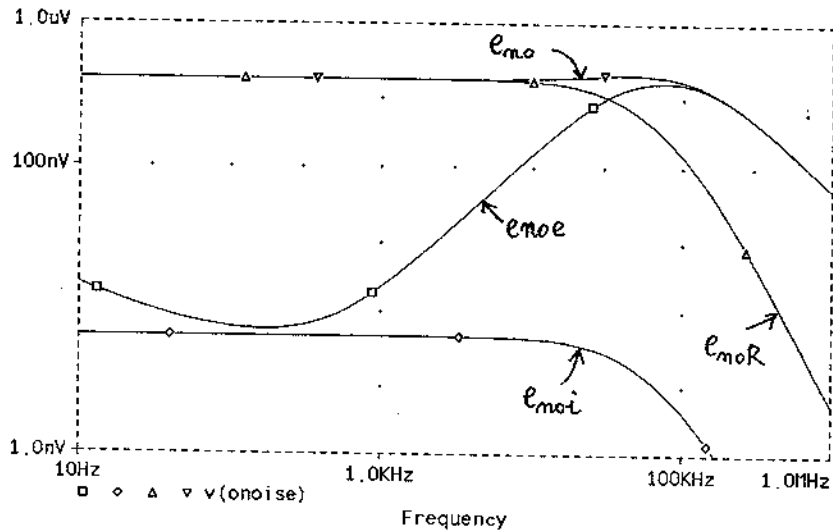7.28

```
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G ;avoids floating nodes
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
R2 2 3 10Meg
C2 2 3 0.5pF
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
```



7.29

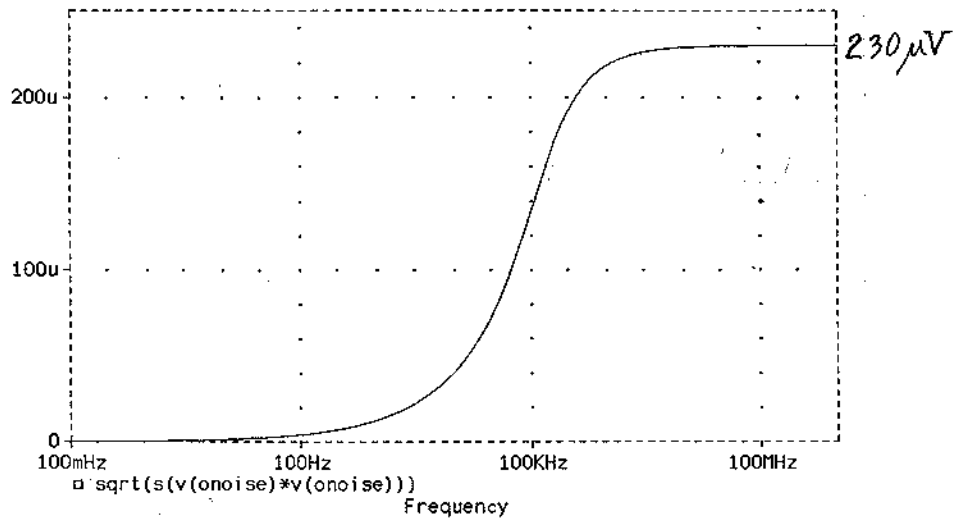

7.31 Adding a 2-pF capacitance in parallel with R_2 increase C_2 by a factor of 5. The main effect is to lower f_p from 31.8 kHz to $31.8/5 = 6.3$ kHz, lower $1/\beta_{00}$ from 91 V/V to 19.2 V/V, and rise f_x from 176 kHz to 833 kHz. We can estimate the new total noise as


$$E_{no(\text{new})} \cong E_{no(\text{old})} \frac{19.2}{91} \sqrt{833/176} \cong 222/2.18$$

$= 102 \mu\text{V}$. These results are confirmed by the accompanying PSpice program, which indicates a bandwidth reduction from 35 kHz to 6.3 kHz, and a noise reduction from $230 \mu\text{V}$ to $107 \mu\text{V}$.

7.30

```
Problem 7.31 (with C2 = 2.5 pF)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G ;avoids floating nodes
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
R2 2 3 10Meg
C2 2 3 2.5pF
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
```

7.31

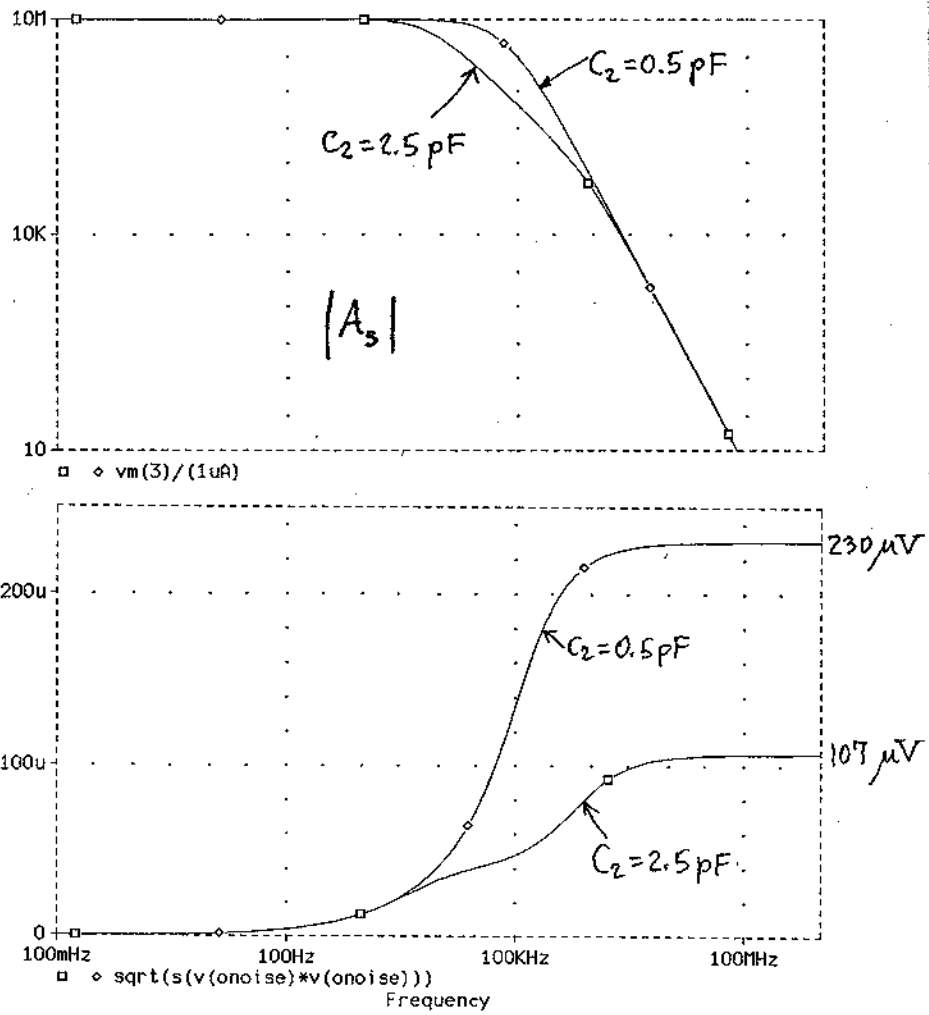


7.32 The accompanying PSpice program and displays indicate that adding a filter with $C_c = 0.5 \text{ pF}$, $R_3 = 1 \text{ k}\Omega$, and $C_3 = 10 \text{ nF}$, lowers noise from $230 \mu\text{V}$ to $80 \mu\text{V}$, while the half-power bandwidth is lowered from 35 kHz to 24 kHz .



7.32

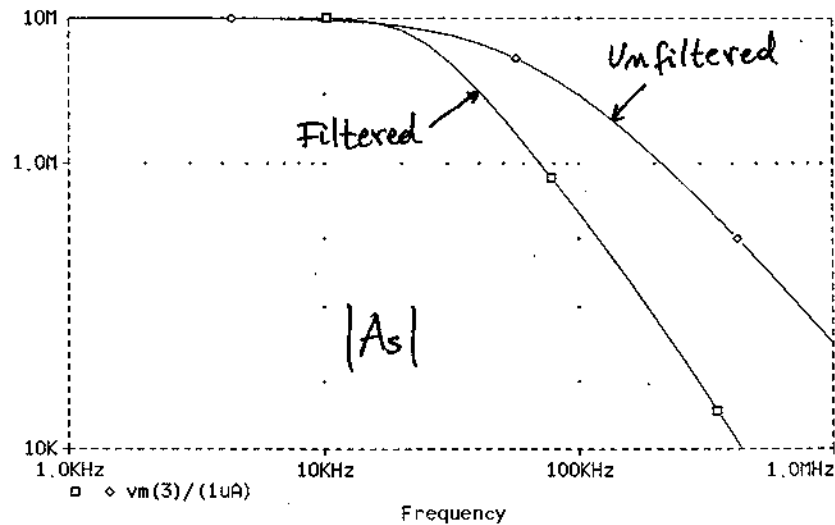Problem 7.32


```
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz), fcin = 0
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
R2 2 3 10Meg
C2 2 3 0.5pF
Cc 2 4 0.5pF
R3 3 4 1k
C3 3 0 10nF
X1 0 2 4 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
```



7.33

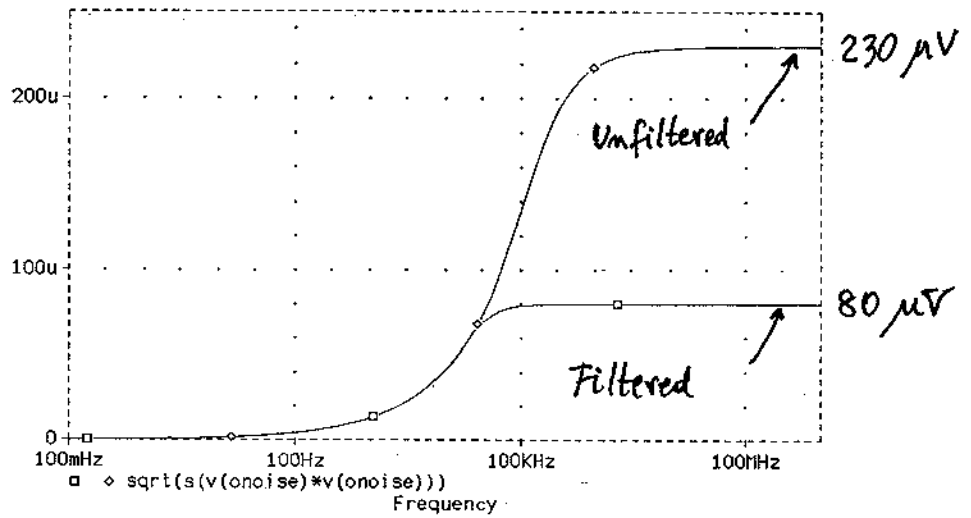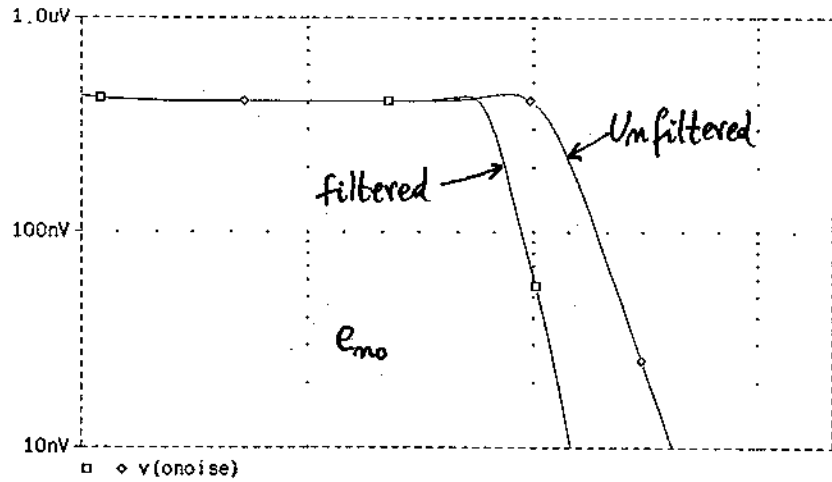

7.33

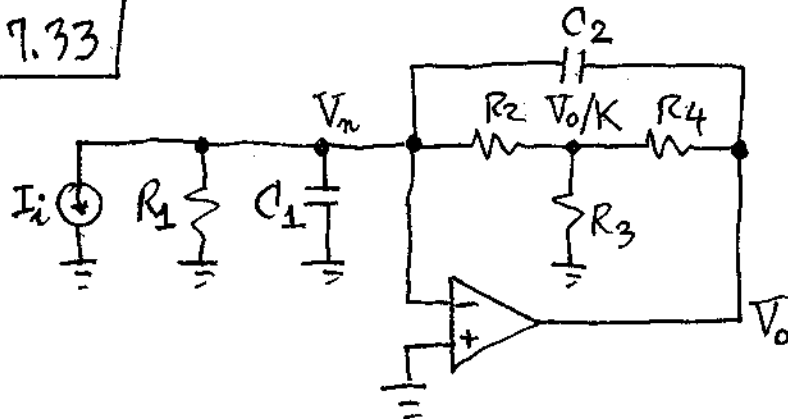

Let $(R_3 \parallel R_4) \ll R_2$, so that $R_{eq} = KR_2$, $K = 1 + R_4/R_3$.

$\beta = (V_n/V_o)_{I_i=0}$. Applying KCL at node V_n ,

$$\frac{V_o/K - V_n}{R_2} + \frac{V_o - V_n}{1/sC_2} = \frac{V_n}{R_1/(1+sR_1C_1)} + I_i \Rightarrow$$

7.34

$$V_o(1+sKR_2C_2) = KV_m \left[1 + sR_2(C_1+C_2) + \frac{R_2}{R_1} \right] + KR_2I_i.$$

$$\frac{1}{\beta} = \frac{V_o}{V_i} \Big|_{I_i=0} = \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_4}{R_3} \right) \frac{1+jf/f_z}{1+jf/f_p},$$

$$f_z = \frac{1}{2\pi(R_1 \parallel R_2)(C_1+C_2)}, \quad f_p = \frac{1}{2\pi(1+R_4/R_3)R_2C_2};$$

$$A_s(\text{ideal}) = \frac{V_o}{I_i} \Big|_{V_m=0} = \frac{(1+R_4/R_3)R_2}{1+jf/f_p}; \quad f_x = \frac{f_t}{1+C_1/C_2}$$


$$A_m = \frac{1}{\beta} \frac{1}{1+jf/f_x}; \quad A_s = A_s(\text{ideal}) \frac{1}{1+jf/f_x}.$$

7.34 $1/\beta_0 \cong 1 + R_4/R_3 = 10 \text{ V/V}; 1/\beta_{\infty} = 1 + C_1/C_2 = 91 \text{ V/V}; f_z = 3.5 \text{ kHz}; f_p = 32 \text{ kHz}; f_x = \beta_{\infty} f_t = 176 \text{ kHz}. E_{\text{noe}} \cong 91 \times 4.5 \times 10^{-9} [1.57 \times (176 - 3.5) 10^3]^{1/2} = 213 \mu\text{V}; E_{\text{nor}} = [(1 + R_4/R_3)kT/C_2]^{1/2} = 287 \mu\text{V}; E_{\text{no}} \cong (213^2 + 287^2)^{1/2} = 357 \mu\text{V}. \text{ This is confirmed by Pspice.}$

7.95

```
Problem 7.34
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1uA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 45pF
R2 2 4 1Meg
C2 2 3 0.5pF
R3 4 0 2k
R4 4 3 18k
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
```

7.36

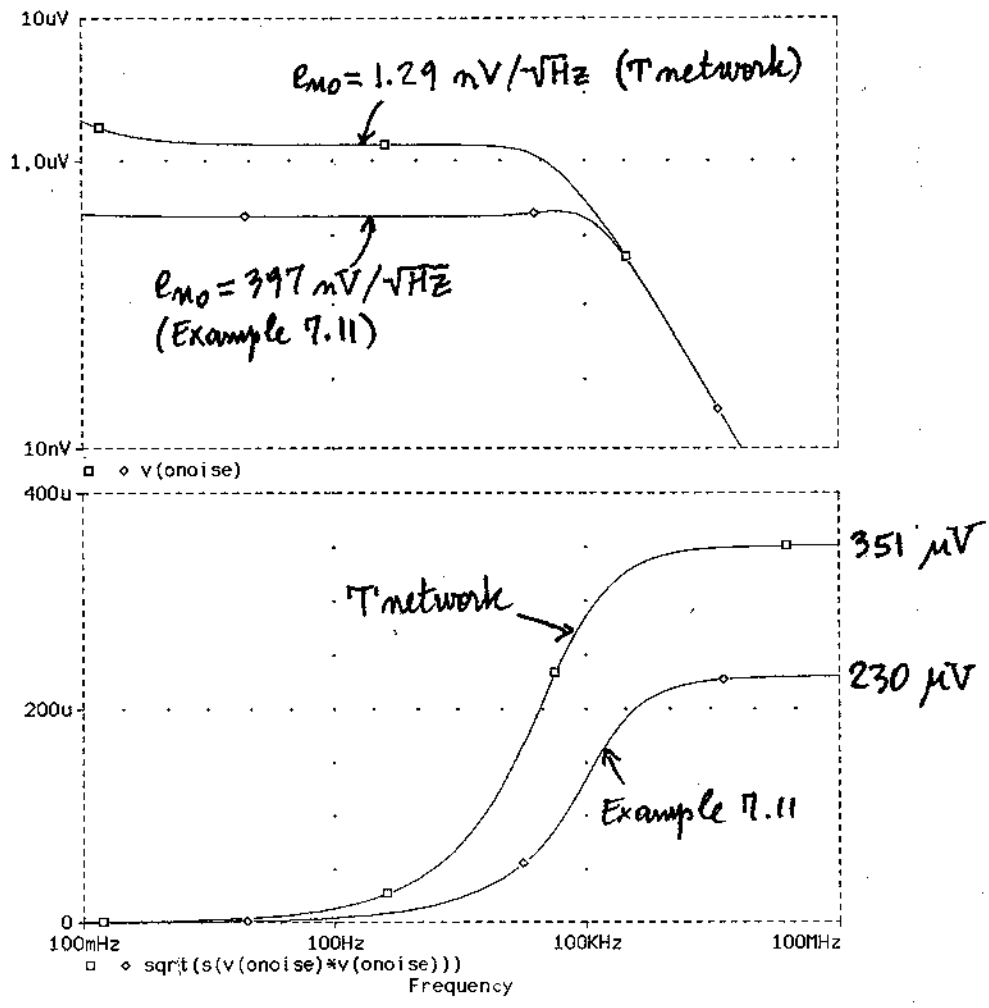

7.35

```

Problem 7.35
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
  
```

7.37




```
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1nA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 2nF
R2 2 4 36.5Meg
C2 2 3 0.5pF
R3 4 0 1k
R4 4 3 26.7k
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.35 (enoe)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1u;***Zero in
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1nA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 2nF
G2 2 4 2 4 27.4E-9; ***noiseless 36.5Meg
C2 2 3 0.5pF
R3 4 0 1k
R4 4 3 26.7k
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.35 (enoR)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
```

7.38

```
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5u;***zero en
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1u;***zero in
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1nA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 2nF
R2 2 4 36.5Meg
C2 2 3 0.5pF
R3 4 0 1k
R4 4 3 26.7k
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
Problem 7.35 (enoi)
.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5u;***zero en
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vsi 22 0 dc 0V
fi 0 vN vsi 1
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
```

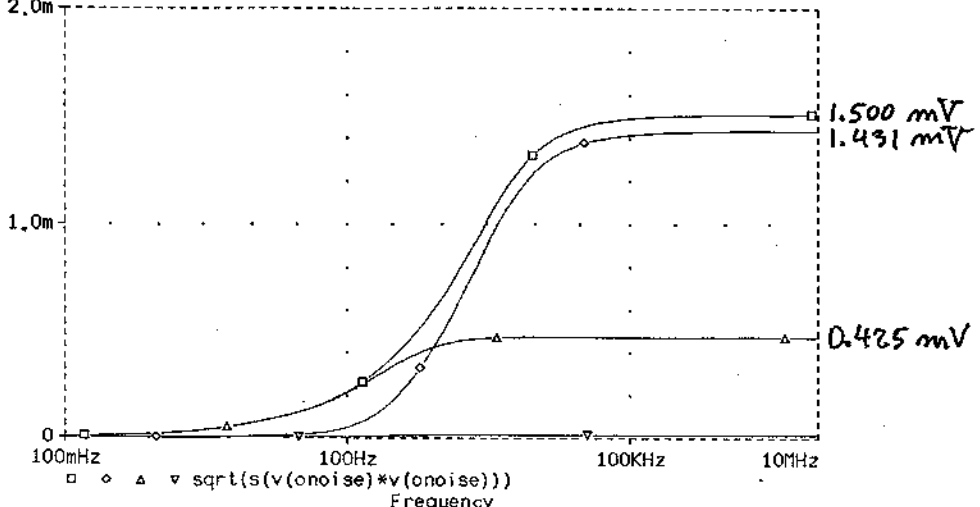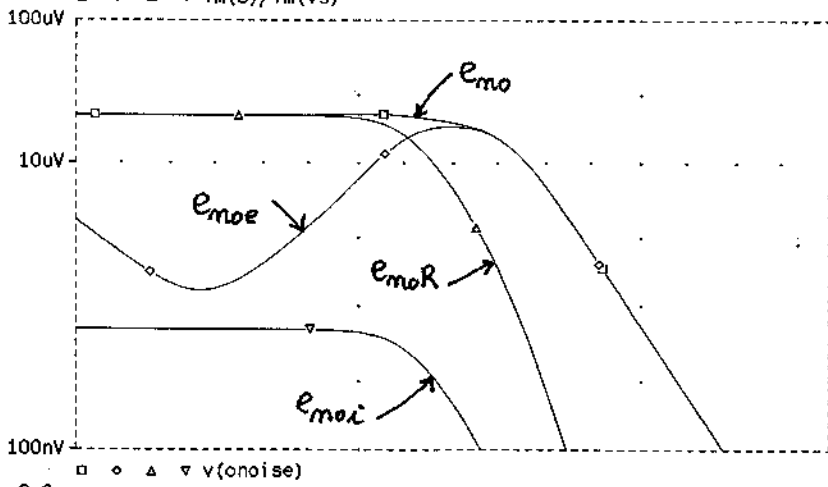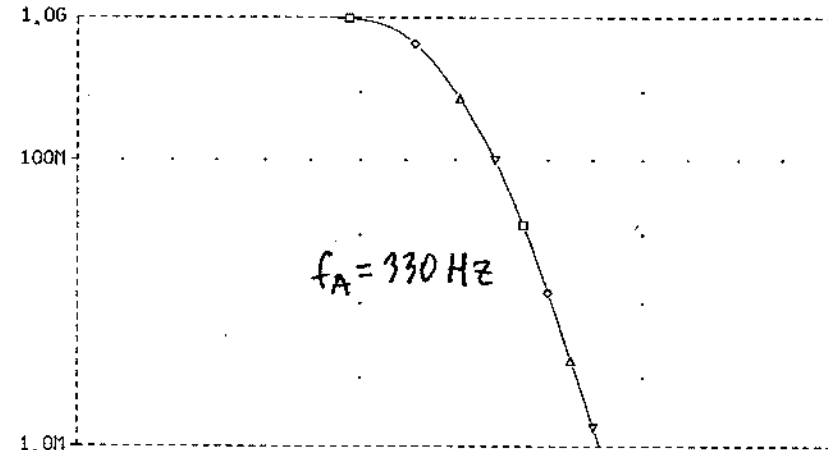
7.39

```
Ii 2 1 ac 1nA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 2nF
g2 2 4 2 4 27.4E-9;***noiseless 36.5Meg
C2 2 3 0.5pF
R3 4 0 1k
R4 4 3 26.7k
X1 0 2 3 opa
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end
```



7.40

7.36

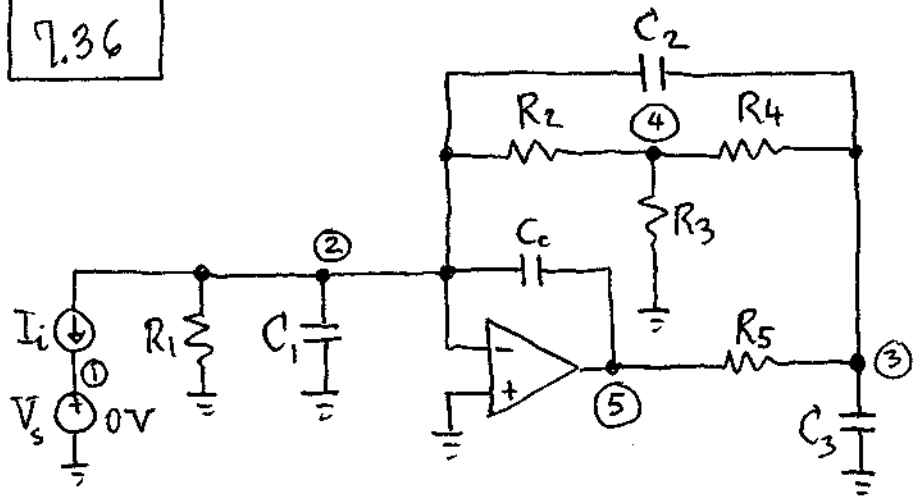

Problem 7.36


```

.subckt opa vP vN vO
*enw = 4.5 nV/sqrt(Hz), fce = 100 Hz
IDe 0 11 dc 3.12uA
De 11 0 De
.model De D (KF=3.204E-17,AF=1)
Ce 11 12 1GF
vse 12 0 dc 0V
he 1 vP vse 4.5k
Rhe 1 vP 1G
*innw = 0.566 fA/sqrt(Hz)
IDi 0 21 dc 1pA
Di 21 0 Di
.model Di D (KF=0)
Ci 21 22 1GF
vs1 22 0 dc 0V
fi 0 vN vs1 1
*Noiseless op amp:
*a0 = 1V/uV, fb = 16 Hz, ft = 16 MHz
ea0 2 0 1 vN 1Meg
Req 2 3 1
Ceq 3 0 9.947mF
ebuf vO 0 3 0 1
.ends opa
*Main circuit:
Ii 2 1 ac 1nA
Vs 1 0 dc 0
R1 2 0 100G
C1 2 0 2nF
R2 2 4 36.5Meg
C2 2 3 0.5pF
R3 4 0 1k
R4 4 3 26.7k
X1 0 2 5 opa
Cc 2 5 0.3pF
R5 5 3 5k
C3 3 0 100nF
.ac dec 10 0.1Hz 1GHz
.noise V(3) Vs 10
.probe
.end

```

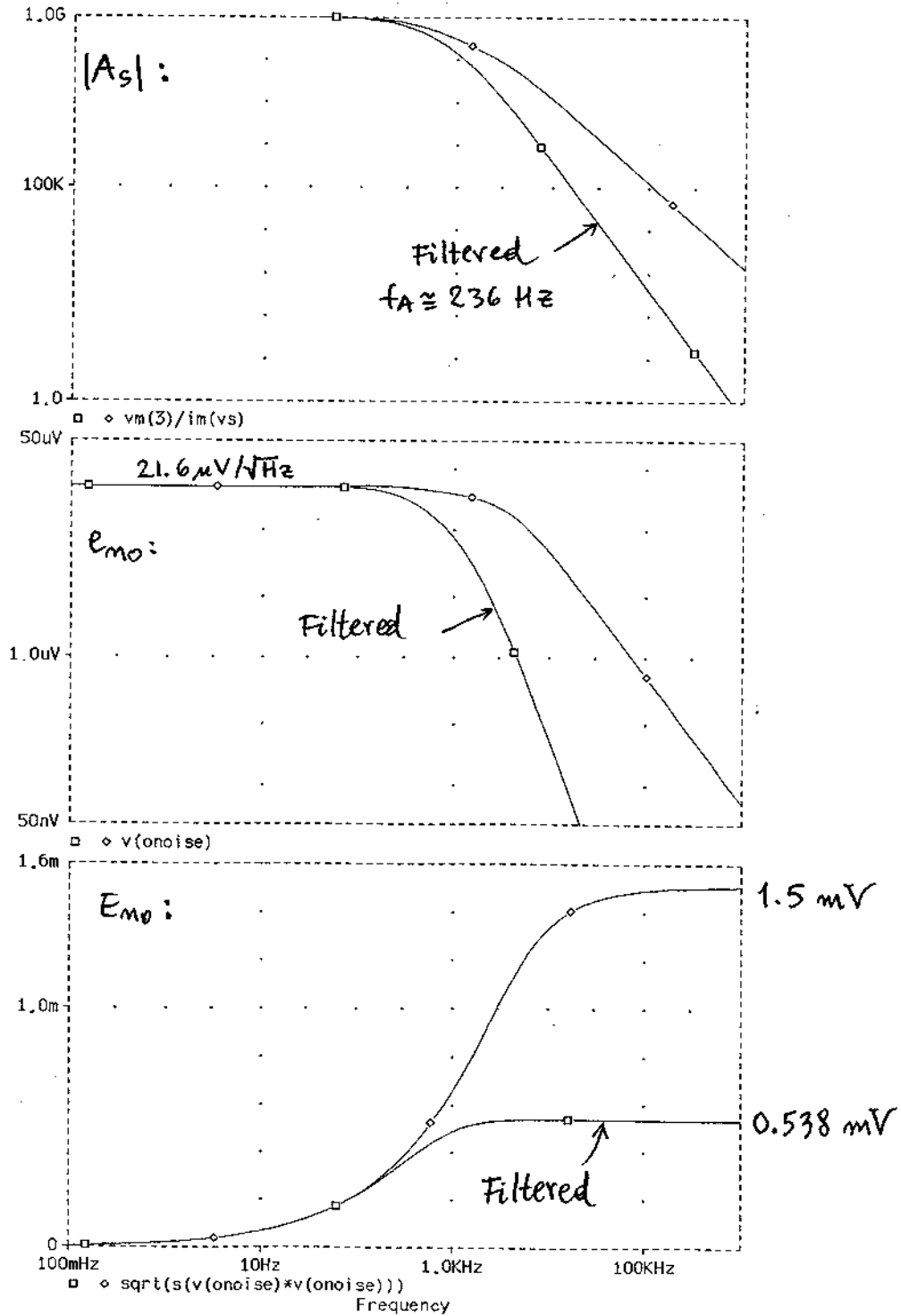
7.41

Using a filter with $C_2 = 0.3 \mu\text{F}$, $R_5 = 5 \text{ k}\Omega$, and $C_3 = 0.1 \mu\text{F}$ reduces E_{no} from 1.5 mV to $530 \mu\text{V}$ at the price of a bandwidth reduction from 330 Hz to 236 Hz .



7.37

(a) Summing noise densities in RMS

$$\text{fashion gives } e_{mo}^2 = (e_{m1}/N)^2 + (e_{m2}/N)^2 + \dots + (e_{mN}/N)^2 \\ = N(e_m/N)^2 = e_m^2/N, \text{ or } e_{mo} = e_m/\sqrt{N}.$$

(b) Imposing $e_{mR}^2 + e_m^2 \leq (1.1e_m)^2$, orwe get $R \leq$ For instance, with $e_m = 10 \text{ mV}/\sqrt{\text{Hz}}$ $10^{-2} \text{ k}\Omega$