
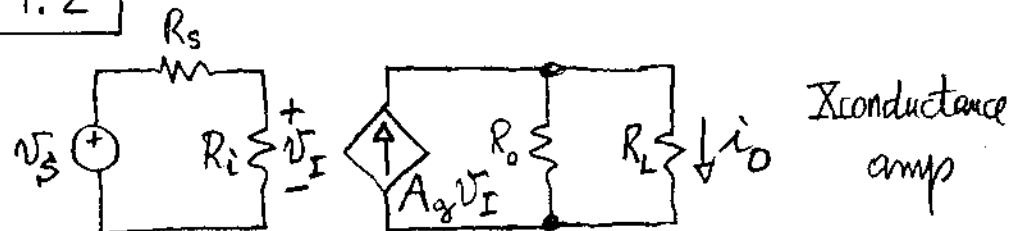


1.1


1.1 $75 \text{ mV} = (100 \text{ mV})R_i / (100 \text{ k}\Omega + R_i) \Rightarrow R_i = 300 \text{ k}\Omega$. $2 = (A_{oc} \times 75 \text{ mV}) 10 / (R_o + 10)$, and $1.8 = (A_{oc} \times 75 \text{ mV}) (30 // 10) / [R_o + (30 // 10)]$; Solving gives $A_{oc} = 40 \text{ V/V}$, $R_o = 5 \Omega$.

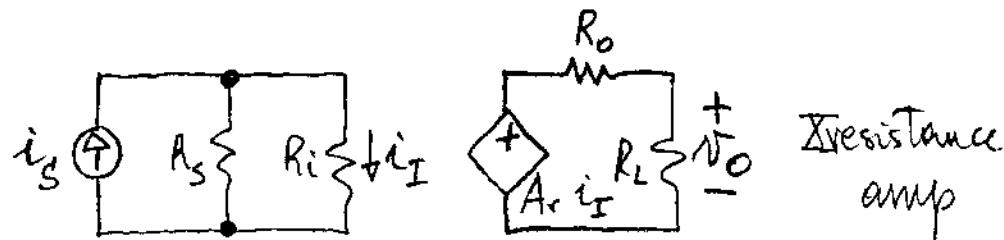1.2

$$i_O = \frac{R_i}{R_s + R_i} A_g \frac{R_o}{R_o + R_L} V_S$$



$$V_O = \frac{R_s}{R_s + R_i} A_v \frac{R_L}{R_o + R_L} i_S$$

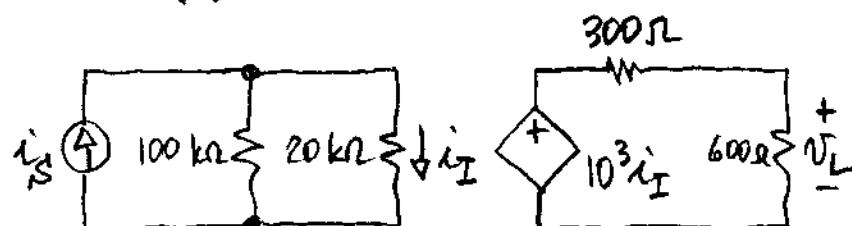1.3 (a)

$$V_L/i_S = \frac{100}{100+20} 10^3 \frac{600}{300+600} = \frac{5}{6} 10^3 \frac{2}{3} = 0.5 \text{ V/mA}$$

$$P_S = [(100 // 20) \text{ k}\Omega] i_S^2 = 16.6 \times 10^3 i_S^2; P_L = V_L^2 / 600;$$

$$P_L/P_S = (V_L/i_S)^2 / (16.6 \times 10^3 \times 600) = 30.86 \text{ mW/W}.$$

$$(b) A_v = 1.8 \text{ V/mA}; 0.1 \text{ W/W}.$$

1.2

1.4

$$25 \text{ mV} = (30 \text{ mV}) R_L / (100 \text{ k}\Omega + R_i) \Rightarrow$$

$R_L = 500 \text{ k}\Omega$. $0.9 = (A_{oc} \times 25 \text{ mV}) R_o / (R_o + 20)$, and
 $0.8 = (A_{oc} \times 25 \text{ mV}) R_o / (R_o + 30)$; solving gives

$A_{oc} = 48 \text{ A/V}$, $R_o = 60 \Omega$. We now have

$$v_T = (33 \text{ mV}) 500 / (100 + 500) = 27.5 \text{ mV},$$

$$v_o = (48 \times 27.5 \text{ mV}) 60 / (60 + 40) = 0.792 \text{ V}.$$

1.5

$$(a) v_o = 10^4 (750.25 - 751.50) 10^{-3} = -12.5 \text{ V};$$

$$(b) v_N = 0 - (-5) / 10^4 = 0.5 \text{ mV}; (c) v_P = 5 +$$

$$5 / 10^4 = 5.0005 \text{ V}; (d) v_N = 1 - (-1 / 10^4) = 1.0001 \text{ V}.$$

1.6

$$i_{r_o} = 5 / 1 = 5 \text{ mA}; v_{r_o} = 75 \times 5 \times 10^{-3} = 0.375 \text{ V}; v_{r_d} = v_o / a = 5 / (200 \times 10^3) = 25 \mu\text{V};$$

$$i_{r_d} = (25 \mu\text{V}) / (2 \text{ M}\Omega) = 12.5 \text{ pA}.$$

1.7

$$(a) A = 1 + 200 / 100 = 3 \text{ V/V}; A = 1 + 200 / (100 + 100) = 2 \text{ V/V}; A = 1 + 200 / (100 // 100) = 5 \text{ V/V}; A = 1 + (200 + 100) / 100 = 4 \text{ V/V}; A = 1 + (200 // 100) / 100 = 5/3 \text{ V/V}. (b) A = 2 \text{ V/V}, -1 \text{ V/V}, -4 \text{ V/V}, -3 \text{ V/V}, -2/3 \text{ V/V}.$$

1.8

$$(a) 1 + R_2 / R_1 = 1 + 100 / R_1 = 5 \Rightarrow R_1 = 25 \text{ k}\Omega$$

(use $24.9 \text{ k}\Omega$).


$$(b) v_o = (1 + R_2 / R_1) v_p = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} v_I.$$

$$R_2 = 0 \Rightarrow R_4 / (R_3 + R_4) = 0.5 \Rightarrow R_3 = R_4.$$


$$R_2 = 100 \text{ k}\Omega \Rightarrow (1 + 100 / R_1) \times 0.5 = 2 \Rightarrow R_1 = \frac{100}{3}.$$

Use $R_1 = R_3 = R_4 = 33 \text{ k}\Omega$.

1.3

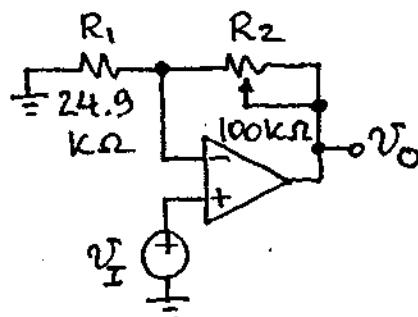

(a)

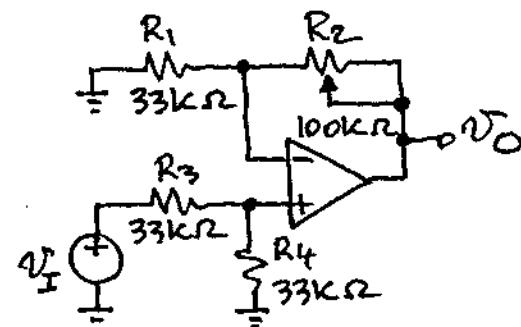

(b)

1.9

(a) $A_{\min} = 1 + 9.5/10.5 \approx 1.9 \text{ V/V}$,
 $A_{\max} = 1 + 10.5/9.5 \approx 2.1 \text{ V/V}$. For the exact calibration, implement R_2 with a 9.1-kΩ resistor in series with a 2-kΩ potentiometer connected as a variable resistor from 0 to 2 kΩ.

(b) $-1.1 \text{ V/V} < A < -0.9 \text{ V/V}$. Implement R_2 as in part (a).

1.10

$$v_O = [-10/(1+11/a)] v_I, v_N = -v_O/a.$$

(a) $v_O = -0.9479 \text{ V}, v_N \approx 10 \text{ mV}$.

(b) $v_O = -0.9989 \text{ V}, v_N \approx 0.1 \text{ mV}$.

(c) $v_O = -0.999989 \text{ V}, v_N \approx 1 \mu\text{V}$.

A gain a is increased, v_O approaches -1 V and v_N approaches 0.

1.11


$$(a) R_2/R_1 = 100/R_1 = 10 \Rightarrow R_1 = 10 \text{ k}\Omega.$$

$$(b) v_O = -[(R_2+R_3)/R_1] v_I.$$

$$R_2 = 0 \Rightarrow R_3/R_1 = 1; R_2 = 100 \text{ k}\Omega \Rightarrow$$

$$(R_3+100)/R_1 = 10 \Rightarrow 1 + 100/R_1 = 10 \Rightarrow R_1 = 100/9 = 11.11 \text{ k}\Omega. \text{ Use } R_1 = R_3 = 11 \text{ k}\Omega.$$


1.4

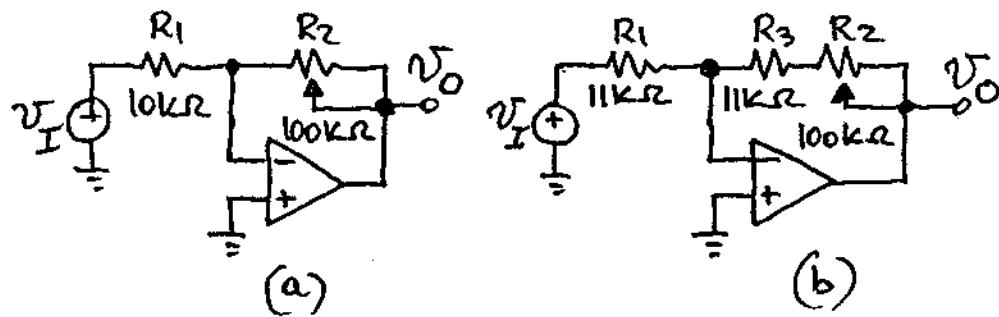

1.12

$$V_O = -[100/(10+20)] \times 2 = -3.33 \times 2 =$$

$$-6.67 \text{ V.}$$

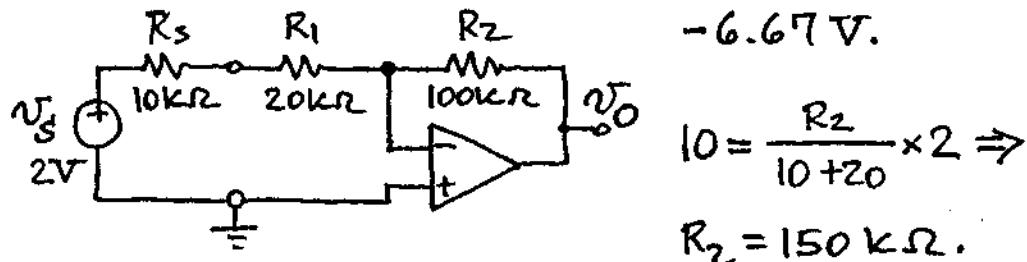


$$10 = \frac{R_2}{10+20} \times 2 \Rightarrow$$

$$R_2 = 150 \text{ k}\Omega.$$


1.13

(a)

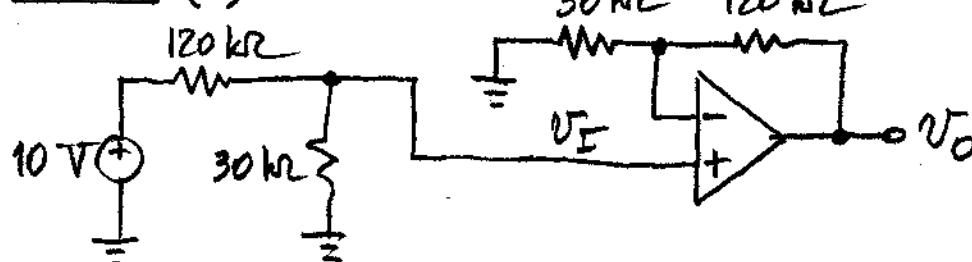

$$V_I = \frac{30}{120+30} 10 = 2 \text{ V}; V_O = \left(1 + \frac{120}{30}\right) 2 = 10 \text{ V.}$$

(b)

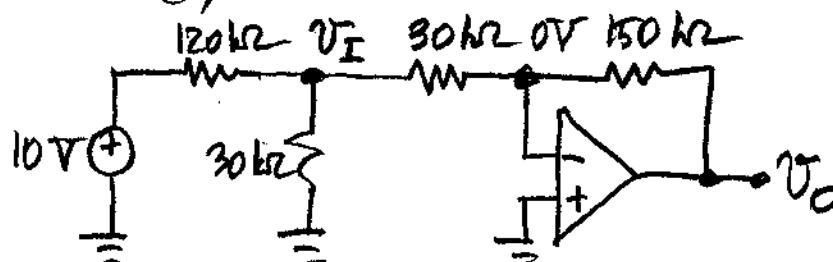


$$V_I = \frac{30/30}{120+(30/30)} 10 = 1.1 \text{ V}; V_O = -\frac{150}{30} 1.1 = -5.5 \text{ V.}$$


In (a) there is no loading by the amplifier; in (b) there is loading.

1.5

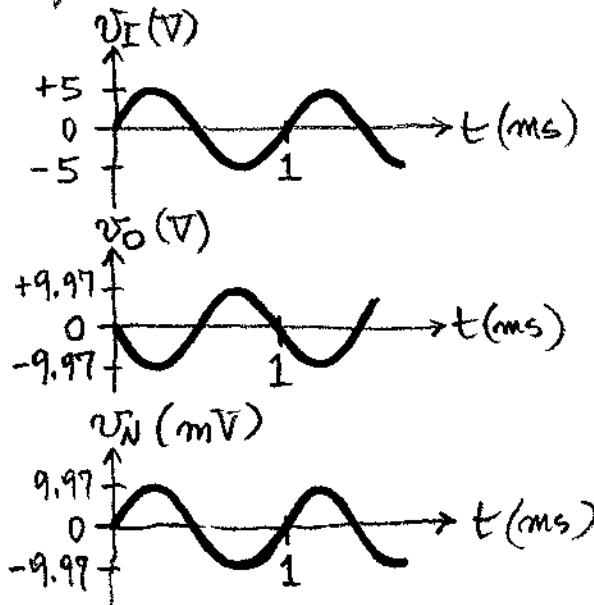1.14 $v_o = A v_i$, $A = (-20/10)/(1+3/10^3) = -1.994$
 $V/V; v_N = -v_o/10^3.$



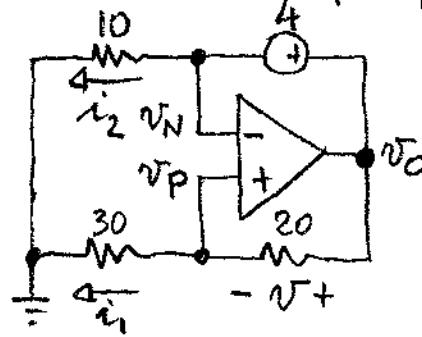
1.15 Since opamp keeps $v_N = v_p$, we have



$v = 4 \text{ V}$. Then, $i_1 = 4/20 = 0.2 \text{ mA}$; $v_N = v_p = 30 i_1 = 6 \text{ V}$; $v_o = v_N + 4 = 10 \text{ V}$;
 $i_2 = v_N/10 = 0.6 \text{ mA}$;
 $P_{4V} = 4 i_2 = 2.4 \text{ mW}$.

To check, recompute v_N and v_p and verify that $v_N = v_p$. KVL: $v_N = v_o - 4 = 6 \text{ V}$; voltage divider: $v_p = v_o 30/(30+20) = 6 \text{ V}$; so, $v_N = v_p$.

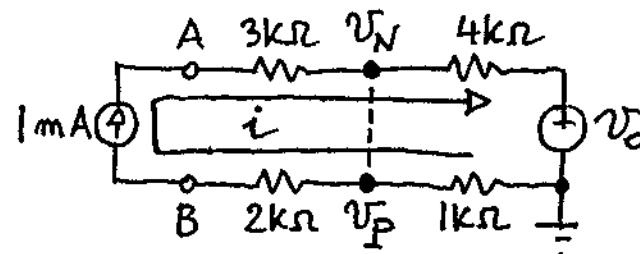1.16 (a) Virtual short keeps $v_N = v_p$;



however, no current flows through it.
Using Ohm's

1.6

law and KVL, $v_p = -1 \times I = -1V$; $v_N = v_p = -1V$; $v_o = v_N - 4 \times i = -1 - 4 = -5V$. Moreover, $v_A = v_N + 3 \times i = -1 + 3 = +2V$; $v_B = v_p - 2 \times i = -1 - 2 = -3V$.

(b) Now source sees $5\text{ k}\Omega$ in parallel with $(3\text{ k}\Omega + R_{VS} + 2\text{ k}\Omega) = 5\text{ k}\Omega$. By the current divider formula we now have $i = (1\text{ mA}) \times 5 / (5+5) = 0.5\text{ mA}$. Then, $v_p = -0.5V$, $v_N = -0.5V$, $v_o = -2.5V$, $v_A = +1V$, $v_B = -1.5V$.

1.17 (a) $v_N = v_p = [10 / (10 + 40)] v_o = 0.2 v_o$.

$$(v_s - v_N) / 50 = (v_N - v_o) / 20 \Rightarrow (9 - 0.2 v_o) / 50 = (0.2 v_o - v_o) / 20 \Rightarrow v_o = -5V, v_N = v_p = -1V.$$

(b) $v_o = -10V \Rightarrow v_N = v_p = -2V$;
 $[9 - (-2)] / 50 = -2 / R + [-2 - (-10)] / 20 \Rightarrow R = 100/9\text{ k}\Omega$.

Problem 1.17(b)

```

Vs 1 0 dc 9
R1 1 2 50k ;node 2 is vN
R2 2 3 20k ;node 3 is vo
R3 0 4 10k ;node 4 is vp
R4 4 3 40k
R 2 0 11.11k
eOA 3 0 4 2 1Meg
.end

```


NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	9.0000	(2)	-2.0002	(3)	-10.0010

NODE	VOLTAGE
(4)	-2.0002

1.18 (a) $V_N = V_P = [20/(20+30)]V_0 = 0.4V_0$;
 $V_0 = V_N - 10 \times 0.3 = 0.4V_0 - 3 \Rightarrow V_0 = -5 \text{ V}$,
 $V_N = V_P = -2 \text{ V}$.

(b) KCL: $0.3 + (0 - V_N)/40 = (V_N - V_0)/10$
 $\Rightarrow 0.3 - 0.4V_0/40 = (0.4V_0 - V_0)/10 \Rightarrow V_0 = -6 \text{ V}$,
 $V_N = V_P = -2.4 \text{ V}$. To check, verify that KCL is satisfied at node V_N . Current into node is $0.3 + 2.4/40 = 0.36 \text{ mA}$; current out of node is $[-2.4 - (-6)]/10 = 0.36 \text{ mA}$

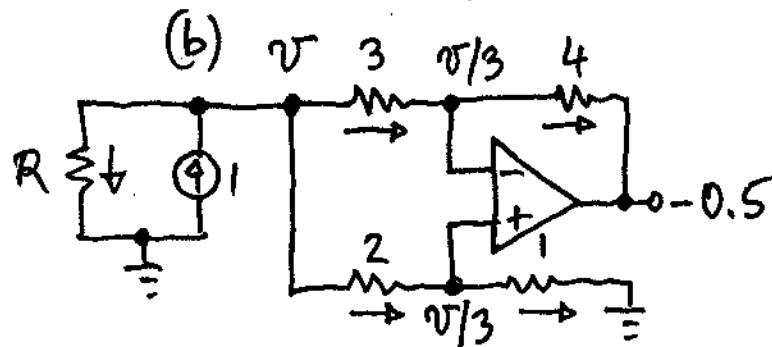1.19 (a) Since $V_N = V_P$, the $3\text{-k}\Omega$ and $2\text{-k}\Omega$ resistances appear in parallel. Hence, $i_{3\text{k}\Omega} = [2/(2+3)]i_S = 0.4 \text{ mA}$, and $i_{2\text{k}\Omega} = 0.6 \text{ mA}$.
 $V_N = V_P = 1 \times 0.6 = 0.6 \text{ V}$; $V_0 = V_N - 4 \times 0.4 = -1 \text{ V}$.




$$V_N = V_P = \frac{1}{2+1} V = V/3. \text{ KCL: } \frac{V - V/3}{3} = \frac{V/3 - (-0.5)}{4} \Rightarrow V = 0.9 \text{ V. KCL again:}$$

$$1 = \frac{0.9}{R} + \frac{0.9}{2+1} + \frac{0.9 - 0.9/3}{3} \Rightarrow R = 1.8 \text{ k}\Omega.$$

1.8

1.20

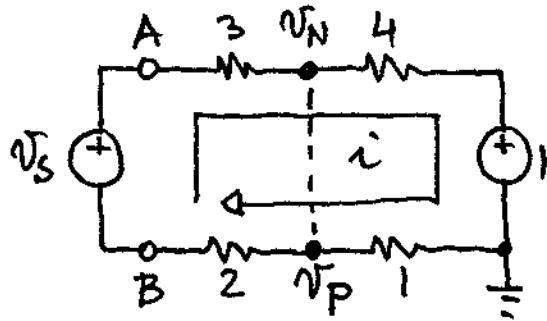
(a) Because of virtual short between v_N and v_P , we have

$$v_N = v_P \text{ and } i = \frac{v_S}{3+2} = \frac{-10}{4+1}$$

$$\Rightarrow v_S = -10 \text{ V}$$

(v_S positive @ B).

(b)

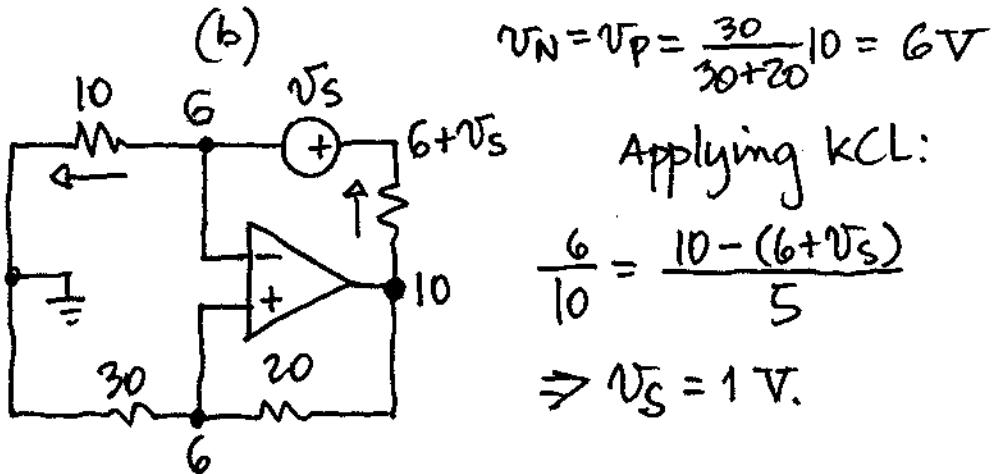

$$v_N = v_P = \frac{30}{30+20} 10 = 6 \text{ V}$$

Applying KCL:

$$\frac{6}{10} = \frac{10 - (6 + v_S)}{5}$$

$$\Rightarrow v_S = 1 \text{ V.}$$

1.21

(a) Switch open $\Rightarrow i_{R_3} = 0$; thus, $v_P = v_I$, $v_N = v_I$, $i_{R_1} = i_{R_2} = 0$, $v_O = v_I$, $A = +1 \text{ V/V}$. Switch closed $\Rightarrow v_P = 0 \Rightarrow v_O = (-R_2/R_1)v_I$.(b) Switch closed $\Rightarrow v_N = v_P = 0$, so R_4 has no effect, and $A = -R_2/R_1$ as before. Switch = open $\Rightarrow v_N = v_P = v_I$, $i_{R_1} = 0$, and $A = 1 + R_2/R_4$.(c) Impose $R_2/R_1 = 2$, and $1 + R_2/R_4 = 2$. A possible set is $R_1 = R_3 = 10 \text{ k}\Omega$, $R_2 = R_4 = 20 \text{ k}\Omega$.

1.9

1.22

(a) $v_p = k v_I$, $0 \leq k \leq 1$. Superposition:

$v_o = (-R_2/R_1)v_I + (1+R_2/R_1)k v_I \Rightarrow A = k + (k-1)R_2/R_1$; as k is varied from 0 to 1, A varies from $-R_2/R_1$ to $+1$ V/V.

(b) KCL: $(v_I - v_N)/R_1 + (v_O - v_N)R_2 = v_N/R_4$;

Substituting $v_N = v_p = k v_I$ gives $A = v_O/v_I = k(1 + R_2/R_1 + R_2/R_4) - R_2/R_1$. As k is varied from 0 to 1, A varies from $-R_2/R_1$ to $1 + R_2/R_4$.

(c) Impose $R_2/R_1 = 5$, and $1 + R_2/R_4 = 5$. A possible set is $R_1 = 4.02 \text{ k}\Omega$, $R_2 = 20.0 \text{ k}\Omega$, $R_4 = 4.99 \text{ k}\Omega$, all 1%. For R_3 , use a 10-k Ω pot.

1.23

Statement (a) is correct ($R_i = \infty$).

Statements (b) and (c) are wrong because it is v_N that follows v_p , not the other way around.

1.24

(a) $v_{p1} = v_{o2} \times R_4 / (R_3 + R_4)$, $v_{o2} = -(R_2/R_1)v_o$. Eliminating v_{o2} and letting $v_{p1} = v_{N1} = v_I$ because of the virtual short at the input of DA_1 , we get $A = v_o/v_I = -(1 + R_3/R_4) R_1/R_2$.

(b) Make $R_3 = 0$ and $R_4 = \infty$ to save components, and choose $R_2 = 1 \text{ k}\Omega$, $R_1 = 100 \text{ k}\Omega$.

1.10

1.25

(a) Wiper down $\Rightarrow V_R = 0$ and $V_L = -\frac{R_2}{10} \frac{10 \parallel 10}{R_1 + 10 \parallel 10} V_I = \frac{-0.5 R_2}{R_1 + 5} V_I$; wiper up $\Rightarrow V_L = 0$ and $V_R = \frac{-0.5 R_2}{R_1 + 5} V_I$; wiper in the middle $\Rightarrow V_L = V_R = -\frac{R_2}{10} \frac{5 \parallel 10}{R_1 + 5 \parallel 10} = -\frac{R_2}{3 R_1 + 10}$

(b) For a gain of -1 V/V at the wiper extremes, impose $0.5 R_2 = R_1 + 5$. For a gain of $-1/\sqrt{2}$ with the wiper in the middle, impose $R_2/(3R_1 + 10) = 1/\sqrt{2}$. Solving gives $R_1 = 24.14 \text{ k}\Omega$ (use $24.3 \text{ k}\Omega$), and $R_2 = 58.28 \text{ k}\Omega$ (use $59.0 \text{ k}\Omega$).


1.26

(a) Let $R_F = 330 \text{ k}\Omega$; then, $R_1 = 330/400 = 825 \Omega$ (use 820Ω); $R_2 = 330/300 = 1.1 \text{ k}\Omega$; $R_3 = 1.65 \text{ k}\Omega$ (use $1.6 \text{ k}\Omega$); $R_4 = 330/100 = 3.3 \text{ k}\Omega$.

(b) We now have $0 = -330(0.02/0.82 + -0.05/1.1 + V_3/1.6 + 0.1/3.3)$, which gives $V_3 = -14.78 \text{ mV}$.

1.27

(a)

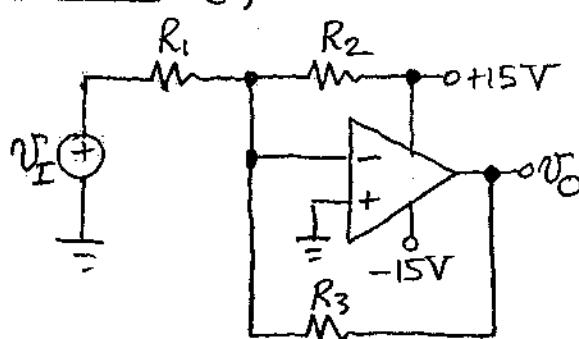


$$\begin{aligned}
 V_O &= -\frac{R_3}{R_1} V_I - \frac{R_3}{R_2} 15 \\
 &= -\frac{R_3}{R_1} \left(V_I + \frac{R_1}{R_2} 15 \right) \\
 \Rightarrow R_3/R_1 &= 10, \\
 15R_1/R_2 &= 1.
 \end{aligned}$$

1.11

Use $R_1 = 10\text{k}\Omega$, $R_2 = 150\text{k}\Omega$, $R_3 = 100\text{k}\Omega$.

(b)

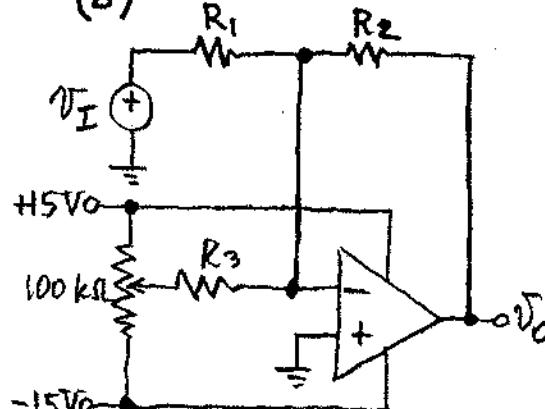we want $R_2/R_1 = 1$. Use $R_1 = R_2 = 100\text{k}\Omega$.

Let $R_3 = 300\text{k}\Omega$.
 With the wiper all the way up, we want $V_{\text{offset}} = -5\text{V}$, so
 $-5 = (-R_2/R_3)15$, or
 $R_3 = 3R_2$; moreover,

1.28

$$V_O = 2V_2 - 3V_1.$$

$$(a) 10 = 2V_2 - 3 \times 3 \Rightarrow V_2 = 9.5\text{V};$$

$$(b) 0 = 2 \times 6 - 3V_1 \Rightarrow V_1 = 4\text{V};$$


$$(c) -10 = 2V_2 - 3 \times 1 \Rightarrow V_2 = 6.5\text{V}$$

$$-10 = 2V_2 - 3 \times 1 \Rightarrow V_2 = -3.5\text{V}$$

Thus, $-3.5\text{V} \leq V_2 \leq 6.5\text{V} \Rightarrow -10\text{V} \leq V_O \leq +10\text{V}$.

1.29

(a)

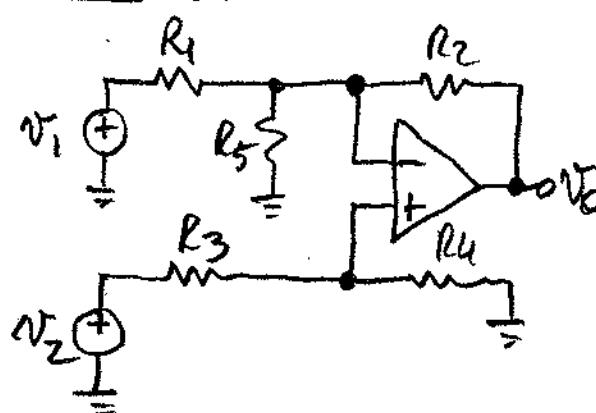


Superposition:

$$A_2 = \left(1 + \frac{R_2}{R_1/R_5}\right) \frac{R_4}{R_3 + R_4}$$

$$A_1 = -R_2/R_1.$$

(b)

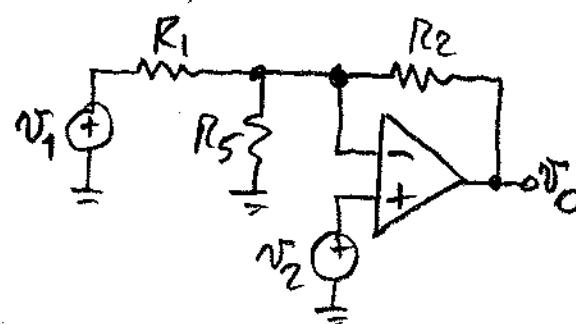

$$A_1 = -5 \Rightarrow R_2/R_1 = 5$$

$$A_2 = 10 \Rightarrow 1 + \frac{R_2}{R_1/R_5} = 10$$

Pick $R_1 = 20\text{k}\Omega$.Then, $R_2 = 100\text{k}\Omega$,
 and $R_5 = 25\text{k}\Omega$.

1.30


$$(a) V_o = 10(v_2 - v_1) = 10 \cos 2\pi 10^3 t \text{ V.}$$

(b) $V_o = -10v_1 + 11 [10/(10+10)] v_2 = 10.009 v_2 - 10v_1 \approx 0.09 \cos 2\pi 60t + 10 \cos 2\pi 10^3 t \text{ V.}$ In (a) we have a true difference amplifier, so the output comprises only the 1-kHz component; the 60-Hz component is completely suppressed. In (b), because of the mismatch in the resistance ratios, the 60-Hz component is not completely suppressed.

1.31

Grounding all inputs except v_1 gives $V_o/v_1 = -R_N/R_1 = -1 \text{ V/V.}$ Grounding all inputs except v_2 gives $V_o/v_2 = [1 + R_N/(R_1||R_3||R_5)] \times (R_p||R_4||R_6)/[R_2 + (R_p||R_4||R_6)] = [1 + R/(R/3)] \times (R/3)/(R+R/3) = 4 \times 1/4 = 1 \text{ V/V.}$ By symmetry, $V_o = v_2 + v_4 + v_6 - v_1 - v_3 - v_5.$

1.32

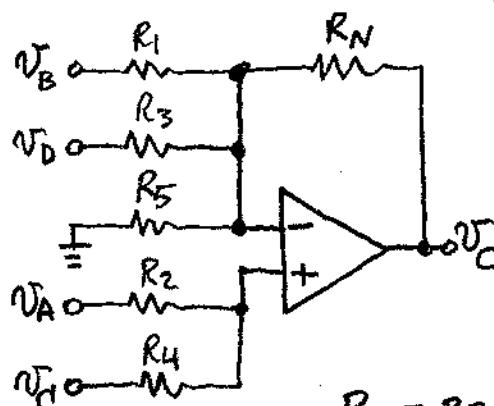

$$\begin{aligned} V_o &= -\frac{R_N}{R_1} V_B - \frac{R_N}{R_3} V_D + \\ &\quad \left(1 + \frac{R_N}{R_1||R_3||R_5}\right) \times \left(\frac{R_4}{R_2+R_4} V_A + \frac{R_2}{R_2+R_4} V_C\right). \end{aligned}$$

Let $R_1 = 10 \text{ k}\Omega.$ Then,


$$R_N = 30 \text{ k}\Omega \text{ and } R_3 = 30 \text{ k}\Omega.$$

We must have $R_4/(R_2+R_4) = 2 R_2/(R_2+R_4)$, or $R_4 = 2 R_2.$ Let $R_2 = 10 \text{ k}\Omega, R_4 = 20 \text{ k}\Omega.$ Improving $[1 + 30/(10||30||R_5)] 20/(10+20) = 4$ gives $R_5 = 30 \text{ k}\Omega.$

1.13

1.33

(a)

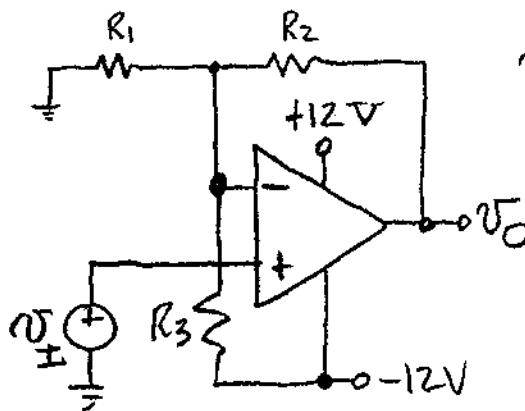

Superposition:

$$V_O = \left(1 + \frac{R_2}{R_1 \parallel R_3}\right) V_I - \frac{R_2}{R_3} (-12)$$

$$= 10 V_I + 5 \text{ V.}$$


Imposing $\frac{R_2}{R_3} 12 = 5$

gives $R_3 = 2.4 R_2$.

Use $R_2 = 10 \text{ k}\Omega$, $R_3 = 24 \text{ k}\Omega$.

Imposing $1 + \frac{10}{R_1} + \frac{10}{24} = 10$ gives $R_1 = 1.165 \text{ k}\Omega$.

(b)

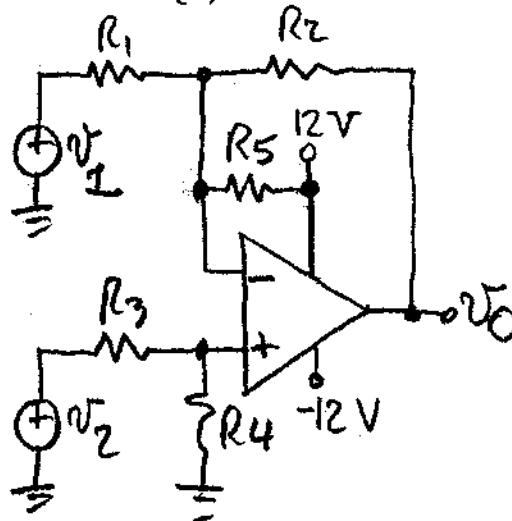

Superposition:

$$V_O = -\frac{R_2}{R_1} V_I - \frac{R_2}{R_5} 12 +$$

$$\left(1 + \frac{R_2}{R_1 \parallel R_5}\right) \frac{R_4}{R_3 + R_4} V_2$$

$$= 10 V_2 - 10 V_I - 5 \text{ V.}$$

Equating coefficients pairwise gives


$R_2 = 10 R_1$, $R_5 = 2.4 R_2$. Use $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_5 = 240 \text{ k}\Omega$. Finally, imposing

$$\left(1 + \frac{100}{10} + \frac{100}{240}\right) \frac{R_4}{R_3 + R_4} = 10 \text{ gives } R_4 = \frac{120}{17} R_3.$$

Use $R_3 = 13 \text{ k}\Omega$, $R_4 = 91 \text{ k}\Omega$.

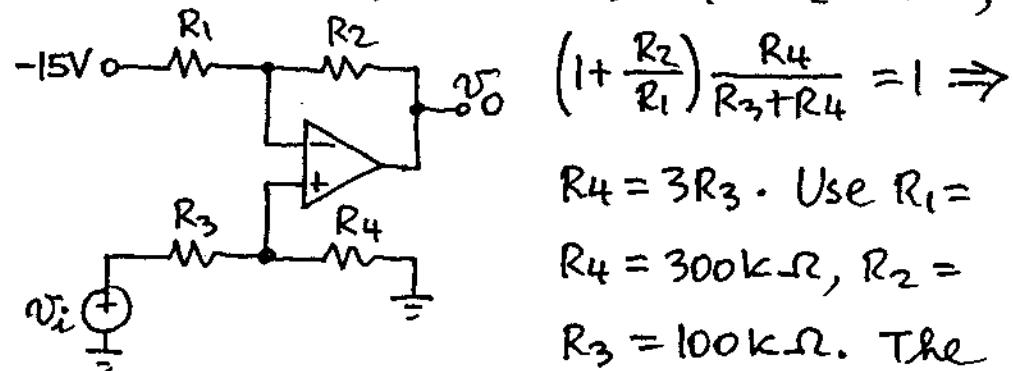1.34


$$-(R_2/R_1)(-15) = 5 \Rightarrow R_1 = 3R_2. \text{ Also,}$$



resistance seen by V_i is $R_3 + R_4 > 100\text{k}\Omega$.

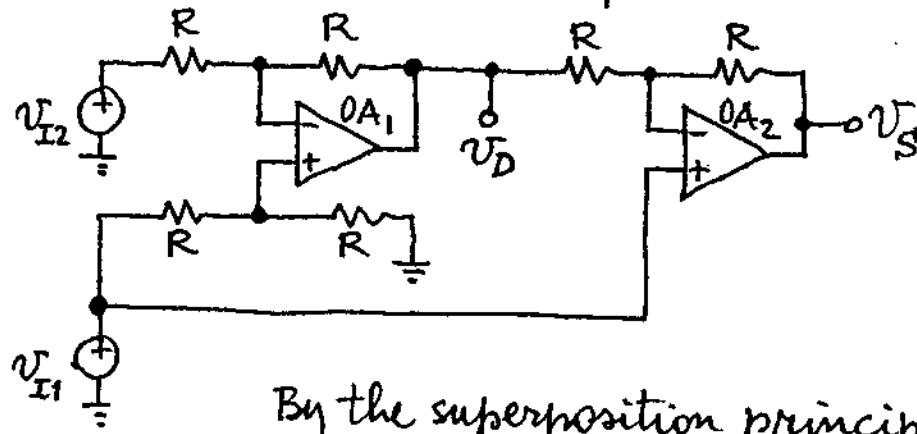1.35


$$\text{OA}_1 \text{ is a diff-amp: } V_D = V_{I1} - V_{I2}$$



By the superposition principle,
 $V_S = 2V_{I1} - V_D = V_{I1} + V_{I2}. \text{ Use } R = 100\text{k}\Omega.$

1.15

1.36

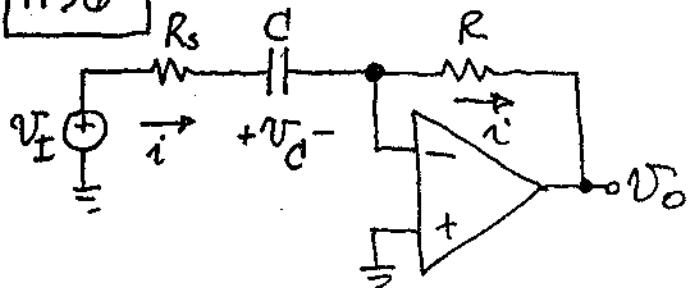


$$V_o = -Ri = -RC \frac{dV_C}{dt} = -RC \frac{d(V_I - R_s i)}{dt}$$

$$V_o = -RC \frac{dV_I}{dt} - R_s C \frac{dV_o}{dt}.$$

If V_I changes slowly, so does i , indicating that $V_C \approx V_I$. So, $V_o \approx -RC \times dV_I/dt$, indicating differentiator behavior.

If V_I changes rapidly, then the derivatives will be much greater than V_o , so we can approximate $\Delta V_o \approx -\frac{R}{R_s} \Delta V_I$, indicating amplifier behavior.

1.37

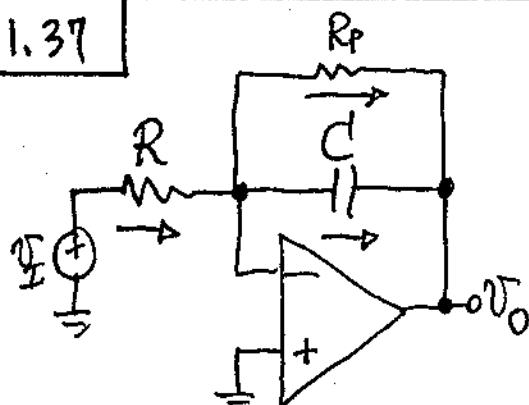

KCL:

$$\frac{V_I}{R} = C \frac{d(-V_o)}{dt} + \frac{-V_o}{R_p} \Rightarrow$$

$$dV_o = \frac{-V_I dt}{RC} - \frac{-V_o dt}{R_p C}$$

Changing t to dummy integration variable,

$$V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_I(\xi) d\xi - \frac{1}{R_p C} \int_0^t V_o(\xi) d\xi.$$

Rapidly changing V_I implies $|i_{R_p}| \ll |i_C|$, so

$$\frac{V_I}{R} \approx C \frac{d(-V_o)}{dt} \Rightarrow V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_I(\xi) d\xi,$$



1.16

indicating integrator behavior.



Slowly changing v_I implies $|i_C| \ll |i_{R_p}|$, so $\frac{v_I}{R} \approx -\frac{v_O}{R_p}$, or $v_O \approx (-\frac{R_p}{R})v_I$, indicating amplifier behavior.

1.38 $\tau = RC = 10^{-3}s$; $T = 1/100 = 10\text{ ms}$.

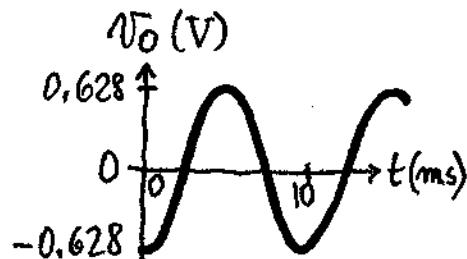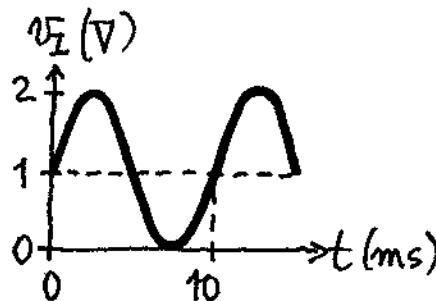(a) $v_I = 1 + 1 \sin 2\pi 10^2 t \text{ V}$; $dv_I/dt = 2\pi 10^2 \cos 2\pi 10^2 t \text{ V/s}$; $v_O = -10^{-3} \times 2\pi 10^2 \times \cos 2\pi 10^2 t = -0.628 \cos 2\pi t / 0.01 \text{ V}$.



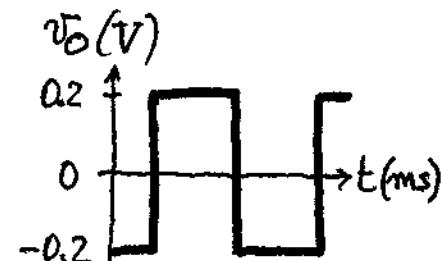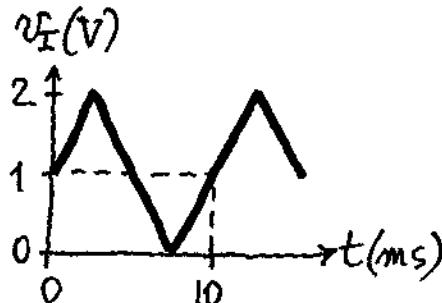
(b) $dv_I/dt = \pm 2/10^{-2} \text{ V/s} \Rightarrow v_O = \mp 10^{-3} \times 2/10^{-2} = \mp 0.2 \text{ V}$.



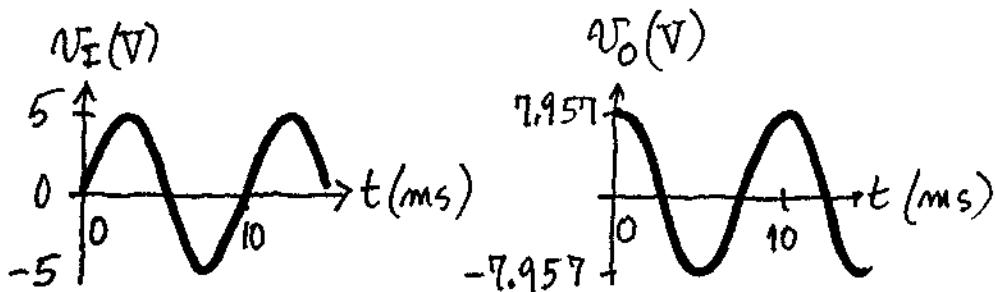
1.17

$$1.39 \quad \tau = RC = 10^{-3} \text{ s}; V_0(t) = V_0(0) - 10^3 \int_0^t V_I(\xi) d\xi.$$

$$(a) V_0 = -10^3 \int_0^t 5 \sin 2\pi 100 \xi d\xi = \\ -\frac{5 \times 10^3}{2\pi 100} (-\cos 2\pi 100 t) = 7.957 \cos 2\pi 100 t \text{ V.}$$



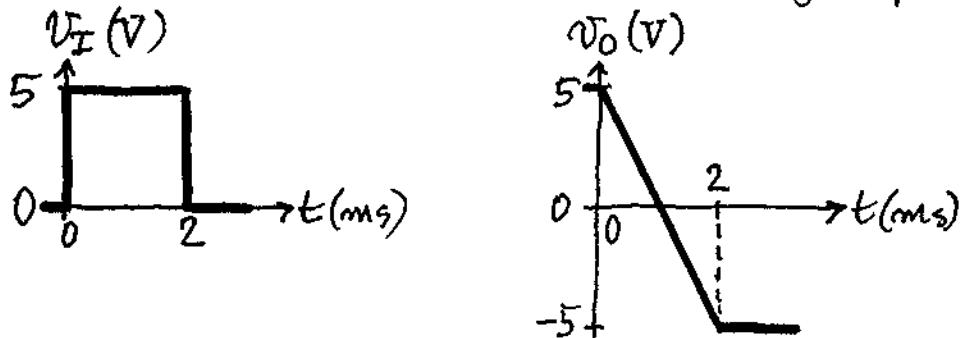
$$(b) V_0(t) = V_0(0) - 10^3 5t \text{ during the pulse.}$$




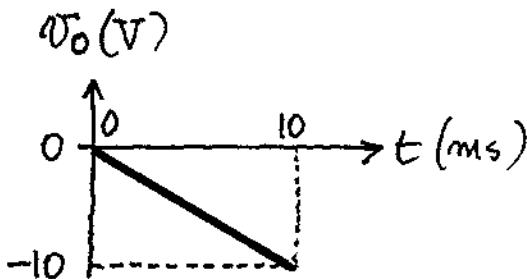1.40

$$(a) V_0 = -t/(10^4 \times 10^{-7}) = -10^3 t \text{ V.}$$


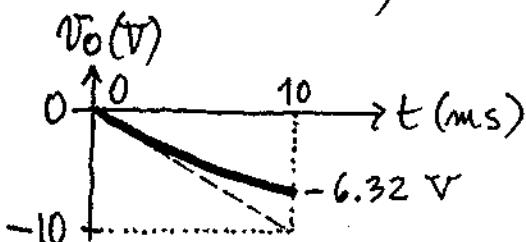
$$(b) V_0(0) = 0; V_0(\infty) = -(100/10)1 = -10 \text{ V;} \\ \tau = R_2 C = 10 \text{ ms;} V_0 = -10(1 - e^{-t/(10 \text{ ms})}) \text{ V.}$$




1.18

1.41

$$(a) i_1 + i_2 + i_3 = i_C \Rightarrow V_1/R_1 + V_2/R_2 + V_3/R_3 = C d(V - V_0)/dt \Rightarrow V_0(t) = V_0(0) - \left(\frac{1}{R_1 C} \int_0^t V_1 d\varsigma + \frac{1}{R_2 C} \int_0^t V_2 d\varsigma + \frac{1}{R_3 C} \int_0^t V_3 d\varsigma \right).$$

(b) $1/(R_1 \times 10^{-8}) = 10^3 \Rightarrow R_1 = 100 \text{ k}\Omega$; likewise, $R_2 = 50 \text{ k}\Omega$ and $R_3 = 200 \text{ k}\Omega$.

1.42

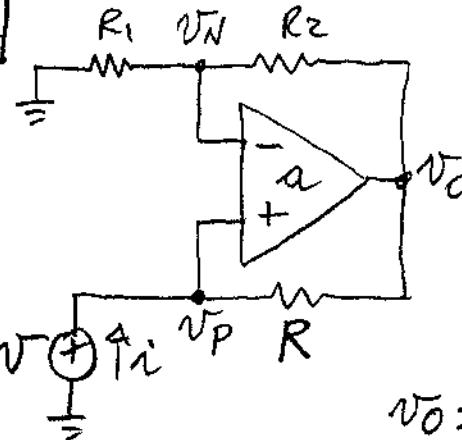

$$V_0 = \alpha (V_p - V_N),$$

$$V_p = V$$

$$V_N = \frac{R_1}{R_1 + R_2} V_0.$$

Substituting gives

$$V_0 = \frac{(R_1 + R_2)\alpha}{R_1 + R_2 + R_1\alpha} V.$$


$$i = \frac{V_p - V_0}{R} = \frac{1}{R} \left[V - \frac{(R_1 + R_2)\alpha}{R_1 + R_2 + R_1\alpha} V \right]$$

$$= \frac{1}{R} \frac{R_1 + R_2 - \alpha R_2}{R_1 + R_2 + \alpha R_1} V = - \frac{1}{R} \frac{R_2}{R_1} \frac{\alpha - 1 - R_1/R_2}{\alpha + 1 + R_2/R_1} V$$

$$R_{eq} = \frac{V}{i} = -R \frac{R_1}{R_2} \frac{1 + (1 + R_2/R_1)/\alpha}{1 - (1 + R_1/R_2)/\alpha}.$$

1.43

Equivalent circuit :

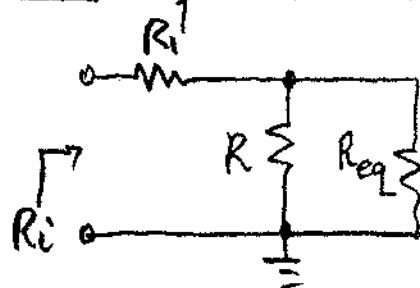


$$R_{eq} = -R_2 \frac{R_1}{R_2} = -R_1;$$

$$R_i = R_1 + (R \parallel -R_1)$$

$$R_i = R_1 - \frac{RR_1}{R-R_1} = \frac{R_1}{1-R/R_1}.$$

$R_i > 0$ for $R < R_1$; $R_i < 0$ for $R > R_1$;
 $R_i = 0$ for $R = R_1$.

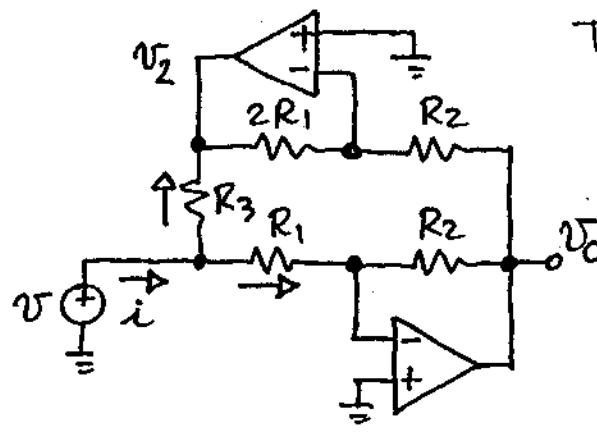1.44 (a) $v_o = -(R_2/R_1)v$, $v_2 = -(2R_1/R_2)v_o$



Thus, $v_2 = 2v$.

$$\begin{aligned} i &= \frac{v}{R_1} + \frac{v-v_2}{R_3} \\ &= v\left(\frac{1}{R_1} - \frac{1}{R_3}\right). \end{aligned}$$

$$\begin{aligned} R_{eq} &= v/i = \\ &R_1 R_3 / (R_3 - R_1). \end{aligned}$$

(b) $R_1 = R_3 = 10.0 \text{ k}\Omega$, $2R_1 = 20.0 \text{ k}\Omega$,
 $R_2 = |A|R_1 = 100 \text{ k}\Omega$.

1.45 (a) $\beta = 10^{-3} \text{ V/V}$; $T = \alpha\beta = 100$; $A = (1/\beta) \times 1/(1+1/T) = 10^3/(1+1/100) = 990 \text{ V/V}$; deviation
is -1% ; $v_o = Av_i = 9.9 \text{ V}$; $v_d = v_o/\alpha = 99 \mu\text{V}$; $v_f = \beta v_o = 9.9 \text{ mV}$.

(b) $\beta = 10^{-2} \text{ V/V}$; $T = 10^3$; $A = 99.9 \text{ V/V}$;
deviation $= -0.1\%$; $v_o = 0.999 \text{ V}$; $v_d = 9.99 \mu\text{V}$; $v_f = 9.99 \text{ mV}$.

(c) $\beta = 10^{-1} \text{ V/V}$; $T = 10^4$; $A = 9.999 \text{ V/V}$;
deviation $= -0.01\%$; $v_o = 99.99 \text{ mV}$; $v_d = 999.9 \text{ nV}$, $v_f = 9.999 \text{ mV}$.


(d) $\beta = 1 \text{ V/V}$; $T = 10^5$; $A = 0.99999 \text{ V/V}$;
deviation $= -10 \text{ ppm}$; $v_o = 9.9999 \text{ mV}$; $v_d = 99.999 \text{ nV}$, $v_f = 9.9999 \text{ mV}$.

1.46 (a) $1+\alpha\beta = \alpha/A = 10$; $\beta = (10-1)/\alpha = 0.009$. (b) $\alpha = 900 \Rightarrow A = 900/(1+900 \times 0.009) = 98.90$ (exactly); $\Delta A/A \cong (\Delta\alpha/\alpha)/(1+\alpha\beta) = -0.1/10 = -0.01 \Rightarrow A = 10^2(1-0.01) = 99$ (appx). (c) $\alpha = 500 \Rightarrow A = 500/(1+500 \times 0.009) = 90.91$ (exactly); $\Delta A/A \cong -0.5/10 = -0.05 \Rightarrow A = 10^2(1-0.05) = 95.00$ (appx). Observations: A dramatic drop in α of 50% affects A by less than 10%; approximated calculations give results a bit more optimistic than exact calculations.

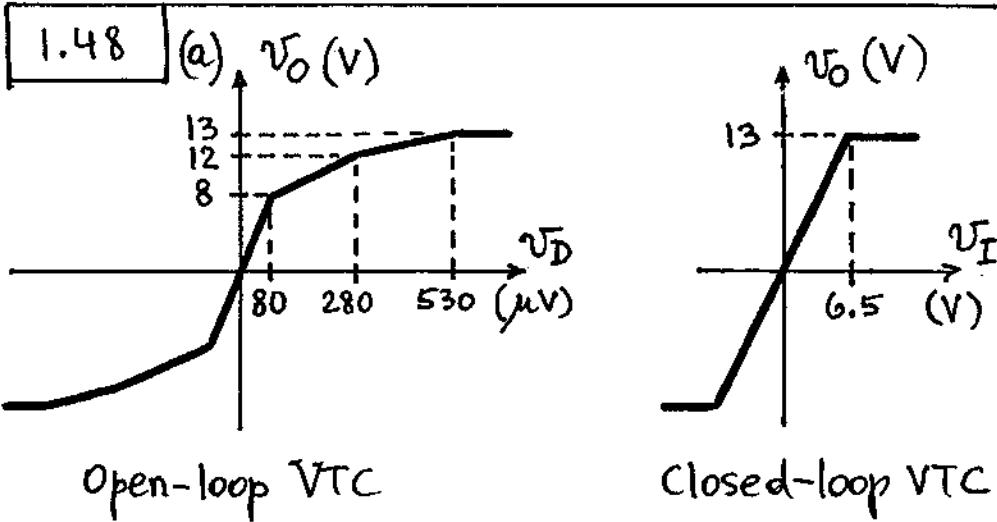1.47 $A = 100 \text{ V/V} \pm 0.1\%$; $\alpha = 10^4 \text{ V/V} \pm 25\%$.

We need to desensitize the $\pm 25\%$ variation to 0.1%, or $1+\alpha\beta = 250$. With a single stage we would have $1+\alpha\beta = \alpha/A = 10^4/10^2 = 100 < 250$.


Try a cascade of two stages with individual gains $A_1 = A_2 = 10 \text{ V/V}$. Then, $1+\alpha\beta_1 = \alpha/A_1 = 10^4/10 = 10^3 > 250$. $\beta_1 = \beta_2 = (10^3 - 1)/\alpha = 0.0999 \text{ V/V}$. Using $A = A_1 \times A_2 = A_1^2 = [\alpha/(1+\alpha\beta_1)]^2$, we find that as gain α varies over the range 9,500 V/V to 12,500 V/V, gain A varies over the range 99.93 V/V to 100.04 V/V, i.e. within $\pm 0.1\%$.



Slope of open-loop VTC is 100,000 for $|v_o| < 8V$, 20,000 for $8V < |v_o| < 12V$, and 4,000 for $12V < |v_o| < 13V$. Using $A = 2/(1 + 2/a)$, the corresponding slopes of the closed-loop VTC are 1.99996, 1.9998, and 1.999, respectively. These values are virtually indistinguishable from 2.

(b) Since $v_o \approx 2v_i$, v_o is essentially an undistorted $\pm 10V$ triangular wave. $v_o(t)$ is obtained from $v_i(t)$ using the open-loop VTC in reverse. We see that thanks to the high loop gain, the amplifier provides an undistorted output while reflecting the effect of nonlinear open-loop VTC back to the error input.

1.22

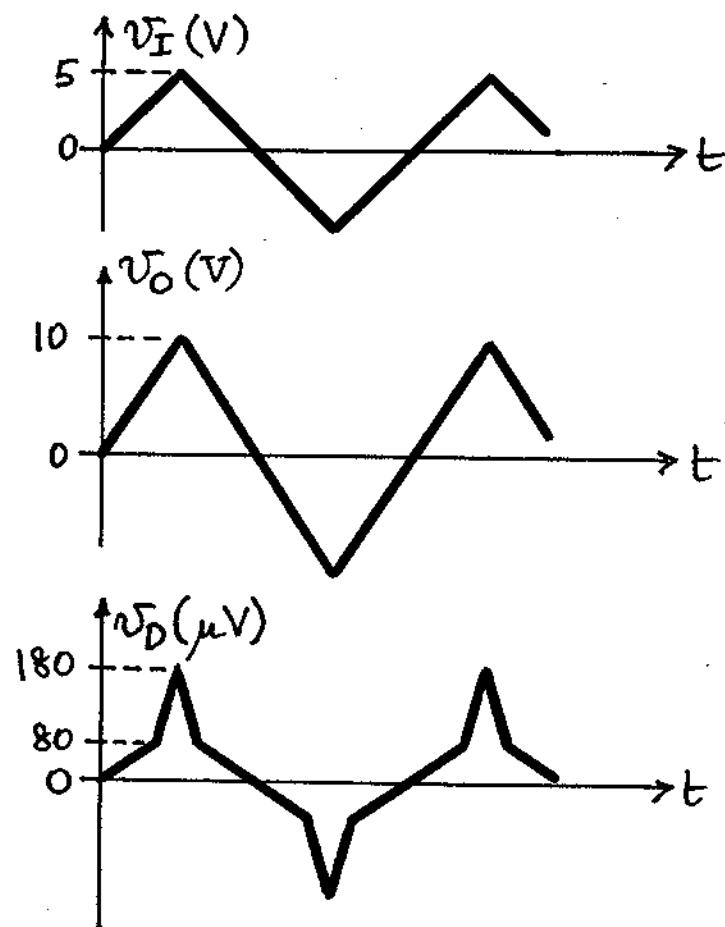


1.23

1.49

(a) The deadband is reduced by the amount of feedback, and is $(\pm 0.7 \text{ V})/(1+100) \approx \pm 7 \text{ mV}$. The slope is $A = 100/(1+100) \approx 0.99 \text{ V/V}$.

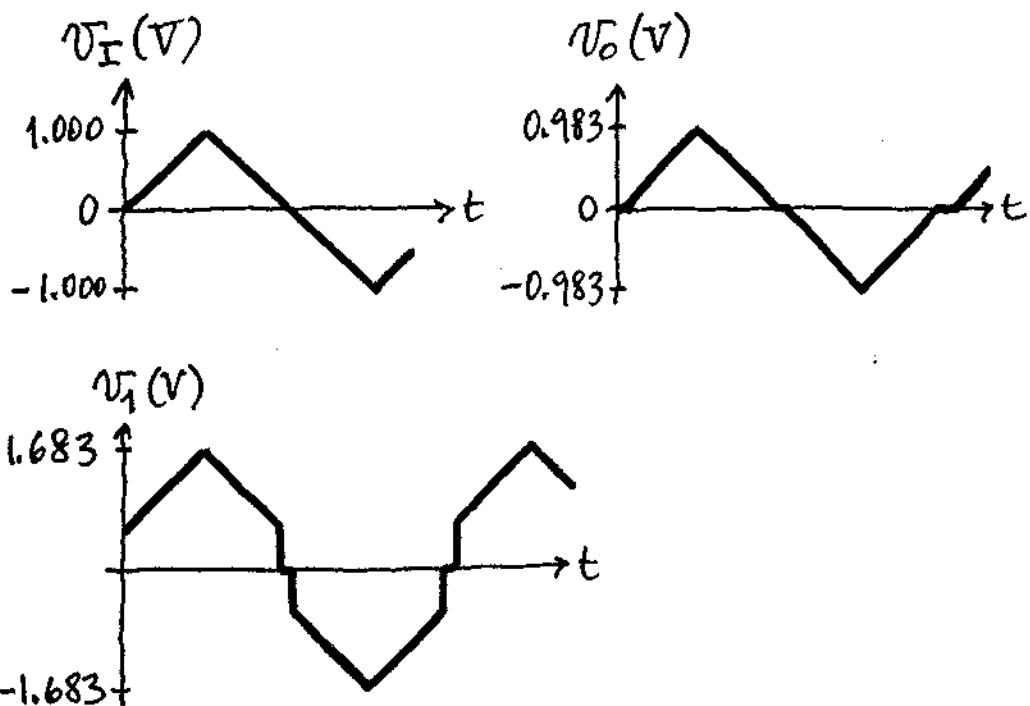(b) The output waveform has a small crossover distortion, and peaks at $\pm(0.99 \times 1 \text{ V} - 7 \text{ mV}) = \pm 0.983 \text{ V}$. Moreover, $v_1 = v_o + 0.7 \text{ V}$ for $v_o > 0$, and $v_1 = v_o - 0.7 \text{ V}$ for $v_o < 0$.



1.50

$$a_1 = 2/(1 \times 10^{-3}) = 2,000 \text{ V/V}.$$

$$1 + a_1 \beta = a_1/A \Rightarrow 1 + 2,000 \beta = 2,000/10$$

$$\Rightarrow \beta = 0.0995 \text{ V/V}.$$

1.24

1.51

$$(a) A = \frac{a}{1+a} = \frac{10^3}{1+10^3} = 0.999 \text{ V/V};$$


$$R_i \approx r_d(1+a) \approx 1 \text{ G}\Omega; R_o \approx \frac{V_o}{1+a} = 1 \text{ }\Omega.$$

$$V_o = \frac{R_o}{R_i + R_o} A \frac{R_L}{R_o + R_L} V_I = 9.970 \text{ V}.$$

(b)

$$V_o = 9.970 - \frac{10^3}{1+10^3} = 9.960 \text{ V}.$$

1.52

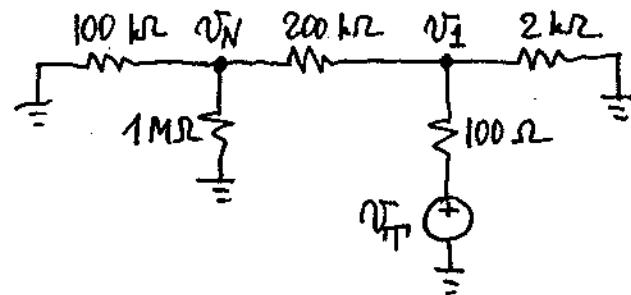

$$V_N = \frac{100//1000}{200 + (100//1000)} V_1 = \frac{1}{3.2} V_1$$

$$V_1 = \frac{2 // [200 + (100//1000)]}{0.1 + 2 // [200 + (100//1000)]} V_o = \frac{V_o}{1.05}$$

$$\beta = 1/(3.2 \times 1.05) = 0.2975 \text{ V/V}.$$

$$(a) 1+a\beta \geq 100 \Rightarrow a \geq 333 \text{ V/V}$$


$$(b) 1+a\beta \geq 10^5 \Rightarrow a \geq 336 \text{ V/mV}.$$

1.53

$\beta = 1 \Rightarrow a\beta = 10^6$. $A = 1/(1+10^6) = 0.999999$; $R_i \approx 10^3(1+10^6) = 1 \text{ G}\Omega$; $R_o \approx 20 \times 10^3/(1+10^6) = 20 \text{ m}\Omega$. Thanks to the large loop gain, the closed-loop parameters are very close to ideal.


1.25

1.54 (a)

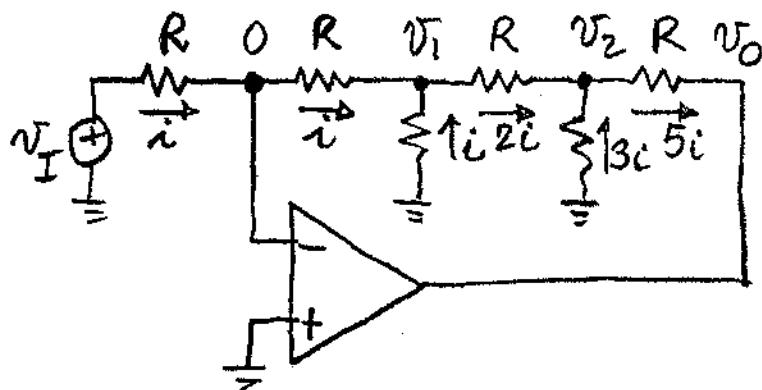


$$i = V_I/R; V_1 = -V_I; V_2 = V_I - R \times 2i = -3V_I; V_O = V_2 - R \times 5i = -8V_I; A_{\text{ideal}} = -8 \text{ V/V}.$$

(b)

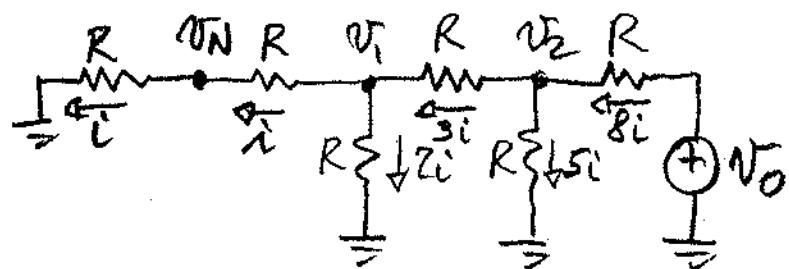

$$i = V_N/R; V_1 = 2V_N; V_2 = V_1 + R \times 3i = 5V_N; V_O = V_2 + R \times 8i = 13V_N; \beta = 1/13 \text{ V/V}; 100/\alpha\beta \leq 0.1 \Rightarrow \alpha \geq 100/0.1\beta = 13,000 \text{ V/V}.$$

1.55 (a)

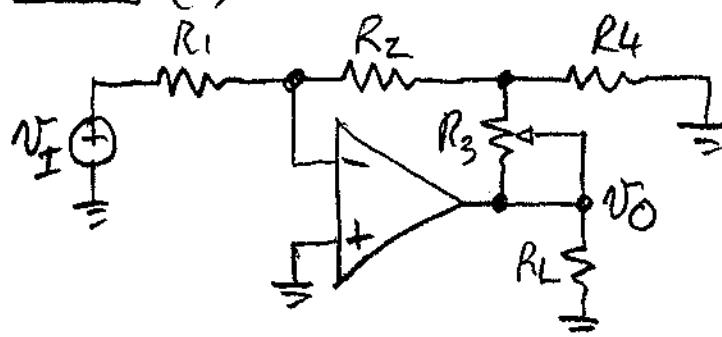


Wiper up $\Rightarrow |A| = |A_{\min}| = R_2/R_1 = 0.5 \text{ V/V} \Rightarrow R_1 = 500 \text{ k}\Omega, R_2 = 250 \text{ k}\Omega$. Wiper down \Rightarrow

1.26

$$|A| = |A_{\max}| = (R_2/R_1)[1 + R_3/(R_2||R_4)] = 10^3 \text{ V/V.}$$

$$0.5(1 + 10^3/250 + 10^3/R_4) = 10^3 \text{ gives } R_4 = 0.501 \text{ k}\Omega.$$

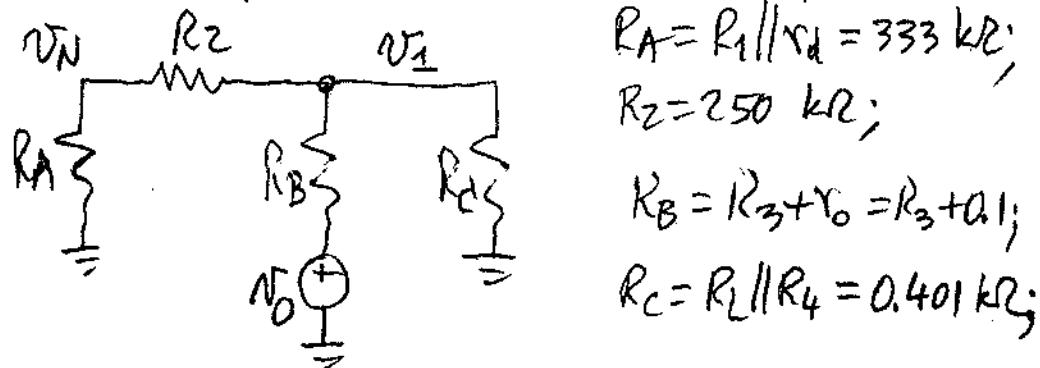(b) Equivalent circuit to find β :

$$V_N = \frac{R_A}{R_A + R_2} V_1 = \frac{V_1}{1.75}. \text{ Since } R_A + R_2 \gg R_C, \text{ we}$$

$$\text{can write } V_1 \approx \frac{R_C}{R_B + R_C} V_O = \frac{V_O}{1 + (R_3 + 0.1)/0.401};$$


$$\text{Thus, } \beta \approx \frac{1}{1.75 [1 + (R_3 + 0.1)/0.401]}$$

Wiper up $\Rightarrow R_3 = 0 \Rightarrow \beta = 0.4574 \text{ V/V};$
 $T = a\beta = 45,737; \text{ gain departure from ideal is } -100/T = -0.002\%.$

Wiper down $\Rightarrow R_3 = 1 \text{ M}\Omega \Rightarrow \beta = 2.29 \times 10^{-4} \text{ V/V}; T \approx 23; \text{ gain departure from ideal is about } -100/23 = -4.3\%.$

1.56

(a)

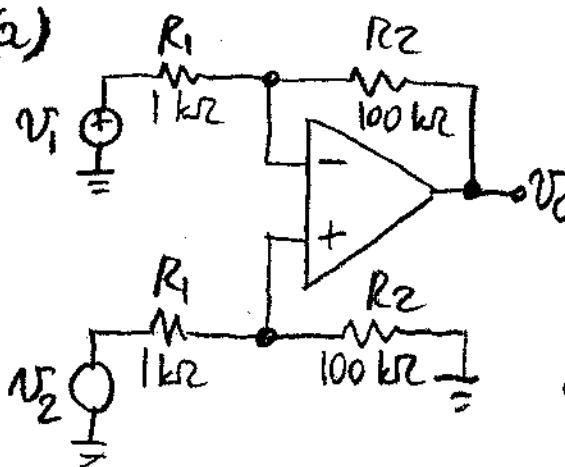

(b)

$$\beta = \frac{1}{101};$$

$$T \geq 10^3;$$

$$a \geq \frac{10^3}{1/101} \Rightarrow a \geq 10^5 \text{ V/V.}$$

1.27

1.57

Fig. P1.15: Suppressing the 4-V source gives $V_D = V_P - V_N = (3/5 - 1)V_O = -(2/5)V_O$; $\beta = -V_D/V_O = 2/5 = 0.4 \text{ V/V}$.

Fig. P1.16: Suppressing the source gives $V_P = 0$ and $V_N = V_O$, so $\beta = 1 \text{ V/V}$.

Fig. P1.17: Suppressing the source gives $V_D = (1/5 - 5/7)V_O = -(18/35)V_O$, so $\beta = 18/35 \text{ V/V}$.

Fig. P1.18: Suppressing the source gives $V_D = (2/5)V_O - V_O = -(3/5)V_O \Rightarrow \beta = 0.6 \text{ V/V}$.

Fig. P1.19: Suppressing the source gives $V_D = V_P - V_N = \frac{1}{1+2+3+4}V_O - \frac{1+2+3}{1+2+3+4}V_O = -0.5V_O \Rightarrow \beta = 0.5 \text{ V/V}$.


1.58

Suppressing the sources gives

$$\beta = \frac{V_N}{V_O} = \frac{10||30}{(10||30)+100} = \frac{3}{34} \text{ V/V.}$$

$$1+\alpha\beta \geq 100 \Rightarrow \alpha \geq 1122 \text{ V/V.}$$

1.59

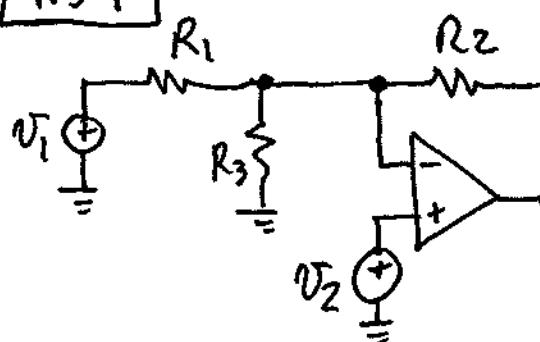

$$V_O = 100(3V_2 - 2V_1)$$

$$= 300V_2 - 200V_1.$$

$$R_2/R_1 = 200 \Rightarrow$$

$$R_1 = 1\text{k}\Omega, R_2 = 200\text{k}\Omega.$$


1.28

$$1 + R_2/(R_1 \parallel R_3) = 1 + R_2/R_1 + R_2/R_3 = 300 \Rightarrow$$

$$1 + 200 + 200k\Omega/R_3 = 300 \Rightarrow R_3 = 2.02 k\Omega.$$

$\beta = (R_1 \parallel R_3)/[(R_1 \parallel R_3) + R_2] = 1/300$. We want
 $T = \alpha \beta \geq 1000 \Rightarrow \alpha \geq 10^3 \times 300 = 300 \text{ V/mV}$.

1.60

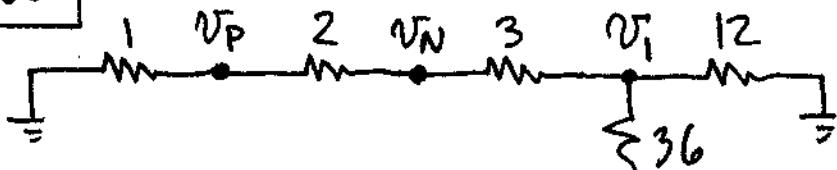

$$V_T = \frac{6/12}{(6/12) + 36} V_T = 0.1 V_T$$

$$V_T = 0.1 V_T$$

$$V_N = \frac{1}{2} V_T = \frac{1}{20} V_T \Rightarrow \beta_N = 1/20$$

$$V_P = \frac{1}{3} V_N = \frac{1}{60} V_T \Rightarrow \beta_P = 1/60$$

$$\beta = \beta_N - \beta_P = 1/30; T = \alpha \beta = \frac{3000}{30} = 100.$$

1.61

(a) Turn the current source into an open circuit; then, $\beta_P = 0, \beta_N = 1, \beta = 1$.


(b) Turn the voltage source into a short circuit; then, $V_P = \frac{1}{1+2+3} V_N \Rightarrow \beta_P = \frac{1}{6} \beta_N; \beta_N = \frac{6}{6+4} = 0.6; \beta = 0.6 - \frac{1}{6} 0.6 = 0.5$.

1.62


(a) Turning V_S into an open circuit gives $V_P = \frac{1}{1+2+3} V_N \Rightarrow \beta_P = \frac{1}{6} \beta_N; \beta_N = \frac{6}{6+4} = 0.6; \beta = 0.6 - 0.6/6 = 0.5$.

(b) Turning V_S into a short circuit gives $\beta_P = 0; \beta_N = 3/(3+4) = 3/7 = \beta$.

1.63

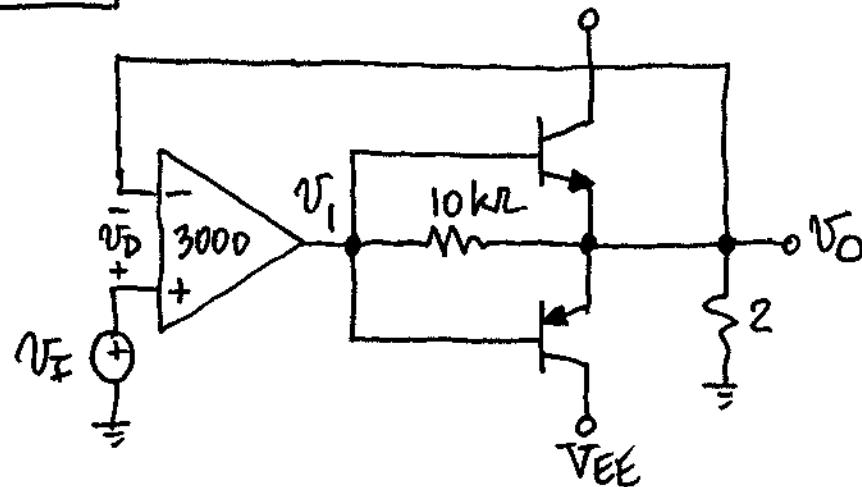


(a) Both BJTs are off for $|V_D| \leq 2 \times \frac{0.7}{10} = 0.14\text{V}$. Over this range we have $V_O = \frac{2}{10+2} 3000 V_D = 500 V_D$, indicating that the open-loop VTC will have a slope of 500V/V over the range $|V_D| \leq \frac{0.14}{500} = 280\mu\text{V}$. For $|V_D| \geq 280\mu\text{V}$, one of the BJTs conducts, and the slope of the open-loop VTC becomes 3000V/V .

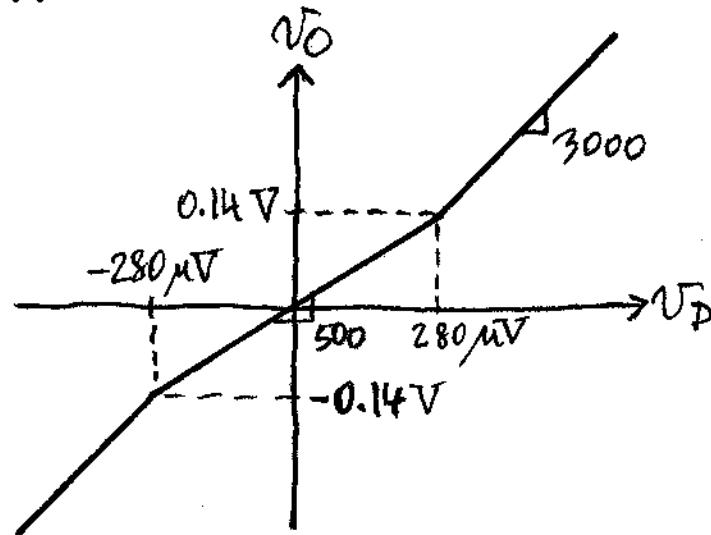


1.30

(b) Since $\beta = 1$, we have $T = 500$ for $|V_0| \leq 0.14 \text{ V}$, and $T = 3000$ for $|V_0| \geq 0.14 \text{ V}$. Thus, the closed-loop gain is $A = \frac{1}{1+1/500} = 0.998 \text{ V/V}$ for $|V_I| \leq 0.14/0.998 = 0.14028 \text{ V}$, and $A = \frac{1}{1+1/3000} = 0.9996 \text{ V/V}$ for $|V_I| \geq 0.14028 \text{ V}$.

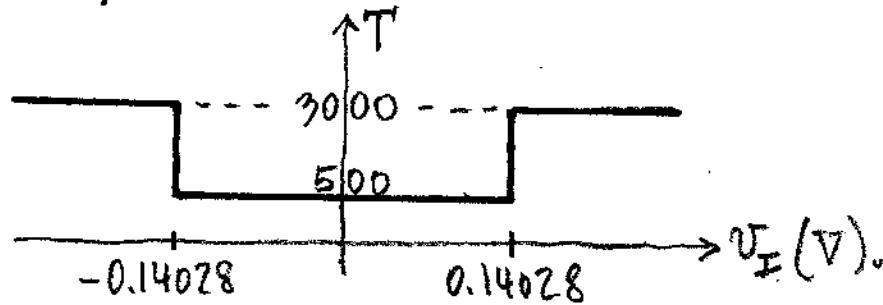

(c) Due to the closeness of A to unity, we have $V_0 \approx V_I$. Moreover, $V_1 = (1+10/2)V_0 = 6V_0$ for $|V_0| \leq 0.14 \text{ V}$, and $V_1 = V_0 + 0.7 \text{ V}$ for $|V_0| \geq 0.14 \text{ V}$; $V_D = V_1/3000$ throughout.

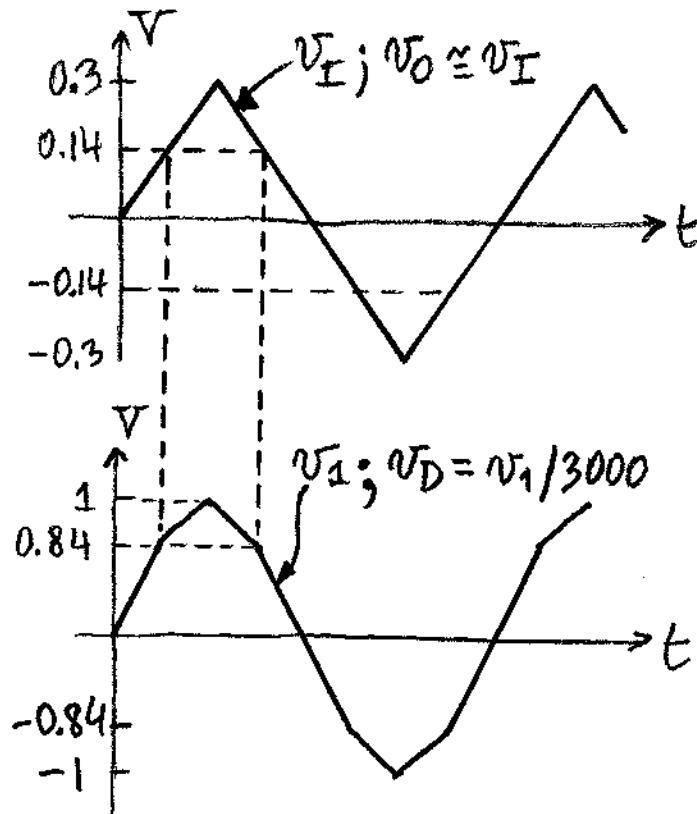

1.31

1.64

(a) $V_0 = -2(-5) = 10 \text{ V}$; $i_L = 5 \text{ mA}$;
 $i_{R_2} = i_{R_1} = 0.5 \text{ mA}$; $i_O = 5.5 \text{ mA}$; $i_{CD} = 0.5 + 5.5 = 6 \text{ mA}$; $i_{EE} = 0.5 \text{ mA}$

(b) $P_{OA} = 30 \times 0.5 + (15-10)5.5 = 42.5 \text{ mW}$.

1.65


$V_N = V_P = -1 \text{ V}$; $V_O = -\frac{30}{10}V_I + \left(1 + \frac{30}{10}\right)(-1)$
 $= -3V_I - 4 \text{ V}$.

(a) $V_I = +2 \text{ V} \Rightarrow V_O = -10 \text{ V}$, $i_{10k\Omega} = i_{30k\Omega} = 0.3 \text{ mA } (\rightarrow)$, $i_{2k\Omega} = 5 \text{ mA } (\uparrow)$,
 $i_O = 5.3 \text{ mA } (\leftarrow)$, $P_{OA} = 30 \times 1.5 + [-10 - (-15)] \times 5.3 = 71.5 \text{ mW}$.

(b) $V_I = -2 \text{ V} \Rightarrow V_O = +2 \text{ V}$, $i_{10k\Omega} = i_{30k\Omega} = 0.1 \text{ mA } (\leftarrow)$, $i_{2k\Omega} = 1 \text{ mA } (\downarrow)$, $i_O = 1.1 \text{ mA } (\rightarrow)$, $P_{OA} = 45 + (15-2)1.1 = 59.3 \text{ mW}$.

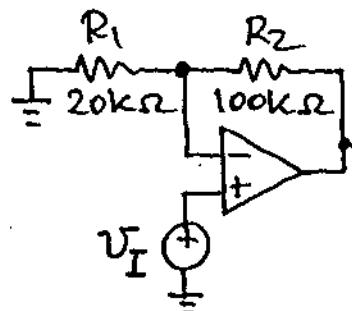1.66

$\pm V_{sat} \equiv \pm 10 \text{ V}$; V_O will clip for




$|V_I| \geq 10/6 = 1.667 \text{ V}$.

During this time,
 $|V_P| > |V_N|$, that is,
 $V_D \neq 0$. By KVL,


$V_D(\max) = 3 - 1.667 = 1.333 \text{ V}$.

The waveforms are shown next:

1.32

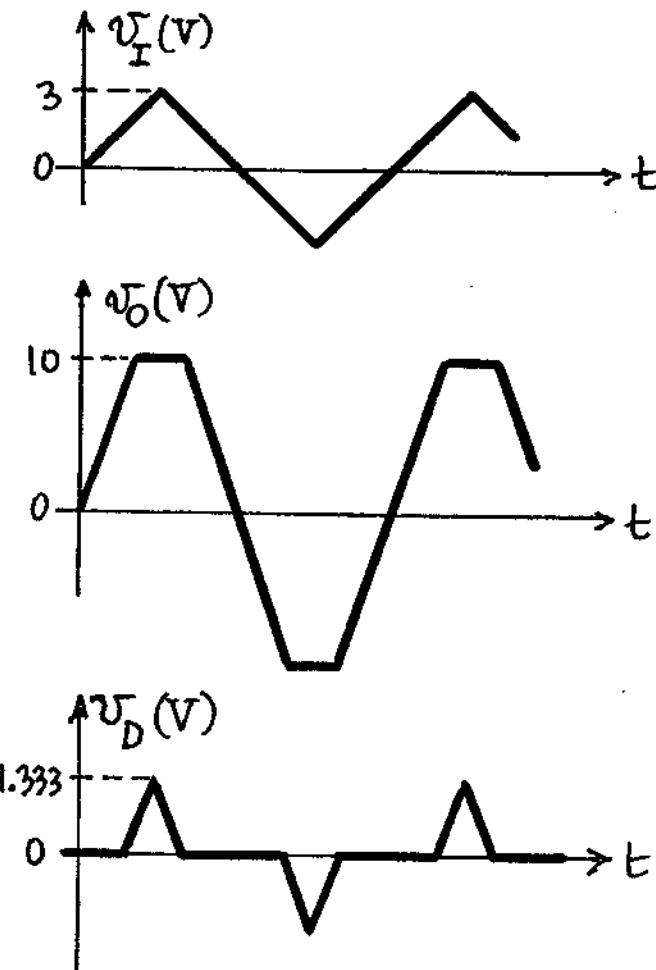

1.67

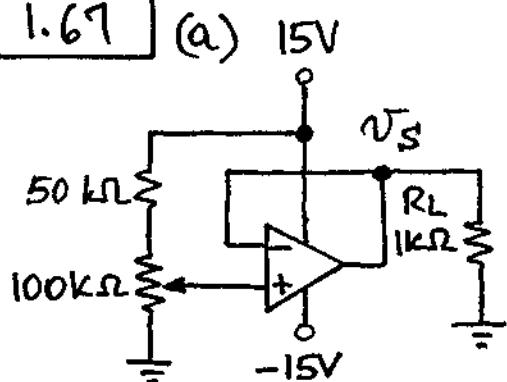

(a) 15V

$$(b) P_{OA} = 30 \times 1.5 +$$

$$(15 - v_S) \frac{v_S}{R_L}$$

$$= 45 + 15v_S - v_S^2 \text{ mW.}$$

$$dP_{OA}/dv_S = 15 - 2v_S$$

$$dP_{OA}/dv_S = 0 \text{ for } v_S = 7.5 \text{ V}$$

$$v_S = 7.5 \text{ V}; P_{OA(\max)} = 45 + (15 - 7.5)7.5 = 101.25 \text{ mW.}$$

1.68

Within the linear region we have $v_O = 5V - 10v_I$, and $v_N \approx v_P = 0$.

(a) v_O is within the linear region, so $v_I = 0$ and $v_N \approx 0$.


1.73

$V_I = (7.5 - 5)(-10) = -0.25 \text{ V}$. For $V_o < 0$, i_o flows into the opamp, and P_{OA} is maximized for $V_o = -7.5 \text{ V}$, which is achieved when $V_I = (-7.5 - 5)/(-10) = 1.25 \text{ V}$; $P_{OA} = 2.625 \text{ mW}$.

(b) With $V_I = 3 \text{ V}$ the opamp would try to give $V_o = 5 - 30 = -25 \text{ V} \Rightarrow V_o = -V_{sat} = -13 \text{ V}$. Find V_N via KCL as

$$\frac{3 - V_N}{10} = \frac{V_N - (-15)}{300} + \frac{V_N - (-13)}{100} \Rightarrow V_N = \frac{18}{17} \text{ V.}$$

1.69

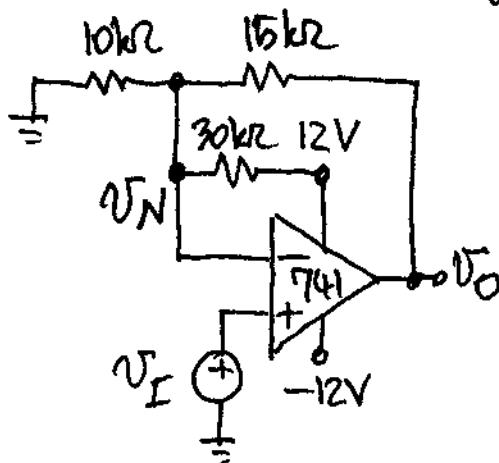

$$V_o = \left(1 + \frac{15}{10/30}\right)V_I - \frac{15}{30}12 \\ = 3V_I - 6\text{V},$$

$$\pm V_{sat} \approx \pm 10 \text{ V}$$

(a) Try $V_o = 3 \times 4 - 6 = 6 \text{ V}$. Since V_o is within

the linear region, we get $V_N = V_I = 4 \text{ V}$.

(b) Now $V_o = 3(-2) - 6 = -12 \text{ V} \Rightarrow$ Saturation $\Rightarrow V_o = -10 \text{ V}$. By KCL at V_N

$$\frac{12 - V_N}{30} = \frac{V_N}{10} + \frac{V_N - (-10)}{15} \Rightarrow V_N = -\frac{4}{3} \text{ V.}$$

1.70

(a) $V_o = -10V_I + 5 \text{ V}$. The output drives a 100-kΩ load to ground, and a 100-kΩ feedback resistor to virtual ground,

1.34

so $i_0 = \frac{v_o}{100\text{k}\Omega} + \frac{v_o}{100\text{k}\Omega} = \frac{v_o}{50\text{k}\Omega}$. For $v_o > 0$, i_0 flows out of the op amp, so $P_{OA} = 30 \times 0.05 + (15 - v_o) v_o / 50$. This is maximized for $v_o = 7.5\text{V}$, at which point $P_{OA} = 2.625\text{mW}$, and $v_I = (7.5 - 5)(-10) = -0.25\text{V}$. For $v_o < 0$, i_0 flows into the op amp, and P_{OA} is maximized when $v_o = -7.5\text{V}$, or $v_I = (-7.5 - 5)/(-10) = 1.25\text{V}$. Then, $P_{OA} = 2.625\text{mW}$.

(b) Imposing $-13\text{V} \leq (-10v_I + 5\text{V}) \leq +13\text{V}$ gives $-0.8\text{V} \leq v_I \leq +1.8\text{V}$.

1.71

$$v_o = -\frac{120}{30}v_1 + \left(1 + \frac{120}{30}\right) \frac{30}{20+30} v_2 = 3v_2 - 4v_1.$$

(a) $v_o = 6 \sin \omega t - 4v_1$. $|v_1|_{\max} = \frac{13-6}{4} = 1.75\text{V}$, so the allowed range is $-1.75\text{V} \leq v_1 \leq +1.75\text{V}$.

$$(b) v_o = -3 - 4 V_m \sin \omega t.$$

$$\begin{aligned} -13 &= -3 - 4 V_m \Rightarrow V_m = 2.5\text{V} \\ +13 &= -3 - 4(-V_m) \Rightarrow V_m = 4\text{V} \end{aligned} \} \Rightarrow V_m \leq 2.5\text{V}.$$

(c) We now have $\pm V_{sat} \cong \pm 9\text{V}$, so we get for (a) $-0.75\text{V} \leq v_1 \leq +0.75\text{V}$, and for (b) $V_m \leq 1.5\text{V}$.

1.72


Fig. P1.17: $v_o = (-20/50)v_s + (1+20/50) \times [10/(10+40)]v_o \Rightarrow v_o = (-5/9)v_s$

$$|v_o| \leq 10\text{V} \Rightarrow |v_s| \leq 18\text{V}.$$

1.35


Fig. P1.19: $i_{2k2} = [3/(2+3)]i_S = 0.6i_S$; $i_{3k2} = 0.4i_S$; $V_P = 1 \times i_{2k2} = 0.6i_S$; $V_O = V_N - 4i_{3k2} = 0.6i_S - 4 \times 0.4i_S = (-1k\Omega)i_S$. $|V_O| \leq 10V \Rightarrow |i_S| \leq 10 \text{ mA}$.

1.73

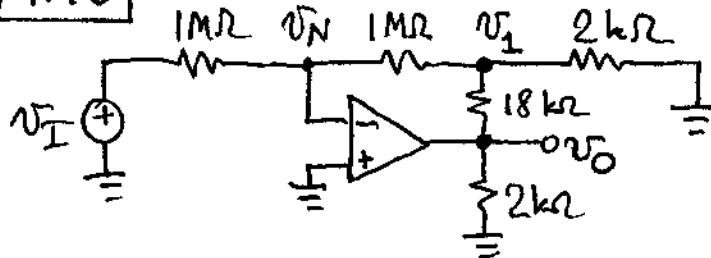


Ideally, $v_N = 0$, $v_1 = -v_I$, $v_O = [1 + 8/(1000||2)]v_1 = 10.018v_1 \approx -10v_I$.

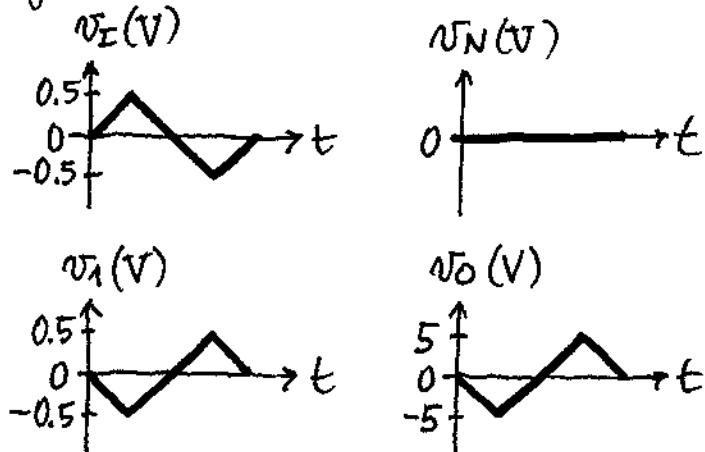
(a) $V_{im} = 0.5V \Rightarrow V_{om} = 10 \times 0.5 = 5V \Rightarrow$ linear region.



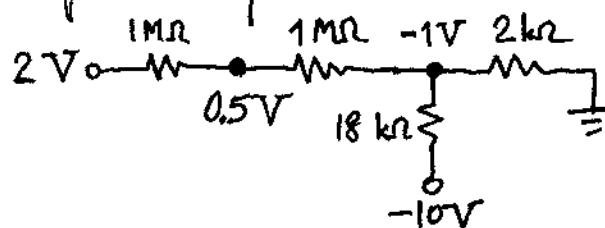(b) $V_{im} = 2V \Rightarrow V_{om} = 10 \times 2 = 20V \Rightarrow$ saturation. Shown below is the situation when v_I reaches its positive peak:



1.36

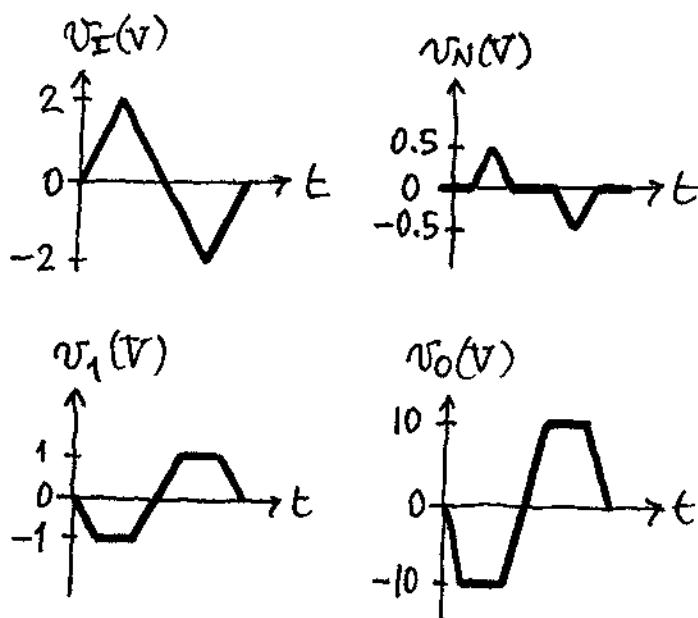


1.74

$$(a) V_o = V_{o1} - V_{o2} = [1 + (A-1) R/R] V_I - [- (AR/R) V_I] = 2AV_I.$$

$$(b) -13V \leq V_{o1} \leq 13V; -13V \leq V_{o2} \leq 13V; -26V \leq V_o \leq 26V, V_o(\text{max}) = 52 \text{ V}_{\text{pk-pk}}.$$

1.75

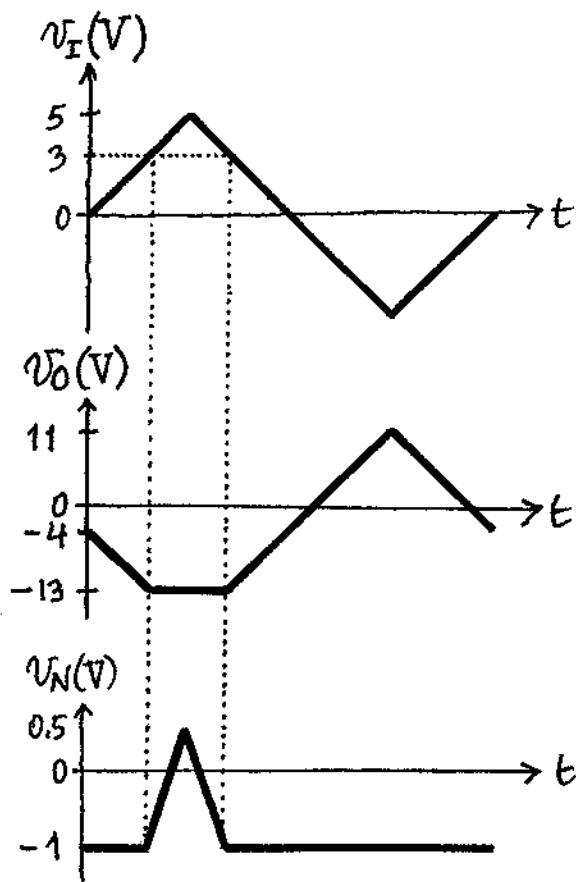

1.37


$V_P = -1V$. When in the linear region, the op amp gives $V_N = -1V$ and $V_O = -3V_I - 4V$.

$V_I = -5V \Rightarrow V_O = 11V \Rightarrow$ linear region.



$V_I = +5V \Rightarrow V_O = -19V \Rightarrow$ saturation. The op amp saturates for $V_I \geq (-13+4)/(-3) = 3V$.

$$V_N(\text{peak}) = [30 \times 5 + 10(-13)] / (10 + 30) = 0.5V.$$

1.76

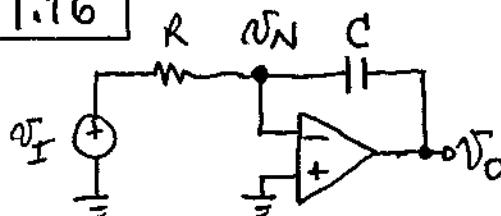

In the linear region,
 $V_O = -10^3 t$

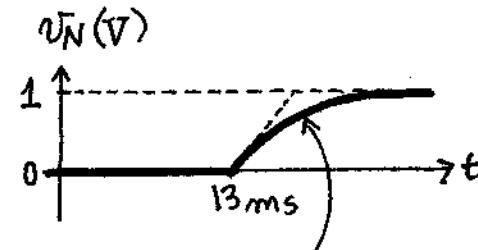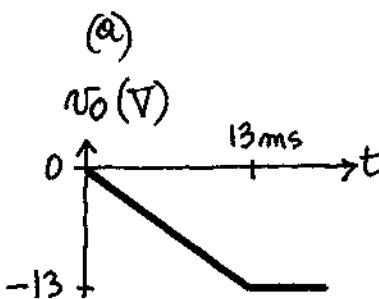

Exponential transient
with $\tau = 1\text{ ms}$

(b) Same as above, except that the ramp now lasts 13 s, and the asymptotic value of V_N is 1 mV.

(c) Same as in (b), except that the voltages now have opposite polarities (V_O saturates at +13V, and V_N tends to -1mV).