
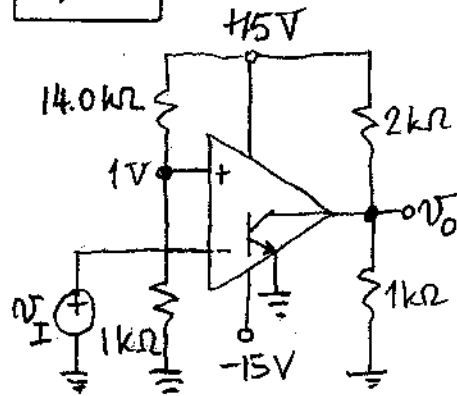


9.1

9.1

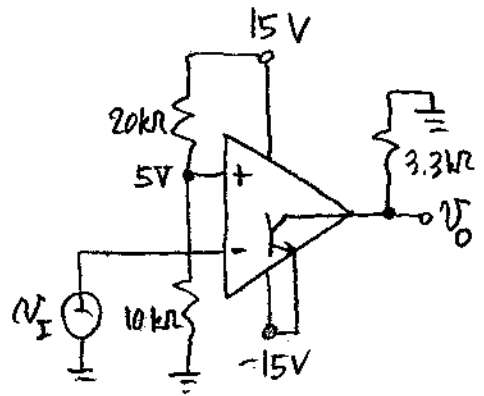


(a)



(b)

9.2

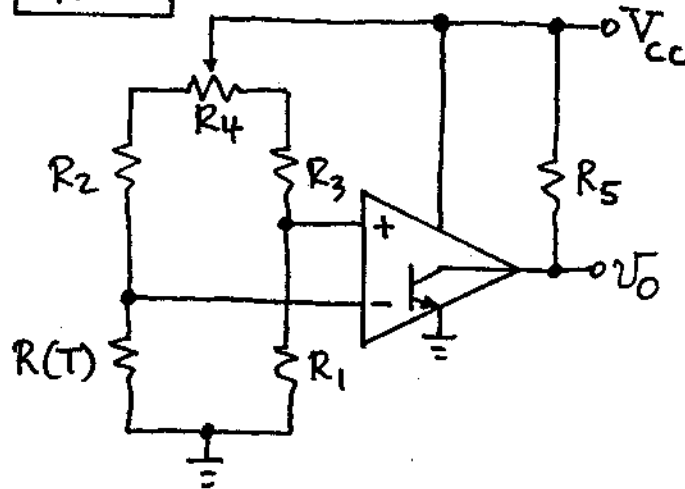


Since the voltage developed by the thermistor decreases with T , it must be

applied to the inverting input. $R(100^\circ\text{C}) = 100\text{ k}\Omega \times \exp[4000(1/373.2 - 1/298.2)] = 6.75\text{ k}\Omega$. Make all bridge resistors nominally $6.75\text{ k}\Omega$. To allow exact calibration, let $R_4 = 1\text{ k}\Omega$ pot and $R_2 = R_3 = 6.75 - 0.5 = 6.25\text{ k}\Omega$. The closest 1% standard values are $R_1 = 6.81\text{ k}\Omega$ and $R_2 = R_3 = 6.19\text{ k}\Omega$. Moreover, let $R_5 = 3.3\text{ k}\Omega$. To calibrate, place the thermistor in


9.2

boiling water and adjust R_4 until V_o bounces back and forth between 0 and V_{cc} .

9.3

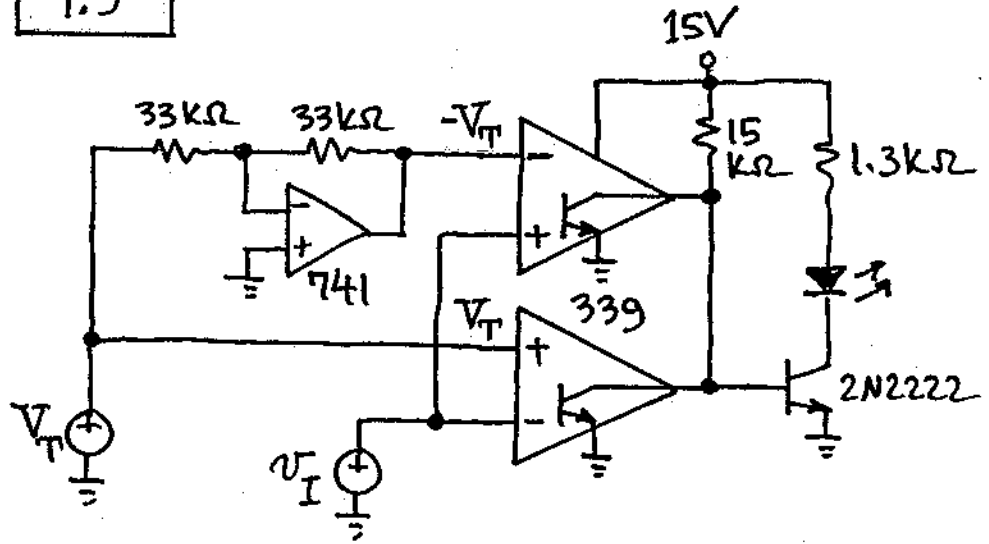

9.4

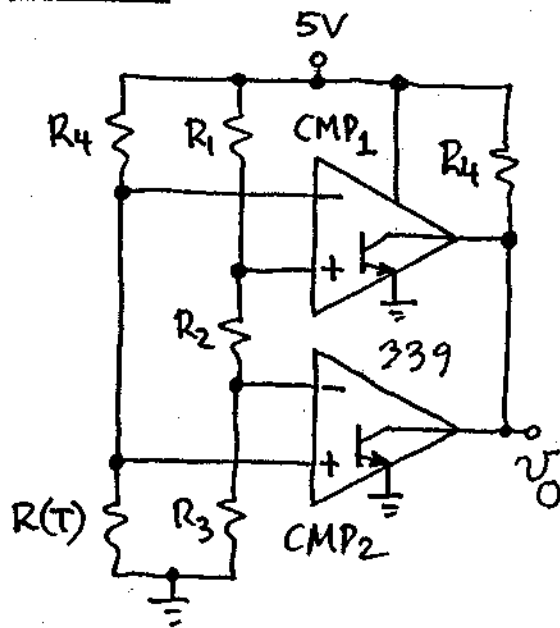

$$R(0^\circ\text{C}) = 34.12 \text{ k}\Omega.$$

$$R(5^\circ\text{C}) = 26.23 \text{ k}\Omega.$$

$$\text{Let } R_4 = 30 \text{ k}\Omega.$$

$$\text{Then, } V_{TL} = 5 \times$$

$$\frac{26.23}{26.23 + 30} = 2.33 \text{ V}$$

$$V_{TH} = 5 \frac{34.12}{34.12 + 30} =$$


$$2.66 \text{ V. Use}$$

$$R_3 = 23.2 \text{ k}\Omega,$$


$$R_2 = 3.32 \text{ k}\Omega, R_1 = 23.4 \text{ k}\Omega.$$

9.3

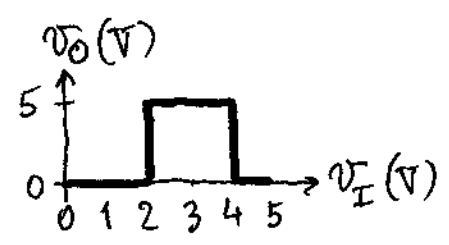9.5 We have $V_{N1} = V_I/2$, $V_{P1} = (V_1 + V_2)/2$, $V_{P2} = (V_I + V_2)/2$, $V_{N2} = V_1/2$. Thus, $V_O = V_{OH}$ for $V_{P1} > V_{N1}$ and $V_{P2} > V_{N2}$, that is, $V_O = V_{OH}$ for $V_1 + V_2 > V_I$ and $V_I + V_2 > V_1$. Summarizing, $V_O = V_{OH}$ for $(V_1 - V_2) < V_I < (V_1 + V_2)$, $V_O = V_{OL}$ otherwise. As exemplified in the figure,



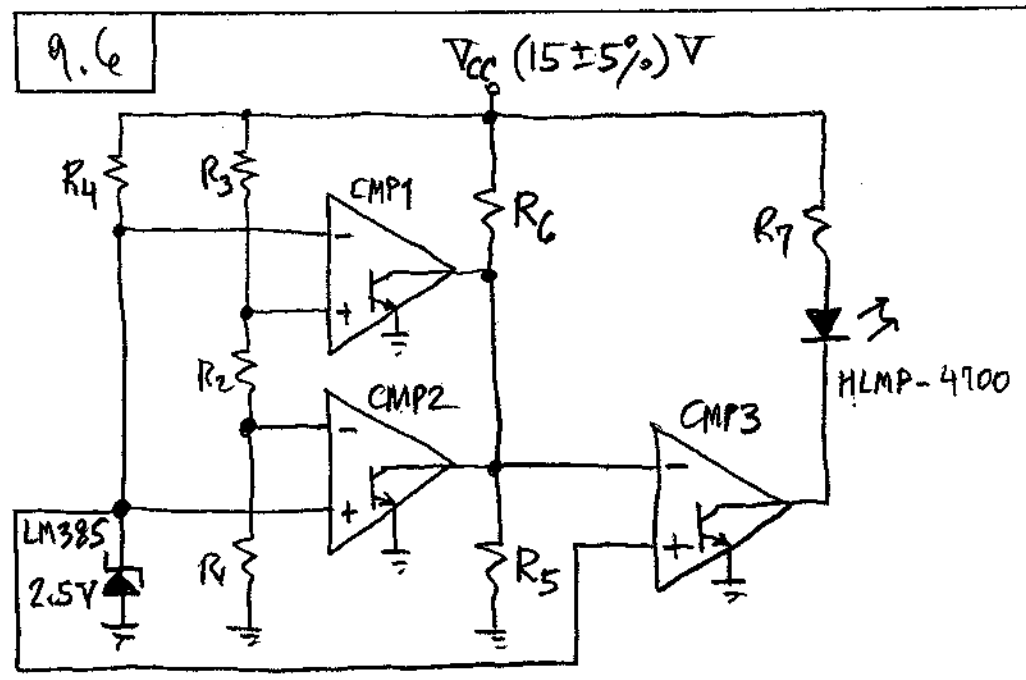the center of the VTC is V_1 , and the width is V_2 .





$$\frac{R_1}{R_1 + R_2 + R_3} = \frac{2.5}{15.75}, \quad \frac{R_1 + R_2}{R_1 + R_2 + R_3} = \frac{2.5}{14.25} \Rightarrow R_1 = 10.0 \text{ k}\Omega$$

$R_2 = 1.05 \text{ k}\Omega$, $R_3 = 52.3 \text{ k}\Omega$, 1%; $R_4 = R_5 = 10 \text{ k}\Omega$, $R_6 = 20 \text{ k}\Omega \Rightarrow V_{N3} \cong 5 \text{ V}$ for V_{CC} within tolerance, $V_{N3} \cong 0 \text{ V}$ otherwise; $V_{P3} = 2.5 \text{ V}$;
 $R_7 = (15 - 1.8)/2 \cong 6.8 \text{ k}\Omega$.


9.4

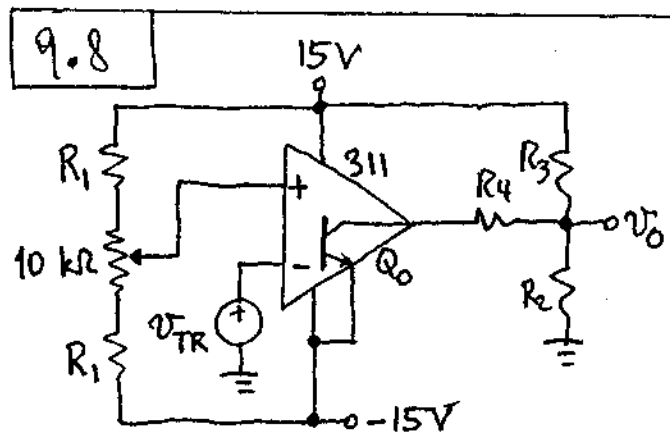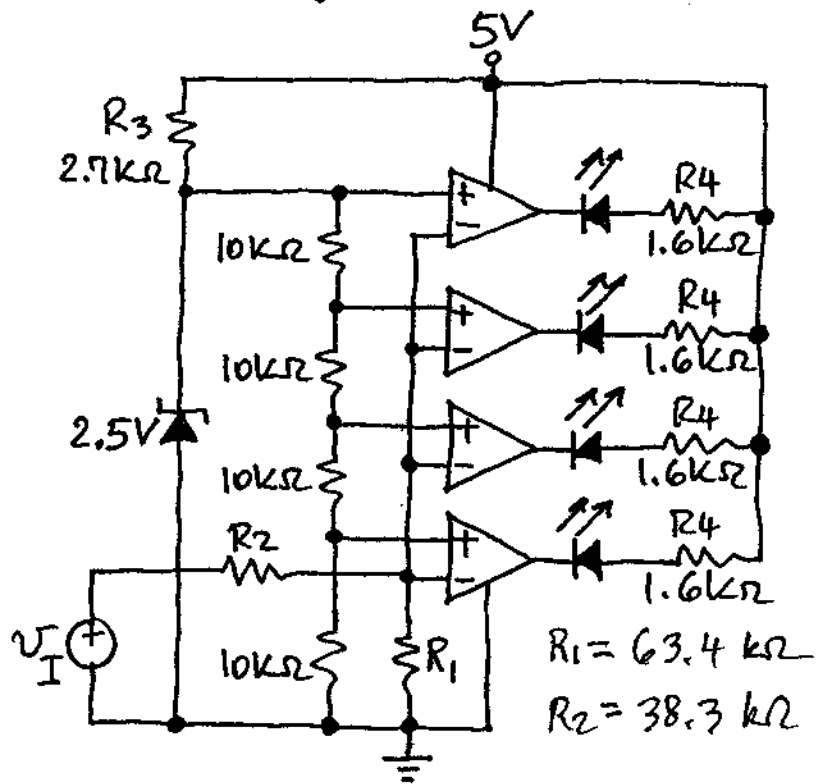9.7 Use four $10\text{-k}\Omega$ resistors to split the reference range into four equal intervals. Bias the reference diode and the four resistors with $R_3 = 2.7\text{k}\Omega$. Use R_1 and R_2 to scale the 4V input range to the 2.5V reference range. This requires $R_2 = 0.6R_1$, or $R_1 = 62.5\text{k}\Omega$ and $R_2 = 37.5\text{k}\Omega$. Finally, $R_4 = (5 - 1.8)/2 = 1.6\text{k}\Omega$.



Wiper up \Rightarrow
 $D(\%) = 95 \Rightarrow$
 $\frac{5}{5 + R_1} \cdot 15 = 9$
 $\Rightarrow R_1 = 3.32$
 $\text{k}\Omega, 1\%$

9.5

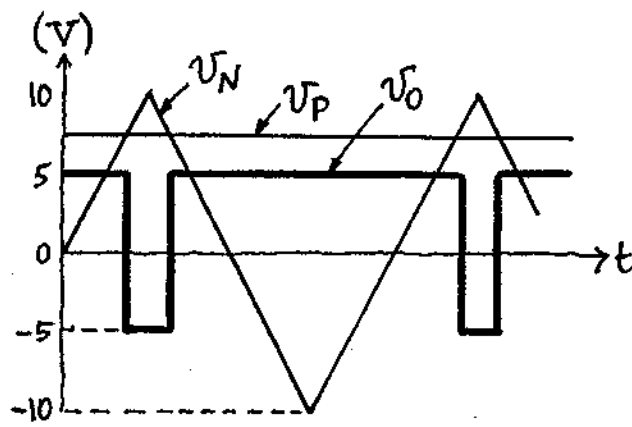

$Q_0 = \text{OFF} \Rightarrow$

$$v_o = \frac{R_2}{R_2 + R_3} 15 = 5$$

$$\Rightarrow R_2 = 10.0 \text{ k}\Omega$$


$$R_3 = 20.0 \text{ k}\Omega.$$

$Q_0 = \text{SAT} \Rightarrow$

$$v_o = -5 \text{ V} \Rightarrow \frac{15 - (-5)}{20} + \frac{0 - (-5)}{10} = \frac{-5 - (-15)}{R_4} \Rightarrow$$

$$R_4 = 6.67 \text{ k}\Omega \text{ (use } 6.65 \text{ k}\Omega, 1\%).$$

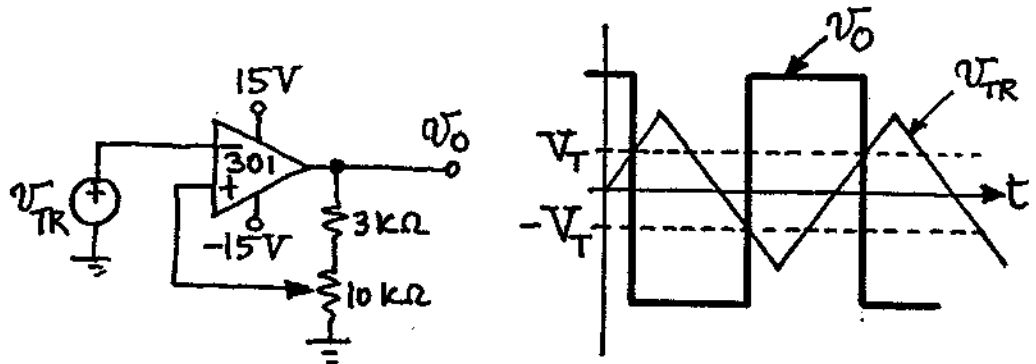9.9 Use a $3 \text{ k}\Omega$ series resistor to make V_T variable from 0 V to 10 V .




9.10 (a) Imposing $v_p = v_N$ with $v_o \cong 0$ and $v_I = V_{TH}$ gives $V_{TH} R_4 / (R_3 + R_4) = V_{CC} R_1 / (R_1 + R_2)$.
 Imposing $v_p = v_N$ with $v_o \cong V_{CC}$ and $v_I = V_{TL}$ gives $V_{TL} R_4 / (R_3 + R_4) + V_{CC} R_3 / (R_3 + R_4) = V_{CC} R_1 / (R_1 + R_2)$. Combining the two equations,

$$\frac{R_3}{R_4} = \frac{V_{TH} - V_{TL}}{V_{CC}} \quad \frac{R_2}{R_1} = \frac{V_{CC} - V_{TH}}{V_{TH}}$$


9.6

(b) $R_3/R_4 = (2.5 - 1.5)/5 = 0.2$; $R_2/R_1 = (5 - 1.5)/2.5 = 1.4$. To ensure $V_{OH} \approx 5V$, impose $R_5 \ll R_3 + R_4$. To minimize the effect of the input bias current, impose $R_1 \parallel R_2 = R_3 \parallel R_4 \ll V_{OS}/I_{OS}$. Assuming a 339 comparator, $V_{OS}/I_{OS} = (2\text{mV})/(5\text{mA}) = 400\text{ k}\Omega$. Let $R_5 = 2.2\text{ k}\Omega$ and $R_4 = 220\text{ k}\Omega$; then $R_3 = 44\text{ k}\Omega$ (use $44.2\text{ k}\Omega$), $R_1 = 62.8\text{ k}\Omega$ (use $63.4\text{ k}\Omega$), and $R_2 = 88\text{ k}\Omega$ (use $88.7\text{ k}\Omega$).

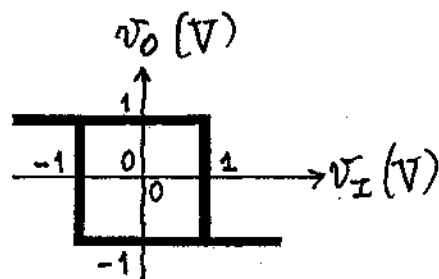9.11 When the 301 saturates at $+13V$, $D_3 = D_2 = ON$, $D_1 = D_4 = OFF$, $v_o = 1 \times (15 - 0.7)/(13.3 + 1) = 1V$. Likewise, when the 301 saturates at $-13V$, $D_1 = D_4 = ON$, $D_2 = D_3 = OFF$, and $v_o = -1V \Rightarrow$



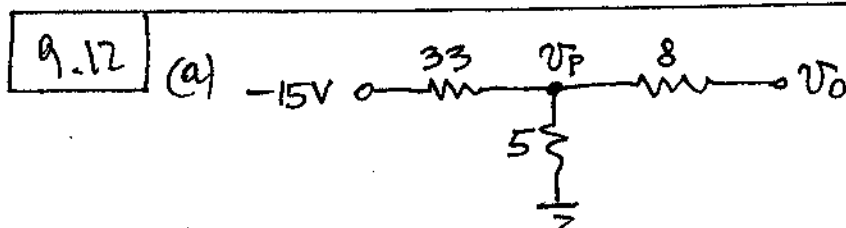Schmitt trigger with $v_o = \pm 1V$ and $\pm V_T = \pm 1V$.




$$v_p = \frac{33 \parallel 5}{33 \parallel 5 + 8} v_o + \frac{8 \parallel 5}{33 + 8 \parallel 5} (-15) = 0.352 v_o - 1.279 V.$$

$$V_{TH} = v_p |_{v_o = 13V} = 3.29 V; \quad V_{TL} = v_p |_{v_o = -13V} = -5.85 V.$$

The result is a VTC with $V_{OH} = 13V$, $V_{OL} = -13V$, $V_{TH} = 3.29V$, $V_{TL} = -5.85V$. Effect of $33\text{ k}\Omega$ is to shift the VTC toward the left.

9.7

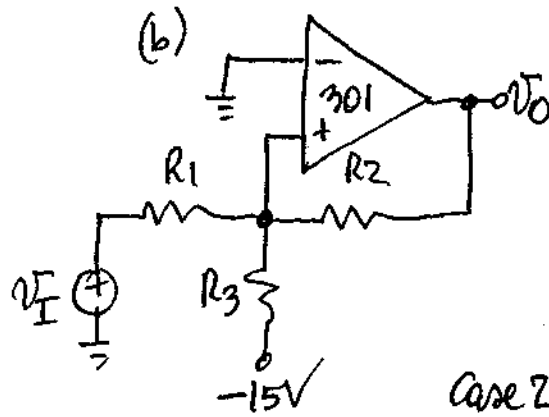

$v_p = 0$ in two cases:

Case 1: $v_O = V_{OL}$ and

$v_I = V_{TH}$; KCL:


$$\frac{2-0}{R_1} = \frac{0-(-15)}{R_3} + \frac{0-(-13)}{R_2}$$

Case 2: $v_O = V_{OH}$ and $v_I = V_{TL}$:

KCL: $\frac{13-0}{R_2} + \frac{1-0}{R_1} = \frac{0-(-15)}{R_3}$. Two equations,

three unknowns. Fix $R_1 = 10 \text{ k}\Omega$; then, $R_3 = 100 \text{ k}\Omega$ and $R_2 = 260 \text{ k}\Omega$ (use $261 \text{ k}\Omega$).

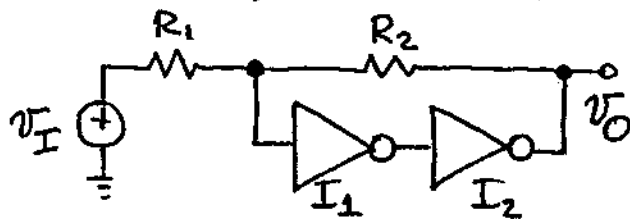9.13 (a) With $v_O = 0$ and $v_I = V_{TH} = (2/3)V_{DD}$




we want the voltage at I_1 's input to be V_T .

Thus, $\frac{R_2}{R_1 + R_2} \frac{2}{3} V_{DD} = \frac{1}{2} V_{DD}$, that is, $R_2 = 3R_1$.

Use $R_1 = 10 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$.

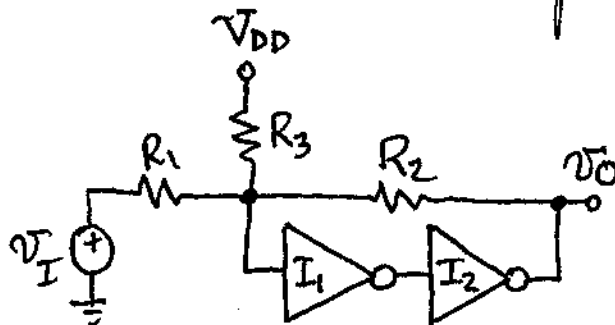(b) We need a pullup resistor to shift the V_{TC} downward.



With $v_O = 0$ we have

$$\frac{V_{DD} - V_T}{R_3} + \frac{V_{TH} - V_T}{R_1} =$$

$$\frac{V_T - 0}{R_2}$$

Letting $V_T = \frac{1}{2} V_{DD}$ and $V_{TH} = \frac{1}{2} V_{DD}$ gives $R_2 = R_3$. With

9.8


with $v_o = v_{DD}$ we have $\frac{v_{DD} - v_T}{R_2 // R_3} = \frac{v_T - v_{TL}}{R_1}$. Letting $v_T = \frac{1}{2} v_{DD}$ and $v_{TL} = \frac{1}{5} v_{DD}$ gives $R_1 = 0.3 R_3$. Use $R_2 = R_3 = 100 \text{ k}\Omega$, $R_1 = 30 \text{ k}\Omega$.

(c) Use an additional inverter at the output.

9.14 $R(100.5^\circ\text{C}) = 100 \text{ k}\Omega \times \exp[4000 \times (1/373.7 - 1/298.2)] = 6.65 \text{ k}\Omega$. Thus, a temperature change of 0.5°C near 100°C induces a thermistor voltage change of value $v_{CC}/2 - v_{CC} \cdot 6.65 / (6.65 + 6.75) = 3.6 \times 10^{-3} v_{CC}$. Connect a resistor R_6 between output and noninverting input to produce a hysteresis width $v_H = 7.2 \times 10^{-6} \times v_{CC}$. Since $v_{OH} - v_{OL} \approx v_{CC}$, impose $\frac{R_1 // (R_3 + R_4/2)}{R_1 // (R_3 + R_4/2) + R_6} v_{CC} = v_H$, that is, $\frac{6.75/2}{6.75/2 + R_6} v_{CC} = 7.2 \times 10^{-3} v_{CC}$. Solving yields $R_6 \approx 470 \text{ k}\Omega$. To calibrate, place the thermistor in boiling water and find the wiper settings that just cause v_o to change state. Then, set the wiper halfway.


9.9

9.15

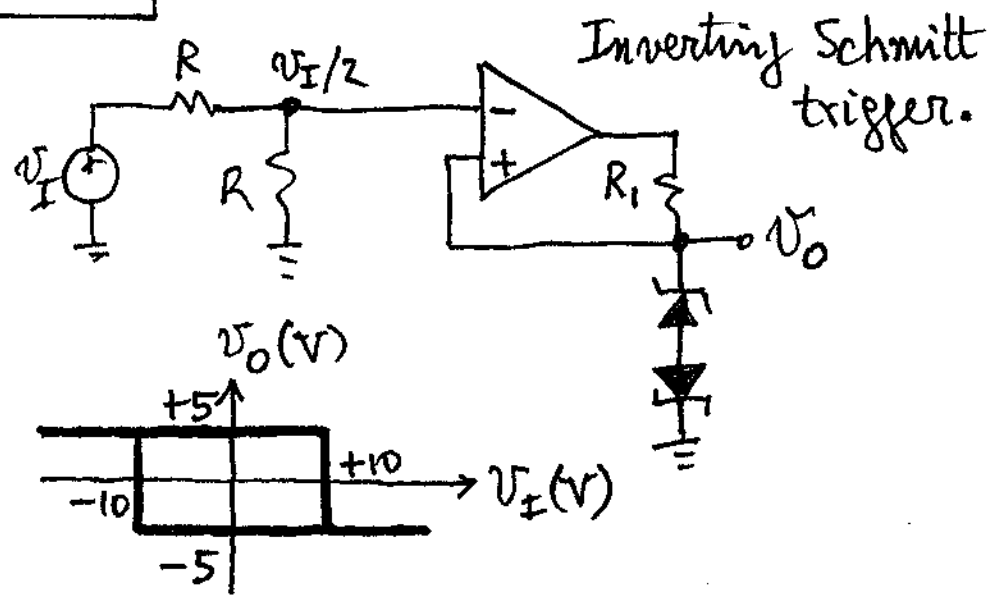

$v_O = \pm (4.3 + 0.7) = \pm 5V$. v_O trips whenever $v_I/2 = \pm 5V$, i.e. whenever $v_I = \pm 10V$.

9.16

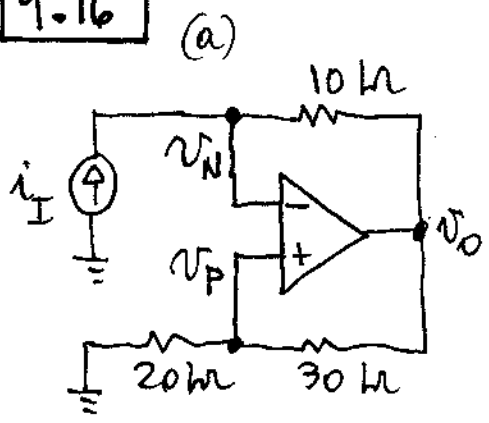


$\beta_N = 1, \beta_P = 2/5 = 0.4$


\Rightarrow negative feedback prevails over positive feedback $\Rightarrow v_N = v_P$.

$v_N = 10^4 i_I + v_O = v_P =$

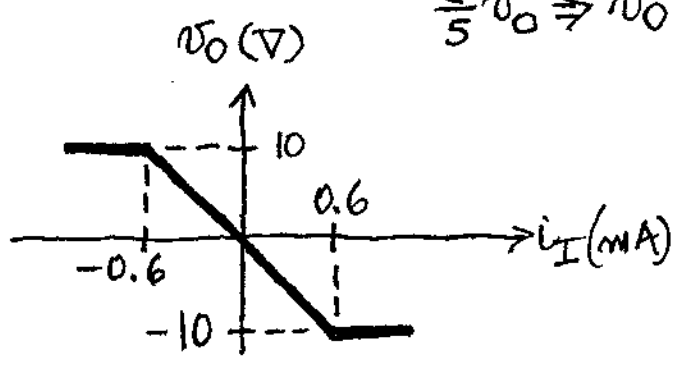$\frac{2}{5} v_O \Rightarrow v_O = -\frac{10 \times 10^3}{0.6} i_I$



9.10

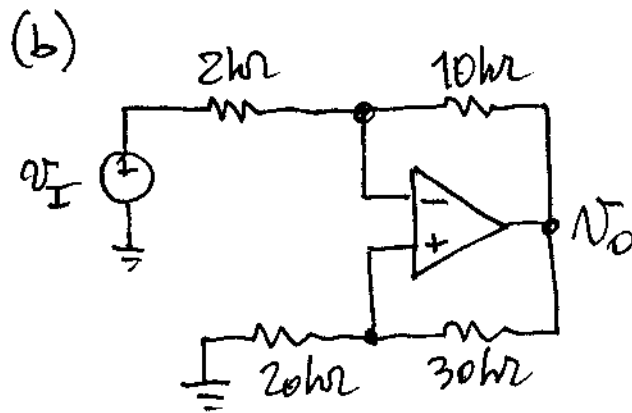


Perform a source transformation, as shown, with $v_I = 2 \times 10^3 i_I$. $\beta_N = 2/10$, $\beta_P = 2/5$, $\beta_P > \beta_N \Rightarrow$ positive feedback \Rightarrow Schmitt-trigger operation (inverting type).

$$v_O = \pm V_{sat} = \pm 10V; v_P = \pm (2/5)10 = \pm 4V.$$

For $v_O = -10V$, $v_P = -4V$ and the value v_{TL} of v_I for which the comparator trips is such that


$$\frac{v_{TL} - (-4)}{2} = \frac{-4 - (-10)}{10}, \text{ or } v_T = -2.8V = -v_{TH}.$$

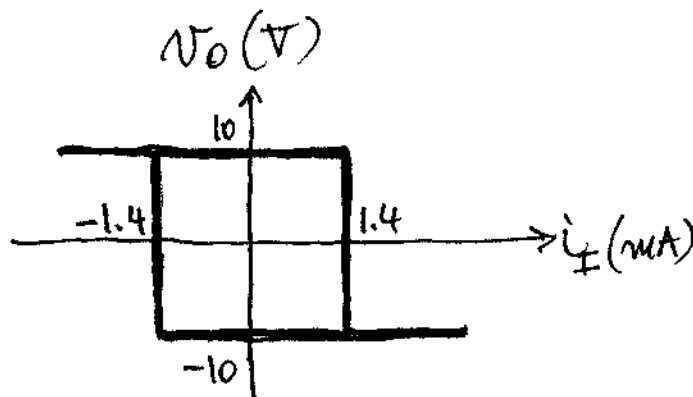The threshold values of i_I are $I_T = \pm v_T / 2k\Omega = \pm 1.4 \text{ mA}$.



9.11



9.17

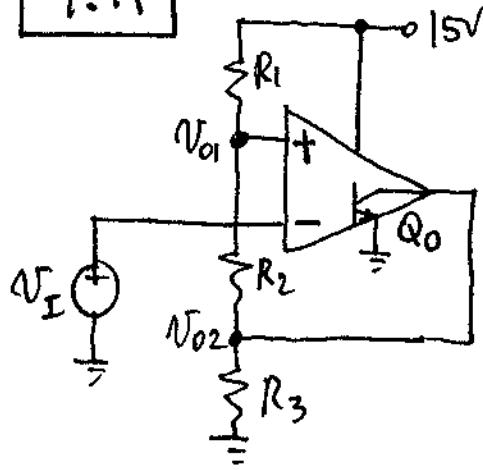


$Q_0 = \text{OPEN} \Rightarrow V_{O2} = 5V,$
 $V_{O1} = 10V.$

$Q_0 = \text{SAT} \Rightarrow V_{O2} \approx 0V,$
 $V_{O1} = 7.5V.$

$V_{TL} = 7.5V, V_{TH} = 10V.$

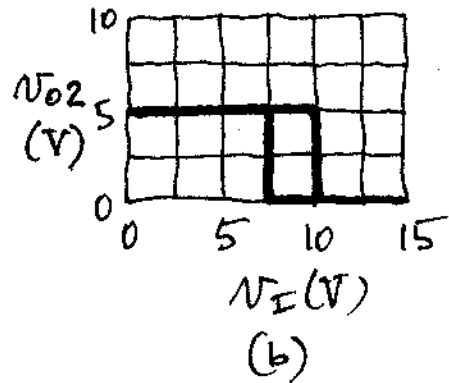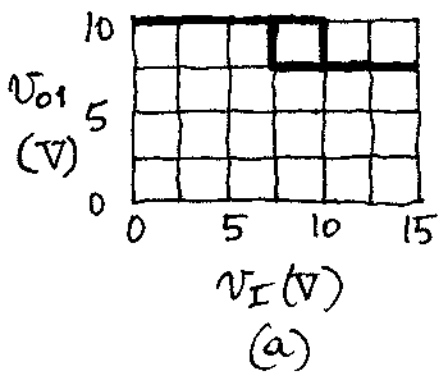


7.18

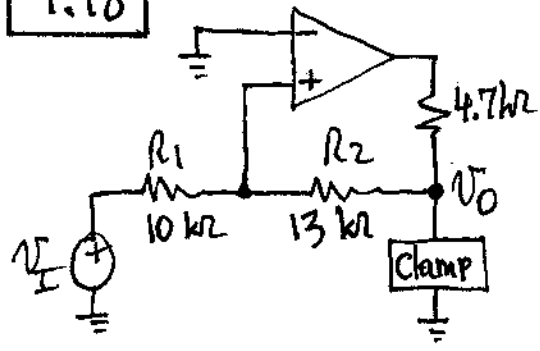

The diode network clamp V_O at
 $V_O = \pm (5.1 + 2 \times 0.7)$
 $= \pm 6.5V$


$V_I = \pm \frac{10}{13} 6.5 = \pm 5V.$

The VTC is thus:


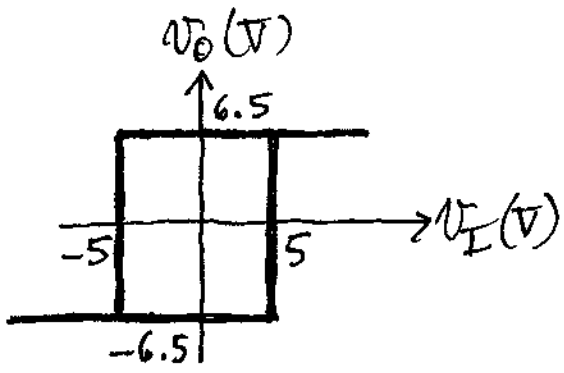


9.12


9.19

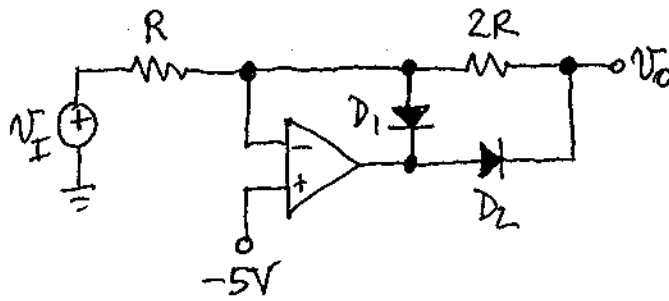

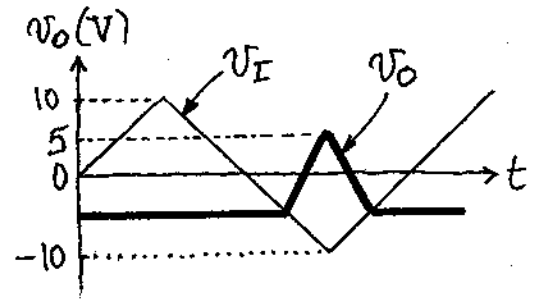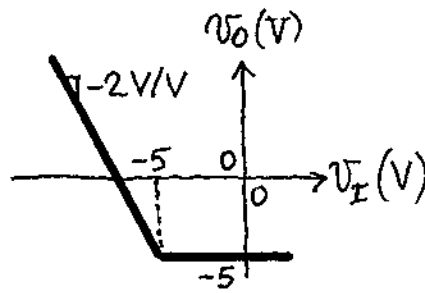$v_I > -5V \Rightarrow (i_R \rightarrow) \Rightarrow D_1 = \text{ON}, D_2 = \text{OFF}, i_{2R} = 0,$
 $v_O = v_N = -5V.$ $v_I < -5V \Rightarrow (i_R \leftarrow) \Rightarrow D_2 =$
 $\text{ON}, D_1 = \text{OFF}, v_O = v_N + 2R \times i_R = -5 + 2R(-5 -$
 $v_I)/R = -5 - 10 - 2v_I = -15 - 2v_I.$



9.20

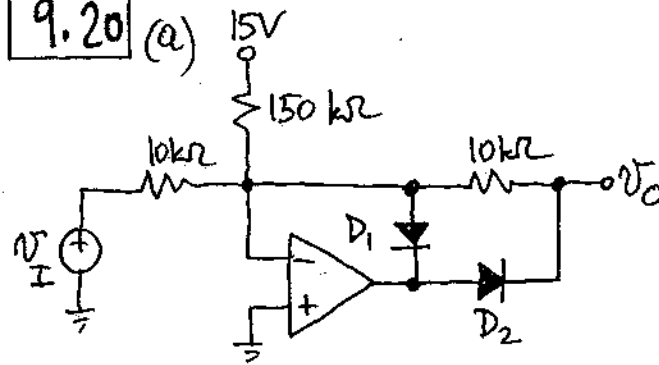


The value of v_I necessary to offset the current supplied by the 150-kΩ resistor

is $v_I = -(10/150)15 = -1V.$ We thus have two cases:
 $v_I > -1V,$ and $v_I < -1V.$ $v_I > -1V \Rightarrow v_O = 0,$
 and $v_I < -1V \Rightarrow v_O/10 + 15/150 = -v_I/10 \Rightarrow$
 $v_O = -v_I - 1V.$


(b) Reversing the diode polarities we

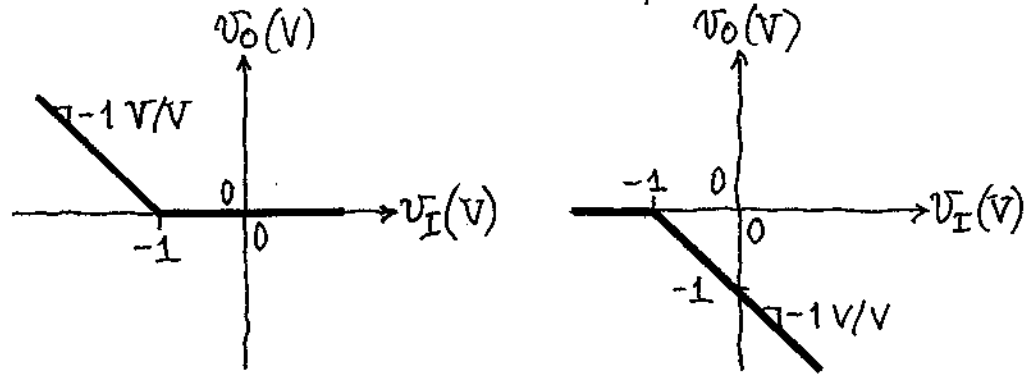9.13

get $v_o = 0$ for $v_I < -1$ V, and $v_o = -v_I - 1$ V for $v_I > -1$ V. VTCs are as follows:



9.21

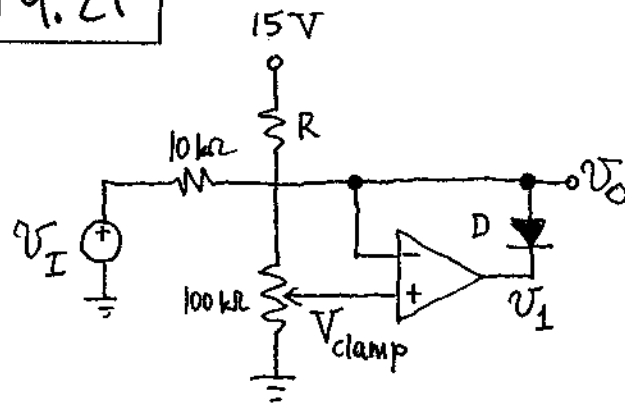

$$0 \leq V_{\text{clamp}} \leq 10 \text{ V} \Rightarrow R = 50 \text{ k}\Omega \text{ (use } 49.9 \text{ k}\Omega).$$

$$v_I > V_{\text{clamp}} \Rightarrow (i_{10\text{k}\Omega} \rightarrow) \Rightarrow D = \text{ON} \Rightarrow v_o = V_{\text{clamp}}.$$



$$v_I < V_{\text{clamp}} \Rightarrow D = \text{OFF} \Rightarrow v_o = v_I \Rightarrow v_1 = V_{\text{OH}}.$$

Advantage: superdiode precision; disadvantage: op amp saturation when $v_I < V_{\text{clamp}}$
 \Rightarrow recovery time.


9.14

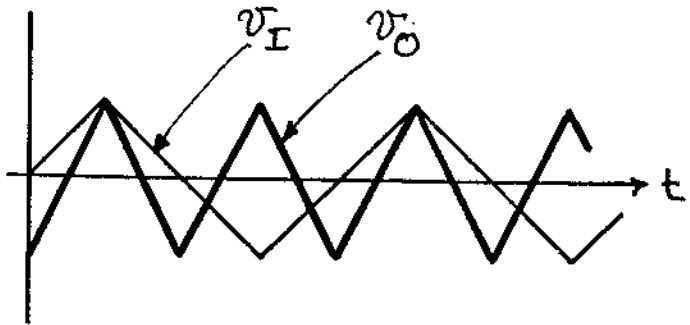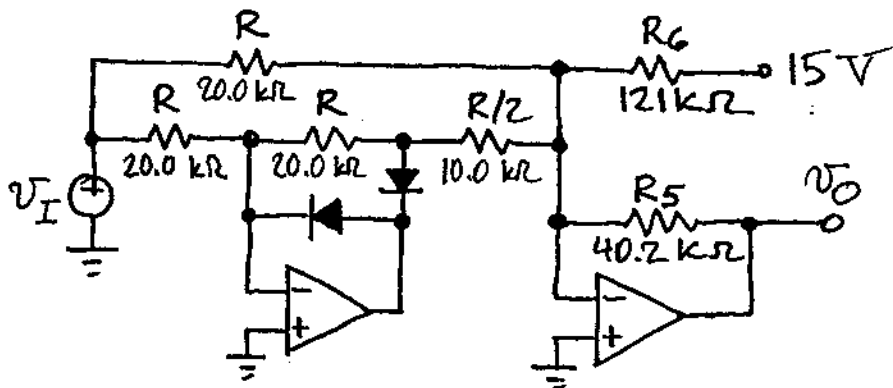9.22 A unity-gain absolute value circuit, when fed with a triangular wave, yields another triangular wave but with twice the frequency and half the amplitude. Thus, we need a gain of two ($R_5 = 2R$).

Moreover, to center the output about 0V, we must offset it by 5V in the negative direction. Use R_6 and +15V, as shown. We want $-5 = -(R_5/R_6)15 \Rightarrow R_6 = 3R_5 = 6R$. Use $R = 20.0 \text{ k}\Omega$, $R_5 = 40.2 \text{ k}\Omega$, and $R_6 = 121 \text{ k}\Omega$.



9.15

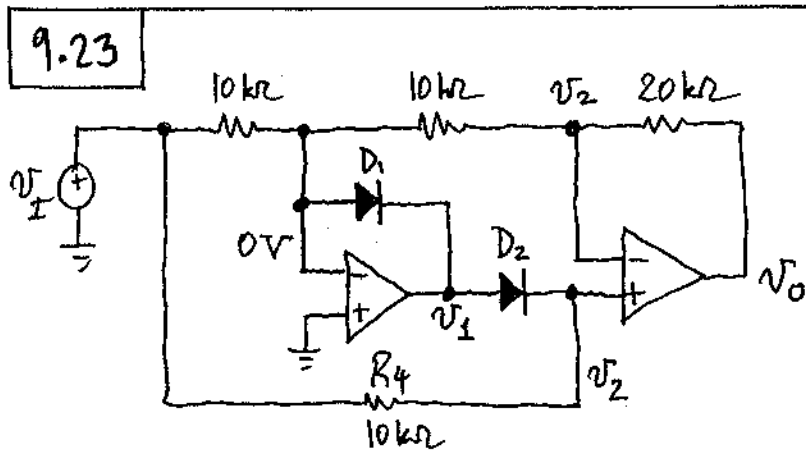

$$v_I = 10 \text{ mV} \Rightarrow D_1 = \text{ON}, D_2 = \text{OFF}; v_2 = 10 \text{ mV}; v_0 = 30 \text{ mV}; i_{D_1} = 2 \times (10 \text{ mV}) / (10 \text{ k}\Omega) = 2 \mu\text{A}; v_1 = -(26 \text{ mV}) \times \ln \left[\frac{(2 \times 10^{-6})}{(20 \times 10^{-15})} \right] = -479 \text{ mV}.$$

$$v_I = 1 \text{ V} \Rightarrow v_2 = 1 \text{ V}, v_0 = 3 \text{ V}, v_1 = -(26 \text{ mV}) \times \ln \left[\frac{(200 \times 10^{-6})}{(20 \times 10^{-15})} \right] = -599 \text{ mV}.$$

$$v_I = -1 \text{ V} \Rightarrow D_1 = \text{OFF}, D_2 = \text{ON}; v_2 = -v_I = 1 \text{ V}; v_0 = 3 \text{ V}; i_{D_2} = (v_2 - v_I) / R_4 = 200 \mu\text{A}; v_1 = v_2 + v_{D_2} = 1 + 0.599 = 1.599 \text{ V}.$$


9.24 A_p is maximized when R_2 is minimized and A_n is minimized when R_2 is minimized and R_1 is maximized.

$$|A_p - A_n|_{\max} = \left[1 + \frac{(A-1)R}{R(1-p)} \right] - \left[\frac{R(1-p)}{R(1+p)} + \frac{(A-1)R}{R(1+p)} \right] \cong$$

$$1 + (A-1)(1+p) - [(1-2p) + (A-1)(1-p)] = 2A_p. \text{ Thus,}$$


$$100 \left| \frac{(A_p - A_n)}{A} \right|_{\max} \cong 200 p, \text{ which is much better than } 800 p.$$

9.16

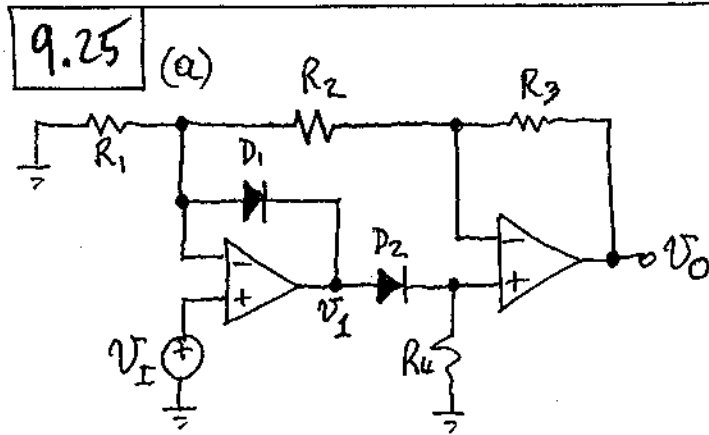

$V_I > 0 \Rightarrow V_1 > 0 \Rightarrow D_2 = \text{ON and } D_1 = \text{OFF} \Rightarrow V_O \times R_1 / (R_1 + R_2 + R_3) = V_I \Rightarrow A_p = V_O / V_I = 1 + (R_2 + R_3) / R_1$
 $V_I < 0 \Rightarrow D_1 = \text{ON and } D_2 = \text{OFF} \Rightarrow V_{p2} = 0, V_O = (-R_3 / R_2) V_{N1} = (-R_3 / R_2) V_I \Rightarrow A_m = -V_O / V_I = R_3 / R_2$. In either case, $V_O > 0$.

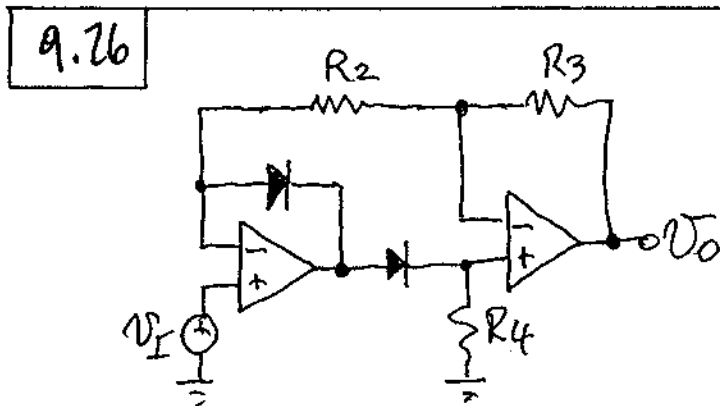(b) $R_3 / R_2 = 5, 1 + (R_2 + R_3) / R_1 = 5 \Rightarrow R_1 / R_2 = 1.5$. Pick $R_2 = 20.0 \text{ k}\Omega, R_1 = 30.0 \text{ k}\Omega, R_3 = 100 \text{ k}\Omega$. Advantages: high input resistance, needs only three matched resistances. Disadvantage: gain must be $> 1 \text{ V/V}$.



$V_I > 0 \Rightarrow V_O = V_I, A_p = 1 \text{ V/V}; V_I < 0 \Rightarrow V_O = -(R_3 / R_2) V_I, A_m = -R_3 / R_2 = -1 \text{ V/V}; V_O = |V_I|$.


9.17

$|A_m|_{\min} = \frac{R(1-p)}{R(1+p)} \cong 1+2p$; $A_p = 1$ regardless of resistance tolerances. Thus, $100|(A_p - A_m)/A|_{\max} \cong 200p$. For instance, with 1% resistances, A_m may depart from 1 V/V by as much as 2%.

9.27 (a) $V_I > 0 \Rightarrow V_{O2} = -13V \Rightarrow D_1 = \text{OFF} \Rightarrow V_{N1} = V_{P1} = V_I \Rightarrow V_O = V_I$. $V_I < 0 \Rightarrow D_1 = \text{ON} \Rightarrow V_{P1} = V_{N2} = V_{P2} = 0 \Rightarrow V_O = -(R_2/R_1)V_I = -V_I$. Thus, $V_O = |V_I|$.

(b) $V_I = +3V \Rightarrow V_{N2} = 3V, V_{O2} = -13V, V_O = 3V$. $V_I = -5V \Rightarrow V_{N2} = 0V, V_{O2} = 0.7V, V_O = +5V$.

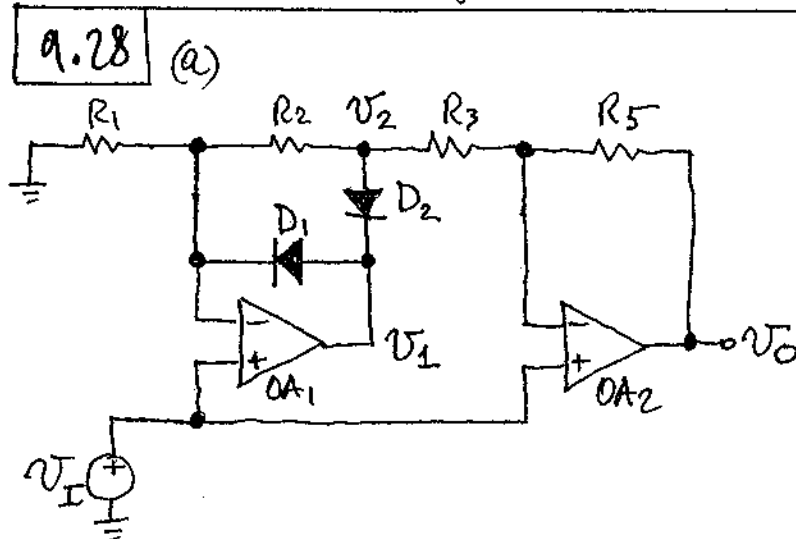(c) Advantages: requires only two matched resistances and one diode. Disadvantage: OA_2 saturates during $V_I > 0$, implying a long recovery time when V_I changes from positive to negative.



9.18


$v_I > 0 \Rightarrow D_1 = \text{ON and } D_2 = \text{OFF}; v_{N1} = v_{N2} = v_I$
 $\Rightarrow i_{R5} = i_{R3} = i_{R2} = 0 \Rightarrow v_0 = v_I.$

$v_I < 0 \Rightarrow D_1 = \text{OFF and } D_2 = \text{ON}; v_2 = (1 + R_2/R_1) \times$
 $v_I = 2v_I; v_0 = -(R_5/R_3)v_2 + (1 + R_5/R_3)v_I =$
 $-2 \times 2v_I + 3v_I = -v_I.$ Consequently, $v_0 = |v_I|.$

(b) $v_I = 2V \Rightarrow v_{N1} = 2V, v_1 = 2.7V,$
 $v_{N2} = 2V, v_2 = 2V, v_0 = 2V. v_I = -3V \Rightarrow$
 $v_{N1} = -3V, v_2 = -6V, v_1 = -6.7V, v_{N2} = -3V,$
 $v_0 = +3V.$

(c) $A_p = 1$ regardless of resistance tolerances.
 $A_m = (R_5/R_3)(1 + R_2/R_1) - (1 + R_5/R_3) =$
 $R_2 R_5 / R_1 R_3 - 1. A_p - A_m = 2 - R_2 R_5 / R_1 R_3.$

$|A_p - A_m|_{\max} = 2 - \frac{R(1-p)2R(1-p)}{R(1+p)R(1+p)} = 2 - 2(1-4p)$
 $= 8p,$ indicating that with 1% resistances,
 A_m can depart from unity by as much as 8%.

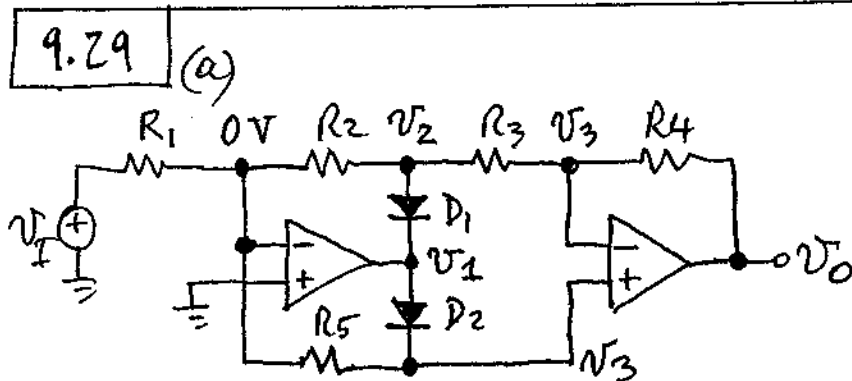

$v_I > 0 \Rightarrow D_1 = \text{ON and } D_2 = \text{OFF} \Rightarrow v_3 = 0,$
 $v_2 = -(R_2/R_1)v_I = -v_I, v_0 = -(R_4/R_3)v_2 =$
 $+v_I.$

9.19


$v_I < 0 \Rightarrow D_1 = \text{OFF}$ and $D_2 = \text{ON}$. KCL:

$$v_3/R_5 + v_3/(R_2+R_3) = -v_I/R_1 \Rightarrow v_3 = -\frac{2}{3}v_I,$$


$$v_0 = v_3 + R_4 v_3/(R_2+R_3) = \frac{3}{2}v_3 = -v_I. \text{ Combining, } v_0 = |v_I|.$$

(b) $v_I = 1V \Rightarrow v_2 = -1V, v_3 = 0, v_1 = -1.7V, v_0 = +1V.$
 $v_I = -3V \Rightarrow v_3 = +2V, v_1 = 2.7V, v_2 = v_3/2 = 1V, v_0 = +3V.$

(c)

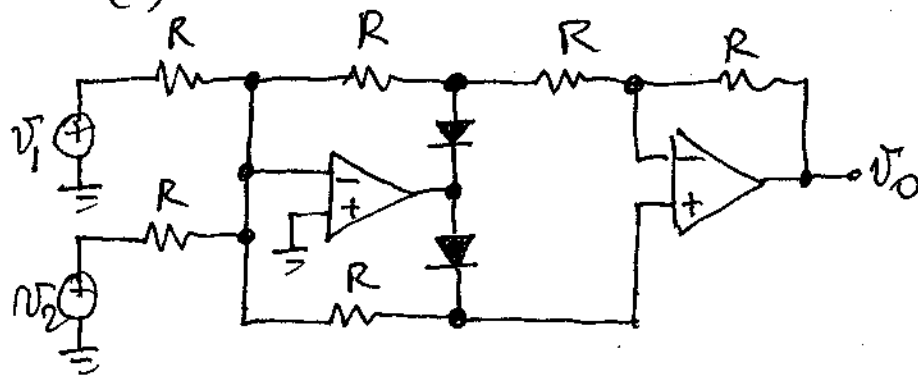

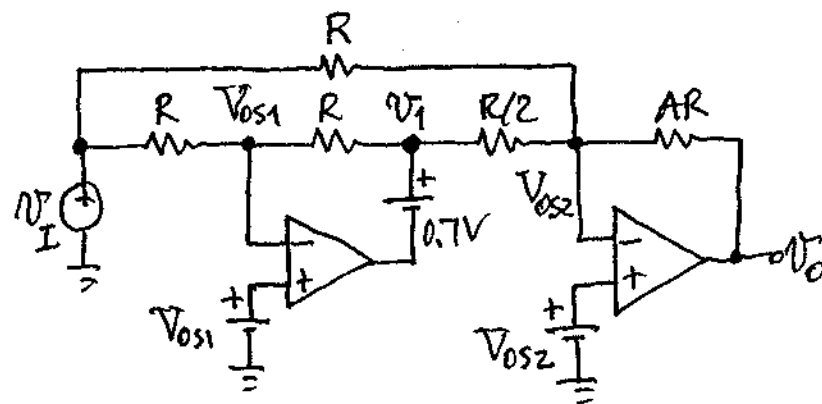
9.30 For $v_I > V_{os1}$, $D_1 = \text{OFF}$ and $D_2 = \text{ON}$:




Superposition: $v_1 = -v_I + 2V_{os1}$; $v_0 = -Av_I - 2Av_1 + [1 + AR/(R \parallel 0.5R)]V_{os2} = -Av_I - 2A(-v_I + 2V_{os1}) + (1 + 3A)V_{os2} = Av_I + (3A + 1)V_{os2} - 4AV_{os1}$. For $A = 1 \text{ V/V}$, $v_0 = v_I + 4(V_{os2} - V_{os1})$.
 The output error can be as large as $8V_{os}$.

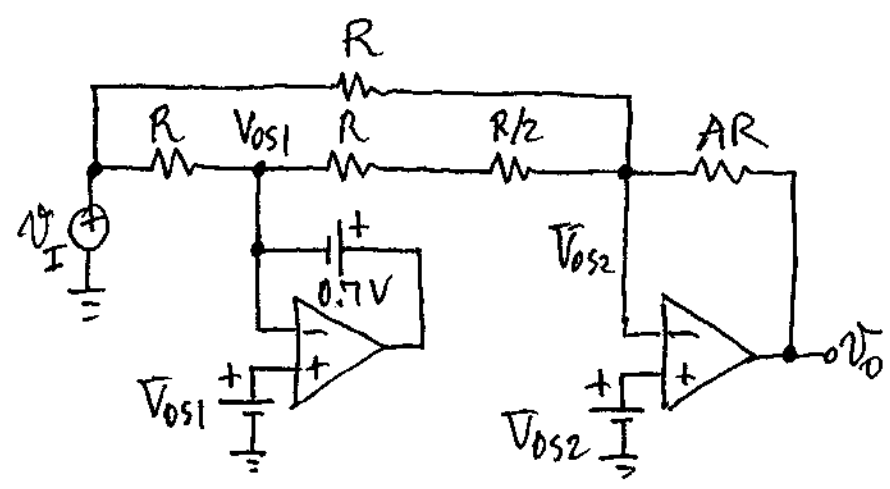9.20


For $V_I < V_{OS1}$, $D_1 = ON$ and $D_2 = OFF$:



Superposition: $V_O = -AV_I - [AR/(R+0.5R)]V_{OS1} + [1 + AR/(R||1.5R)]V_{OS2} = -AV_I + (5A/3 + 1)V_{OS2} - (2/3)V_{OS1}$. For $A = 1 V/V$, $V_O = -V_I + \frac{1}{3}(8V_{OS2} - 2V_{OS1})$. The output error can be as large as $(10/3)V_{OS}$. The accompanying figure illustrates the case $A = 1 V/V$, and $V_{OS1} = V_{OS2} = V_{OS}$.

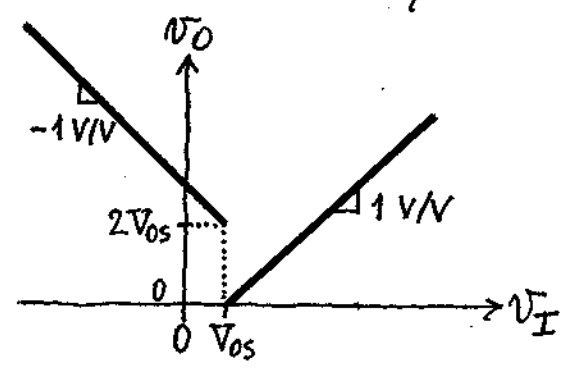

9.21

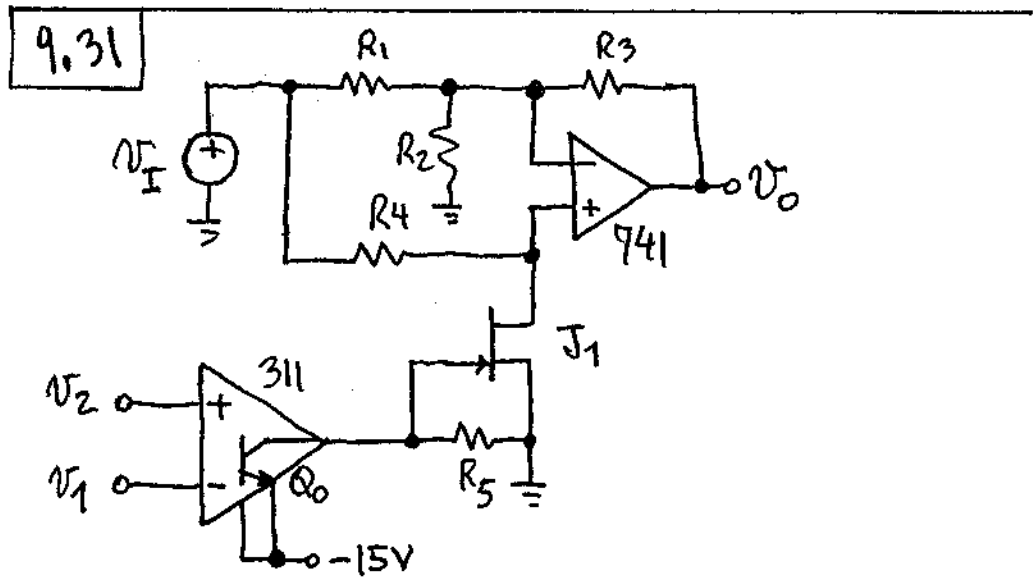

$$V_1 > V_2 \Rightarrow Q_0 = \text{Set} \Rightarrow J_1 = \text{OFF} \Rightarrow i_{R_4} = 0 \Rightarrow i_{R_1} = 0$$

$$\Rightarrow V_0 = (1 + R_3/R_2)V_I \Rightarrow R_3 = 9R_2.$$

$$V_1 < V_2 \Rightarrow Q_0 = \text{OFF} \Rightarrow J_1 = \text{ON} \Rightarrow V_{R_2} = 0 \Rightarrow$$

$$V_0 = -(R_3/R_1)V_I \Rightarrow R_3 = 10R_1. \text{ Use } R_2 = 20 \text{ k}\Omega,$$

$$R_3 = 180 \text{ k}\Omega, R_1 = 18 \text{ k}\Omega; \text{ moreover, let } R_4 =$$

$$20 \text{ k}\Omega, R_5 = 3.3 \text{ k}\Omega.$$

9.32 For $V_I = +5V$, $V_{GSM} = 0 \Rightarrow M_n = \text{OFF}$,
 and $|V_{GSP}| = 10V$; so, $r_{dsn(on)} = \infty$, and $r_{dsp(on)}$
 $= 1/[100 \times 10^{-6} \times (10 - 2.5)] = 1.33 \text{ k}\Omega.$

For $V_I = 2.5V$, $V_{GSM} = 2.5V \Rightarrow M_n$
 still off, and $|V_{GSP}| = 7.5V$; so, $r_{dsn(on)} = \infty$,
 and $r_{dsp(on)} = 1/[10^{-4} (7.5 - 2.5)] = 2 \text{ k}\Omega.$


For $V_I = 0V$, $V_{GSM} = 5V$ and $|V_{GSP}| =$
 $5V$; $r_{dsn} = r_{dsp} = 1/[10^{-4} \times (5 - 2.5)] = 4 \text{ k}\Omega$;
 $r_{dsp(on)} \parallel r_{dsn(on)} = 2 \text{ k}\Omega.$ Proceeding in similar

9.22

fashion, we find that


$$\begin{aligned} r_{ds}(\pm 5V) &= 1.33 \text{ k}\Omega, \quad r_{ds}(\pm 2.5V) = 2 \text{ k}\Omega, \quad r_{ds}(0) \\ &= 2 \text{ k}\Omega; \quad v_o(\pm 5V) = (100/101.33)(\pm 5) = \pm 4.934 \\ \text{V}, \quad v_o(\pm 2.5V) &= (100/102)(\pm 2.5) = \pm 2.451 \text{ V}, \\ v_o(0) &= 0. \end{aligned}$$

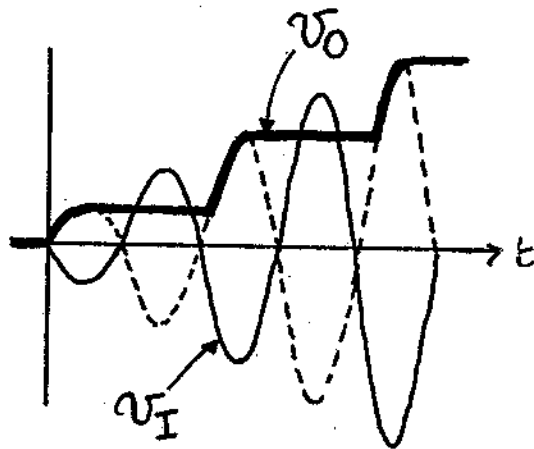9.33 As v_I swings in the negative direction, D_1 goes off and D_2 goes on, charging C_H so as to make $v_o = -v_I$. After v_I peaks out in the negative direction, the circuit holds the output at $v_o = -(R_2/R_1)v_{I(\text{min})}$. If $R_2 > R_1$, the circuit will also provide gain.




9.23

9.34

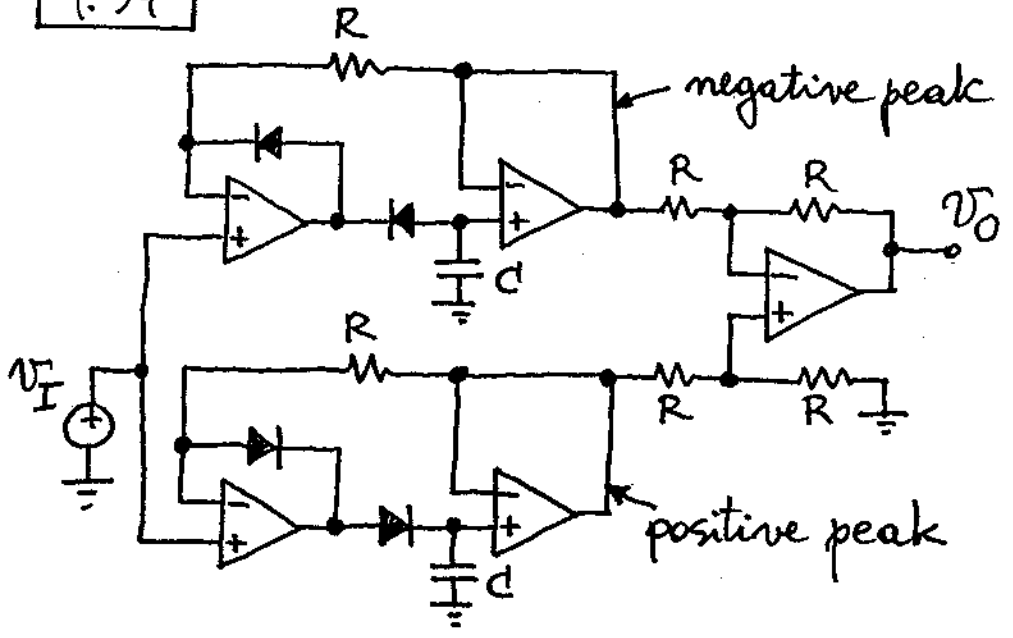


9.35

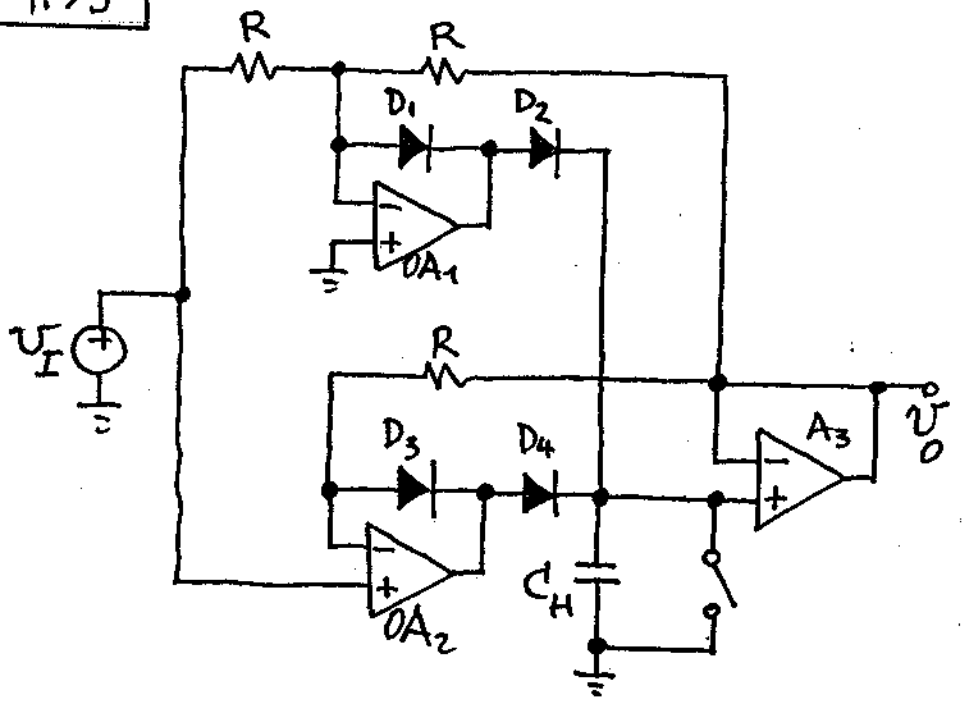

OA2 works as a voltage follower for positive peaks. OA2, a unity-gain inverting amplifier, processes negative peaks.


9.24

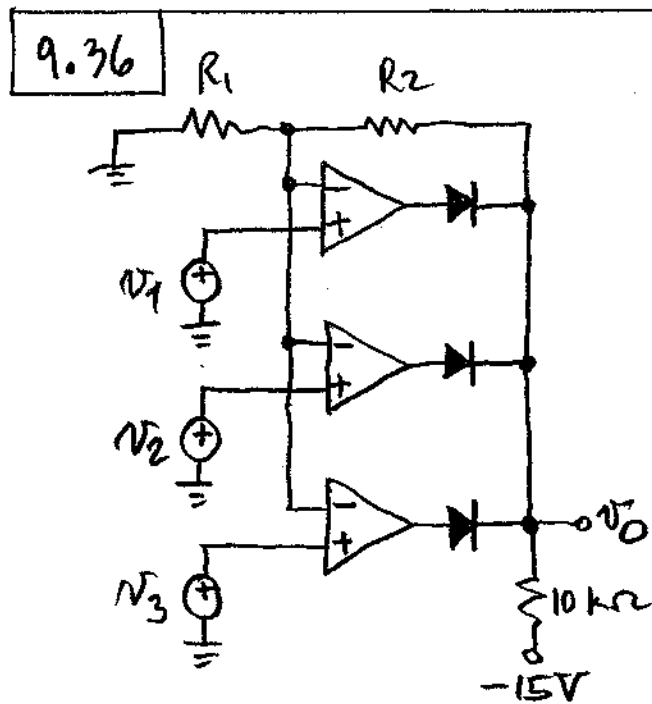

The op amp whose input is the most positive will succeed in making $v_N = v_P$. The remaining op amps will saturate at V_{OL} . With $R_1 = \infty$ and $R_2 = 0$, the circuit thus gives $v_0 = \max(V_1, V_2, V_3)$. With the voltage divider present, $v_0 = (1 + R_2/R_1) \times \max(V_1, V_2, V_3)$. If the diode polarities are reversed (and the $10\text{-k}\Omega$ resistance is returned to $+15\text{ V}$!), the circuit gives $v_0 = (1 + R_2/R_1) \times \min(V_1, V_2, V_3)$.

9.25

9.37

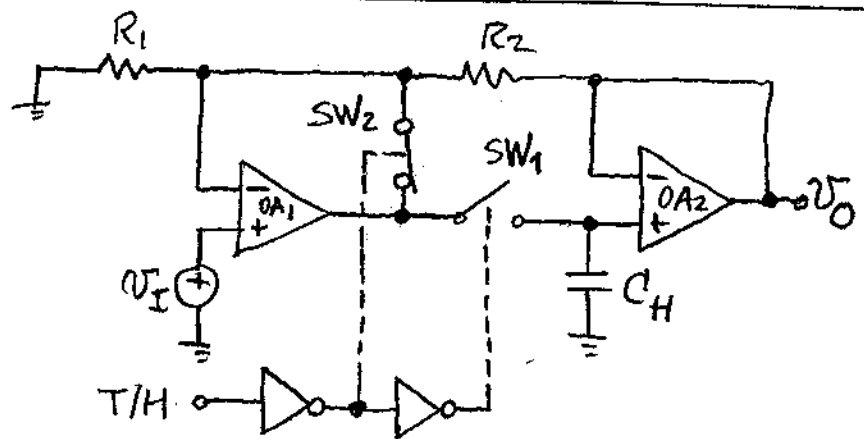

For a gain of 2 V/V , use $R_1 = R_2$. Because of the nonzero voltage difference between v_{O1} and v_{N1} during the track mode, the diodes must be removed. To prevent OA_1 from saturating during the hold mode, use an additional switch SW_2 and drive it in antiphase with respect to SW_1 to close the loop around OA_1 during the hold mode.

9.38

(a) $SW = \text{CLOSED} \Rightarrow v_O = -(R/R)v_I = -1.000 \text{ V}$. As the SW driver swings from 0 V to -15 V to open SW, a charge $\Delta Q = 15 \text{ V} \times 1 \text{ pF} = 15 \text{ pC}$ is pulled out of C_H , thus causing an output change $\Delta v_O = \Delta Q / C_H = 15 \times 10^{-12} / 10^{-9} = 15 \text{ mV}$, so $v_O = -1.000 + 0.015 = -0.985 \text{ V}$.

(b) $C_H \Delta v_O = I_L \times \Delta T \Rightarrow \Delta v_O = 1 \text{ mA} \times 50 \text{ ms} / 1 \text{ nF} = 50 \text{ mV}$. Thus, $v_O = -0.985 + 0.050 = -0.935 \text{ V}$.

9.26

9.39 (a) $T/H = -15V \Rightarrow J_1 = \text{closed and } J_2 = J_3 = \text{open}$. This is the hold mode, during which the droop due to leakage in C_H is compensated for by the droop due to leakage in C_F . Moreover, J_1 provides unity-feedback around A_1 to prevent saturation and speed up recovery when switching from T to S.
 $T/H = +15V \Rightarrow J_1 = \text{open and } J_2 = J_3 = \text{closed}$. This is the sample mode, during which J_3 closes the path from A_1 to C_H and J_2 discharges C_F and provides unity-feedback around A_2 .

(b) 5% of 1 mA is 50 pA. Thus,
 $\Delta V_0/\Delta t = 50 \times 10^{-12} / 10^{-9} = 50 \text{ mV/s} = 0.05 \text{ } \mu\text{V}/\mu\text{s}$. Without droop compensation we would have $\Delta V_0/\Delta t = 1 \text{ V/s} = 1 \text{ } \mu\text{V}/\mu\text{s}$.