

4.1

$$4.1 \quad (a) \quad A(\omega) = 10 \log_{10} [1 + \epsilon^2 (\omega/\omega_c)^{2m}] .$$

$$A_{\max} = 1 \text{ dB} \Rightarrow A(\omega_c) = 10 \log_{10} (1 + \epsilon^2) = 1 \Rightarrow \epsilon = 0.5088$$

$$A_{\min} = 10 \log_{10} [1 + \epsilon^2 (\omega_s/\omega_c)^{2m}] \Rightarrow \epsilon^2 (\omega_s/\omega_c)^{2m} = 10^{A_{\min}/10} - 1 \Rightarrow 1.2^{2m} = (10^{20/10} - 1) / 0.5088^2 \Rightarrow$$

$$m = 16.3 \Rightarrow \text{use } m = 17.$$

$$(b) \quad A(\omega_s) = 10 \log_{10} [1 + 0.5088^2 (1.2)^{34}] = 21.09 \text{ dB}.$$

$$(c) \quad \epsilon^2 = (10^{20/10} - 1) / (1.2)^{34} \Rightarrow \epsilon = 0.4485$$

$$A_{\max} = 10 \log_{10} (1 + 0.4485^2) = 0.7959 \text{ dB}.$$

4.2 $A_{\max} = 1 \text{ dB} \Rightarrow A(\omega_c) = 10 \log_{10} (1 + \epsilon^2) \Rightarrow \epsilon = 0.5088$. $A(\omega_s) = 10 \log_{10} [1 + \epsilon^2 C_m^2(\omega_s/\omega_c)] = 10 \log_{10} [1 + 0.5088^2 \cosh^2(m \cosh^{-1} 2)] = 10 \log_{10} [1 + 0.5088^2 \cosh^2(1.317m)]$. Trying out different values of m , we find that $A(\omega_s) = 11.36 \text{ dB}$ for $m = 2$, and $A(\omega_s) = 22.46 \text{ dB}$ for $m = 3$. We thus choose $m = 3$, which is substantially less than $m = 7$ of Example 4.1.

$$4.3 \quad |H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \cos^2 [7 \cos^{-1}(\omega/\omega_c)]}}$$

Peaks occur for $\cos [7 \cos^{-1}(\omega/\omega_c)] = 0$, valleys for $\cos [7 \cos^{-1}(\omega/\omega_c)] = \pm 1$.

4.2

Peaks: $\angle \cos^{-1}(\omega_p/\omega_c) = 2(k+1)\frac{\pi}{2}, k=0,1,2,3.$


$\omega_p = \omega_c \cos[(2k+1)\frac{\pi}{4}] = 0.975\omega_c, 0.7818\omega_c, 0.434\omega_c, 0.$

Valleys: $\angle \cos^{-1}(\omega_v/\omega_c) = k\pi, k=0,1,2,3.$

$\omega_v = \omega_c \cos \frac{k\pi}{4} = \omega_c, 0.901\omega_c, 0.623\omega_c, 0.223\omega_c.$

$A_{max} = 0.5 \text{ dB} \Rightarrow 0.5 = 10 \log_{10}(1 + \epsilon^2) \Rightarrow \epsilon = 0.3493;$
 $\angle \cosh^{-1} 2 = 9.219; A(2\omega_c) = 10 \times \log [1 + \epsilon^2 \cosh^2 9.219] = 64.9 \text{ dB}.$
 $\angle \cos^{-1} 10 = 20.95;$
 $A(10\omega_c) = 10 \log_{10}[1 + \epsilon^2 \cosh^2 20.95] = 166.8 \text{ dB}.$

4.4 (a) $|H| \text{ (dB)}$

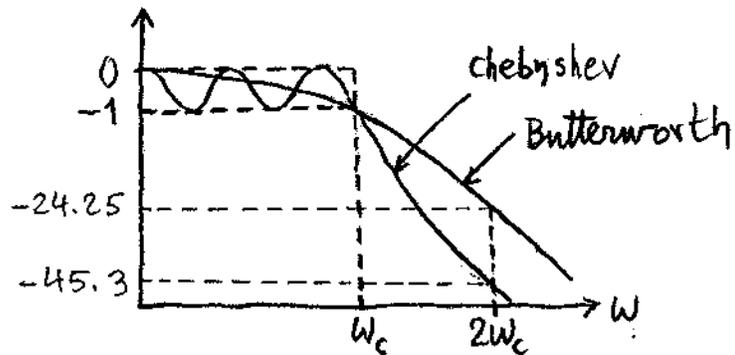

(b) $A_{max} = 1 \text{ dB} \Rightarrow 10 \log_{10}(1 + \epsilon^2) = 1 \Rightarrow \epsilon = 0.5088.$

Butterworth: $A(2\omega_c) = 10 \log_{10}[1 + \epsilon^2 \times 2^{2 \times 5}] = 24.25 \text{ dB}.$


Chebyshev: $A(2\omega_c) = 10 \log_{10}[1 + \epsilon^2 \cosh^2(5 \cosh^{-1} 2)] = 45.3 \text{ dB}.$

4.3

4.5 (a)

$$|H|^2 = \frac{1}{[1 - 2(\omega/\omega_c)^2]^2 + [2(\omega/\omega_c) - (\omega/\omega_c)^3]^2}$$

$$|H|^2 = \frac{1}{1 + (\omega/\omega_c)^6}$$

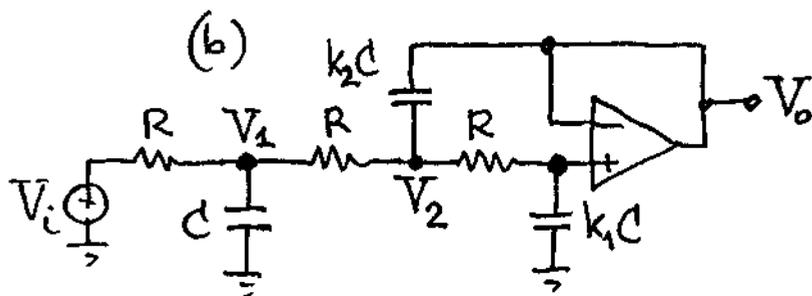

$$V_o = \frac{1}{1 + j\omega k_1 RC} V_2 \Rightarrow V_2 = (1 + j\omega k_1 RC) V_o.$$

$$\frac{V_i - V_1}{R} = j\omega C V_1 + \frac{V_1 - V_2}{R}, \text{ that is,}$$

$$V_i = (2 + j\omega RC) V_1 - V_2.$$

$$\frac{V_1 - V_2}{R} = j\omega k_2 C (V_2 - V_o) + \frac{V_2 - V_o}{R}, \text{ that is,}$$

$$V_1 = V_2 (j\omega k_2 RC + 2) - V_o (j\omega k_2 RC + 1).$$

Eliminating V_1 and V_2 and collecting,

$$H = \frac{1}{1 - j(\omega RC)^3 k_1 k_2 - (\omega RC)^2 2k_1(k_2 + 1) + j\omega RC(3k_1 + 1)}$$

$$\text{Letting } (\omega RC)^3 k_1 k_2 = (\omega/\omega_c)^3 \text{ yields } \omega_c = \frac{1}{(k_1 k_2)^{1/3} RC}.$$

$$\text{Letting } (\omega RC)^2 2k_1(k_2 + 1) = 2(\omega/\omega_c)^2 \text{ and}$$

$$\omega RC(3k_1 + 1) = 2 \text{ yields, respectively,}$$

$$\frac{k_1(k_2 + 1)}{(k_1 k_2)^{2/3}} = 1 \text{ and } \frac{3k_1 + 1}{(k_1 k_2)^{1/3}} = 2. \text{ Eliminat-}$$


44

ing the product $k_1 k_2$ yields $(3k_1 + 1)^2 = 4k_1 (k_2 + 1)$. Eliminating the product $k_1 k_2$ once more, $27k_1^3 + 9k_1^2 + 5k_1 - 1 = 0$. Solving by iteration starting with $k_1 = 0$ yields $k_1 = 0.14537$. Backsubstituting, $k_2 = 2.5468$.

(c) Let $R = 100 \text{ k}\Omega$. Then, $C = 1 / [2\pi \times 10^3 \times 10^5 \times (0.14537 \times 2.5468)^{1/3}] = 2.216 \text{ nF}$, $mC = 322.2 \text{ pF}$, $mC = 5.645 \text{ nF}$.

$$\boxed{4.6} \quad (a) |H|^2 = \frac{1}{[1 - (\omega/\omega_c)^2]^2 + (2 - \sqrt{2})(\omega/\omega_c)^2} \times \frac{1}{[1 - (\omega/\omega_c)^2]^2 + (2 + \sqrt{2})(\omega/\omega_c)^2} = \frac{1}{1 + (\omega/\omega_c)^8}$$

(b)

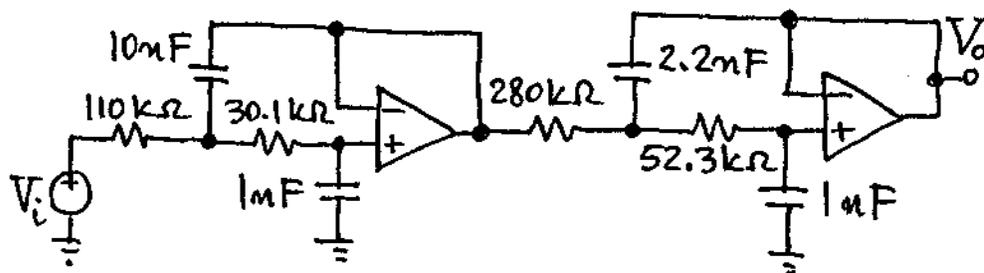

4.5


4.7 1st stage: leave it unchanged since the component spread is low.

2^d stage: Use $K=2$. Then, $Q = \sqrt{m} = 2.20 \Rightarrow m = 4.84$. Let $C = 1 \text{ mF}$. Then, $R = 1/(2\pi Q f_0 C) = 1/(2\pi \times 2.2 \times 9.56 \times 10^3 \times 10^{-9}) = 7.567 \text{ k}\Omega$, $mR = 36.62 \text{ k}\Omega$.

3^d stage: Use $m=n=1$, $C = 1 \text{ mF}$. Then, $R = 1/(2\pi f_0 C) = 1/(2\pi \times 12.74 \times 10^3 \times 10^{-9}) = 12.492 \text{ k}\Omega$. $K = 3 - 1/Q = 3 - 1/8 = 2.875 \Rightarrow R_B/R_A = 1.875$. Let $R_A = 10.2 \text{ k}\Omega$, $R_B = 19.1 \text{ k}\Omega$.

Dc Gain: $H_0 = K_2 \times K_3 = 2 \times 2.875 = 5.75$. To achieve $H_0 = 1$, split the first resistor of the third stage into two resistors, R_1 and R_2 , such that $R_2/(R_1 + R_2) = 1/5.75$ and $R_1 // R_2 = 12.49 \text{ k}\Omega$. Thus, $R_1 R_2 / (R_1 + R_2) = R_1 / 5.75 = 12.49 \Rightarrow R_1 = 71.83 \text{ k}\Omega$ and $R_2 = 15.12 \text{ k}\Omega$. To calibrate Q_3 , it may be advisable to make the $19.1 \text{ k}\Omega$ resistor adjustable.

4.6

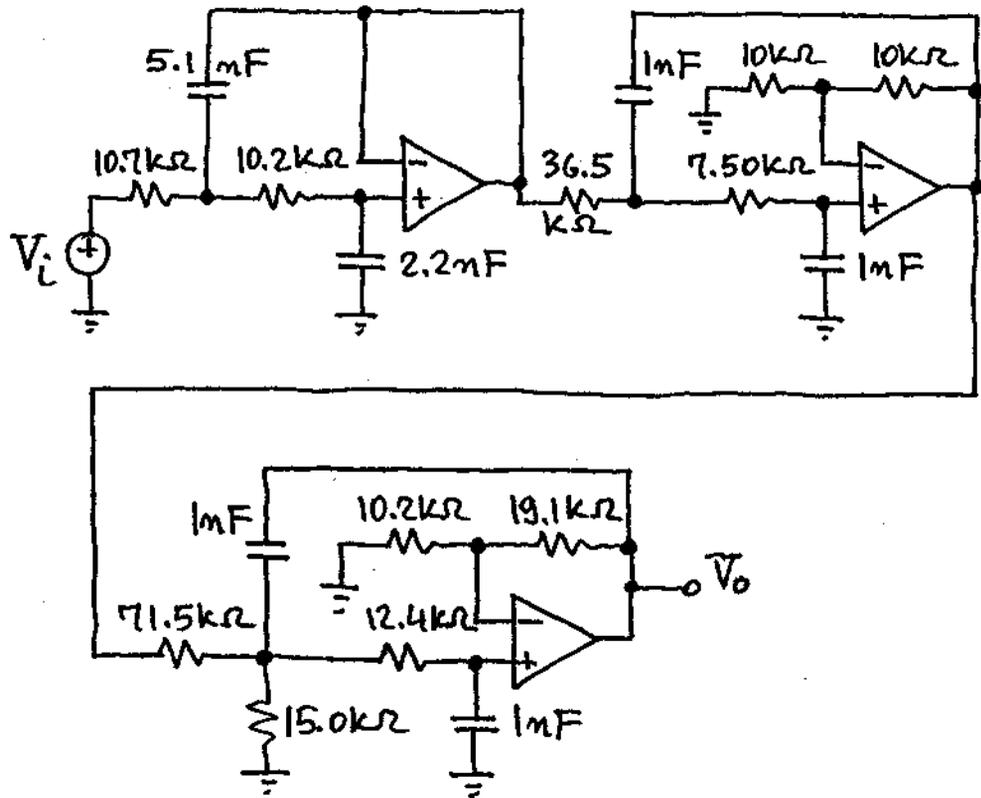

4.8

Retracing the steps of Example 3.10, we find the following values:

$$C = 2 \text{ nF}, mC = 3.3 \text{ nF}, R = 12.51 \text{ k}\Omega, mR = 19.43 \text{ k}\Omega.$$

$$C = 1.2 \text{ nF}, mC = 10 \text{ nF}, R = 3.96 \text{ k}\Omega, mR = 9.41 \text{ k}\Omega.$$


$$C = 390 \text{ pF}, mC = 10 \text{ nF}, R = 5.57 \text{ k}\Omega, mR = 9.465 \text{ k}\Omega.$$

$$C = 330 \text{ pF}, mC = 30 \text{ nF}, R = 3.22 \text{ k}\Omega, mR = 4.21 \text{ k}\Omega.$$

$$C = 100 \text{ pF}, mC = 0.1 \mu\text{F}, R = 2.456 \text{ k}\Omega, mR = 4.478 \text{ k}\Omega.$$

The implementation with 1% rounded off values is shown in the figure.

4.7

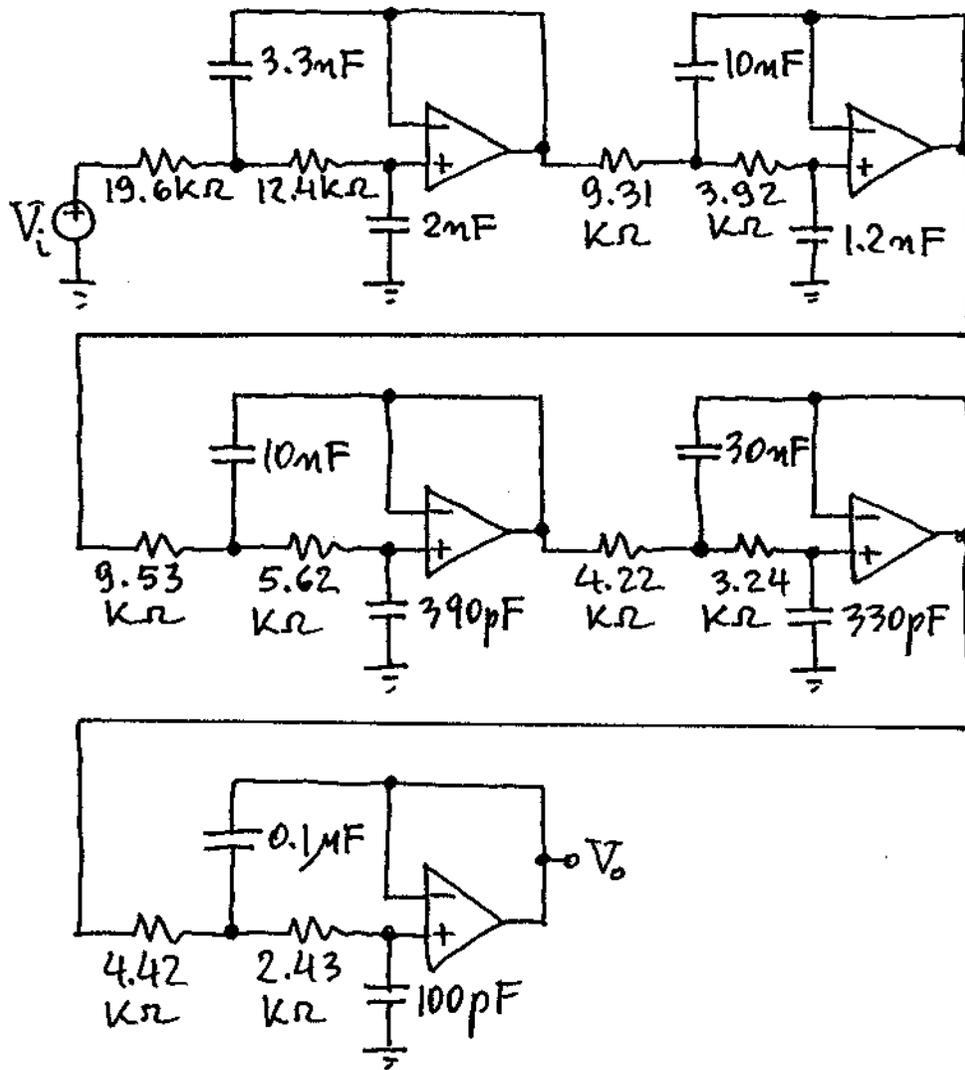

4.9 Using Table 4.1, we find:


1st Stage: $f_0 = 1.561 \text{ kHz}$, $Q = 0.564$.

Let $C = 10 \text{ mF}$. Then, $R = 1 / (2\pi \times 1.561 \times 10^3) = 10.2 \text{ k}\Omega$. $K = 3 - 1/Q = 3 - 1/0.564 = 1.227$
 $\Rightarrow R_B/R_A = 0.227$. Use $R_A = 10.0 \text{ k}\Omega$, $R_B = 2.26 \text{ k}\Omega$.

2d stage: $f_0 = 1.760 \text{ kHz}$, $Q = 0.917$.
 $C = 10 \text{ mF}$, $R = 9.04 \text{ k}\Omega$, $R_A = 10.0 \text{ k}\Omega$, $R_B = 9.09 \text{ k}\Omega$.

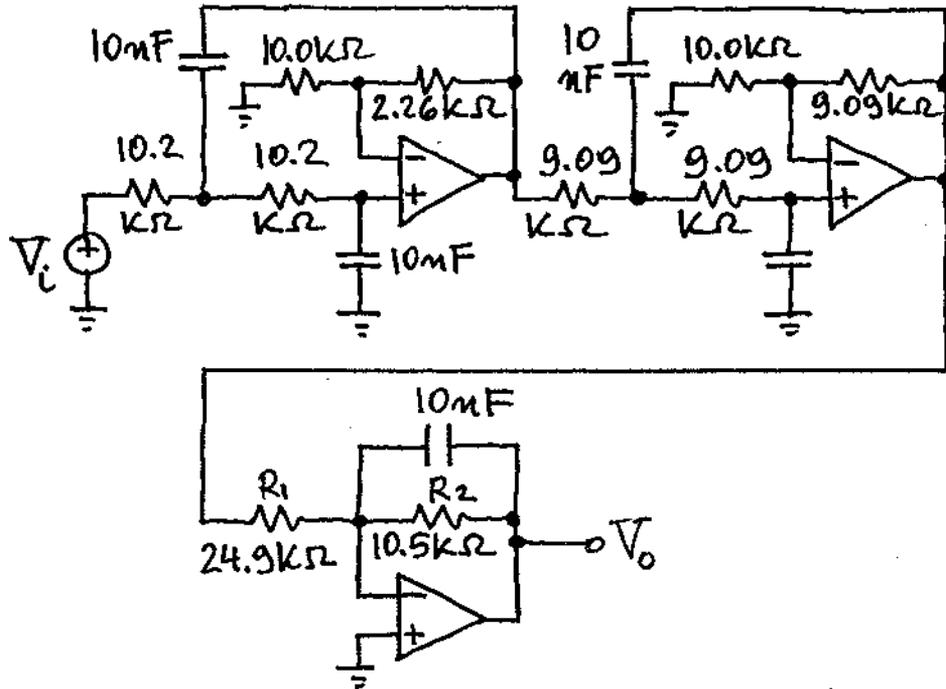4.8

3rd stage: $f_0 = 1.507 \text{ kHz}$, $C = 10 \text{ mF}$, $R_2 = 1/(2\pi f_0 C) = 1/(2\pi \times 1.507 \times 10^{-3}) = 10.56 \text{ k}\Omega$.
 For 0 dB dc gain we need $R_2/R_1 \times K_1 \times K_2 = 1 \Rightarrow R_1 = 10.56 \times 1.227 \times 1.909 = 24.73 \text{ k}\Omega$.



4.10 From Table 4.1, we need three second-order stages with $Q_1 = 0.555$, $Q_2 = 0.802$, $Q_3 = 2.247$, and a first-order stage. Use $C = 1 \text{ mF}$ throughout. Then:


1st stage: $Q = \sqrt{m} = 0.555 \Rightarrow m = 0.308$;
 $R = 1/2\pi Q f_0 C = 1/(2\pi \times 0.555 \times 10^4 \times 10^{-9}) = 28.67 \text{ k}\Omega$; $mR = 8.83 \text{ k}\Omega$. Similarly:

2nd stage: $R = 19.84 \text{ k}\Omega$, $mR = 12.76 \text{ k}\Omega$.

3rd stage: $R = 7.083 \text{ k}\Omega$, $mR = 35.76 \text{ k}\Omega$

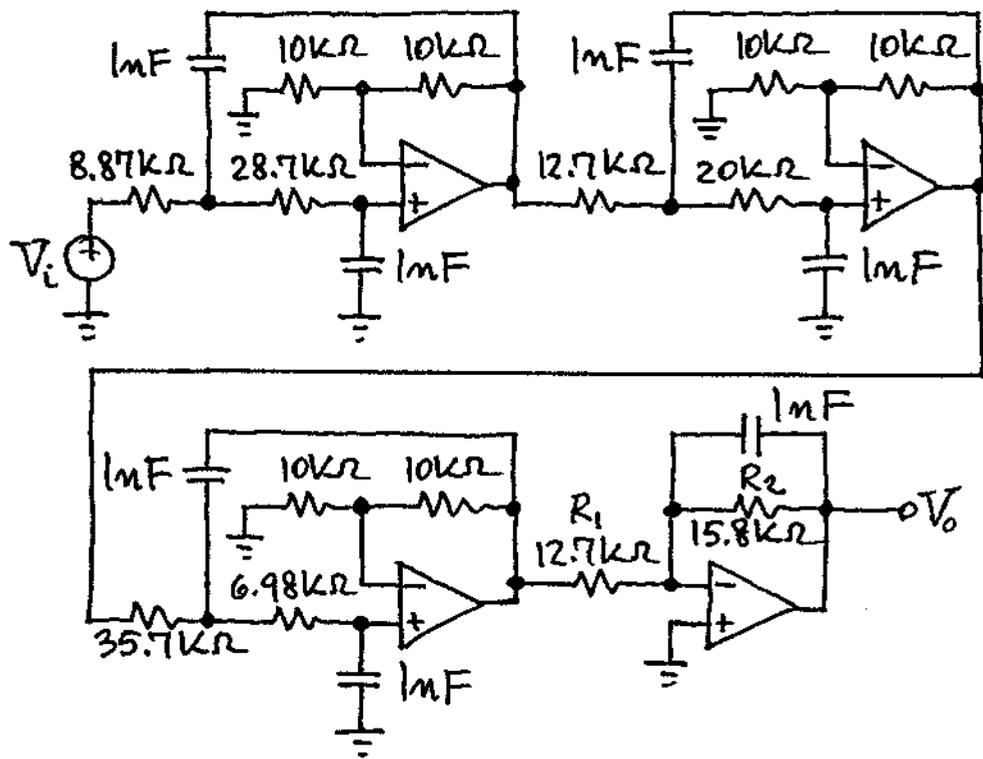4.9

1st-order stage: $C = 1\text{mF}$, $R_2 = 1/(2\pi f_0 C) = 1/(2\pi \times 10^4 \times 10^{-9}) = 15.9\text{k}\Omega$.
 $(R_2/R_1) \times 2 \times 2 \times 2 = 20\text{dB} = 10 \Rightarrow R_1 = (8/10)R_2 = 12.73\text{k}\Omega$.




4.11 From Table 4.1 we see that we need two second-order stages with $f_{01} = 360/0.994 = 362.17\text{Hz}$, $Q_1 = 5.556$, and $f_{02} = 360/0.655 = 549.62\text{Hz}$, $Q_2 = 1.399$; and a first-order stage with $f_{03} = 360/0.289 = 1,245.7\text{Hz}$.

1st stage: Let $C = 10\text{mF}$ and $m = 1$.
 Then, $Q = (\sqrt{m})/2 = 5.556 \Rightarrow m = 123.48$
 $R = 1/(2\pi \sqrt{m} f_{01} C) = 1/(2\pi \times 2 \times 5.556 \times 362.17 \times 10^{-8}) = 3.955\text{k}\Omega$, $mR = 488.3\text{k}\Omega$.



2^d Stage: $C = 10\text{mF}$, $R = 10.35\text{k}\Omega$,
 $mR = 81.07\text{k}\Omega$.

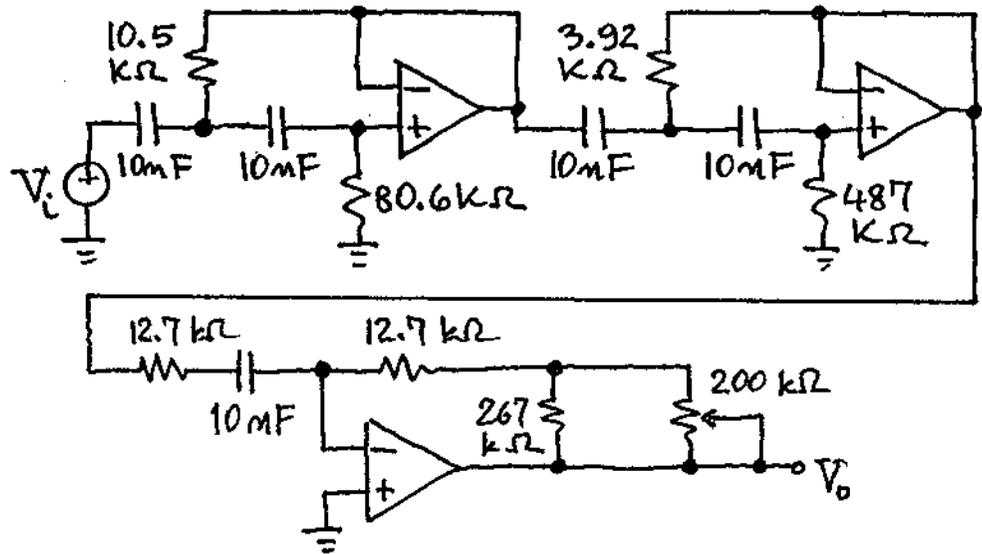4.10

3rd stage: let $C_1 = 10\text{mF}$. Then, $R_1 = 1/(2\pi f_{03} C) = 1/(2\pi \times 1,245.7 \times 10^{-8}) = 12.77\text{ k}\Omega$. 20 dB high-frequency gain $\Rightarrow R_1 \leq R_2 \leq 10R_1$, $R_1 = 12.7\text{ k}\Omega$, $10R_1 = 127\text{ k}\Omega$.



4.12

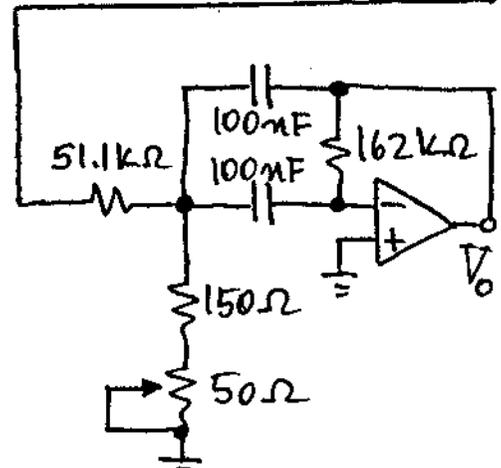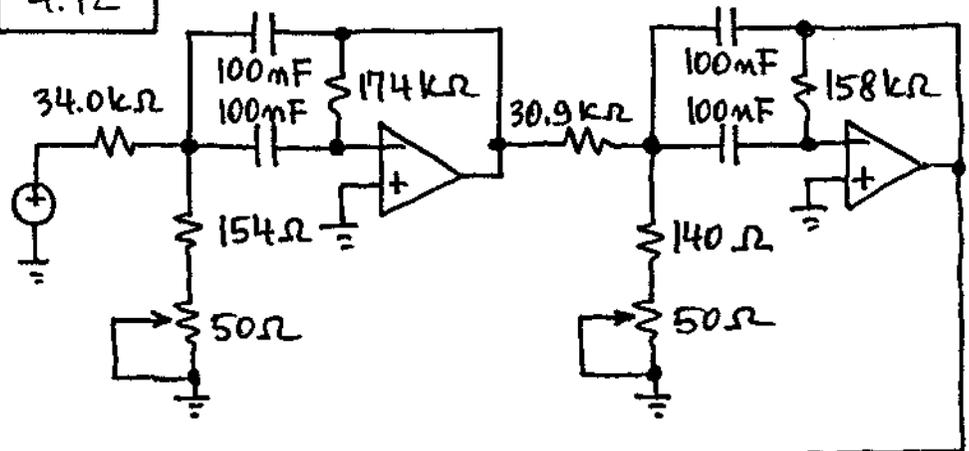

4.11




4.13 Use $C = 1 \text{ mF}$ throughout.

$$\begin{aligned} \text{1st stage: } R &= 1/(2\pi f_{o1} C) = 1/(2\pi \times \\ &3460.05 \times 10^{-9}) = 45.99 \text{ k}\Omega. R_1 = Q_1 R = 31.4 \times \\ &45.99 = 1.444 \text{ M}\Omega. \text{ Let } R_2 = 10 \text{ k}\Omega. \text{ Then,} \\ R_4 &= (R_2/Q_1) f_{o1}^2 / |f_{o1}^2 - f_{z1}^2| = (10^4/31.4) \times \\ &3460.05^2 / |3460.05^2 - 3600^2| = 3.859 \\ &\text{k}\Omega. R_5 = R_2 (f_{o1}/f_{z1})^2 = 10^4 (3460.05/ \\ &3600)^2 = 9.238 \text{ k}\Omega. \end{aligned}$$

$$\begin{aligned} \text{2d stage: } R &= 42.491 \text{ k}\Omega, R_1 = \\ &1.334 \text{ M}\Omega, R_4 = 4.177 \text{ k}\Omega, R_5 = 10 \text{ k}\Omega. \end{aligned}$$

$$\begin{aligned} \text{3d stage: } R &= 1/(2\pi f_{o3} C) = 1/ \\ &(2\pi \times 3600 \times 10^{-9}) = 44.21 \text{ k}\Omega. R_1 = Q_3 R = \\ &8.92 \times 44.21 = 385.5 \text{ k}\Omega. \end{aligned}$$

4.12

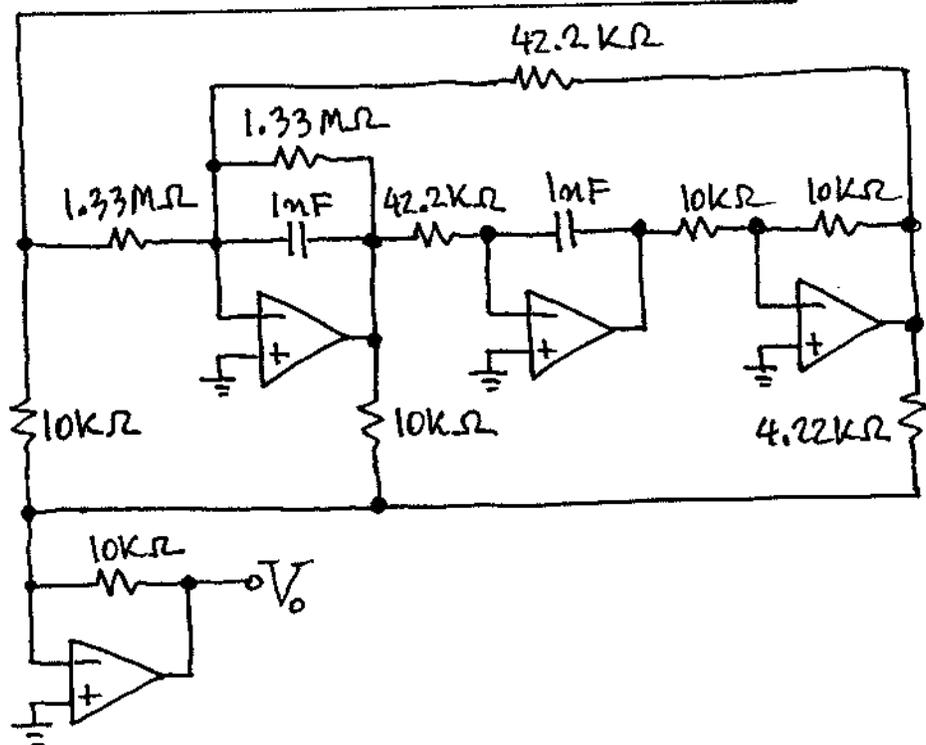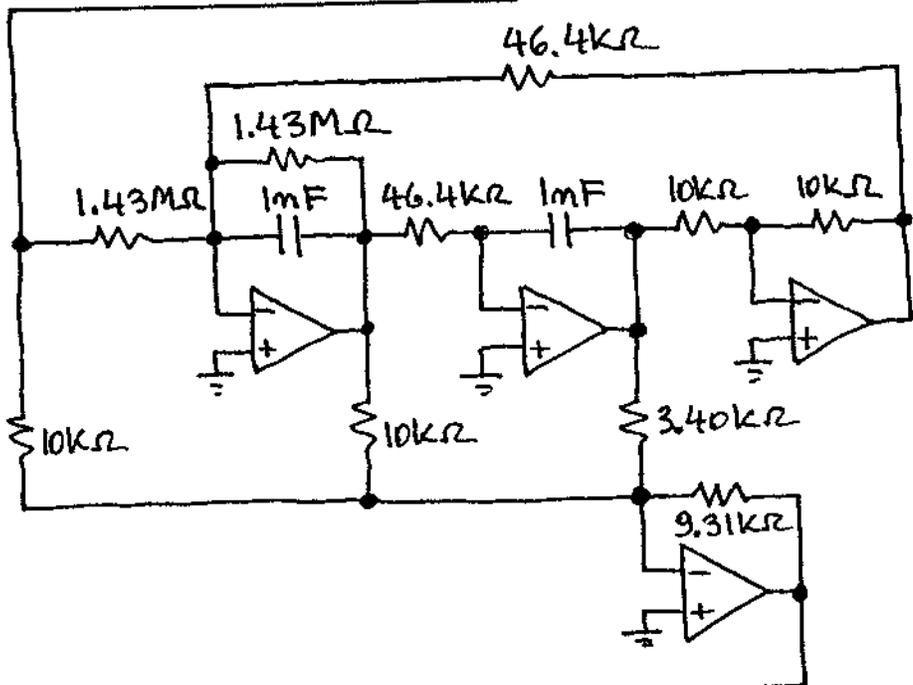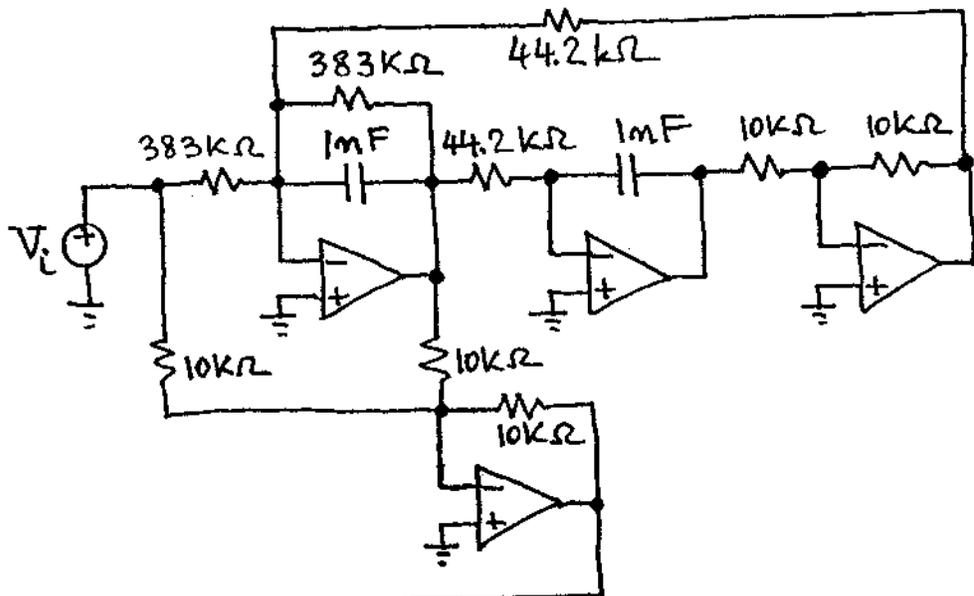

4.13


4.14 Using the FILDES Program, we find that a 7th order filter with the following individual-stage parameters

Stage No	f_0 (kHz)	Q
1	10.08	8.84
2	8.23	2.57
3	5.04	1.09
4	2.56	

will provide an attenuation of 64.9 dB at 20 kHz. For the first three stages use the unity-gain KRC configuration, for which

$$\omega_0 = \frac{1}{\sqrt{mn}RC} \quad Q = \frac{\sqrt{mn}}{m+1} \quad H_{0LP} = 1 \text{ V/V.}$$

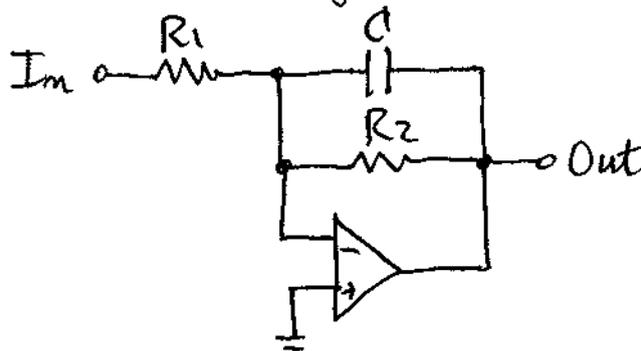For the last stage use the 1st order circuit



$$\text{with } \omega_0 = \frac{1}{R_2 C} \quad H_0 = -\frac{R_2}{R_1}.$$

Pick $C = 0.1 \mu\text{F}$, $R_2 = 62.17 \text{ k}\Omega$, $R_1 = 15.6 \text{ k}\Omega$.
For the other stages use the following:



4.14

Stage No 1: $C = 1\text{mF}$, $mC = 330\text{mF}$,
 $R = 688\Omega$, $mR = 1.098\text{ k}\Omega$.

Stage No 2: $C = 1\text{mF}$, $mC = 33\text{mF}$,
 $R = 2.08\text{ k}\Omega$, $mR = 5.44\text{ k}\Omega$.


stage No 3: $C = 1\text{mF}$, $mC = 5\text{mF}$
 $R = 11.26\text{ k}\Omega$, $mR = 17.71\text{ k}\Omega$

Computer simulation gives the following:

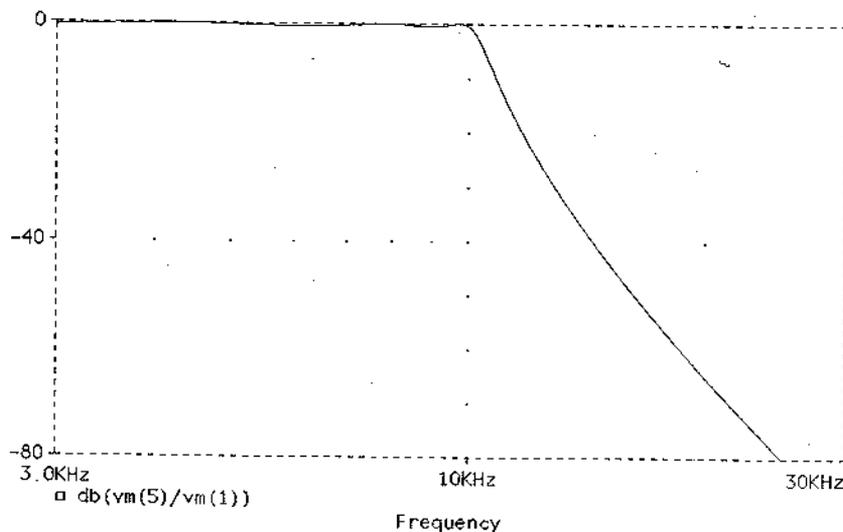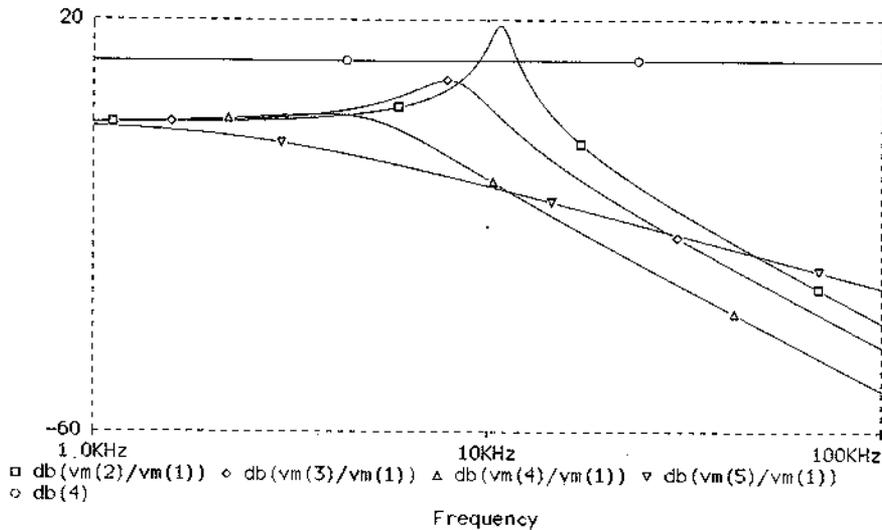


4.15

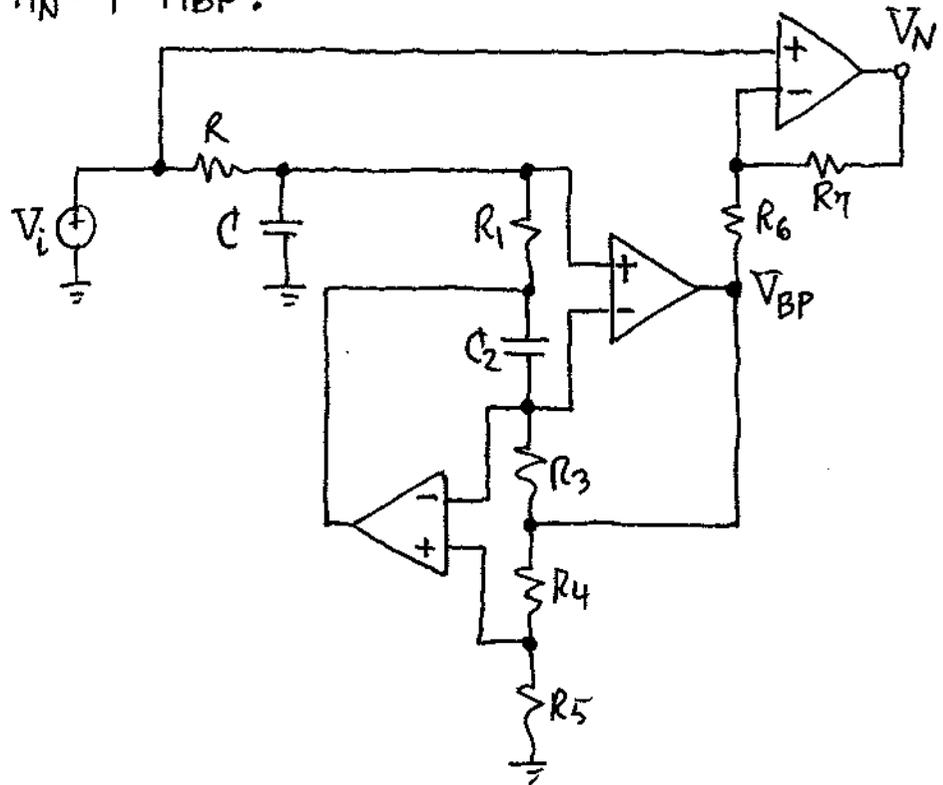4.15 (a) Implement the notch response as $H_N = 1 - H_{BP}$.



Let $R_4 = R_5$, so that $V_{BP} = 2H_{BP}V_i$; let $R_6 = R_7$, so that $V_N = 2V_i - 2H_{BP}V_i = H_{ON}H_NV_i$, $H_{ON} = 2 V/V$.
 Let $C_2 = C = 0.1 \mu F$. Then, $R_1 = R_3 = 13.26 \text{ k}\Omega$ (use $13.3 \text{ k}\Omega$), $R = 20R_1 = 267 \text{ k}\Omega$. Use $R_3 = R_4 = R_6 = R_7 = 10.0 \text{ k}\Omega$.

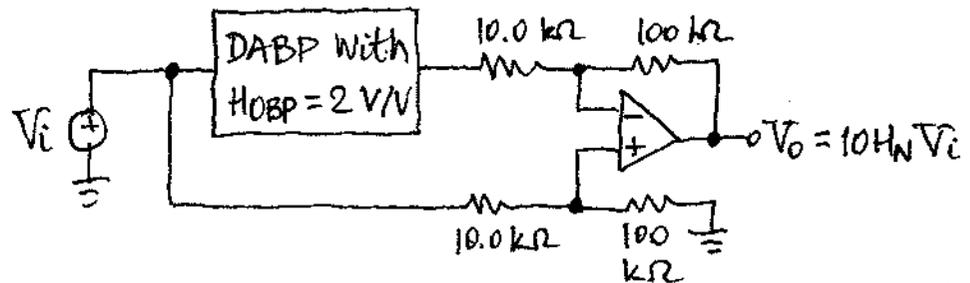(b) Implement the AP response as $H_{AP} = 1 - 2H_{BP}$.




4.16

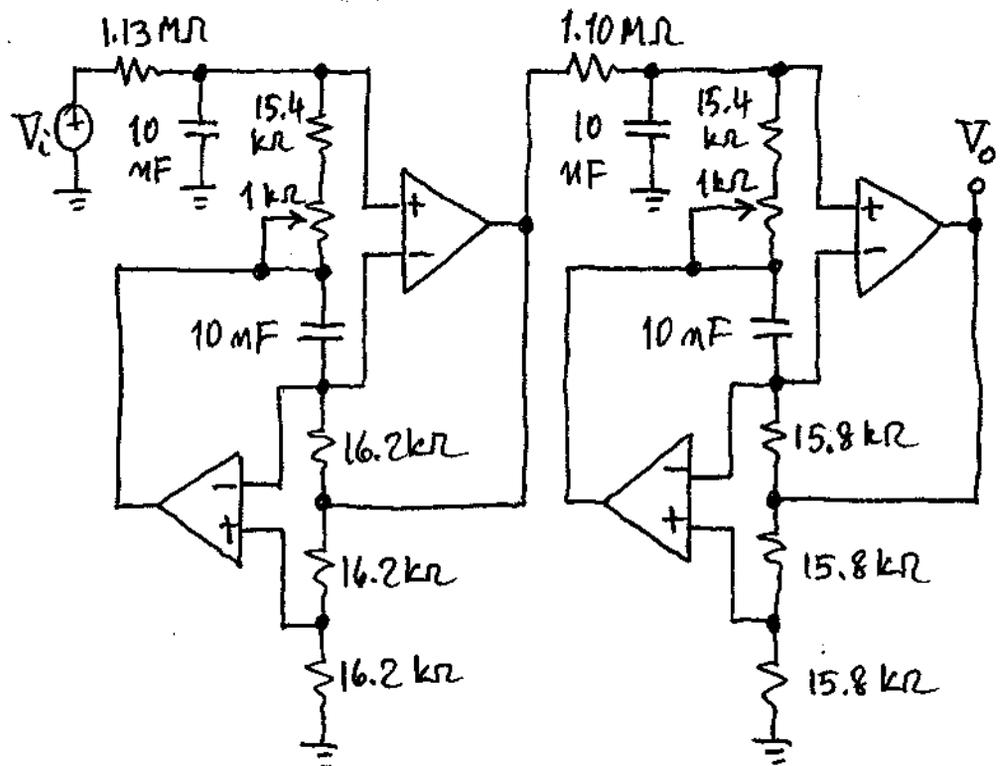4.16 Use $C = 10 \text{ mF}$ throughout, as well as $R_1 = R_3 = R_4 = R_5$.


1st stage: $R_1 = 1/(2\pi f_{01} C) = 16.03 \text{ k}\Omega$; $R = QR_1 = 1.123 \text{ M}\Omega$.

2nd stage: $R_1 = 15.8 \text{ k}\Omega$, $R = 1.107 \text{ M}\Omega$.



4.17

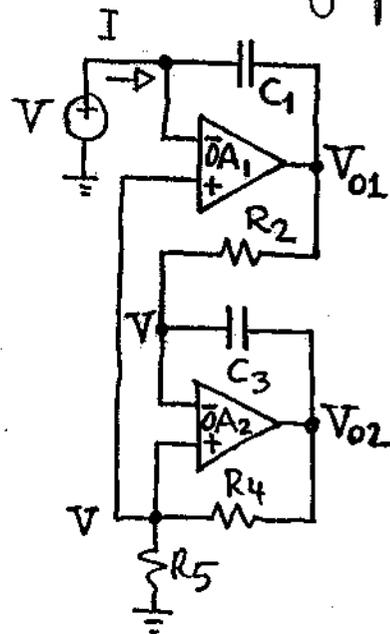4.17 (a) By op amp action, $V_{p2} = V_{m2} = V_{p1} = V_{m1} = V$. By Ohm's law, $I = j\omega C_1 (V - V_{o1})$.



By KCL,

$$\frac{V_{o1} - V}{R_2} = j\omega C_3 (V - V_{o2})$$

By the voltage divider,


$$V_{p2} = V = \frac{R_5}{R_4 + R_5} V_{o2}$$

Eliminating V_{o1} and V_{o2} ,

$$I = -\omega^2 \frac{C_1 R_2 C_3 R_4}{R_5} V = -\omega^2 D V \text{ . Thus,}$$

$$Z = V / I = 1 / (-\omega^2 D), \quad D = C_1 R_2 C_3 R_4 / R_5$$

(b) Let $C = 0.1 \mu\text{F}$. Then,

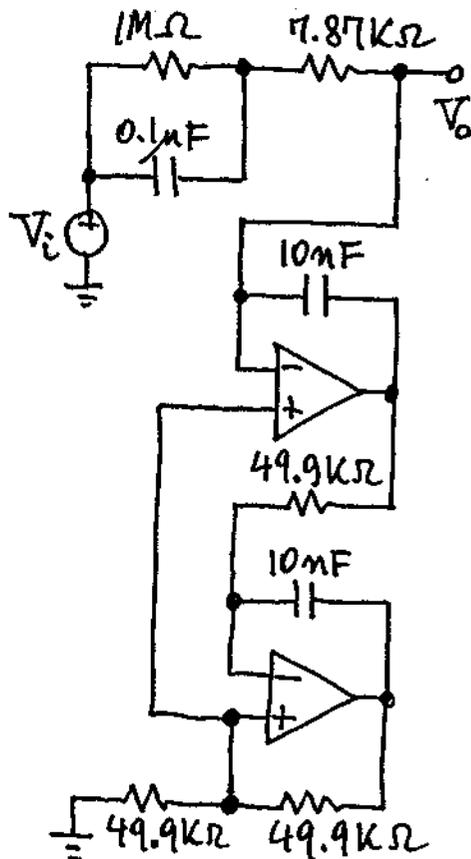

$$D = C / (2\pi Q f_0) =$$

$$10^{-7} / (2\pi \times 4 \times 800) = 4.973 \times 10^{-12} \text{ s}^2 / \Omega$$

$$R = D (Q / C)^2 =$$

$$4.973 \times 10^{-12} (4 / 10^{-7})^2$$

$$= 7.96 \text{ k}\Omega \text{ (use}$$

$$7.87 \text{ k}\Omega) \text{ . Let } C_1 =$$

$$C_3 = 10 \text{ nF, } R_2 = R_4 = R_5$$

$$\text{Then, } R_2 = D / C_1^2 =$$


$$4.973 \times 10^{-12} / (10^{-8})^2$$

$$= 49.7 \text{ k}\Omega \text{ (use}$$


$$49.9 \text{ k}\Omega)$$

4.18

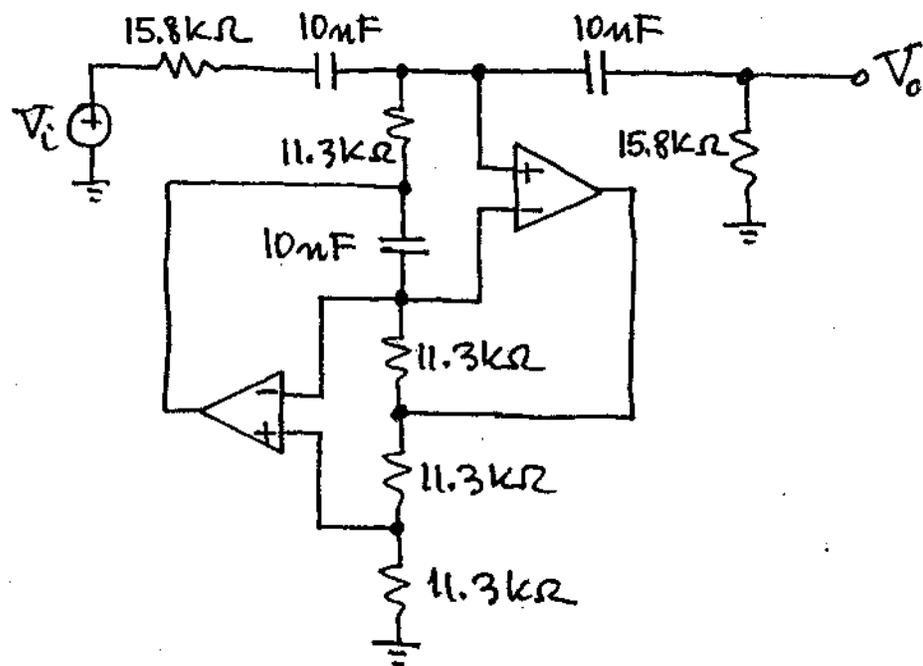4.18 Let $C = 10\text{mF}$. Then, $L = 1/[(2\pi f_0)^2 \times 2C] = 1/[(2\pi \times 10^3)^2 \times 2 \times 10^{-8}] = 1.267\text{H}$. $R = (2 \times 1.267 / 10^{-8})^{1/2} = 15.92\text{k}\Omega$. To find the component values for the GIC, impose equal resistors and equal, 10mF , capacitances. Then, $R_k^2 \times 10\text{mF} = 1.267 \Rightarrow R_k = 11.25\text{k}\Omega$, $k = 1, 3, 4, 5$. Actual realization:



4.19

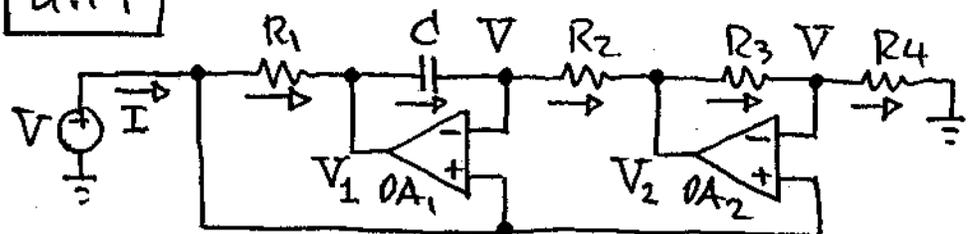


$$I = \frac{V - V_1}{R_1}; \quad j\omega C(V_1 - V) = \frac{V - V_2}{R_2}; \quad V_2 = \left(1 + \frac{R_3}{R_4}\right) \times V.$$

Eliminating V_1 and V_2 and collecting,


$$V/I = j\omega L, \quad L = (R_1 R_2 R_4 / R_3) C.$$

4.19

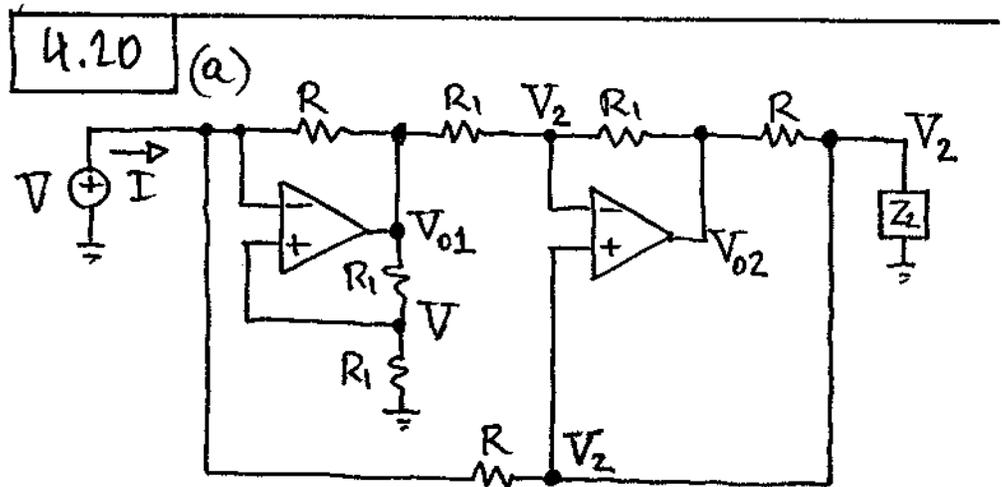

$$V_{o1} = 2V; \quad V_{o2} = -V_{o1} + 2V_2; \quad I = \frac{V - V_{o1}}{R} + \frac{V - V_2}{R}; \quad \frac{V - V_2}{R} = \frac{V_2 - V_{o2}}{R} + \frac{V_2}{Z_2} \cdot \text{Eliminating } V_{o1}, V_{o2}, \text{ and } V_2 \text{ and collecting, } Z_1 = \frac{V}{I} = \frac{R^2}{Z_2}$$


(b)

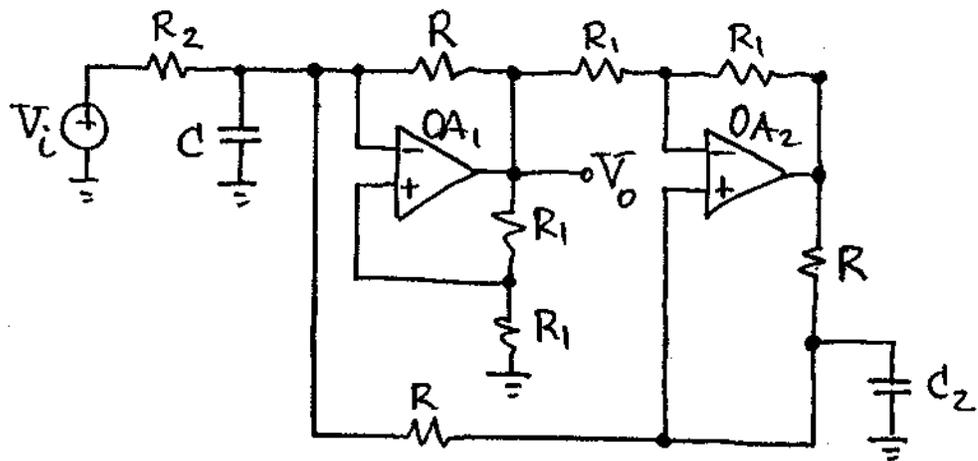

Let $C = 1 \mu\text{F}$. Then, $L = 1/[(2\pi f_0)^2 C] = 1/[(2\pi)^2 10^{-6}] = 25.33 \text{ KH}$. Use $C_2 = 1 \mu\text{F}$, $R = \sqrt{L/C_2} = \sqrt{25,330 \times 10^6} = 158 \text{ k}\Omega$, $R_1 = 100 \text{ k}\Omega$, $R_2 = Q \sqrt{L/C} = 10 \sqrt{25,330 \times 10^6} = 1.58 \text{ M}\Omega$. Obtain V_0 from OA_1 's output, where the output impedance is low. Then, $H_{\text{OBP}} = 2V/V$.


4.20

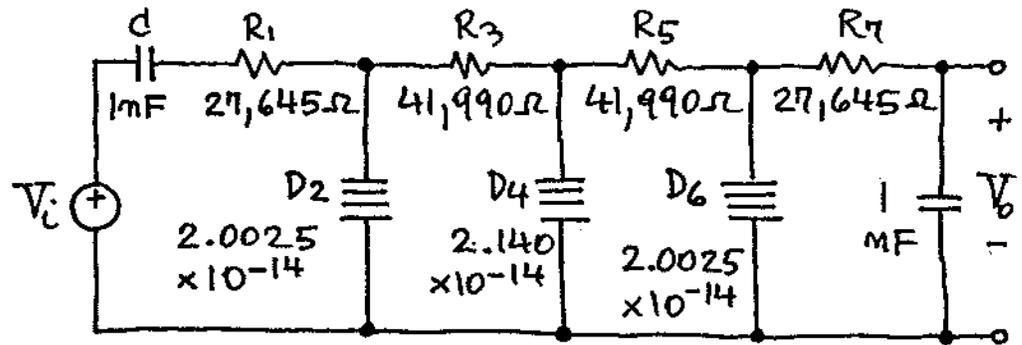4.21 Use 1mF capacitors, so that $K_2 = 10^9 \Omega^2/\text{s}$. Then, $C_{(\text{new})} = 10^{-9} R_{(\text{old})}$; $R_{(\text{new})} = 15,915 L_{(\text{old})}$, $D_{(\text{new})} = 1.592 \times 10^{-14} C_{(\text{old})}$. The transformed ladder is as follows:




In the FDNRs let $C_1 = C_3 = 1\text{mF}$, $R_2 = R_5 = R_4$. Then, $D = R_2 C_1^2 \Rightarrow R_2 = D/C_1^2 = 10^{18} D$. Thus, for D_2 and D_6 we have $R_2 = R_5 = R_4 = 10^{18} \times 2.0025 \times 10^{-14} = 20.025 \text{ k}\Omega$. For D_4 we have $R_2 = R_5 = R_4 = 10^{18} \times 2.140 \times 10^{-14} = 21.4 \text{ k}\Omega$.

4.21

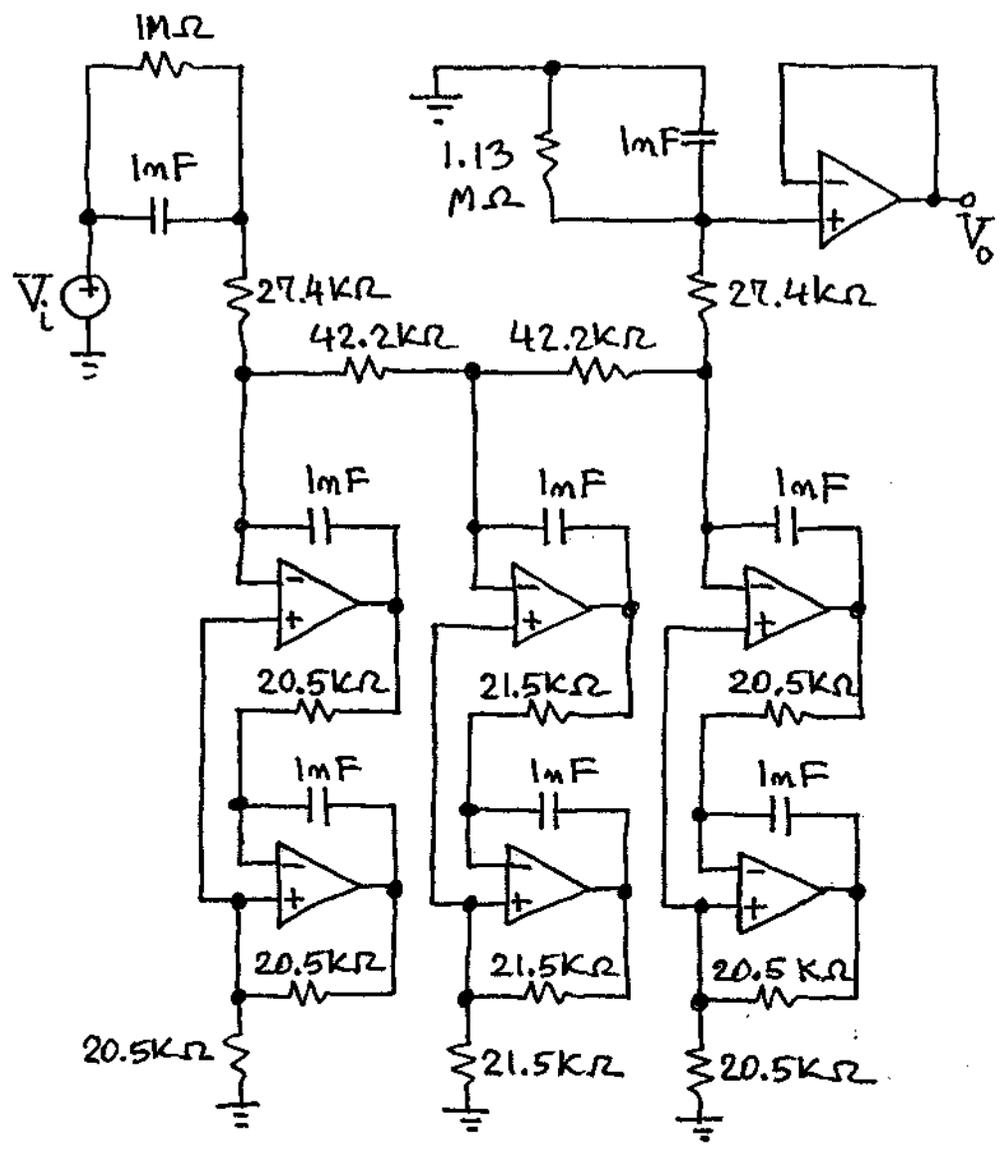


4.22

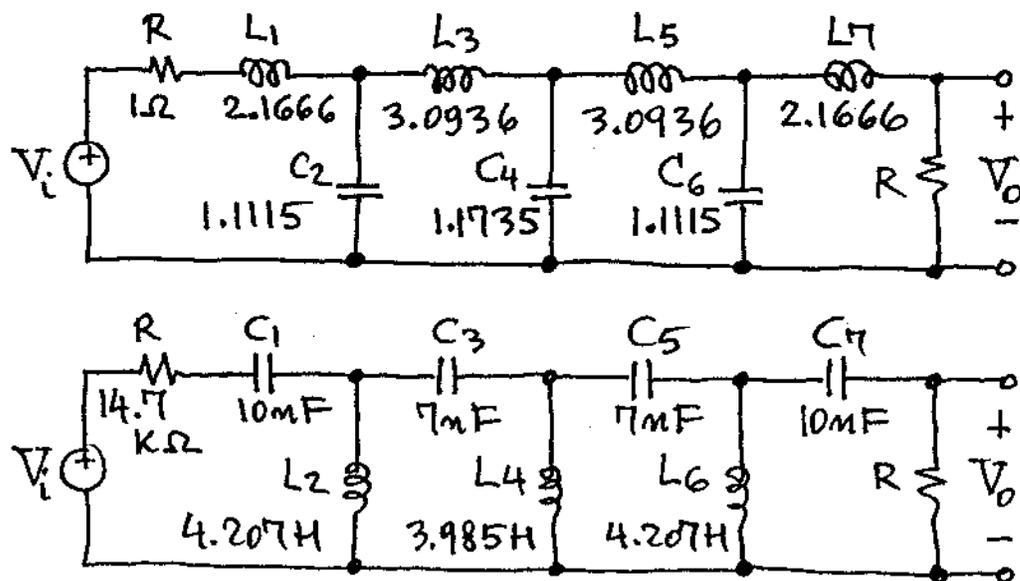4.22 The prototype ladder is shown on top. Arbitrarily choose K_Z so that L_1 and L_7 are changed into 10 mF capacitors. Thus, $10 \times 10^{-9} = 1 / (2\pi \times 500 \times K_Z \times 2.1666) \Rightarrow K_Z = 14,692$. $R_{(new)} = K_Z / R_{(old)} = 14.69$ K Ω . $C_1 = C_7 = 10$ mF. $C_3 = C_5 = 1 / (2\pi \times 500 \times 14,692 \times 3.0936) = 7$ mF. $L_2 = L_6 = 14,692 / (2\pi \times 500 \times 1.1115) = 4.207$ H. $L_4 = 14,692 / (2\pi \times 500 \times 1.1735) = 3.985$ H. The high-pass ladder is shown at the bottom.



To find the element values in the GICs, impose equal resistances and $C = 10$ mF throughout. For the 1st and 3rd GIC we obtain $R_k^2 = 4.207 / 10^{-8} \Rightarrow R_k = 20.51$ K Ω . For the 2nd GIC, $R_k^2 = 3.985 / 10^{-8} \Rightarrow R_k = 19.96$ K Ω . Actual implementation:

4.23

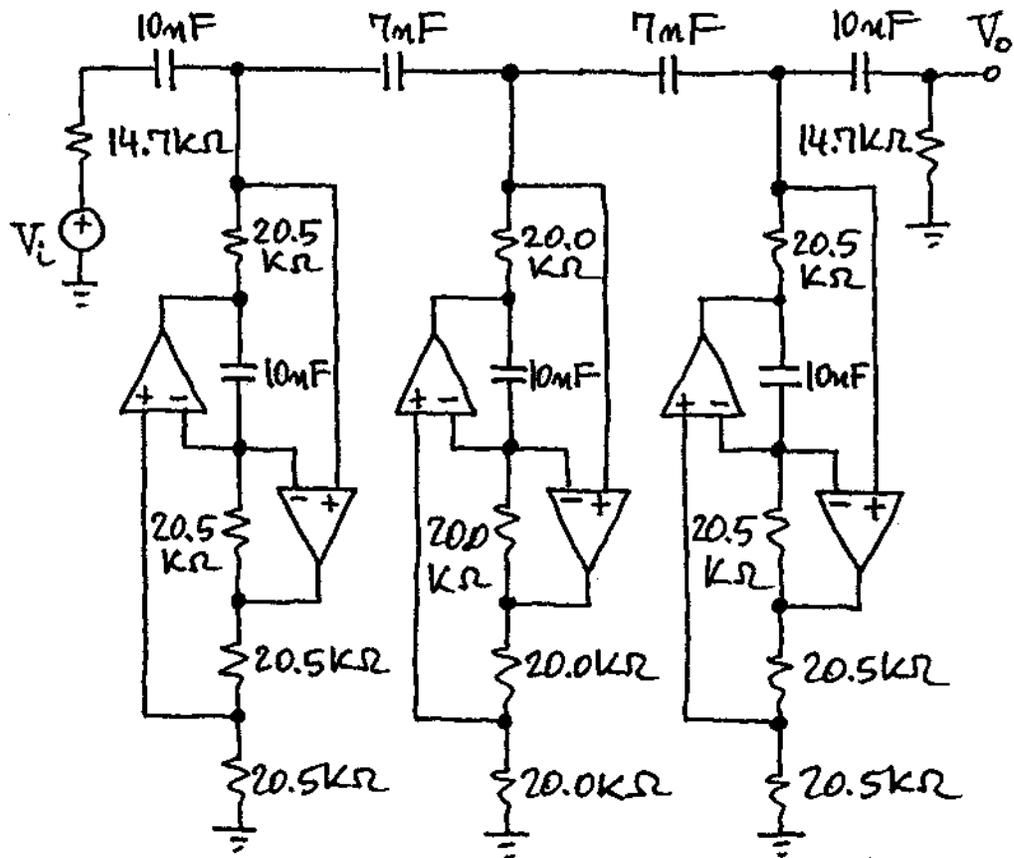

4.23 (a) C_1 implements $Req_1 = 1/C_1 f_{ck}$, and C_2 implements $Req_2 = 1/C_2 f_{ck}$. Consequently,

$$V_o = -\frac{1}{sReq_1 C_3} V_1 - \frac{1}{sReq_2 C_3} V_2 = -\frac{1}{s/\omega_1} V_1 - \frac{1}{s/\omega_2} V_2, \omega_1 = (C_1/C_3) f_{ck}, \omega_2 = (C_2/C_3) f_{ck}.$$
 Summing integrator.

(b) Flipping the switches to the left charges C_1 to $V_1 - V_2$, flipping the switches to the right dumps the charge $C(V_1 - V_2)$ into the summing junction of the op amp. The average current is $I_{avg} = f_{ck} C_1 (V_1 - V_2)$, and $V_o = -\frac{1}{sC_2} I_{avg} = \frac{1}{s/\omega_0} (V_2 - V_1)$, $\omega_0 = (C_1/C_2) f_{ck}$. Difference integrator.

4.24

4.24 (a) Denoting the current flowing into the summing junction of the op amp as I_{avg} , we have, by the superposition principle,

$$V_o = -\frac{1}{sC_2} I_{avg} = -\frac{1}{sC_2} f_{ck} C_1 (V_1 - V_2 + V_3) \\ = \frac{1}{s/\omega_0} (V_2 - V_1 - V_3), \quad \omega_0 = \frac{C_1}{C_2} f_{ck}.$$

(b) switches flipped to ground $\Rightarrow C_1$ and C_2 are discharged. Switches flipped in the position shown $\Rightarrow C_1$ charges to V_i and C_2 to V_o . The current into the summing junction is thus $I_{avg} = f_{ck} (C_1 V_i + C_2 V_o)$, and $V_o = -(1/sC_2) I_{avg} = -(f_{ck}/sC_2) (C_1 V_i + C_2 V_o)$. Collecting terms,

$$H = \frac{V_o}{V_i} = -\frac{C_1}{C_2} \frac{1}{1 + s/\omega_0}, \quad \omega_0 = \frac{C_2}{C_3} f_{ck}.$$

4.25 (a) let V_1 be the output of OA₁. Then, $V_o = -[(1/sC_2)/(1/sC_2)]V_i + [1/(s/\omega_0)]V_1 = -V_i + [1/(s/\omega_0)]V_1$, $\omega_0 = (C_0/C_2)f_{ck}$; $V_1 = -[(1/sC_2)/(1/sC_1)]V_o - [1/(s/\omega_0)](V_i + V_o) = -(C_1/C_2)V_o - [1/(s/\omega_0)](V_i + V_o)$. Eliminating V_1 ,

$$H = \frac{V_o}{V_i} = \frac{-[1 - (\omega/\omega_0)^2]}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q} = -H_N,$$

4.25

$$Q = C_2/C_1, \omega_0 = (C_0/C_2) f_{clk}.$$

$$(b) C_0 = 1 \text{ pF}, C_2 = 15.9 \text{ pF}, C_1 = 1.59 \text{ pF}.$$

4.26 (a) $C_2/C_1 = 250 / (2\pi \cdot 2) = 19.9$;
 $C_1/C_3 = Q = 2/1$. Use $C_3 = 1 \text{ pF}$, $C_1 = 2 \text{ pF}$, $C_2 = 39.8 \text{ pF}$.

(b) $C_2/C_1 = 19.9$; $C_1/C_3 = 2/0.1 = 20$.
Use $C_3 = 1 \text{ pF}$, $C_1 = 20 \text{ pF}$, $C_2 = 398 \text{ pF}$, quite large.

4.27 (a) $V_{BP} = \frac{1/j\omega C_2}{1/C_3 f_{clk}} V_{HP} = \frac{1}{j\omega/\omega_0} V_{HP}$,

$$\omega_0 = \frac{C_3}{C_2} f_{clk}.$$

$$\begin{aligned} V_{HP} &= -\frac{1/j\omega C_2}{1/j\omega C_1} V_i - \frac{1/j\omega C_2}{1/j\omega C_1} V_{BP} - \frac{1/j\omega C_2}{1/j\omega C_3} V_{BP} \\ &= -\frac{C_1}{C_2} V_i - \frac{C_1}{C_2} V_{BP} - \frac{1}{j\omega/\omega_0} V_{BP}. \end{aligned}$$

Eliminating V_{HP} ,

$$V_{BP} = \frac{1}{j\omega/\omega_0} \left[-\frac{C_1}{C_2} V_i - \frac{C_1}{C_2} V_{BP} - \frac{1}{j\omega/\omega_0} V_{BP} \right].$$

Multiplying both sides by $(j\omega/\omega_0)^2$ and collecting,

$$V_{BP} \left[-(\omega/\omega_0)^2 + \frac{j}{Q} (\omega/\omega_0) + 1 \right] = -\frac{j}{Q} (\omega/\omega_0) V_i, \quad Q = \frac{C_2}{C_1}.$$

4.26

$$\frac{V_{BP}}{V_i} = - \frac{(j\omega/\omega_0)/Q}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q} = -H_{BP}$$

$$\frac{V_{HP}}{V_i} = \frac{V_{HP}}{V_{BP}} \frac{V_{BP}}{V_i} = j(\omega/\omega_0) \times (-H_{BP}) = -\frac{1}{Q} H_{HP}$$

(b) $C_2/C_3 = 200/(2\pi) = 31.8$;
 $C_2/C_1 = 10$. Use $C_3 = 1 \text{ pF}$, $C_2 = 31.8 \text{ pF}$, $C_1 = 3.18 \text{ pF}$.

(c) $C_2/C_3 = 31.8$; $C_2/C_1 = 100$. Use $C_1 = 1 \text{ pF}$, $C_2 = 100 \text{ pF}$, $C_3 = 3.14 \text{ pF}$, a very reasonable spread considering the high Q value.

4.28 The normalized element values are $C_1 = C_5 = 1.14681$, $L_2 = L_4 = 1.37121$, $C_3 = 1.97500$. Using Eq. (4.29), $C_{C_1}/C_0 = 1.14681 \times 128 \times 10^3 / (2\pi \times 3.4 \times 10^3) = 6.871$. $C_{L_2}/C_0 = 8.216$; $C_{C_3}/C_0 = 11.83$. A suitable set of capacitances is $C_0 = 1 \text{ pF}$, $C_{C_1} = C_{C_5} = 6.871 \text{ pF}$, $C_{L_2} = C_{L_4} = 8.216 \text{ pF}$, $C_{C_3} = 11.83 \text{ pF}$, $C_{R_i} = C_{R_o} = 1 \text{ pF}$.

4.27

4.29 (a) Let $f_1 = f_{ck}/100(50)$. Then, $V_{BP} = [1/(jf/f_1)]V_{HP}$ and $V_{LP} = [1/(jf/f_1)]V_{BP} = -[1/(f/f_1)^2]V_{HP}$. Using superposition,

$$V_{HP} = -\frac{R_2}{R_1}V_i - \frac{R_2}{R_4} \left[\frac{-1}{(f/f_1)^2} V_{HP} \right] - \frac{R_2}{R_3} \frac{1}{j(f/f_1)} V_{HP}.$$

Multiplying both sides by $\frac{R_4}{R_2} [j(f/f_1)]^2$,

$$V_{HP} \left[-\frac{R_4}{R_2} \left(\frac{f}{f_1}\right)^2 + 1 + \frac{R_4}{R_3} j \left(\frac{f}{f_1}\right) \right] = \frac{R_4}{R_1} \left(\frac{f}{f_1}\right)^2 V_i.$$

Let $\frac{R_4}{R_2} \left(\frac{f}{f_1}\right)^2 = \left(\frac{f}{f_0}\right)^2$, so that $f_0 = \sqrt{\frac{R_2}{R_4}} f_1$

$= \sqrt{\frac{R_2}{R_4}} \frac{f_{ck}}{100(50)}$. Then, $\frac{R_4}{R_3} j \left(\frac{f}{f_1}\right) = \frac{R_4}{R_3} \times$

$$\sqrt{\frac{R_2}{R_4}} \sqrt{\frac{R_4}{R_2}} j \left(\frac{f}{f_1}\right) = \frac{j}{Q} \left(\frac{f}{f_0}\right), \quad Q = \frac{R_3}{R_2} \sqrt{\frac{R_2}{R_4}}.$$

Moreover, $\frac{R_4}{R_1} \left(\frac{f}{f_1}\right)^2 = \frac{R_2}{R_1} \frac{R_4}{R_2} \left(\frac{f}{f_1}\right)^2 = \frac{R_2}{R_1} \left(\frac{f}{f_0}\right)^2$. Thus,

$$\frac{V_{HP}}{V_i} = \frac{(R_2/R_1) \left(\frac{f}{f_0}\right)^2}{1 - \left(\frac{f}{f_0}\right)^2 + (jf/f_0)/Q} = -\frac{R_2}{R_1} H_{HP}.$$

$$\frac{V_{BP}}{V_i} = \frac{V_{BP}}{V_{HP}} \frac{V_{HP}}{V_i} = \frac{1}{jf/f_1} \frac{V_{HP}}{V_i} =$$

$$\frac{\sqrt{R_4/R_2}}{\sqrt{R_4/R_2} (jf/f_1)} \frac{V_{HP}}{V_i} = \sqrt{\frac{R_4}{R_2}} \times \left(-\frac{R_2}{R_1}\right) \frac{1}{jf/f_0} H_{HP}$$

4.28

$$= -\frac{\sqrt{\frac{R_4}{R_2}} \frac{R_2}{R_3} \frac{R_3}{R_1} j(f/f_0)}{1 - (f/f_0)^2 + (jf/f_0)/Q} = -\frac{R_3}{R_1} \frac{(jf/f_0)/Q}{1 - (f/f_0)^2 + (jf/f_0)/Q}$$

$$= -\frac{R_3}{R_1} H_{BP} \cdot \text{Finally,}$$

$$\frac{V_{LP}}{V_i} = \frac{V_{LP}}{V_{HP}} \frac{V_{HP}}{V_i} = \frac{-1}{(f/f_1)^2} \frac{V_{HP}}{V_i} = \frac{-R_4/R_2}{(R_4/R_2)(f/f_1)^2} \frac{V_{HP}}{V_i}$$

$$= -\frac{R_4}{R_2} \frac{1}{(f/f_0)^2} \frac{R_2}{R_1} \frac{(f/f_0)^2}{1 - (f/f_0)^2 + (jf/f_0)/Q}$$

$$= -\frac{R_4}{R_1} H_{LP} \cdot$$

$$(b) V_N = -\frac{R_G}{R_L} V_{LP} - \frac{R_G}{R_H} V_{HP} \cdot \text{Eq. (4.34):}$$

$$H_N = \frac{V_N}{V_i} = -\frac{R_G}{R_L} H_{OLP} H_{LP} - \frac{R_G}{R_H} H_{OHP} H_{HP} \cdot$$

$$\lim_{f \rightarrow 0} H_N = -\frac{R_G}{R_L} H_{OLP} = \frac{R_G}{R_L} \frac{R_4}{R_1} \cdot$$

$$\lim_{f \rightarrow f_{ck}/2} H_N = -\frac{R_G}{R_H} H_{OHP} = \frac{R_G}{R_H} \frac{R_2}{R_1} \cdot \text{Moreover,}$$


$$H_N = -\frac{R_G}{R_L} H_{OLP} \frac{1 + \frac{R_L}{R_G} \frac{R_G}{R_H} \frac{H_{OHP}}{H_{OLP}} [-(f/f_0)^2]}{1 - (f/f_0)^2 + (jf/f_0)/Q}$$

$$= -\frac{R_G}{R_L} H_{OLP} \frac{1 - (f/f_z)^2}{1 - (f/f_0)^2 + (jf/f_0)/Q}, \text{ where}$$

$$\frac{1}{f_z^2} = \frac{R_L}{R_H} \frac{R_2}{R_4} \frac{1}{f_0^2} = \frac{R_L}{R_4} \frac{1}{f_x^2} \Rightarrow f_z = \sqrt{\frac{R_H}{R_L} \frac{f_{ck}}{100(50)}} \cdot$$

4.29

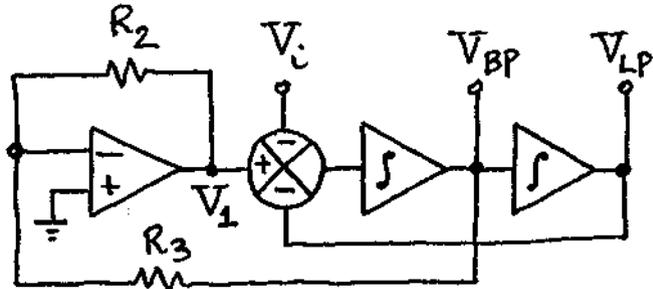4.30 (a) $V_1 = -(R_2/R_3)V_{BP}$. $V_{BP} = \frac{1}{jf/f_0} \times$



$(V_1 - V_i - V_{LP})$

$V_{LP} = \frac{1}{jf/f_0} V_{BP}$

Substituting,

$$V_{BP} = \frac{1}{jf/f_0} \left[-\frac{R_2}{R_3} V_{BP} - V_i - \frac{1}{jf/f_0} V_{BP} \right]$$

Multiply both sides by $[j(f/f_0)]^2$. Then,

$$V_{BP} \left[-\left(\frac{f}{f_0}\right)^2 + (jf/f_0)/Q + 1 \right] = -(jf/f_0)V_i, \quad Q = \frac{R_3}{R_2}$$

$$\frac{V_{BP}}{V_i} = \frac{-Q \times (jf/f_0)/Q}{1 - (f/f_0)^2 + (jf/f_0)/Q} = -QH_{BP}$$

$$\frac{V_{LP}}{V_i} = \frac{V_{LP}}{V_{BP}} \frac{V_{BP}}{V_i} = \frac{1}{jf/f_0} \times (-QH_{BP}) = -H_{LP}$$

(b) Tie the 50/100/CL pin to ground to make $f_0 = f_{clk}/100$. Then, $f_{clk} = 100 \times 500 = 50 \text{ kHz}$, $R_3/R_2 = Q = 10$. Use $R_2 = 10 \text{ k}\Omega$, $R_3 = 100 \text{ k}\Omega$.

4.30

$$4.31 \quad V_N = -\frac{R_2}{R_1} V_i - \frac{R_2}{R_3} V_{BP} - \frac{R_2}{R_4} V_{LP};$$

$$V_{LP} = \frac{1}{jf/f_1} V_{BP}; \quad V_{BP} = \frac{1}{jf/f_1} (V_N - V_{LP}),$$

$$f_1 = \frac{f_{ck}}{100(50)}. \text{ Eliminating } V_{LP} \text{ and } V_{BP},$$

collecting and solving for the ratio V_N/V_i ,

$$\frac{V_N}{V_i} = \frac{-\frac{R_2}{R_1} \frac{R_4}{R_2+R_4} [1 - (f/f_1)^2]}{1 - \frac{R_4}{R_2+R_4} (f/f_1)^2 + \frac{R_2}{R_3} \frac{R_4}{R_2+R_4} (jf/f_1)}$$

$$\text{Letting } f_z = \frac{f_{ck}}{100(50)}, \quad f_0 = f_z \sqrt{1 + R_2/R_4},$$

$$Q = \frac{R_3}{R_2} \sqrt{1 + \frac{R_2}{R_4}} \text{ gives } \frac{V_N}{V_i} = H_{ON} H_N, \quad H_{ON} = \frac{-R_2/R_1}{1 + R_2/R_4}$$

$$4.32 \quad V_{AP} = -\frac{R_2}{R_1} V_i - \frac{R_2}{R_3} V_{BP}; \quad V_{BP} =$$

$$\frac{1}{jf/f_0} (V_{AP} - V_i - V_{LP}); \quad V_{LP} = \frac{1}{jf/f_0} V_{BP},$$

$$f_0 = \frac{f_{ck}}{100(50)}. \text{ Eliminating } V_{BP} \text{ and } V_{LP},$$

collecting, and solving for the ratio V_{AP}/V_i ,


$$\frac{V_{AP}}{V_i} = \frac{\frac{R_3/R_1}{R_3/R_2} [1 - (f/f_0)^2] + (R_1/R_3) (jf/f_0)}{1 - (f/f_0)^2 + (R_2/R_3) (jf/f_0)}$$

$$\text{By inspection, } H_{OAP} = -R_2/R_1, \quad f_0 =$$

$$f_{ck}/[100(50)], \quad Q = R_3/R_2, \quad Q_z = R_3/R_1.$$

4.31

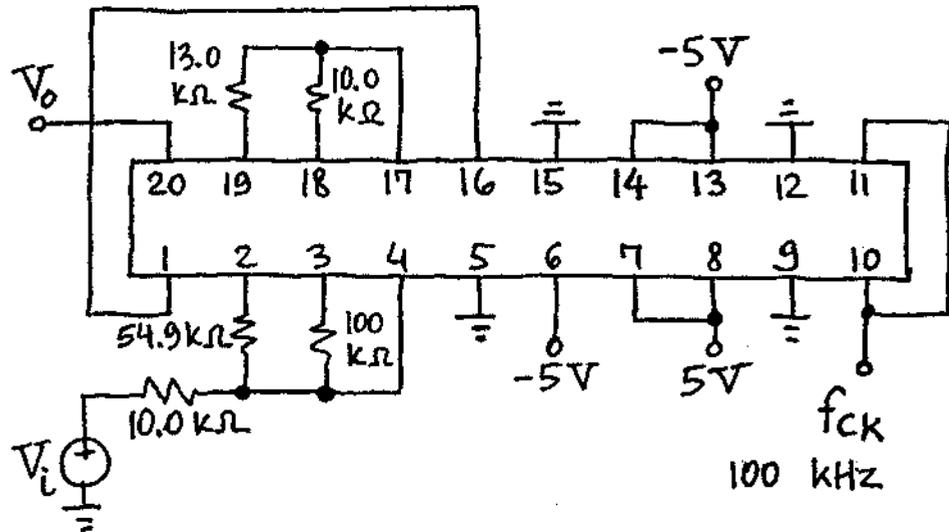4.33 Table 4.1 indicates that we need two stages with $Q_1 = 0.5418$ and $Q_2 = 1.3065$, respectively. Let the first stage be as in Fig. 4.36. Then, $R_3/R_2 = 0.542$ and $R_2/R_1 = 10$. Use $R_1 = 10.0 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, and $R_3 = 54.9 \text{ k}\Omega$, all 1%. Let the second stage be as in Problem 4.30. Then, $R_3/R_2 = 1.3065$. Use $R_2 = 10.0 \text{ k}\Omega$, $R_3 = 13.0 \text{ k}\Omega$, 1%.



4.34 Use two configurations of the type of Fig. 4.37. 1st stage: $R_1 = R_3 = 20.0 \text{ k}\Omega$, $R_2 = 5.36 \text{ k}\Omega$, $R_4 = 8.87 \text{ k}\Omega$. 2d stage: $R_1 = 20.0 \text{ k}\Omega$, $R_2 = 28.0 \text{ k}\Omega$, $R_3 = 63.4 \text{ k}\Omega$, $R_4 = 16.9 \text{ k}\Omega$. Impose $f_0 = f_{ck}/100$, $f_{ck} = 200 \text{ kHz}$.


Q.32

4.35 Use the configuration of Fig. 4.40.
1st stage: $R_1 = 392 \text{ k}\Omega$, $R_2 = 19.6 \text{ k}\Omega$, $R_3 = 374 \text{ k}\Omega$, $R_4 = 17.8 \text{ k}\Omega$, $R_H = 10.0 \text{ k}\Omega$, $R_L = 10.0 \text{ k}\Omega$.
2nd stage: $R_2 = 20.0 \text{ k}\Omega$, $R_3 = 422 \text{ k}\Omega$, $R_4 = 21.5 \text{ k}\Omega$, $R_H = 20.0 \text{ k}\Omega$, $R_L = 20.0 \text{ k}\Omega$, $R_G = 20.0 \text{ k}\Omega$.

4.36 Stage 1: Let $R_1 = R_4 = 20.0 \text{ k}\Omega$.
Then, $R_2/R_4 = (1.948/2)^2 \Rightarrow R_2 = 18.97 \text{ k}\Omega$
(use $18.7 \text{ k}\Omega$). $R_3 = Q\sqrt{R_2 R_4} = 574.3 \text{ k}\Omega$
(use $576 \text{ k}\Omega$). Let $R_{HA} = 20.0 \text{ k}\Omega$. Then,
 $R_{LA} = R_{HA}/(1.802/2)^2 = 24.6 \text{ k}\Omega$ (use $24.9 \text{ k}\Omega$).

Stage 2: Let $R_4 = 20.0 \text{ k}\Omega$. Then,
 $R_2 = 24.9 \text{ k}\Omega$, $R_3 = 654 \text{ k}\Omega$, $R_{LA} = 20.0 \text{ k}\Omega$,
 $R_{HA} = 24.9 \text{ k}\Omega$. R_F controls the resonance gain.

4.33

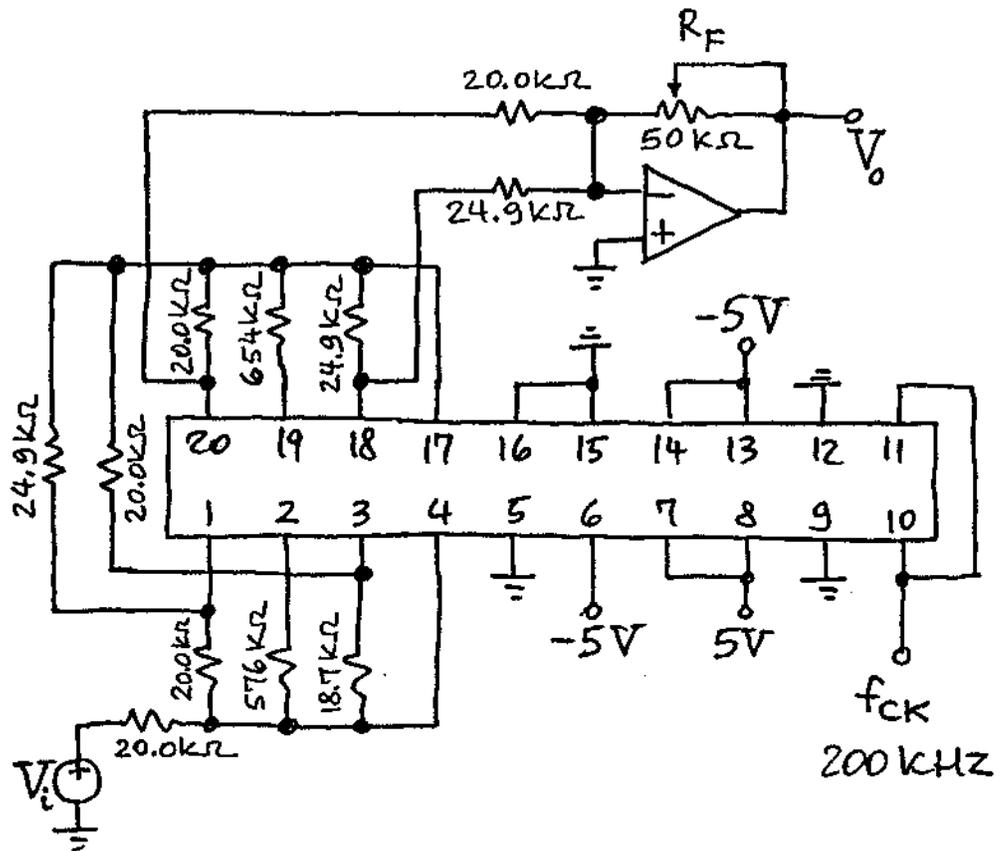

4.37 From Table 4.1,

$$f_{01} = 500 / 1.034 = 483.56 \text{ Hz}, Q_1 = 8.082$$

$$f_{02} = 500 / 0.894 = 559.28 \text{ Hz}, Q_2 = 2.453$$

$$f_{03} = 500 / 0.645 = 775.19 \text{ Hz}, Q_3 = 1.183$$

$$f_{04} = 500 / 0.382 = 1308.9 \text{ Hz}, Q_4 = 0.593$$

Stage 1: $\sqrt{R_2/R_4} = 1/1.034 \Rightarrow$
 $R_2/R_4 = 1/1.034^2 = 0.935$; $R_3/R_2 = Q_1 / \sqrt{R_2/R_4} = 8.082 \times 1.034 = 8.357$; $R_2/R_1 = H_{0HP} = 1$. Let $R_1 = R_2 = 20.0 \text{ k}\Omega$. Then, $R_3 = 8.357 \times 20 = 167.14 \text{ k}\Omega$ (use $169 \text{ k}\Omega$) and $R_4 = 20 / 0.935 = 21.4 \text{ k}\Omega$ (use $21.5 \text{ k}\Omega$).

4.34

Stage 2: $R_2/R_4 = 1.251$; $R_3/R_2 = 2.193$; $R_2/R_1 = 1$. Use $R_1 = R_2 = 20.0 \text{ k}\Omega$, $R_3 = 44.2 \text{ k}\Omega$, $R_4 = 15.8 \text{ k}\Omega$.

Stage 3: $R_2/R_4 = 2.40$; $R_3/R_2 = 0.763$; $R_2/R_1 = 1$. Use $R_1 = R_2 = 20 \text{ k}\Omega$, $R_3 = 15.4 \text{ k}\Omega$, $R_4 = 8.45 \text{ k}\Omega$.

Stage 4: $R_2/R_4 = 6.853$; $R_3/R_2 = 0.2265$; $R_2/R_1 = 1$. Use $R_1 = R_2 = 20.0 \text{ k}\Omega$, $R_3 = 4.53 \text{ k}\Omega$, $R_4 = 2.94 \text{ k}\Omega$.

