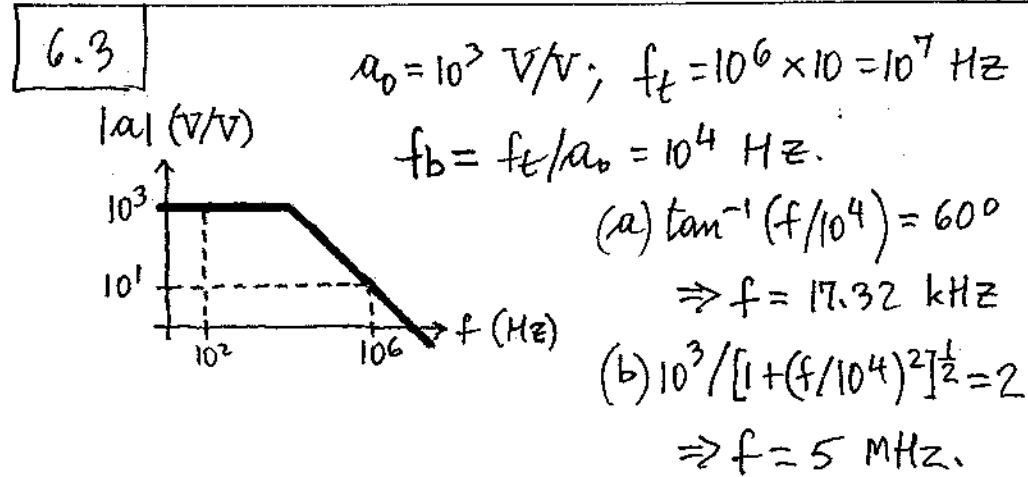


6.1

6.1 (a) By Eq. (6.1), $\alpha_0 = k_1 \times \alpha_2$; by Eq. (6.9), f_t is independent of α_2 ; by Eq. (6.5), $f_b = k_2 / \alpha_2$. Thus, a $\pm 20\%$ variation of α_2 causes a $\pm 20\%$ variation of α_0 and a variation of about $\mp 20\%$ of f_b .

(b) By Eq. (6.9), $f_t = k_3 / C_c$; by Eq. (6.1), α_0 is independent of C_c ; by Eq. (6.5), $f_b = k_4 / d$. Thus, a $\pm 10\%$ variation of C_c causes variations of about $\mp 10\%$ in both f_b and f_t .

6.2 $-\tan^{-1}(80/f_a) = -58^\circ \Rightarrow f_b = 50 \text{ Hz}$;
Since $1 \text{ Hz} \ll 50 \text{ Hz}$, $\alpha_0 \approx |a(j1 \text{ Hz})| = 10^5 \text{ V/V}$;
 $f_t = \alpha_0 f_b = 5 \text{ MHz}$.



6.4

$$A = \left(\frac{A_1}{1 + j f/f_{B1}} \right)^2 = \frac{A_1^2}{1 - (f/f_{B1})^2 + 2j f/f_{B1}} = H_{OLP} H_{LP},$$

$$H_{OLP} = A_1^2 = 10^3 \text{ V/V}, f_{B1} = 31.6 \text{ kHz}, Q = 1/2.$$

(6.2)


6.5

(a) Impose $\{A_0/[1+(f/f_{B0})^2]^{1/2}\}^n = A_0^n/2^{1/2}$
 $\Rightarrow [1+(f/f_{B0})^2]^n = 2 \Rightarrow f = f_{B0}\sqrt{2^{1/n}-1}, f_{B0} = f_t/A_0$.

(b) The same expression holds, but with f_t/A_0 replaced by $f_t/(A_0+1)$.

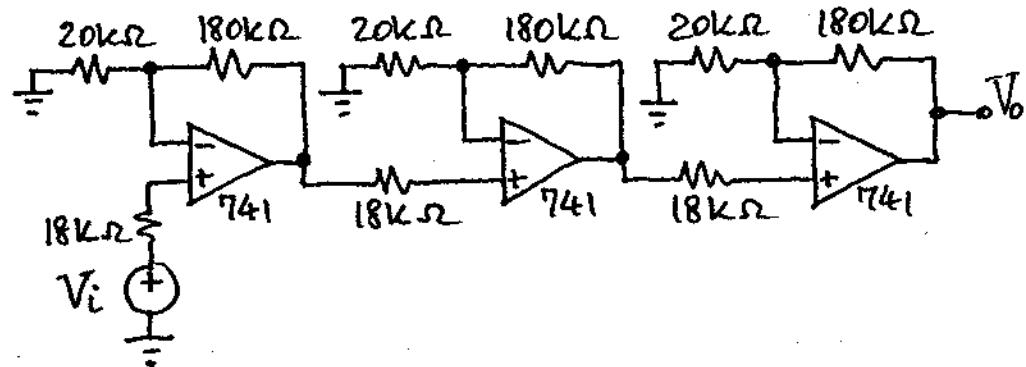6.6

$A_1 = A_2 = A_3 = 10/[1+j(f/100\text{kHz})]$.



$A = A_1^3 \Rightarrow |A| = 1,000/[1+(f/10^5)^2]^3$. We wish to find the frequency f_B at which $|A|=1000/\sqrt{2}$, that is,

$$\frac{1,000}{[\sqrt{1+(f_B/10^5)^2}]^3} = \frac{1,000}{\sqrt{2}}.$$

$f_B = 10^5 \sqrt{2^{1/3}-1} = 51\text{kHz}$. As expected, decreasing the individual gains increases the overall bandwidth.

6.7


(a) $A = \frac{2}{1+jf/(5/2\text{ MHz})} \times \frac{-2}{1+jf/(5/3\text{ MHz})}$

Imposing $[1+(f/2.5)^2]^{1/2} \times [1+(f/1.6)^2]^{1/2} = 2^{1/2}$ gives $f_{-3\text{dB}} = 1.276\text{ MHz}$.


(b) Imposing $|A| = 0.99 \times 4$ gives $f_{-1\%} =$

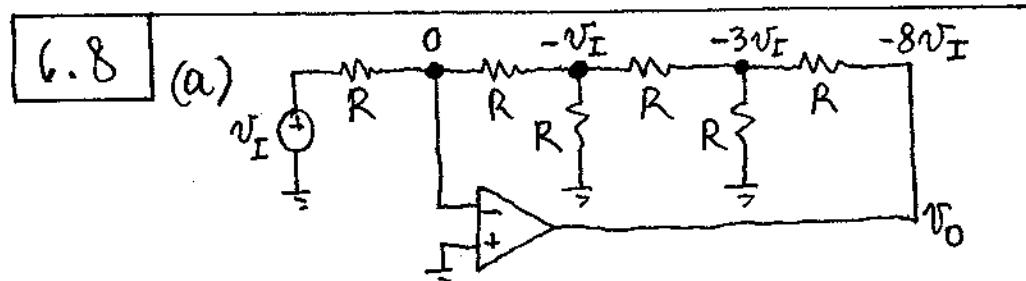6.3


196 kHz. Imposing $\tan^{-1}(f/2.5) + \tan^{-1}(f/1.6) = 5^\circ$ gives $f_{-50} = 87.3$ kHz.




$$A_0 = -8 \text{ V/V}; \beta = \frac{R}{R+R} \times \frac{R \parallel 2R}{R+(R \parallel 2R)} \times \frac{R \parallel [R+(R \parallel 2R)]}{R+R \parallel [R+(R \parallel 2R)]} = \frac{1}{13} \text{ V/V}; f_B = \beta f_t = \frac{4}{13} \text{ MHz}; GBP = |A_0| f_B = \frac{32}{13} \text{ MHz.}$$

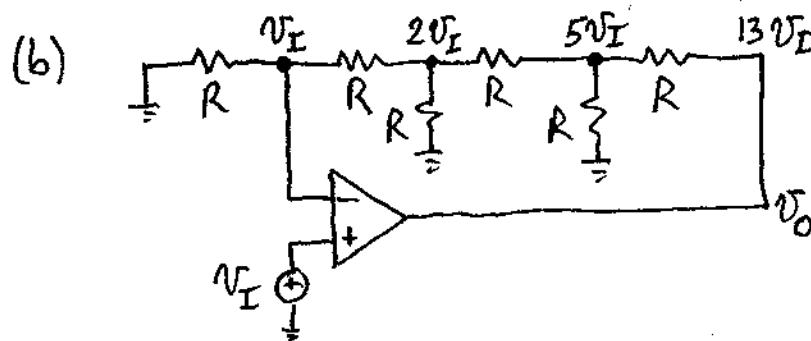
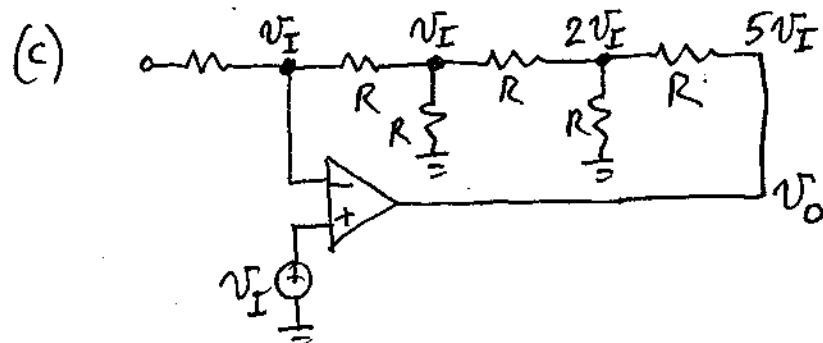
$$A_0 = 13 \text{ V/V}; \beta = 1/13 \text{ V/V}; GBP = A_0 \beta f_t = 4 \text{ MHz.}$$


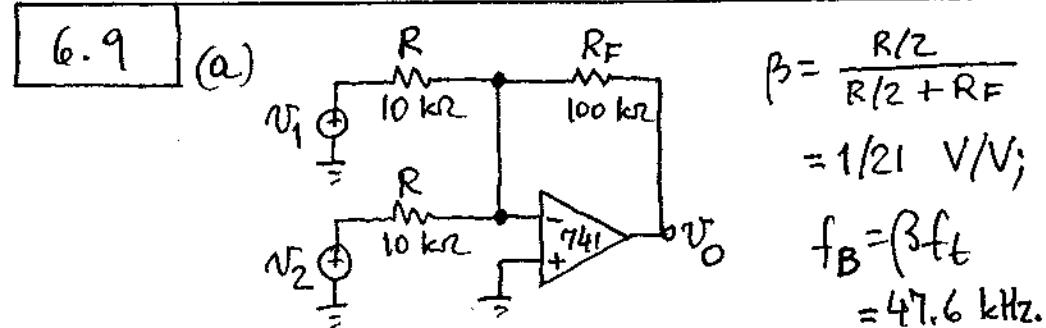
$$A_0 = 1/\beta = 5 \text{ V/V}; GBP = 4 \text{ MHz.}$$



$$\beta = \frac{R/2}{R/2 + R_F} = 1/21 \text{ V/V};$$

$$f_B = \beta f_t = 47.6 \text{ kHz.}$$

6.14

(b) With five inputs instead of two, we get $\beta = (R/5)/[R/5 + R_F] = 1/51 \text{ V/V}$, so $f_B = 19.6 \text{ kHz}$. Increasing the number of inputs decreases β and, hence, the -3 dB frequency.

6.10

$$f_{-3\text{dB}} = \beta f_t = \beta 10^6 \text{ Hz.}$$

Fig. P1.17: $\beta = 50/(50+20) - 10/(10+40) = \frac{18}{35} \text{ V/V}$; $f_{-3\text{dB}} = 514 \text{ kHz}$.

Fig. P1.19: $\beta = \frac{3+2+1}{4+3+2+1} - \frac{1}{1+2+3+4} = 0.5 \text{ V/V}$; $f_{-3\text{dB}} = 500 \text{ kHz}$.

Fig. P1.21: $\beta = R_1/(R_1+R_2) = 0.5 \text{ V/V}$, regardless of the switch position; $f_{-3\text{dB}} = 500 \text{ kHz}$.

Fig. P1.61: $\beta = 10/(10+30) = 1/4 \text{ V/V}$; $f_{-3\text{dB}} = 250 \text{ kHz}$.

6.11

$$\beta_{II} = (1+R_2/R_1)^{-1} = 2/3 \text{ V/V}; f_{II} = \beta_{II} f_t = 5.3 \text{ MHz}. \quad \beta_I = (1+2R_3/R_G)^{-1}, 50\Omega \leq R_G \leq 100.05 \text{ k}\Omega; \\ 1/2000 \text{ V/V} \leq \beta_I \leq 1/2 \text{ V/V}; 4 \text{ kHz} \leq f_I \leq 4 \text{ MHz}.$$

Wiper up: $H = \frac{V_0}{V_2 - V_1} = \frac{2000}{1+\eta f/(4 \text{ kHz})} \times \frac{0.5}{1+\eta f/(5.3 \text{ MHz})}$

First stage dominates, so $f_{-3\text{dB}} \approx 4 \text{ kHz}$.

Wiper down:


$$H = \frac{1}{1+\eta f/(4 \text{ MHz})} \times \frac{0.5}{1+\eta f/(5.3 \text{ MHz})}$$

$$\text{Impose } \left\{ \left[1 + \left(\frac{f}{4 \text{ MHz}} \right)^2 \right] \left[1 + \left(\frac{f}{5.3 \text{ MHz}} \right)^2 \right] \right\}^{1/2} = \sqrt{2}$$

$$\text{gives } f_{-3\text{dB}} = 2.93 \text{ MHz.}$$

6.5

6.12

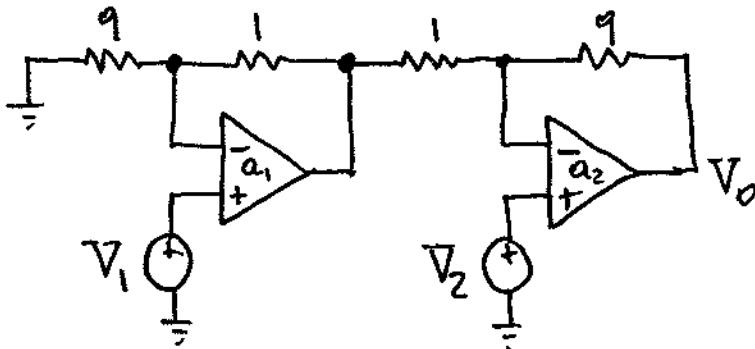

$$\beta_1 = 0.9 \text{ V/V}; f_1 = 900 \text{ kHz}; \beta_2 = 0.1; f_2 = 100 \text{ kHz}.$$

$$\begin{aligned} V_0 &= \frac{10}{1+jf/10^5} V_2 - \frac{q}{1+jf/10^5} \frac{1/0.9}{1+jf/(900 \times 10^3)} V_1 \\ &= \frac{10}{1+jf/10^5} \left[V_2 - \frac{1}{1+jf/(0.9 \times 10^5)} V_1 \right] \end{aligned}$$

Clearly, V_2 is processed with $f_{-3dB} = 100 \text{ kHz}$.


To find that of V_1 , impose $\sqrt{1 + (f/10^5)^2} \times \sqrt{1 + [f/(0.9 \times 10^5)]^2} = \sqrt{2}$. Then, $f_{-3dB} = 61 \text{ kHz}$.

6.13

Let $V_1 = V_2 = V_{cm}$. From Prob. 6.12:

$$V_0 = \frac{A_{cm}}{1+jf/10^5} \left[1 - \frac{1}{1+jf/(0.9 \times 10^5)} \right] V_{cm} = A_{cm} V_{cm}$$

$$CMRR = \frac{A_{cm}}{A_{cm}} = \frac{[1+jf/10^5] \times [1+jf/(0.9 \times 10^5)]}{jf/(0.9 \times 10^5)}$$

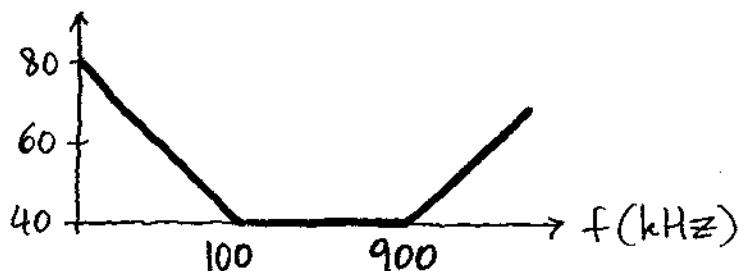 $CMRR_{dB}$ 

6.6

6.14

By the superposition principle,

$$E_o = 10(V_{os2} - V_{os1}) + (1 + A_{II})V_{os3};$$


$E_o(\max) = (21 + A_{II})V_{os}$. Thus, to minimize $E_o(\max)$ one should specify A_{II} as small as possible.

For instance, letting $A_I = 10 \text{ V/V}$ and $A_{II} = 1 \text{ V/V}$ gives $E_o(\max) = 22 V_{os}$.


We have $\beta_I = 1/A_I$ and $\beta_{II} = 1/(A_{II} + 1)$.

So, $f_I = \beta_I f_t$ and $f_{II} = \beta_{II} f_t$. The overall bandwidth is maximized when $f_I = f_{II}$, i.e. when $A_I = A_{II} + 1$; but, $A_I \times A_{II} = 10 \text{ V/V}$, so $(A_{II} + 1)A_{II} = 10 \Rightarrow A_{II} = 2.7 \text{ V/V}$ and $A_I = 3.7 \text{ V/V}$. In this case we get $E_o(\max) = 23.7 V_{os}$.

6.15

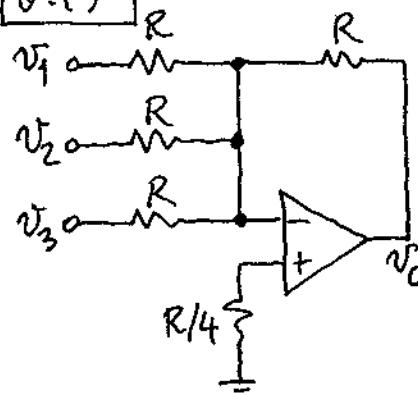

(a)

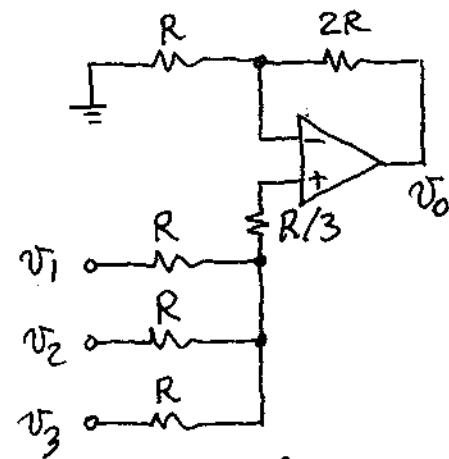

(b)

$$(a): \beta = (R/3)/(R/3 + R) = 1/4 \text{ V/V}; E_o = 4E_I;$$

$$f_B = f_t/4.$$

$$(b): \beta = R/(R+2R) = 1/3 \text{ V/V}; E_o = 3E_I; f_B = f_t/3; (b) \text{ is preferable in both cases.}$$

6.7


6.16 (a) $f_{-3dB} = f_t$, $R_i = \infty$, $R_o = 0$, least No. of components; lack of flexibility.

(b) $f_{-3dB} = f_t/2$, $R_i = \infty$, $R_o \neq 0$, more complex; gain can be altered by changing the resistors.

(c) $f_{-3dB} = (f_t/2)\sqrt{\sqrt{2}-1} = f_t/3.1$, $R_i \neq \infty$, $R_o = 0$; most complex, most flexible.

6.17 Large open-loop dc gain implies $I_{2kr} \rightarrow 0$; consequently, $I_{1kr} = I_{3kr} \rightarrow 0$, and $V_o = (1+32/16)V_i = 4V_i \Rightarrow A_o = 4 \text{ V/V}$. From Prob. 1.60, $\beta = 1/30$; $f_B = 3 \times 10^6 / 30 = 100 \text{ kHz}$.

6.18

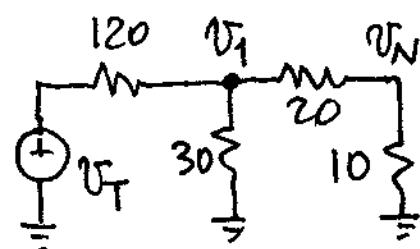


$$\begin{aligned} V_N &= \frac{10}{20+10} V_T \\ &= \frac{1}{3} \frac{30/130}{120+(30/130)} V_T \end{aligned}$$

$$\beta = V_N / V_T = 1/27.$$

$$f_B = \frac{27}{27} = 1 \text{ MHz}; A_o = -\frac{20}{10} \left(1 + \frac{120}{20} + \frac{120}{30}\right) = -22 \text{ V/V}. GBP = 22 \text{ MHz}.$$

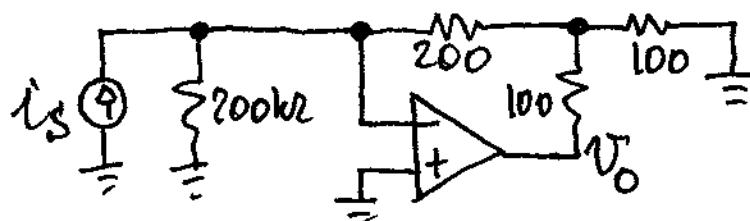
6.19

$$f_L = 10^{80/20} \times 1.8 \times 1.8 \times 10^3 = 18 \text{ MHz}.$$



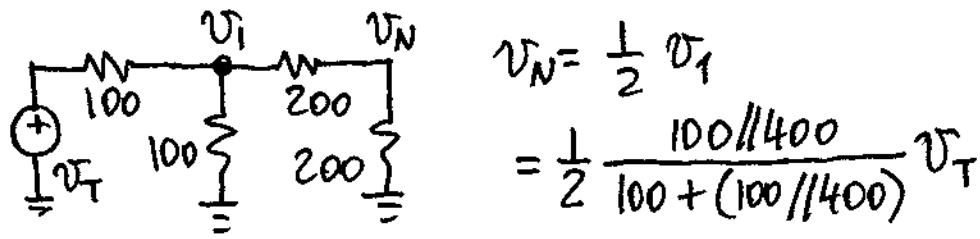6.8


$$V_o = -200 \left(1 + \frac{100}{200} + \frac{100}{100}\right) i_s \Rightarrow A_o = -0.5 V/\mu A.$$



$$\beta = V_N/V_T = 2/9; f_B = (2/9)18 = 4 \text{ MHz.}$$

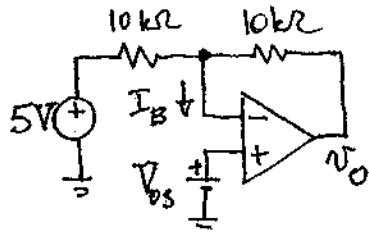6.20

$f_{-3\text{dB}} = \beta f_t = 0.5 f_t = 500 \text{ kHz}$ regardless of the switch position. Switch closed:



$$E_I(\text{max}) = V_{050} + |V_o|/a_o +$$


$$0.5R I_B = 0.75 \times 10^{-3} + 5/50,000$$

$$+ 0.5 \times 10^4 \times 50 \times 10^{-9} = 1.1 \text{ mV};$$

$$E_o(\text{max}) = (1/\beta) E_I(\text{max}) = 2.2 \text{ mV} \Rightarrow V_o = -4.9978 \text{ V.}$$

Switch open:
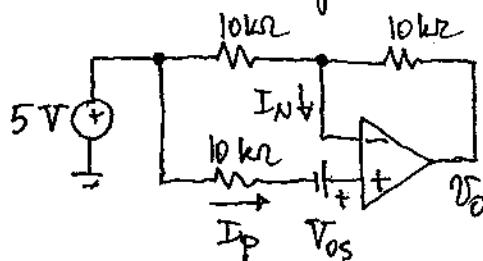
$$E_I = \pm V_{050} \pm 5/\text{CMRR} -$$



$$5/a_o + 0.5R I_N - R I_P$$

$$= \pm V_{050} \pm 5/\text{CMRR} -$$


$$5/a_o - 0.5R I_B$$

$$E_I(\text{max}) = -[0.75 \times 10^{-3} +$$

$$5/10^{100/20} + 5/50,000 + 0.5 \times 10^4 \times 50 \times 10^{-9} = 1.15 \text{ mV};$$

$$E_o(\text{max}) = 2.3 \text{ mV.}$$

6.21

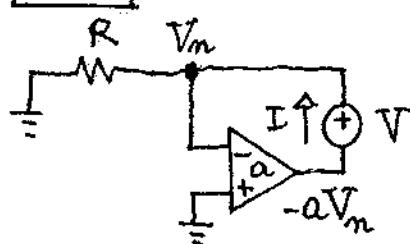


$$\text{KVL: } V = V_m - (-a)V_m = (1+a)V_m$$

$$\Rightarrow V_m = V/(1+a)$$

$$Z_o = \frac{V}{I} = \frac{V}{V_m/R} = R(1+a)$$

6.9

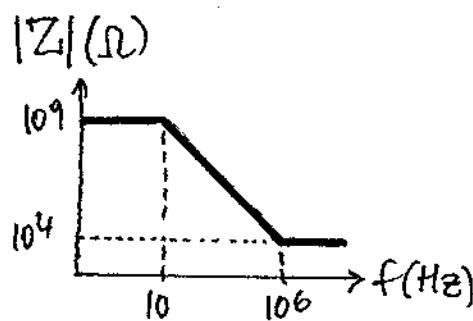

$$Z_o = R \left[1 + \frac{a_0}{1+jf/f_a} \right]$$


$$\approx R(1+a_0) \frac{1+jf/f_t}{1+jf/f_a}$$

$$\approx 10^9 \frac{1+jf/10^6}{1+jf/10} \Omega.$$

Capacitive impedance :

$$R_p = 10^9 \Omega, R_s = 10^4 \Omega, C_{eq} = 1/(2\pi \times 10^9 \times 10) = 15.9 \text{ pF.}$$

6.22

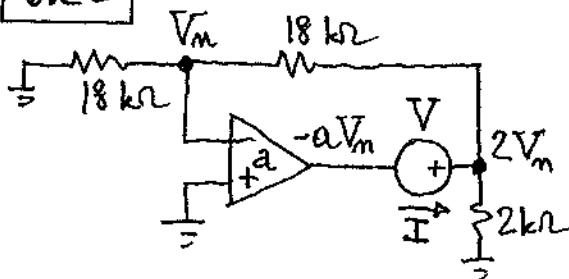

$$\text{KVL: } V = 2V_m - (-aV_m)$$


$$\Rightarrow V_m = V / (2+a);$$

$$\text{KCL: } I = 2V_m \times \left(\frac{1}{2k\Omega} + \frac{1}{36k\Omega} \right);$$

$$I = \frac{19}{18k\Omega} \frac{V}{2+a}; Z_o = \frac{V}{I} = \frac{18k\Omega}{19} \left(2 + \frac{10^5}{1+jf/10} \right)$$

$$Z_o = \frac{18}{19} 10^8 \frac{1+jf/(500 \text{ kHz})}{1+jf/(10 \text{ Hz})} \Omega; \text{ capacitive.}$$

6.23

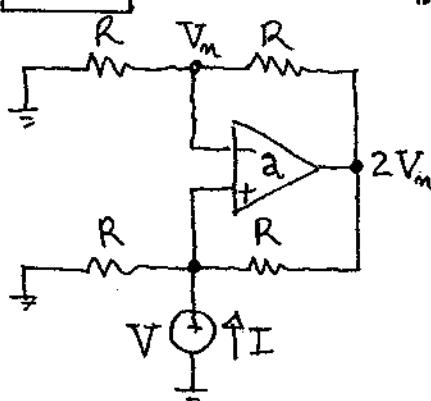

By op-amp action,

$$2V_m = a(V - V_m) \Rightarrow$$

$$V_m = Va/(2+a); \text{ KCL:}$$


$$I = \frac{V}{R} + \frac{V - 2V_m}{R} = \frac{2V}{R(1+a/2)}$$

$$Z_o = \frac{V}{I} = \frac{R}{2} \left(1 + \frac{a}{2} \right)$$

$$= (5 \text{ k}\Omega) \left(1 + \frac{10^5/2}{1+jf/10} \right)$$


$$\approx 2.5 \times 10^8 \frac{1+jf/(500 \text{ kHz})}{1+jf/10} \Omega$$

⇒ Capacitive impedance.
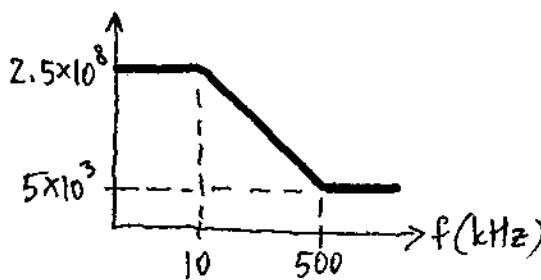
|Z_o| (Ω)

6.10

At low frequencies, where α is high, Z_0 is also high (ideally, $Z_0 \rightarrow \infty$ for $\alpha \rightarrow \infty$). As gain α starts to roll off, so does Z_0 . At high frequencies, where $\alpha \rightarrow 0$ and the op amp output thus behaves as a 0-V source, we have:
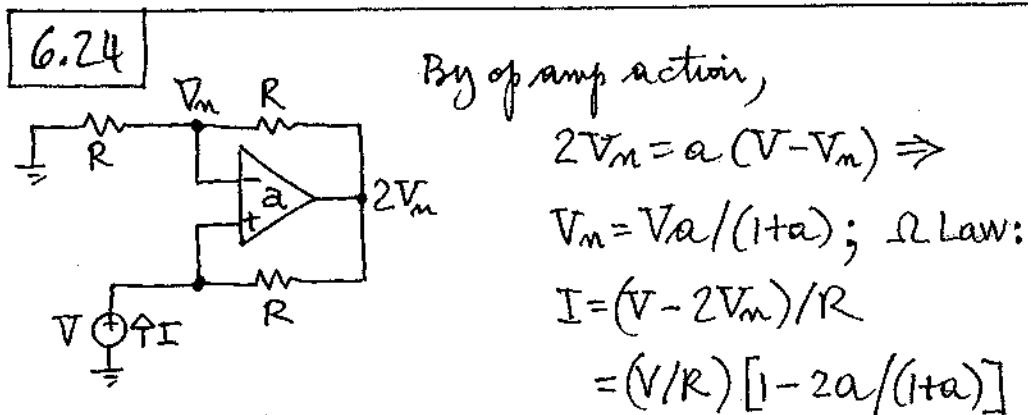
$$Z_0 \rightarrow R//R = 5 \text{ k}\Omega.$$


$$Z_{eq} = \frac{V}{I} = R \frac{1 + \alpha/2}{1 - \alpha/2} = R \frac{1 + \alpha_0/2}{1 - \alpha_0/2} \frac{1 + jf/[f_a(1 + \alpha_0/2)]}{1 - jf/[f_a(1 + \alpha_0/2)]}.$$

Ignoring 1 compared to $\alpha_0/2$, and letting $f_b \alpha_0 = f_t$ gives


$$Z_{eq} = -R \frac{1 + jf/(f_t/2)}{1 - jf/(f_t/2)} = -10^4 \frac{1 + jf/500 \text{ kHz}}{1 - jf/(500 \text{ kHz})} \Omega.$$

As f is varied from 0 to ∞ , Z_{eq} changes from $-10 \text{ k}\Omega$ to $+10 \text{ k}\Omega$; moreover, $|Z_{eq}| = 10 \text{ k}\Omega = \text{constant}$ regardless of frequency.

6.11

6.25

Circuit to find the gain $A = I_o/I_s$:

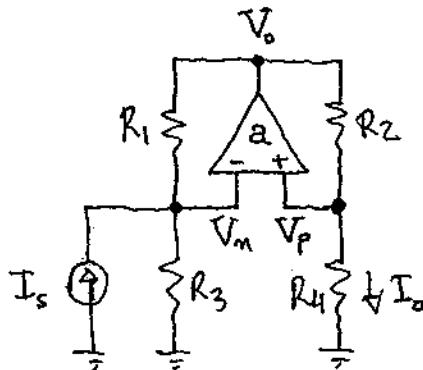

$$V_o = (R_2 + R_4) I_o; V_p = R_4 I_o;$$

$$V_o = a(V_p - V_m) \Rightarrow V_m = V_p - V_o/a$$

$$\Rightarrow V_m = \left(R_4 - \frac{R_2 + R_4}{a} \right) I_o; \text{ kcl:}$$


$$I_s + \frac{0 - V_m}{R_3} + \frac{V_o - V_m}{R_1} = 0$$

Eliminating V_m , collecting,

and substituting the resistance values gives:

$$A = \frac{I_o}{I_s} = \frac{-15/2}{7+12/a} = \frac{-7.5}{7+12(1+jf/f_b)/a_0} \approx \frac{-(15/14) A/A}{1+jf/(7f_t/12)} .$$

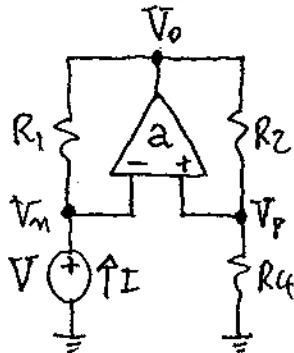Circuit to find the input impedance Z_i :



$$V_p = \frac{R_4}{R_2 + R_4} V_o = \frac{1}{6} V_o$$


$$V_o = a(V_p - V_m) = a\left(\frac{1}{6}V_o - V\right)$$

$$\Rightarrow V_0 = 6aV/(a-6)$$

$$I = \frac{V - V_0}{R_1} = \frac{1}{R_1} \left(V - \frac{6a}{a-6} V \right)$$

$$Z_c = \frac{V}{I} = (-2 \text{ k}\Omega) \frac{a-6}{a+1.2} \cong (-2 \text{ k}\Omega) \times \frac{1 - jf/(f_t/6)}{1 + jf/(f_t/1.2)} .$$

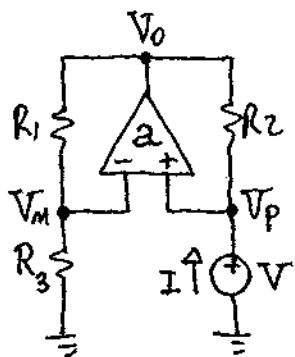Circuit to find the output impedance Z_o :



$$V_m = \frac{R_3}{R_1 + R_3} V_o = 0.75 V_o$$


$$V_o = \alpha(V_p - V_m) = \alpha(V - 0.75V_o)$$

$$\Rightarrow V_0 = aV / (1 + 0.75a)$$

$$I = \frac{V - V_o}{R_2} = \frac{1}{R_2} \left(V - \frac{a}{1+0.75a} V \right)$$

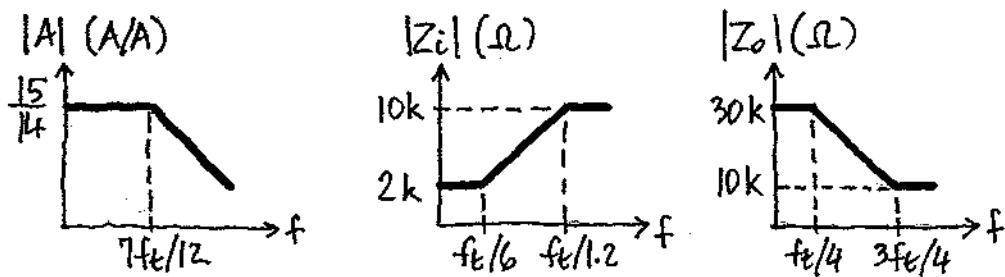6.12

$$Z_0 = \frac{V}{I} = (-30 \text{ k}\Omega) \frac{a+4/3}{a-4} = (-30 \text{ k}\Omega) \frac{1+jf/(0.75 \text{ ft})}{1-jf/(0.25 \text{ ft})}$$




6.26 $\beta = 10/(10+20) = 1/3 \text{ V/V.}$


$$Z_0(f \rightarrow 0) = \frac{R_o}{1 + a_0 \beta_0} = \frac{100}{1 + 10^5/3} = 3 \text{ m}\Omega.$$

$$f_b = f_t/a_0 = 40 \text{ Hz. } L_{eq} = Z_0(f \rightarrow 0)/2\pi f_b = \\ 3 \times 10^{-3}/2\pi 40 = 11.9 \mu\text{H. } f_{res} = 1/2\pi\sqrt{LC} = 146 \\ \text{ kHz. } Q = 1/\sqrt{(3 \times 10^{-3}) \times \sqrt{C/L}} = 3641.$$

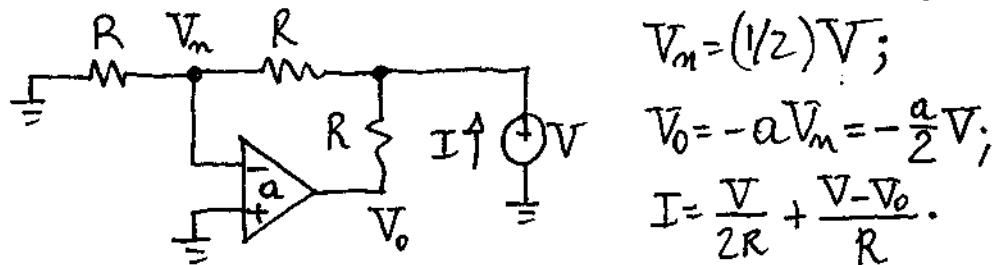6.27 $f_t = 300 \times 10^3 \times 10 = 3 \text{ MHz. Test voltage:}$




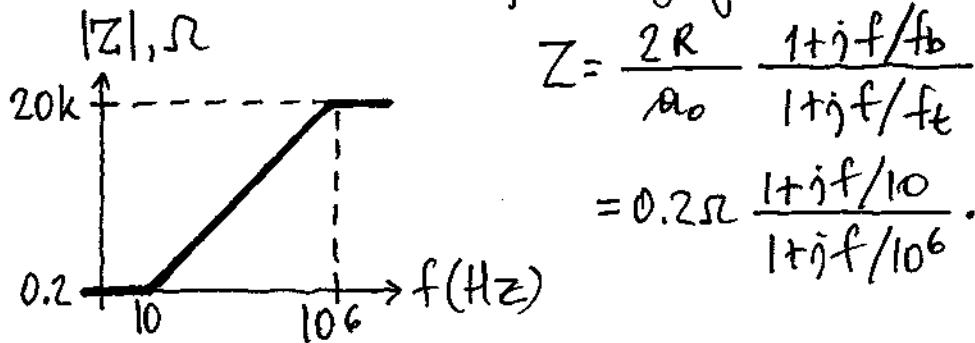Eliminating V_o gives $Z = \frac{V}{I} = \frac{2R}{3+a}$. Letting $a = 300,000/[1+jf/10]$ finally gives



6.13

6.28

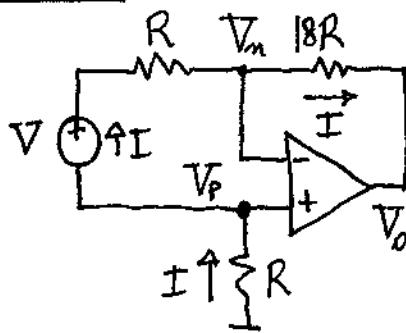

$$V_p = -RI; V_m = V - 2RI$$

$$V_o = \alpha(V_p - V_m) = \alpha(RI - V)$$


$$I = \frac{V_m - V_o}{18R} = \frac{V(1+\alpha) - RI(2+\alpha)}{18R}$$

Collecting,

$$Z = \frac{V}{I} = R \frac{20+\alpha}{1+\alpha}. \text{ Sub-}$$

stituting $\alpha \approx 1/(f/f_t)$,


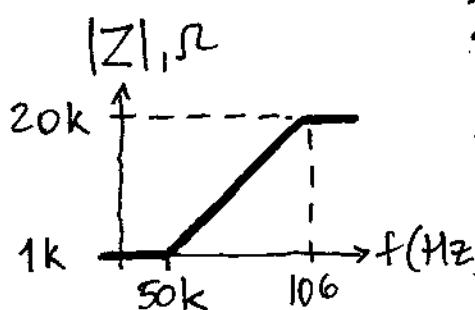
$$Z = 1k\Omega \frac{1 + jf/(5 \times 10^4)}{1 + jf/10^6}.$$



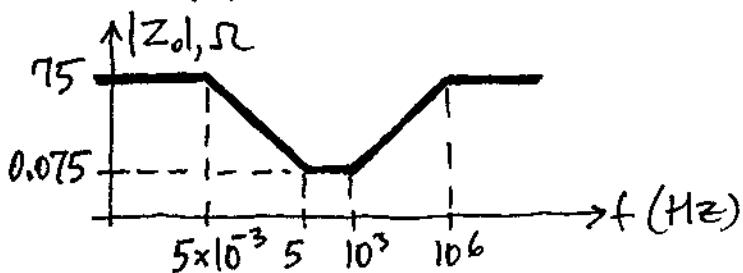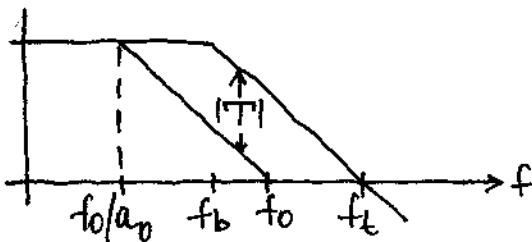
6.29

$$f_b = 5 \text{ Hz}; a_0 = 200 \text{ V/mV}; f_t = 1 \text{ MHz},$$

$$r_o = 75 \Omega; f_0 = 1/2\pi RC = 1 \text{ kHz}. Z_o = \frac{r_o}{1 + j\pi}$$



6.30

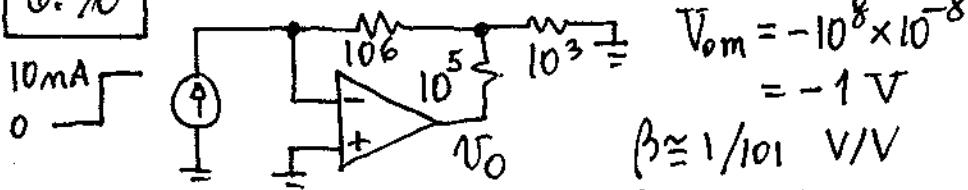

$$V_{om} = -10^8 \times 10^{-8} = -1 \text{ V}$$


$$\beta \approx 1/101 \text{ V/V}$$

$$f_B \approx 10 \text{ kHz.}$$

$\tau = 1/2\pi f_B \approx 16 \mu\text{s}$. $V_{om}(\text{sat}) \approx 80 \text{ V} \Rightarrow$ small-signal limited. $V_o(t) = -1(1 - e^{-t/16\mu\text{s}}) V$.

6.14

6.31

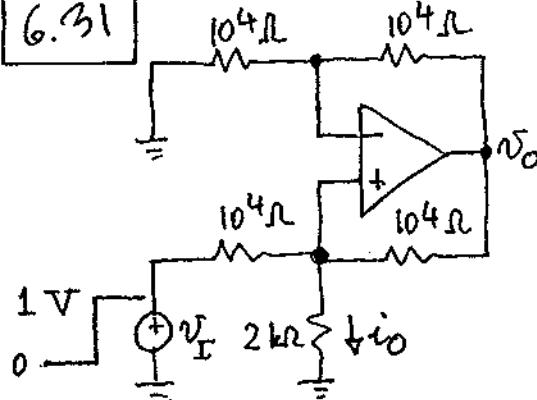


$$\beta = \frac{10}{10+10} - \frac{10//2}{10//2+10} = 5/14 \text{ V/V}$$

$$f_A = \beta f_t = 357 \text{ kHz}$$

$$\tau = 1/2\pi f_A = 446 \text{ ms.}$$

$$V_{om} = (1 + 10/10)V_{pm} = 2R_L \frac{V_{im}}{R_i} = 2 \times 2 \times 1/10 = 0.4 \text{ V;}$$

$V_{om(\text{crit})} = SR \times \tau = 0.5 \times 10^6 \times 446 \times 10^{-3} = 0.223 \text{ V} \Rightarrow SR$ -limited for $V_O < 0.4 - 0.223 = 0.177 \text{ V}$, small-signal limited thereafter. $i_o = V_p / R_L = (1/R_L) \frac{10//2}{10//2 + 10} (V_I + V_0)$

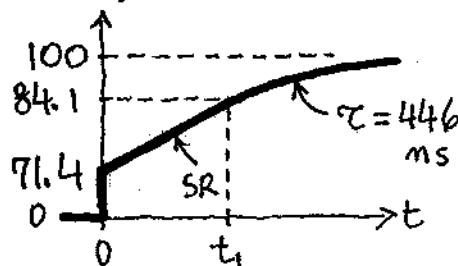 $i_o (\mu\text{A})$ 


$$\therefore i_o = (V_I + V_0) / (14 \text{ k}\Omega).$$

$$i_o(0) = 1/14 = 71.4 \mu\text{A}$$

$$i_o(t_1) = \frac{1+0.177}{14} = 84.1 \mu\text{A}$$

For $0 \leq t \leq t_1$, $V_O(t) = 0.5 \times 10^6 t$, so t_1 is
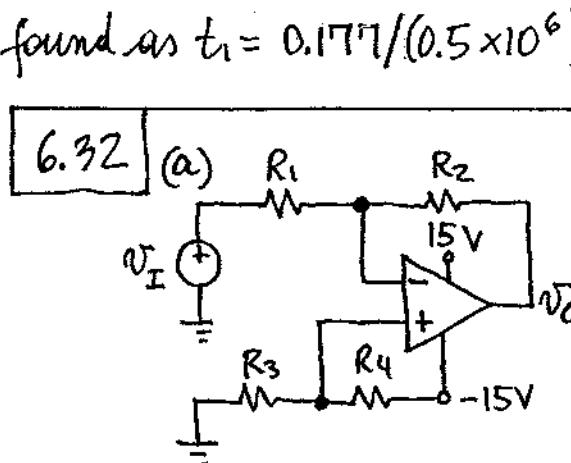
$$= 0.177 / (0.5 \times 10^6) = 354 \text{ ms.}$$



Maximize β by avoiding any additional resistances at the inverting input.

Use $R_1 = R_2 = R_4 = 100 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$.

(b) $\beta = 0.5 \text{ V/V}$, $f_A = 500 \text{ kHz}$, $\text{FPB} = 6.1 \text{ kHz}$.

6.15

6.33 $T = 1/(250 \times 10^3) = 4 \mu s$. During $T/2$ (or $2 \mu s$) the output changes by $|A| \times 2V_{im} = 2 \times 2 \times 2.5 = 10 V$. Consequently, $SR = \Delta V_o / \Delta t = (10 V) / (2 \mu s) = 5 V/\mu s$. By Eq. (6.27), $V_{om(crit)} = SR / 2\pi f_A \Rightarrow f_A = SR / 2\pi V_{om(crit)} \approx 2 \text{ MHz}$. Small-signal bandwidth = $f_A = 2 \text{ MHz}$; large-signal bandwidth = $SR / [2\pi V_{om}] = 5 \times 10^6 / [2\pi \times 2 \times 3.5 \times \sqrt{2}] \approx 80 \text{ kHz}$. \Rightarrow Useful bandwidth = 80 kHz , SR limited.

6.34 $f_1 = f_2 = \beta f_L = 10^6 / \sqrt{10^3} = 31.6 \text{ kHz}$; $\tau_1 = \tau_2 = 1/2\pi \times 31.6 \times 10^3 \approx 5 \mu s$. The output of OA₁ is $V_1 = (31.6 \text{ mV}) (1 - e^{-t/5 \mu s})$, without any SR limiting effects because $31.6 \text{ mV} < 80 \text{ mV}$. The initial rate of change of V_o is $dV_o/dt|_{t=0} = A_{o2} \times dV_i/dt|_{t=0} = 31.6 \times \frac{31.6 \text{ mV}}{5 \mu s} = 0.2 \text{ V/s}$. Since this is less than $0.5 \text{ V}/\mu s$, there are no SR limiting effects at the output of OA₂ either. We can therefore apply linear analysis techniques (Laplace Xform).

$$V_o(t) = \mathcal{L}^{-1} V_o(s), V_o(s) = A(s) V_i(s) = \frac{10^3}{[1 + s/(2\pi f_1)]^2} \times$$

$$\frac{10^{-3}}{s} = \frac{1}{s[1 + s/(2 \times 10^5)]^2} = \frac{4 \times 10^{10}}{s[s + 2 \times 10^5]^2} = \frac{A_1}{s} +$$

$$\frac{A_2}{[s + 2 \times 10^5]^2} + \frac{A_3}{s + 2 \times 10^5}. \text{ We have}$$


6.16

$$A_1 = V_o(s) \times s \Big|_{s=0} = 1$$

$$A_2 = V_o(s) \times [s + 2 \times 10^5]^2 \Big|_{s=-2 \times 10^5} = \frac{1}{s} \Big|_{s=-2 \times 10^5} = -2 \times 10^5$$

$$A_3 = \frac{d}{ds} \frac{1}{s} \Big|_{s=-2 \times 10^5} = -1$$
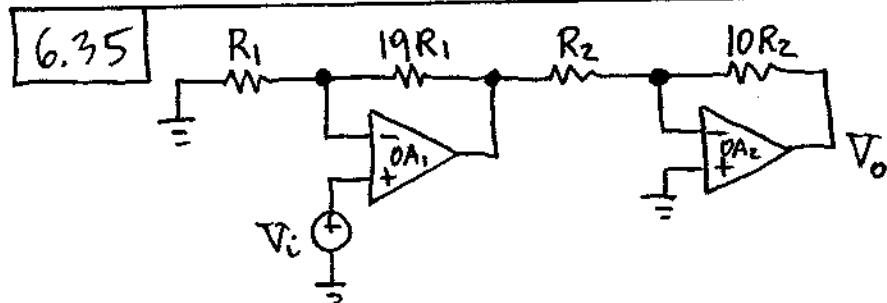
$$\begin{aligned} V_o(t) &= [A_1 + (A_2 t + A_3) e^{-t/5\mu s}] u(t) \\ &= [1 - (2 \times 10^5 t + 1) e^{-t/5\mu s}] u(t) \text{ V.} \end{aligned}$$




$$SR_2 \geq 2\pi f V_{o2m} = 2\pi \times 10^5 \times 5 \times \sqrt{2} = 4.44 \text{ V}/\mu\text{s}$$

$$SR_1 \geq SR_2/10 = 0.44 \text{ V}/\mu\text{s}$$

$$f_{t1} \geq f/\beta_1 = 10^5 \times 20 = 2 \text{ MHz}$$
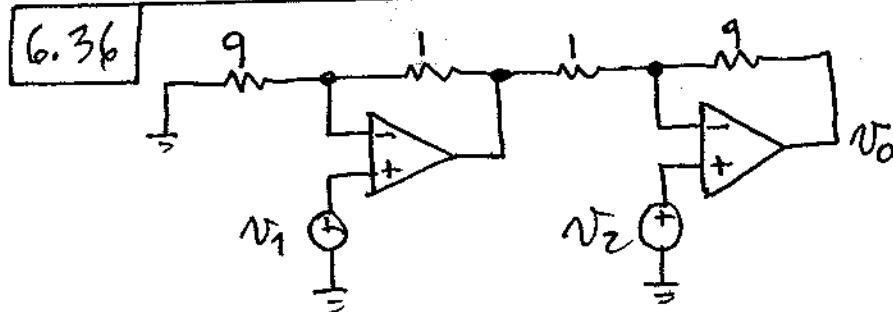
$$f_{t2} \geq f/\beta_2 = 10^5 \times 11 = 1.1 \text{ MHz.}$$



$$\beta_1 = 0.9 \text{ V/V}, \beta_2 = 0.1 \text{ V/V}, \omega_1 = 2\pi\beta_1 f_{t1} = 5.65 \times 10^6 \text{ rad/s,}$$

$$\omega_2 = 2\pi\beta_2 f_{t2} = 0.628 \times 10^6 \text{ rad/s.}$$

$$V_o(s) = \frac{10}{1+s/\omega_2} \left[V_2(s) - \frac{1}{1+s/\omega_1} V_1(s) \right] = \frac{10\omega_2}{s+\omega_2} \left[V_2 - \frac{\omega_1}{s+\omega_1} V_1 \right].$$

6.17

(a) Let $v_2(t) = V_{im} u(t)$, so that $V_2(s) = V_{im}/s$.

$$V_o(s) = \frac{10\omega_2}{s+\omega_2} \times \frac{V_{im}}{s} = \frac{A_0}{s} + \frac{A_2}{s+\omega_2}$$

$$A_0 = V_o(s) \times s \Big|_{s=0} = 10 V_{im}$$

$$A_2 = V_o(s) \times (s+\omega_2) \Big|_{s=-\omega_2} = -10 V_{im}$$

$$\begin{aligned} V_o(t) &= \mathcal{L}^{-1}[V_o(s)] = \mathcal{L}^{-1}\left[\frac{10V_{im}}{s} - \frac{10V_{im}}{s+\omega_2}\right] \\ &= 10V_{im}(1 - e^{-\omega_2 t})u(t) = 10V_{im}[1 - e^{-t/(1.59\mu s)}]u(t). \end{aligned}$$

(b) Let $V_1(s) = V_{im}/s$. Then,

$$V_o(s) = \frac{-10\omega_1\omega_2}{(s+\omega_2)(s+\omega_1)} \times \frac{V_{im}}{s} = -10V_{im}\left[\frac{1}{s} + \frac{1/8}{s+\omega_1} - \frac{9/8}{s+\omega_2}\right]$$

$$\begin{aligned} V_o(t) &= -10V_{im}\left[1 + \frac{1}{8}e^{-\omega_1 t} - \frac{9}{8}e^{-\omega_2 t}\right]u(t) \\ &= -10V_{im}\left[1 + \frac{1}{8}e^{-t/(177\text{ms})} - \frac{9}{8}e^{-t/(1.59\mu s)}\right]u(t). \end{aligned}$$

(c) $V_1(s) = V_2(s) = V_{im}/s$.

$$\begin{aligned} V_o(s) &= \frac{10\omega_2}{s+\omega_2} \left[1 - \frac{\omega_1}{s+\omega_1}\right] \times \frac{V_{im}}{s} = 10V_{im} \frac{\omega_2}{(s+\omega_1)(s+\omega_2)} \\ &= \frac{10}{8}V_{im}\left[\frac{1}{s+\omega_2} - \frac{1}{s+\omega_1}\right] \end{aligned}$$

$$V_o(t) = 1.25V_{im}\left[e^{-t/(1.59\mu s)} - e^{-t/(177\text{ms})}\right]u(t).$$

6.37

(a) Let $A_1 = A_2 = 10$. To simplify offset nulling, use inverting configuration. Let $R_1 = R_3 = 10\text{ k}\Omega$, $R_2 = R_4 = 100\text{ k}\Omega$. With $v_I = 0$,


$$E_o = \left(1 + \frac{R_4}{R_3}\right)V_{os2} - \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right)(V_{os1} + V_{RA}) =$$

(6.18)

$11V_{OS2} - 110V_{OS1} - 110V_{RA}$. Thus,

$$|V_{RA}| \leq [110V_{OS1}(\max) + 11V_{OS2}(\max)]/110 = 11mV.$$

Impose $|V_{RA}|_{\max} = 15mV$ to make sure. This can be achieved with $R_A = 1k\Omega$, $R_B = 1M\Omega$, $R_C = 100k\Omega$.

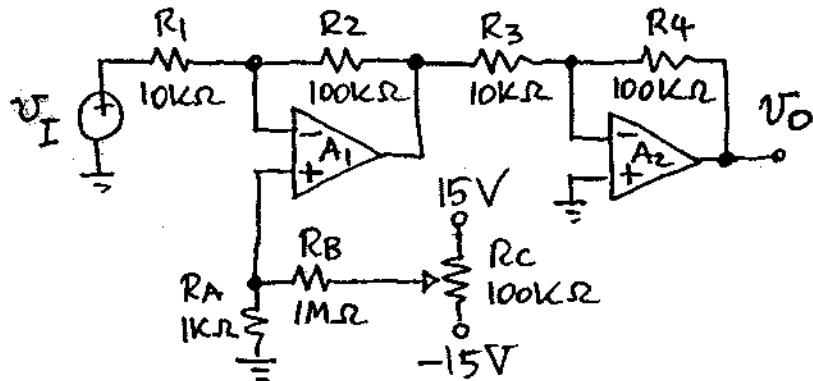

(b) $f_{A_1} = f_{A_2} = f_t / (1 + 100/10) = 4/11 = 365 \text{ kHz}$. $f_A = 365(\sqrt{2}-1)^{1/2} = 235 \text{ kHz}$.
 $\text{FPB} = 13 \times 10^6 / (2\pi \times 10) = 207 \text{ kHz}$.

(c) $V_{om} = 100 \times \sqrt{2} \times 50 \times 10^{-3} = 7.07 \text{ V}$.
 $f = 13 \times 10^6 / (2\pi \times 70.7) = 292 \text{ kHz}$. Useful range is up to 235 kHz, small-signal limited.

6.38

$(R_2/R_1)/a_o = 10/200,000 = 5 \times 10^{-5}$; $f_a = f_t/a_o = 3 \times 10^6/200,000 = 15 \text{ Hz}$; $f_A = f_t / (1 + R_2/R_1) = 3 \times 10^6 / (1+10) = 273 \text{ kHz}$. Thus,

$$V_N(\text{pk-pk}) = (50 \mu\text{V}) \sqrt{\frac{1 + (f/15)^2}{1 + [f/(273 \times 10^3)]^2}}. \text{ This}$$

relation holds up to $f = SR / (2\pi V_{om}) = 13 \times 10^6 / (2\pi \times 5) = 414 \text{ kHz}$, after which slew-rate limiting introduces distortion.

6.19

f	$V_N(\text{pk-pk})$
1 Hz	50.1 μV
10 Hz	60.1 μV
100 Hz	337 mV
1 kHz	3.33 mV
10 kHz	33.3 mV
100 kHz	0.313 V
400 kHz	0.752 V

Above 414 kHz, V_N distorts somewhat, and its pk-pk amplitude approaches 0.91 V.

6.39 $\beta = R_1/(R_1+R_2) = 1/4 \text{ V/V}; A_0 = 10^5 \times 4 = 0.4 \text{ V}/\mu\text{A}; f_B = \beta f_t = (1/4)4 = 1 \text{ MHz}. V_{om(\text{crit})} = SR/2\pi f_B = 15 \times 10^6 / (2\pi 10^6) = 2.39 \text{ V}; V_{om} = 0.4 \times 10^6 \times 20 \times 10^{-6} = 8 \text{ V} > V_{om(\text{crit})} \Rightarrow \text{slew-rate limited, and } f \leq SR/2\pi V_{om} \cong 300 \text{ kHz.}$

6.40 $\pi \sim \sin \pi \approx \pi$

(6) $A_0 = 2 \text{ V/V}, \beta = 0.5, V_{om} = 2 \text{ V}$

$2 \text{ mV}, V_{om(\text{crit})} \cong 80 \text{ mV}$

(7) $A_0 = 2 \text{ V/V}, \beta = 1/3, V_{om} =$

$239 \text{ mV}, V_{om(\text{crit})} \cong 120 \text{ mV}$

6.40

6.41

For this circuit, $A_0 = -8 \text{ V/V}$, and $\beta = 1/13 \text{ V/V}$. We want $f_B = \beta f_t \geq 1 \text{ MHz}$, or $f_t \geq 13 \text{ MHz}$, and $SR \geq 2\pi f V_{om} = 2\pi \times 10^6 \times 8 \times 1 \approx 50 \text{ V/}\mu\text{s}$.


6.42

In the upper audio range we have

$$\frac{1}{\beta} \approx \left(1 + \frac{R_2}{R_1}\right) \frac{1 + \eta f/f_p}{1 + \eta f/f_z}, \quad 1 + \frac{R_2}{R_1} = 11 \text{ V/V}, \quad f_z =$$

$$\frac{1}{2\pi(R_1||R_2)C_2} = 224 \text{ kHz}, \quad f_p = \frac{1}{2\pi R_2 C_2} = 20 \text{ kHz}.$$

Gain

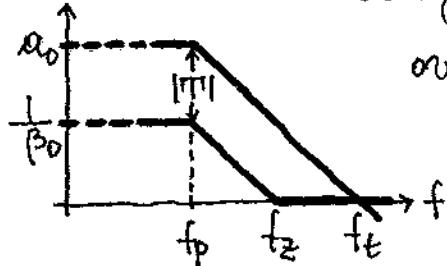

For a gain error of less than 1%


over the entire audio range

we need $|T(j20 \text{ kHz})| \geq 100$, or $A_0 \geq 1,100 \text{ V/V}$,

and $f_t \geq A_0 f_p = 22 \text{ MHz}$. Moreover, $SR \geq 2\pi \times (20 \text{ kHz}) \times (10 \text{ V}) = 1.3 \text{ V/}\mu\text{s}$.

6.43

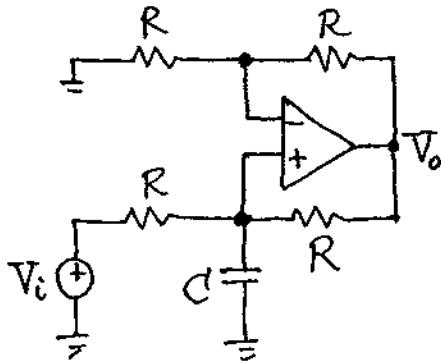(a) $R = 2/(2\pi \times 10^3 \times 10 \times 10^{-9}) = 13.6 \text{ k}\Omega$, 1%.



(b) To find β , suppress V_i , break the wire at the op amp output, and apply a test voltage V_t . Then, $\beta = (V_m - V_p)/V_t$:

$$\beta = \frac{R}{R+R} - \frac{R||1/sC}{R+R||1/sC} = \frac{1}{2} - \frac{1}{1+R/[R||1/s]}$$

$$= \frac{1}{2} - \frac{1}{2+sRC} = \frac{1}{2} \frac{jf/f_0}{1+jf/f_0}, \quad f_0 = 1 \text{ kHz}.$$


(6.21)

$$\frac{1}{\beta} = 2 \frac{1+if/f_0}{if/f_0}; \quad \frac{1}{\beta_0} = \frac{1}{if/2f_0}; \quad \frac{1}{\beta_{00}} = 2 V/V.$$


The $|1/\beta_0|$ curve intercepts the $|a|$ curve at a frequency f_1 such that $1/(f_1/2f_0) = a_0$, or $f_1 = 2f_0/a_0 = 2 \times 10^3 / 200,000 = 0.01 \text{ Hz}$; the $|1/\beta_{00}|$ curve intercepts the $|a|$ curve at a frequency f_2 such that $2 = 1/(f_2/f_t)$, or $f_2 = f_t/2 = 500 \text{ kHz}$.

The transfer function is $H(if) = H_{\text{ideal}} \times \frac{1/(1+1/T)}{[1/(if/f_0)]/(1+1/T)}$. For $f_1 \ll f \ll f_2$, where $|T| \gg 1$, we have $H \approx H_{\text{ideal}}$. For $f \ll f_1$, $H \rightarrow [1/(if/f_0)] a_0 \beta_0 = a_0/2$. For $f \gg f_2$, $H \rightarrow [1/(if/f_0)] a_{00} \beta_{00} = \frac{1}{if/f_0} \times \frac{1}{if/f_2}$, indicating a breakpoint at f_1 and another at f_2 :
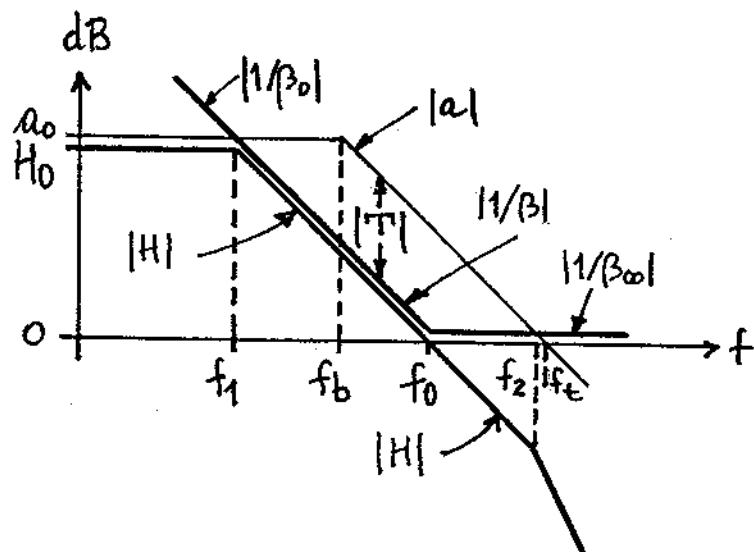
$$H(if) = \frac{a_0/2}{[1+if/f_1][1+if/f_2]} = \frac{10^5}{[1+if/0.01][1+if/(5 \times 10^5)]}$$



6.22

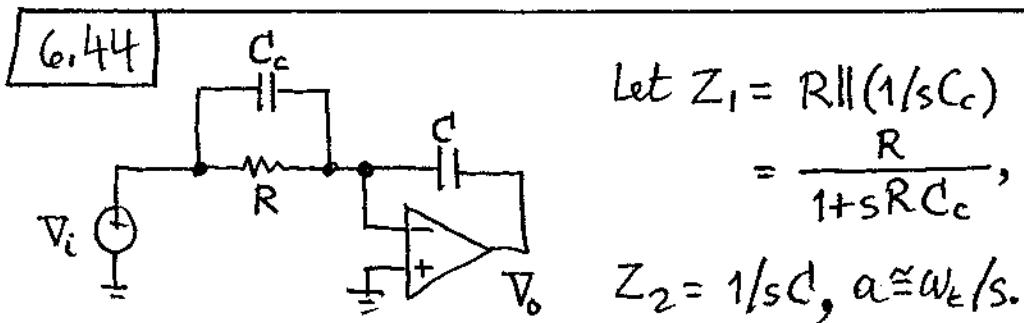

$$\text{Let } Z_1 = R \parallel (1/sC_c)$$

$$= \frac{R}{1+sRC_c},$$

$$Z_2 = 1/sC, \alpha \approx \omega_t/s.$$

$$\begin{aligned} H = \frac{V_o}{V_i} &= -\frac{Z_2}{Z_1} \frac{1}{1 + (1 + \frac{Z_2}{Z_1}) \frac{1}{\alpha}} = -\frac{1+sRC_c}{SRC} \frac{1}{1 + \left(1 + \frac{1+sRC_c}{SRC}\right) \frac{s}{\omega_t}} \\ &= -\frac{1}{s/\omega_0} \times \frac{1+sRC_c}{1 + \frac{s}{\omega_t} + \frac{\omega_0}{\omega_t} + s \frac{\omega_0 RC_c}{\omega_t}} \approx -\frac{1}{s/\omega_0} \times \frac{1+sRC_c}{1 + s \frac{1+\omega_0 RC_c}{\omega_t}}. \end{aligned}$$

(b) To make the error function unity, impose $RC_c = (1 + \omega_0 RC_c)/\omega_t$. Using $R = 1/\omega_0 C$, this gives $C_c = C/(f_t/f_0 - 1)$.

(c) $C = 1\text{nF}$, $R = 1/2\pi f_0 C = 15.91\text{k}\Omega$, $C_c = C/(10^6/10^4 - 1) = 10.1\text{pF}$.

The following PSpice files show the response first without and then with C_c .

Problem 6.44

```

Vi 1 0 ac 1V
R 1 2 15.91k
Cc 1 2 1fF
C 2 3 1nF
eopamp 3 0 Laplace {V(0,2)}={200k/(1+s/31.42)}
.ac dec 10 1k 10Meg
.probe
.end

```



Problem 6.44

```

Vi 1 0 ac 1V
R 1 2 15.91k
Cc 1 2 10.1pF
C 2 3 1nF
eopamp 3 0 Laplace {V(0,2)}={200k/(1+s/31.42)}
.ac dec 10 1k 10Meg
.probe
.end


```

(6,23)

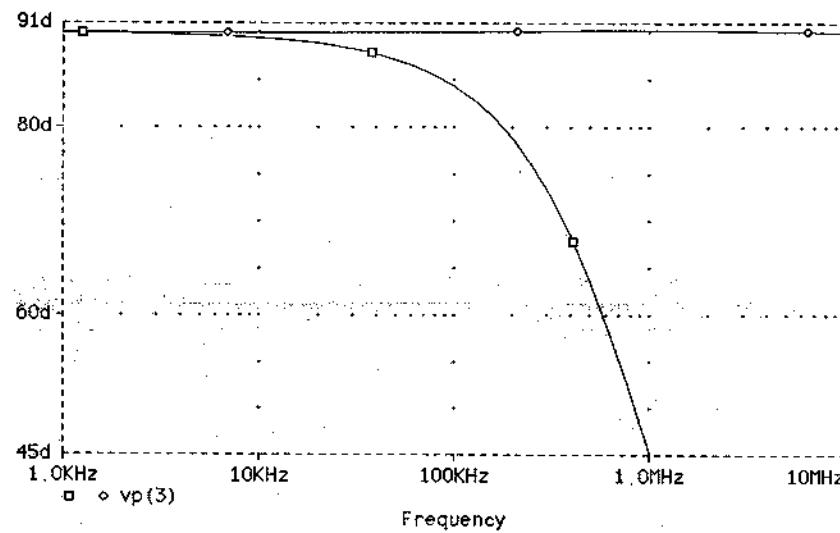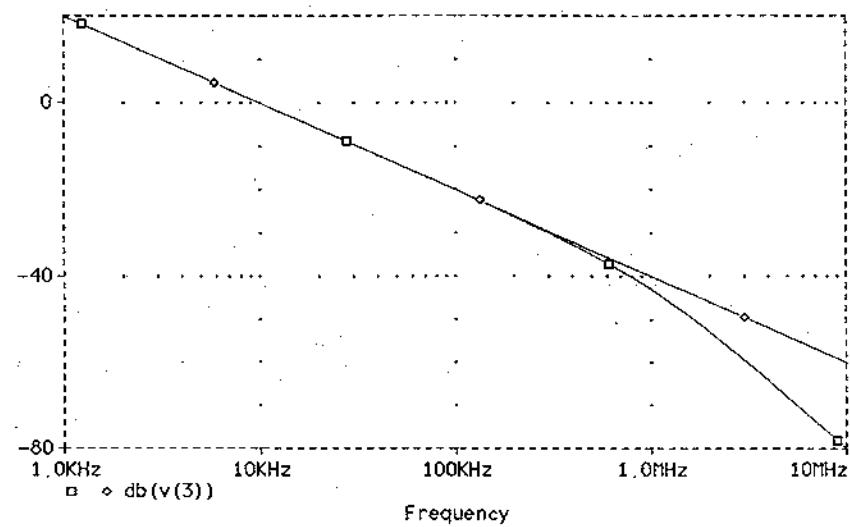

6.24

6.45 (a)

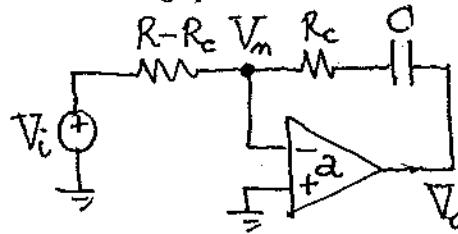

$$\alpha \approx \frac{w_t}{s}; \text{superposition:}$$

$$\begin{aligned} V_m &= \frac{(R_c + 1/sC)V_i + (R - R_c)V_o}{R + 1/sC} \\ &= \frac{(sR_cC + 1)V_i + s(R - R_c)C V_o}{1 + sRC} \end{aligned}$$

$$V_o = -\alpha V_m = -\frac{w_t}{s} \frac{(sR_cC + 1)V_i + s(R - R_c)C V_o}{1 + sRC}; \text{ collecting,}$$

$$H = \frac{V_o}{V_i} = -\frac{sR_cC + 1}{sRC(s/w_t + 1) + s(1/w_t - R_cC)}$$

(b) Imposing $1/w_t = R_c C$, or $R_c = 1/2\pi f_t C$ has the double effect of eliminating the second s -term in the denominator, and simplifying H to $H = -(s/w_t + 1) / [sRC(s/w_t + 1)] = -1/sRC$.




(c) To contain the effect of $r_o \neq 0$, make $R_c \gg r_o$, e.g. $R_c = 1 k\Omega$. Then, $R = (f_t/f_0)R_c = (10^6/10^4)10^3 = 100 k\Omega$, so $R - R_c = 99 k\Omega$, and $C = 1/2\pi f_0 R = 159.15 \mu F$.

The following PSpice code shows the uncompensated response, as well as the compensated response for the ideal case $r_o = 0$ and the more practical case $r_o = 100 \Omega$.

6.25

```
Problem 6.45
Vi 1 0 ac 1V
R 1 2 100k
Rc 2 4 1m
C 4 3 159.154pF
eopamp 5 0 Laplace {V(0,2)}={200k/(1+s/31.42) }
ro 5 3 100
.ac dec 10 1k 10Meg
.probe
.end
Problem 6.45
Vi 1 0 ac 1V
R 1 2 99k
Rc 2 4 1k
C 4 3 159.154pF
eopamp 5 0 Laplace {V(0,2)}={200k/(1+s/31.42) }
ro 5 3 1m
.ac dec 10 1k 10Meg
.probe
.end
Problem 6.45
Vi 1 0 ac 1V
R 1 2 99k
Rc 2 4 1k
C 4 3 159.154pF
eopamp 5 0 Laplace {V(0,2)}={200k/(1+s/31.42) }
ro 5 3 100
.ac dec 10 1k 10Meg
.probe
.end
```

(6.26)

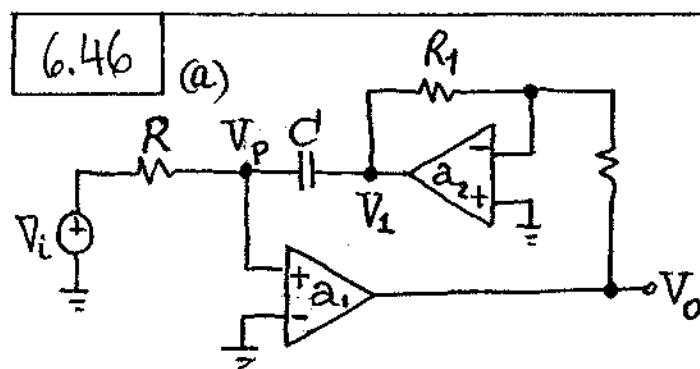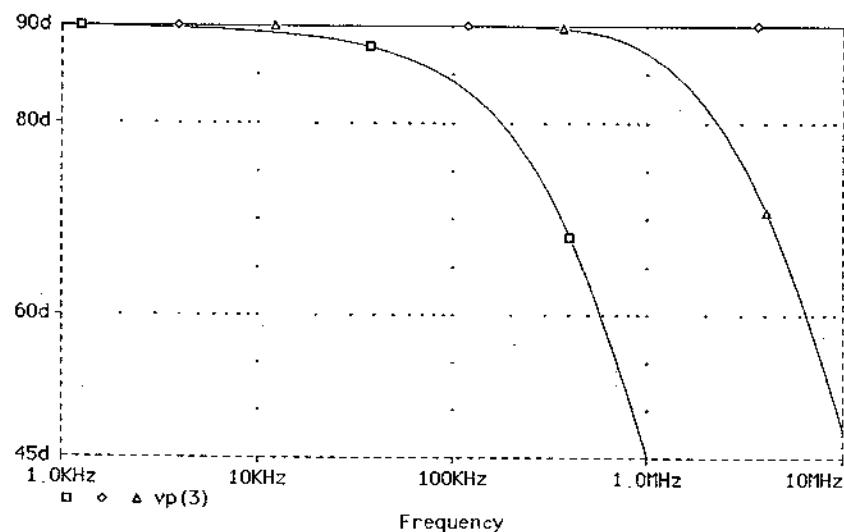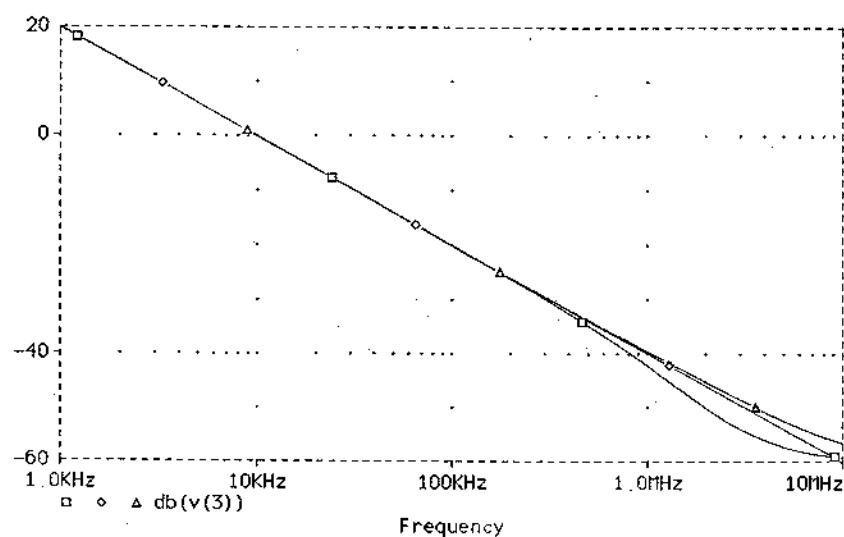

$$V_o = a_1 V_p, \quad V_p = \frac{1}{1+s/w_0} V_i + \frac{s/w_b}{1+ts/w_0} V_1, \quad V_1 = -\frac{1}{1+s/(w_{t_2}/2)} V_o, \quad a_1 \approx w_{t_1}/s. \text{ Combining and letting } w_{t_1} = w_{t_2} = w_t \text{ gives}$$

(6.27)

$$H = \frac{V_o}{V_i} = + \frac{1}{s/w_0} \times \frac{1+s/(w_t/2)}{1+\frac{w_0}{w_t} + \frac{s}{w_t} \left(1 + \frac{w_0}{w_t/2}\right) + \frac{s^2}{w_t^2/2}}$$

$$\cong + \frac{1}{s/w_0} \times \frac{1+s/(w_t/2)}{1+\frac{s}{w_t} + \frac{s^2}{w_t^2/2}}.$$

Letting $s/w_t = jf/f_t = jx$, the error function is

$$\frac{1+j2x}{1-2x^2+jx} = \frac{(1+j2x)(1-2x^2-jx)}{(1-2x^2)^2+x^2} = \frac{1+jx-j2x^3}{1-3x^2+4x^4}.$$

For $x \ll 1$ this reduces approximately to $1+jx$, indicating $E_\phi \cong x = f/f_t$.

(b) The following PSpice code shows the response without compensation ($OA_2 \sim$ ideal) and with compensation.

Problem 6.46

```

Vi 1 0 ac 1V
R 1 2 15.9154k
C 2 5 1nF
eoal 3 0 Laplace {V(2,0)}={200k/(1+s/31.42)}
r1 3 4 10k
r2 4 5 10k
eoaz 5 0 Laplace {V(0,4)}={1G}
.ac dec 10 1k 10Meg
.probe
.end

```



Problem 6.46

```

Vi 1 0 ac 1V
R 1 2 15.9154k
C 2 5 1nF
eoal 3 0 Laplace {V(2,0)}={200k/(1+s/31.42)}
r1 3 4 10k
r2 4 5 10k
eoaz 5 0 Laplace {V(0,4)}={200k/(1+s/31.42)}
.ac dec 10 1k 10Meg
.probe
.end


```

6.28

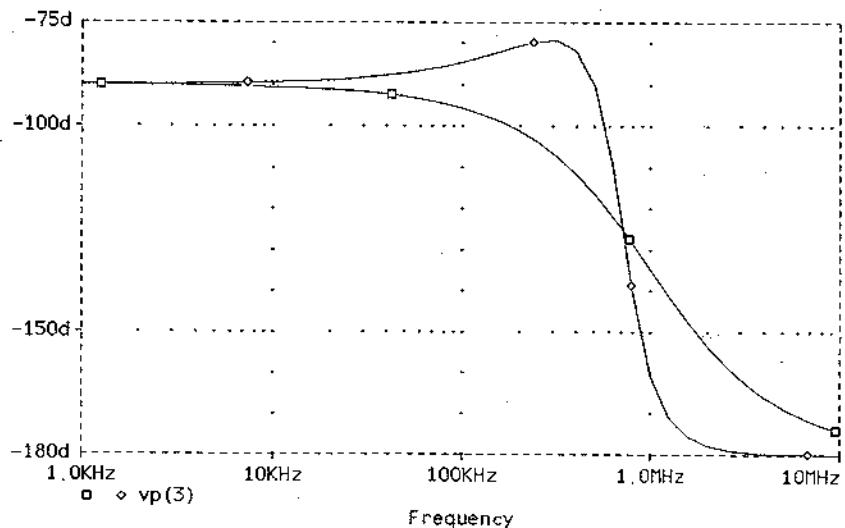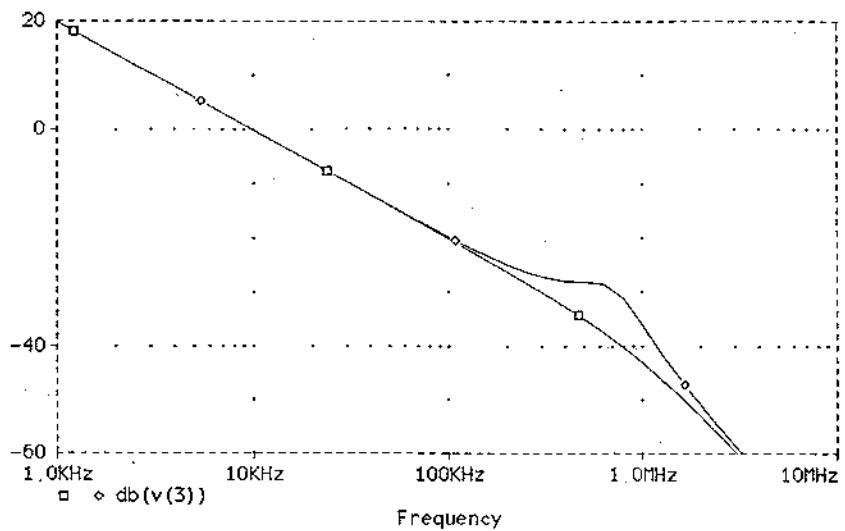

6.47

(a)

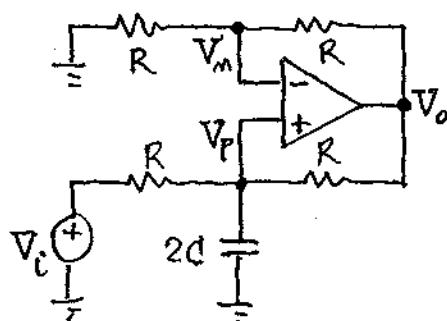

$$V_o = \alpha(V_p - V_m); \quad V_m = V_o/2;$$

$$V_p = \frac{R \parallel (1/2sC)}{R + R \parallel (1/2sC)} (V_i + V_o)$$

$$\frac{V_p}{V_i + V_o} = \frac{1/2}{1 + sRC} = \frac{1/2}{1 + s/w_0}, \quad w_0 = \frac{1}{RC}$$

Letting $\alpha = w_0/s$ & combining,

$$H = \frac{V_o}{V_i} = \frac{1}{s/w_0} \frac{1}{1 + 2w_0/w_t + 2s/w_t} \cong \frac{1}{jf/f_0} \times \frac{1}{1 + jf/(f_t/2)}$$

$$\varepsilon_\phi \cong -f/(f_t/2) \text{ for } f \ll f_t/2$$

6.29

We now have

$$V_p = \frac{R \parallel (R_c + 1/sC)}{R + R \parallel (R_c + 1/sC)} (V_i + V_o) = \frac{1}{2} \frac{1+sR_cC}{1+s(R+2R_c)C} (V_i + V_o)$$

Substituting and collecting,

$$\begin{aligned} H &= \frac{V_o}{V_i} = \frac{1}{s/w_0} \frac{1+2sR_cC}{1+2\frac{w_0}{w_t} + 2\frac{w_0}{w_t}s(R+2R_c)C} \\ &\approx \frac{1}{s/w_0} \frac{1+2sR_cC}{1+2s\frac{w_0}{w_t}(R+2R_c)C}. \end{aligned}$$

To drive the error term to unity, impose

$$R_c = \frac{w_0}{w_t} (R+2R_c), \text{ or } R_c = R/(w_t/w_0 - 2).$$

6.48

The closed-loop gain of the second op amp is $A_2 = [(1+R_2/R_1) - R_2/R_1]/(1+s/w_2) = 1/(1+s/w_2)$, $w_2 = \beta_2 w_{t_2} = [R_1/(R_1+R_2)]w_{t_2}$. The first op amp gives

$$V_o = -a_1 \left[\frac{1}{1+s/w_0} V_i + \frac{s/w_0}{1+s/w_0} A_2 V_o \right],$$

$w_0 = 1/RC$. Substituting A_2 and $a_1 = w_1/s$, $w_1 = w_{t_1}$, we get, after collecting,

$$H = \frac{V_o}{V_i} = \frac{-1}{s/w_0} \frac{1+s/w_2}{1+\frac{w_0}{w_1} + \frac{s}{w_1} \left(1+\frac{w_0}{w_2}\right) + \frac{s^2}{w_1 w_2}}. \text{ For } w_0 \ll w_1,$$

and $w_0 \ll w_2$, this simplifies to

$$H = \frac{-1}{s/w_0} \frac{1+s/w_2}{1+s/w_1 + s^2/w_1 w_2} = \frac{-1}{j f/f_0} \frac{1+jf/(\beta_2 f_{t_2})}{1-f^2/(\beta_2 f_{t_1} f_{t_2} + j f/f_{t_1})}.$$

For $f_{t_1} = f_{t_2} = f_t$ and $R_1 = R_2 (\Rightarrow \beta_2 = 0.5)$ we get

6.30

$$\text{Error function} = \frac{1+2jf/f_t}{1-2(f/f_t)^2+jf/f_t} = \frac{1+j2x}{1-2x^2+jx}$$

$$= \frac{(1+j2x)(1-2x^2-jx)}{(1-2x^2)^2+x^2} = \frac{1+jx-j4x^3}{1-3x^2+4x^4}, \text{ indicating}$$

that for $x \ll 1$ ($f \ll f_t$) we have $\epsilon_f \approx + (f/f_t)$.

Compared to the ordinary inverting integrator, which gives a negative ϵ_f (see Eq. 6.35), the present integrator gives a positive ϵ_f (of the type of Eq. 6.40); it can be used to compensate for the negative ϵ_f 's of other integrators or amplifiers in the same loops.

6.49

The second op. amp provides a closed-loop gain of

$$A_2 = \left[\left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \right] \frac{1}{1+s/w_2} = \frac{1}{1+s/w_2}, \quad w_2 =$$

$$\beta_2 w_{t2} = \frac{R_1}{R_1 + R_2} w_{t2}. \quad \text{The first op. amp gives } V_o =$$

$$\alpha_1 (V_{p1} - V_{m1}), \text{ where } \alpha_1 \approx w_1/s, \quad w_1 = w_{t1}, \quad V_{m1} =$$

$$(1/2) A_2 V_o, \text{ and } V_{p1} = [0.5/(1+s/w_0)] (V_i + V_o), \quad w_0 = \frac{1}{RC}.$$

Combining and collecting gives

$$H = \frac{V_o}{V_i} = \frac{1}{s/w_0} \frac{1 + \frac{s}{w_2}}{2 \frac{w_0}{w_1} + 2 \frac{s}{w_1} \left(1 + \frac{w_0}{w_2} \right) - \frac{w_0}{w_2} + 2 \frac{s^2}{w_1 w_2} + 1}$$

$$\approx \frac{1}{s/w_0} \frac{1 + \frac{s}{w_2}}{1 + 2 \frac{s}{w_1} + 2 \frac{s^2}{w_1 w_2}}.$$

For $w_{t1} = w_{t2} = w_t$ and $R_1 = R_2 (\Rightarrow \beta = 0.5 \text{ V/V})$



(6.31)

the error function becomes

$$\frac{1+jf/0.5f_t}{1-(f/0.5f_t)^2+jf/0.5f_t}; \text{ this is of the same type}$$

of Eq. (6.38), but with $f_t/2$ instead of f_t . We thus conclude that $E_\phi \approx -(f/0.5f_t)^3$ for $f \ll f_t/2$.

(6.50)

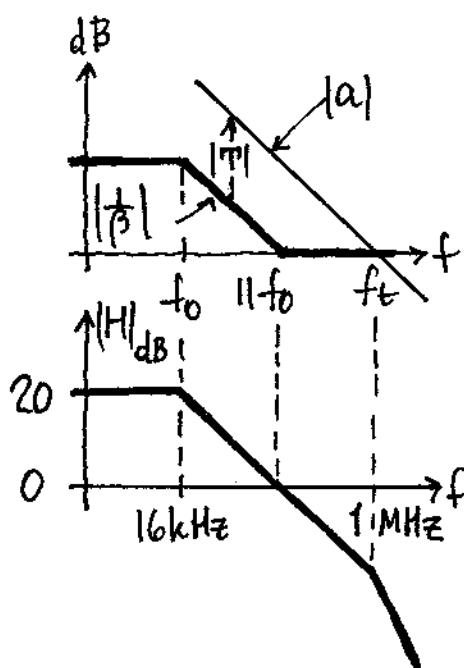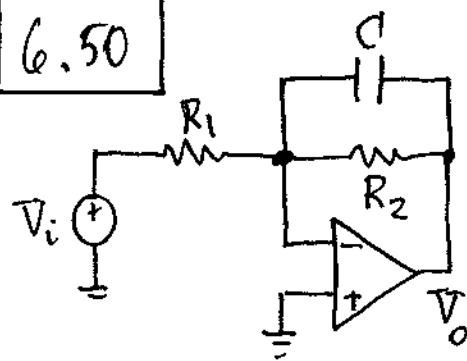

$$\text{let } Z_2 = R_2 // (1/sC) = \frac{R_2}{1+jf/f_0}, f_0 = \frac{1}{2\pi R_2 C} = 16 \text{ kHz. Then}$$

$$\begin{aligned} \frac{1}{\beta} &= 1 + \frac{Z_2}{R_1} = 1 + \frac{10}{1+jf/f_0} \\ &= 1 + \frac{1+jf/(16f_0)}{1+jf/f_0} \end{aligned}$$

H has a pole at f_0 and another at f_t :

$$H = \frac{-10 \text{ V/V}}{\left(1+j\frac{f}{16 \text{ kHz}}\right)\left(1+j\frac{f}{1 \text{ MHz}}\right)}$$

(6.51)

$$\beta = 0.5 \text{ V/V}; \beta f_t = 0.5 f_t; H = H_{\text{ideal}} \frac{1}{1+j1/T}$$

$$H = \frac{1-jf/f_0}{1+jf/f_0} \times \frac{1}{1+jf/0.5f_t} \cdot |H| \text{ is constant only up to } 0.5 f_t, \text{ after which it rolls off with } f.$$

6.32

We also have a phase error $\epsilon_\phi = -\tan^{-1}(f/f_t)$.

For instance, if $f_0 = 10 \text{ kHz}$ and $f_t = 1 \text{ MHz}$,

we get $H(j10^4 \text{ Hz}) = 0.9998 \text{ V/V } [-91.15^\circ]$ instead of the ideal value $1 \text{ V/V } [-90^\circ]$.

6.52

For simplicity, assume equal R 's and matched OAs, so that

$$a_1 = a_2 = a = \frac{w_t}{s} \text{ at}$$

high frequencies.

By inspection,

$V_1 = a(0.5V_2 - V_3)$, $V_2 = a(V - V_3)$. By the superposition principle,

$$V_3 = \frac{V_2 + (s/w_0)V_1}{1+s/w_0}, w_0 = \frac{1}{RC} \text{ . System of 3}$$


equations in 3 unknowns. Cramer's rule:

$$V_1 = \frac{0.5a^2(s/w_0 - 1)}{1+a+(1+a+0.5a^2)s/w_0} V$$

$$I = \frac{V - V_1}{R} = \frac{1}{R} \frac{(1+a)s/w_0 + 1+a+0.5a^2}{1+a+(1+a+0.5a^2)s/w_0} V$$

Setting $a = w_t/s$ and exploiting the fact that $w_0 \ll w_t$, we obtain
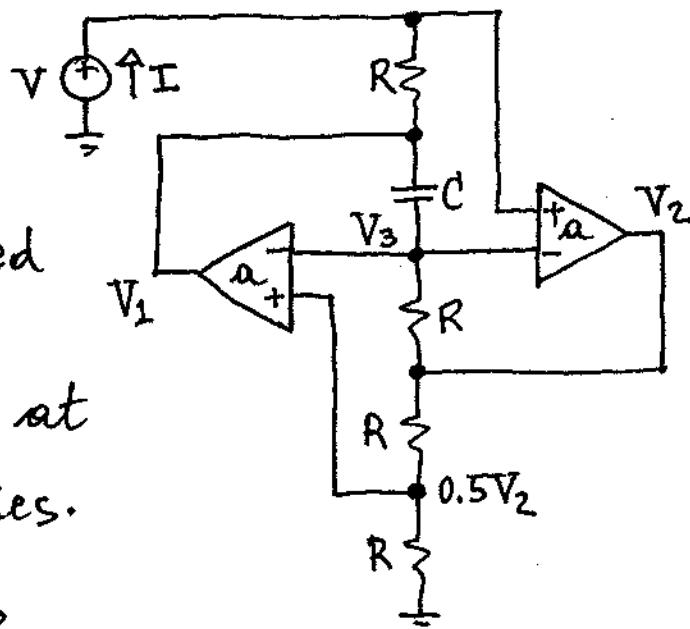
$$Z = \frac{V}{I} \approx L_s \frac{0.5 + s/w_t + (s/w_t)^2}{0.5 + s/w_t + s^2/w_0 w_t + s^3/w_0 w_t^2}, L = R^2 C.$$



6.33

As a check: $Z(s \rightarrow 0) = Ls$, and $Z(w_f \rightarrow \infty) = Ls$.


Moreover, $Z(s \rightarrow \infty) = R$, as expected using physical insight. The error function departs significantly from 1 as f is increased, and it exhibits even peaking, as revealed by Fig. 1.

Problem 6.52: L simulator using ideal op amps

```
Ii 0 1 ac 1
R1 1 2 7.96k
C2 2 3 10n
R3 3 4 7.96k
R4 4 5 7.96k
R5 5 0 7.96k
e1 2 0 5 3 1G
e2 4 0 1 3 1G
.ac dec 100 1k 10Meg
.probe
.end
```

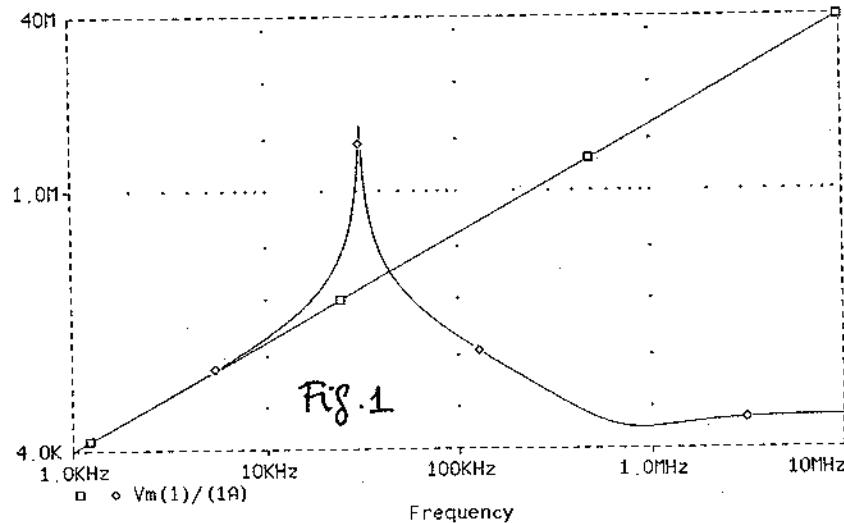Problem 6.52: L simulator using OAs with $ft=1$ MHz

```
Ii 0 1 ac 1
R1 1 2 7.96k
C2 2 3 10n
R3 3 4 7.96k
R4 4 5 7.96k
R5 5 0 7.96k
e1 2 0 Laplace {V(5,3)}={1Meg/(1+s/6.283)}
e2 4 0 Laplace {V(1,3)}={1Meg/(1+s/6.283)}
.ac dec 100 1k 10Meg
.probe
.end
```



It is intriguing that in spite of the poor inductance behavior at high frequencies, the response of the actual DABP filter is fairly close to the ideal over a far wider range (Fig. 2.) As shown in greater detail in Fig. 3, the effect is a downshift from $f_0 = 2.0 \text{ kHz}$ to $f_0 = 1.984 \text{ kHz}$, which is readily compensated for using predistortion.

Problem 6.52: DABP using ideal op amps

```

Vi 10 0 ac 1
R 10 1 199k
C 1 0 10nF
R1 1 2 7.96k
C2 2 3 10n
R3 3 4 7.96k
R4 4 5 7.96k
R5 5 0 7.96k
e1 2 0 5 3 1G
e2 4 0 1 3 1G
.ac dec 100 0.1k 10Meg
.probe
.end

```



Problem 6.52: DABP using op amps with $f_t=1 \text{ MHz}$

```

Vi 10 0 ac 1
R 10 1 199k
C 1 0 10nF
R1 1 2 7.96k
C2 2 3 10n
R3 3 4 7.96k
R4 4 5 7.96k
R5 5 0 7.96k
e1 2 0 Laplace {V(5,3)}={1Meg/(1+s/6.283)}
e2 4 0 Laplace {V(1,3)}={1Meg/(1+s/6.283)}
.ac dec 100 0.1k 10Meg
.probe
.end

```

6.35

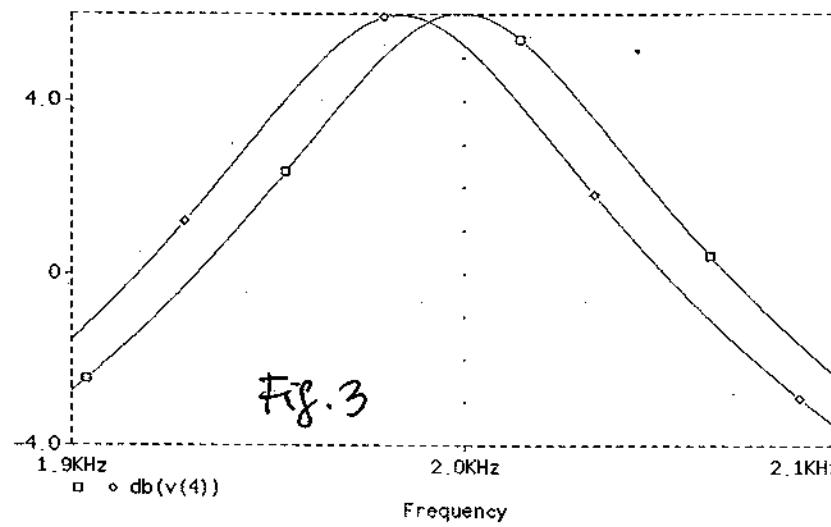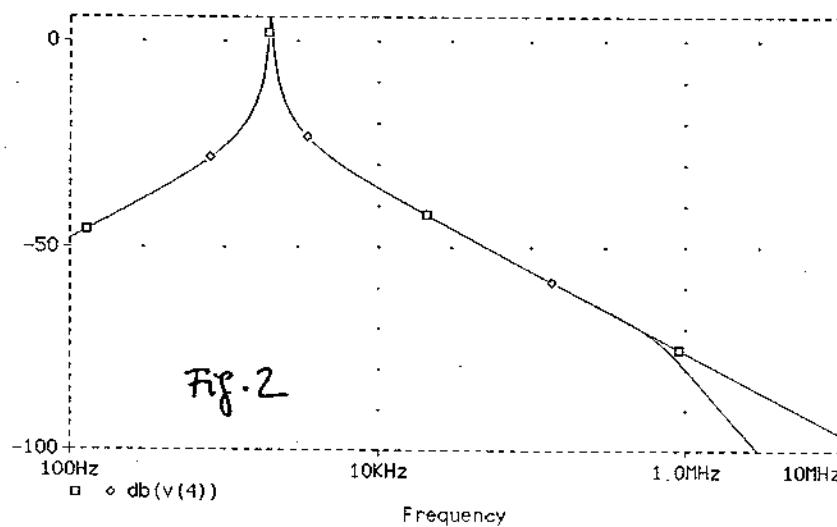

6.36

6.53 For the LP filter of Fig. 3.23 we have:

$$H = \frac{A}{R_1 C_1 R_2 C_2 s^2 + [(1-A)R_1 C_1 + R_1 C_2 + R_2 C_2]s + 1}$$

Letting $\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$

$$\frac{1}{\omega_0 Q} = (1-K)R_1 C_1 + R_1 C_2 + R_2 C_2$$

$$A = \frac{K}{1+s/(w_t/K)} = \frac{K}{1+Ks/w_t}$$

$$K = 1 + RB/RA$$

we get $1-A = [(1-K) + Ks/w_t]/[1+Ks/w_t]$.

Substituting,

$$H = \frac{\frac{K}{1+Ks/w_t}}{\left(\frac{s}{\omega_0}\right)^2 + \left[\frac{1-K+Ks/w_t}{1+Ks/w_t} R_1 C_1 + R_1 C_2 + R_2 C_2\right]s + 1}$$

$$= \frac{K}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{\omega_0 Q} + 1 + \frac{Ks}{w_t} \left[\left(\frac{s}{\omega_0}\right)^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2)s + 1\right]}$$

But, $R_1 C_1 + R_1 C_2 + R_2 C_2 = \frac{1}{\omega_0 Q} + KR_1 C_1 = \frac{1}{\omega_0 Q} \left(1 + QK\sqrt{\frac{R_1 C_1}{R_2 C_2}}\right)$

$$\therefore H(s) = \frac{K}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + 1 + \frac{Ks}{w_t} \left[\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) \left(1 + QK\sqrt{\frac{R_1 C_1}{R_2 C_2}}\right) + 1\right]}$$

3.37

6.54 Using the PSpice code shown, we find that the effects of finite GBPs are a steeper rolloff at high frequencies (Fig. 1) as well as a shift in f_0 from 1 kHz to 995 Hz, and a reduction in Q from 100 to 67 (Fig. 2).

Changing the capacitances from 10 nF to 9.95 nF, and adding a compensating capacitance $C_c = 50 \text{ pF}$ in parallel with R_6 restores the desired response (Fig. 3).

Problem 6.54: SV filter with ideal OAs

```

Vi 1 0 ac 1
r1 1 3 1k
r2 3 6 299k
r3 1 2 15.92k
r4 2 8 15.92k
r5 2 4 15.92k
r6 4 5 15.92k
r7 6 7 15.92k
c1 5 6 10n
c2 7 8 10n
eoal 4 0 3 2 1G
eoal 6 0 0 5 1G
eoal 8 0 0 7 1G
.ac dec 100 100 1Meg
.probe
.end

```




Problem 6.54: SV filter with 1-MHz OAs

```

Vi 1 0 ac 1
r1 1 3 1k
r2 3 6 299k
r3 1 2 15.92k
r4 2 8 15.92k
r5 2 4 15.92k
r6 4 5 15.92k
r7 6 7 15.92k
c1 5 6 10n
c2 7 8 10n
eoal 4 0 Laplace {V(3,2)}={200k/(1+s/6.283)}
eoal 6 0 Laplace {V(0,5)}={200k/(1+s/6.283)}
eoal 8 0 Laplace {V(0,7)}={200k/(1+s/6.283)}
.ac dec 100 100 1Meg
.probe
.end

```

6.58

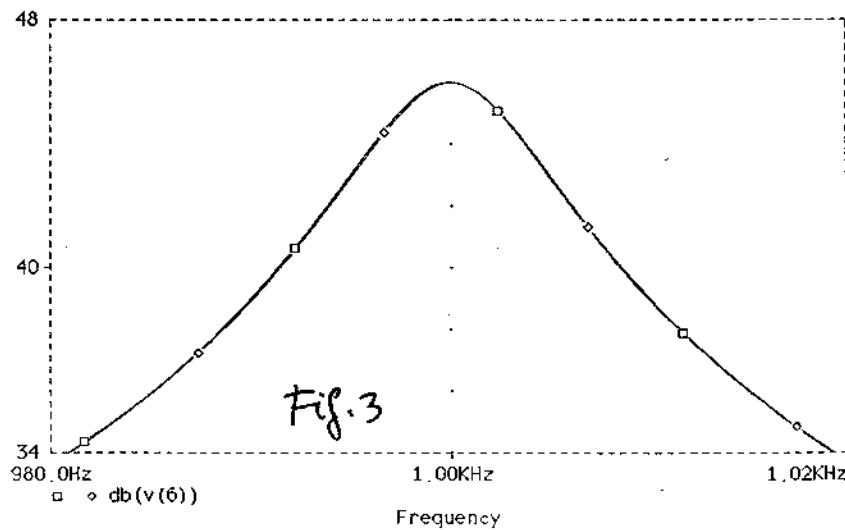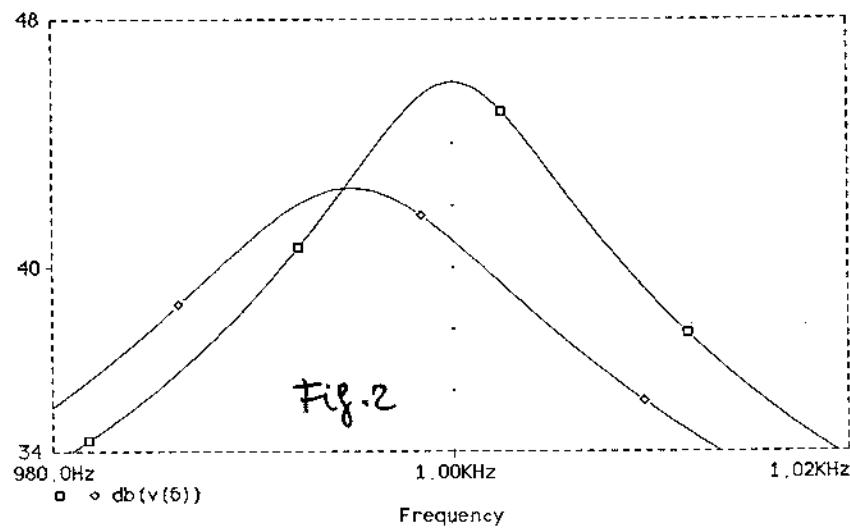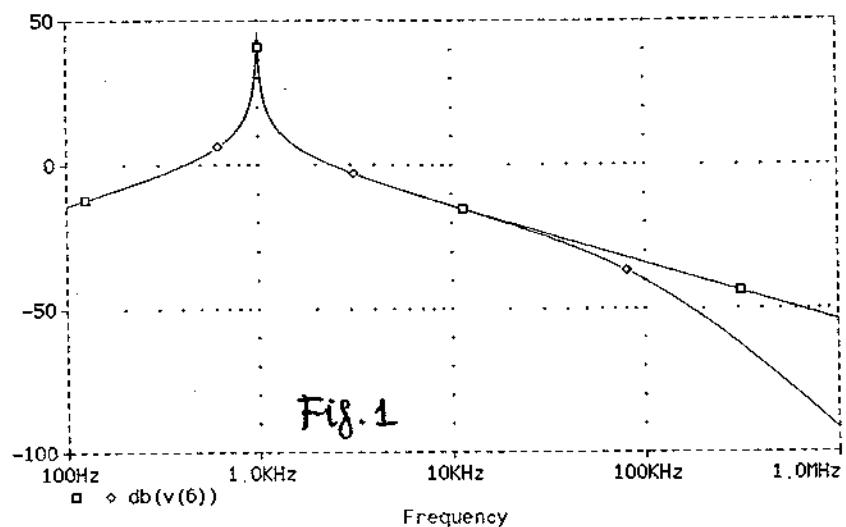

6.39

6.55 Using the PSpice code shown, we find that the finite GBP has little effect on the location of the notch (Fig 1: $f_0 = 60\text{ Hz}$). The GBP of 1 MHz causes the actual response to roll off with frequency past 100 kHz (Fig.2).

Problem 6.55: Notch with ideal OA

```

Vi 0 1 ac 1
r1 1 2 26.526k
r2 2 4 26.526k
r3 3 0 13.263k
c1 1 3 100n
c2 3 4 100n
c3 2 5 200n
ra 6 0 10k
rb 5 6 29.167k
eoa 5 0 4 6 100G
.ac lin 500 59 61
.probe
.end


```

Problem 6.55: Notch with OA with $f_t = 1\text{MHz}$


```

Vi 0 1 ac 1
r1 1 2 26.526k
r2 2 4 26.526k
r3 3 0 13.263k
c1 1 3 100n
c2 3 4 100n
c3 2 5 200n
ra 6 0 10k
rb 5 6 29.167k
eoa 5 0 Laplace {V(4,6)}={1Meg/(1+s/6.283)}
.ac lin 500 59 61
.probe
.end


```

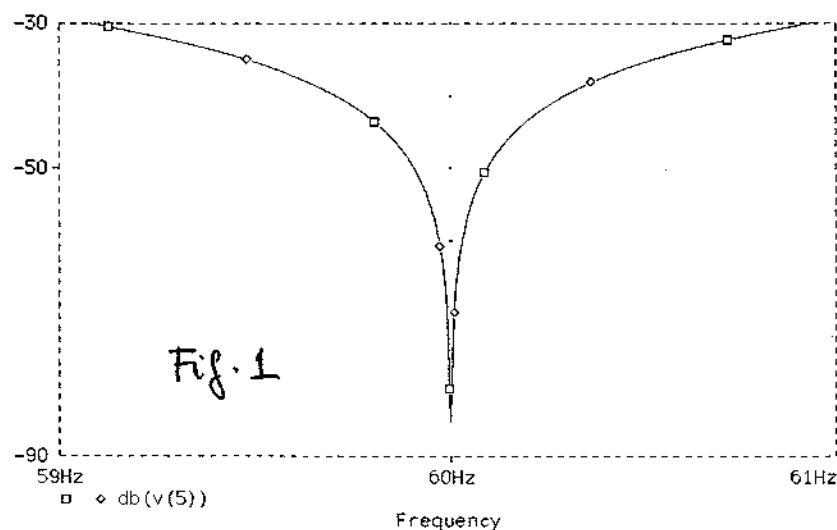

C.40

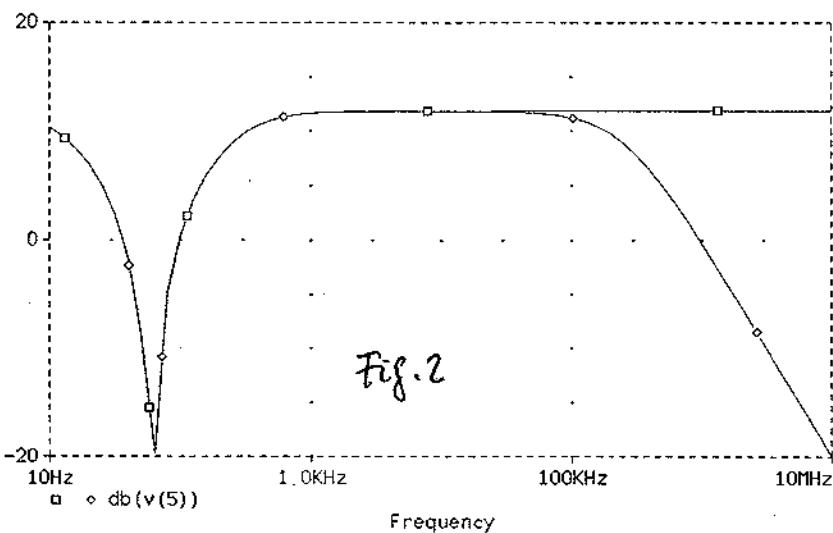

6.56 (a)

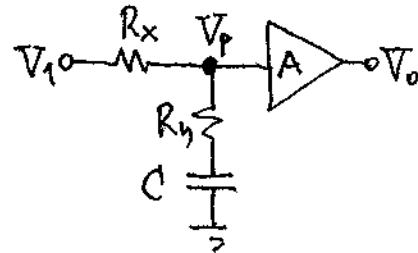

$$\begin{aligned} V_o &= A V_p = A \frac{R_y + 1/sC}{R_x + R_y + 1/sC} V_i \\ &= \frac{A_0}{1+s/\omega_B} \frac{1+sR_y C}{1+s(R_x+R_y)C} V_i \end{aligned}$$

Imposing $R_y C = 1/\omega_A$ and $R_x + R_y = R$ gives $V_o = A_0 V_i / (1 + sRC)$, i.e. the same relationship as an R-C stage followed by an ideal amplifier with gain A_0 .

(b) $A_0 = 1 \text{ V/V}$, $\omega_B = \omega_T = 2\pi f_T = 10^6 \text{ Hz}$, $R_C = 1/2\pi f_T C = 159 \Omega$ (use $158 \Omega, 1\%$), $R - R_C = 2199 - 159 = 2.04 \text{ k}\Omega$ (use $2.05 \text{ k}\Omega, 1\%$).

6.41

6.57 $\left(\frac{1}{\beta}\right)_{\min} = 10^3 \text{ V/A}; f_t = \frac{1}{2\pi \times 10^3 \times 1.59 \times 10^{-12}} = 100 \text{ MHz}$

Design for $\eta_b = 0.5 \times \frac{10^6}{10^3} = 500$ and $f_B = f_t$ in each case.

(a) $R_2/R_1 = 2$; $1+R_2/R_1 = 3$; impose

$$R_2 + R_m (1+R_2/R_1) = 10^3 \Rightarrow R_2 = 10^3 - 25 \times 3 = 925 \Omega$$

(use $931 \Omega, 1\%$), $R_1 = \frac{1}{2} R_2 = 464 \Omega, 1\%$.

(b) $1+R_2/R_1 = 11$; $R_2 = 10^3 - 25 \times 11 = 732 \Omega, 1\%$, $R_1 = 73.2 \Omega, 1\%$.

(c) $R_1 = R_2 = 10^3 - 25 \times 2 = 953 \Omega, 1\%$.


6.58

(a) $R_1 = \infty, R_2 = 10^3 - 25 = 975 \Omega$

(b) $R_1 = R_2 = 10^3 - 25(1+1) = 950 \Omega$

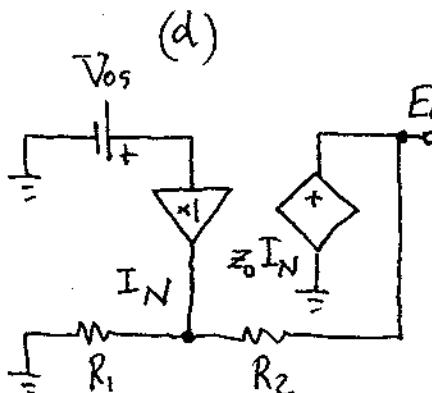(c) $R_1 = \infty, R_2 = 2 \times 10^3 - 25 = 1975 \Omega$

$R_1 = R_2 = 2 \times 10^3 - 50 = 1950 \Omega$



(d)

$$E_o = (1+R_2/R_1)V_{OS} + R_2 I_N$$

$$(a) E_o(\max) = 1 \times V_{OS} +$$

$$975 \times I_N = 2.95 \text{ mV};$$

$$(b) E_o(\max) = 2V_{OS} + 950 I_N \\ = 3.9 \text{ mV}.$$

$$(c) E_o(\max) = 4.95 \text{ mV}, 5.9 \text{ mV}.$$

6.42

6.59 (a)

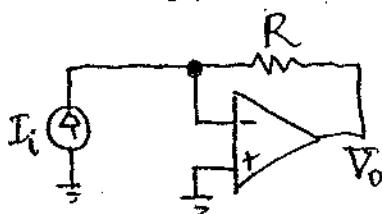


Fig. 1

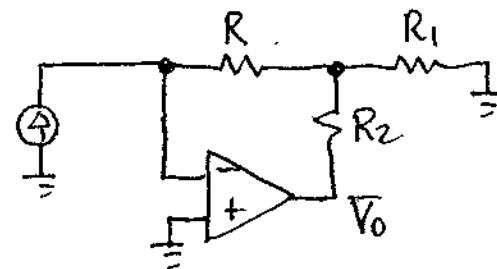


Fig. 2

$$V_o/I_i = -10 \text{ V/mA} = -10^4 \text{ V/A} \Rightarrow R = 10 \text{ k}\Omega \text{ in}$$

$$\text{Fig. 1, and } R(1 + R_2/R_1 + R_2/C_m) = 10^4 \text{ in Fig. 2.}$$

2. Pick $R = R_2 = 1 \text{ k}\Omega$; then $R_1 = 125 \text{ }\Omega$.

(b) In Fig. 1, $\beta = 1/(R + C_m) = 1/10,025 \text{ A/V}$.

$$f_B = (10,000/10,025) f_t = 99.75 \text{ MHz. } E_o = V_{os} + REN \\ = 1 \text{ mV} + 20 \text{ mV} = 21 \text{ mV maximum.}$$


In Fig. 2, $\beta = \frac{R_1}{R + C_m + R_1} \times \frac{1}{R_2 + R_1/(R + C_m)} \\ = 1/10,235 \text{ A/V; } f_B = (10,000/10,235) f_t = 97.7 \text{ MHz. } E_o = (1 + R_2/R_1)V_{os} + 10^4 E_N = 8 \text{ mV} + 20 \text{ mV} \\ = 28 \text{ mV maximum. Bandwidth is about the same; maximum error is worst in Fig. 2 because of the increased noise gain for } V_{os}.$

6.60

Replace C_m with $C_m + R_{\text{pot}}$. Wiper at the right: $f_B = f_t / [1 + C_m / (1000 \parallel 110)] \\ = 10^8 / [1 + 25/99.1] = 79.9 \text{ MHz; } \tau_R \cong 2.2 / (2\pi \times 79.9 \times 10^6) \cong 4.4 \text{ ms. Wiper at the left: } f_B = 10^8 / [1 + 1025/99.1] \cong 8.8 \text{ MHz, } \tau_R \cong 39.7 \text{ ms.}$

6.43


6.61

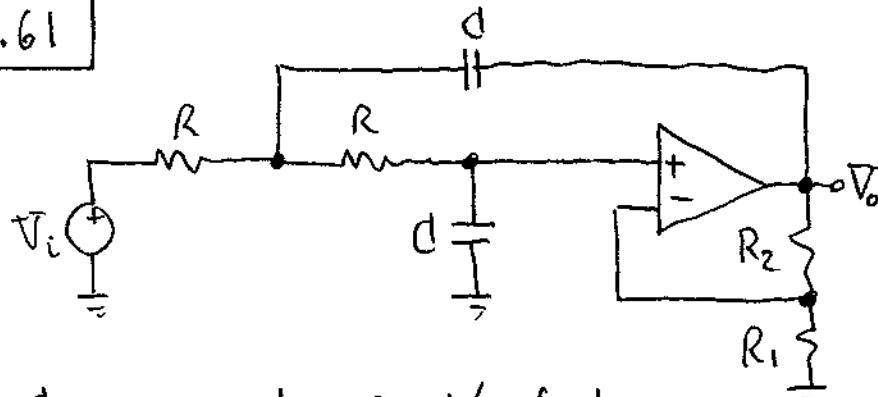

let $C = 100 \mu F$. Then, $R = 1/(2\pi f_0 C) = 1/(2\pi \times 10^7 \times 10^{-10}) = 159 \Omega$ (Use $158 \Omega, 1\%$).

$Q = 1/(3 - k) = 5 \Rightarrow k = 1 + R_2/R_1 = 2.8 \Rightarrow R_1 = R_2/1.8 = 1.5 \times 10^3 / 1.8 = 833 \Omega$ (Use $845 \Omega, 1\%$)

6.62 (a)

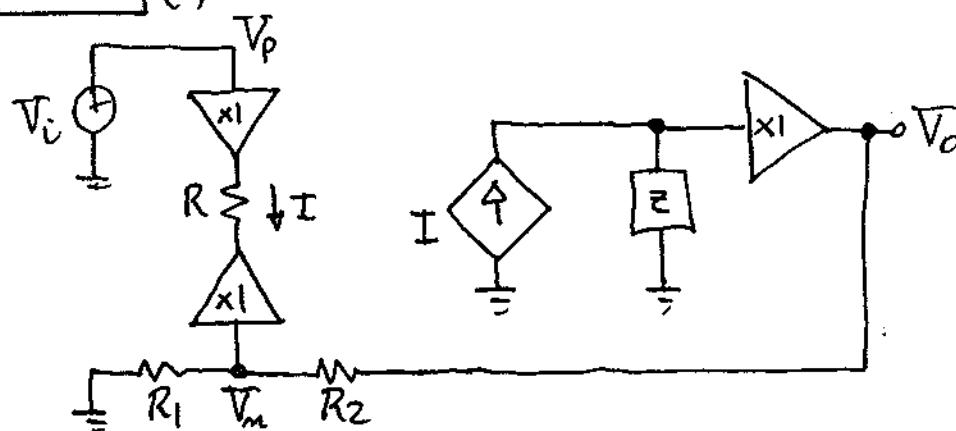

$$V_o = ZI = Z \frac{V_p - V_m}{R + 2r_o} = A(V_p - V_m), A = \frac{Z}{R + 2r_o}$$

$$SR = I/C_{eq} = (V_p - V_m)/[(R + 2r_o)C_{eq}]$$

$$(b) A_o = \frac{R_{eq}}{R + 2r_o} = \frac{10^6}{500 + 2 \times 25} = 1818 \text{ V/V}$$

$$f_b = 1/(2\pi R_{eq} C_{eq}) \approx 80 \text{ kHz}; f_t = A_0 f_b = 145 \text{ MHz}$$

$$\beta = 0.5; T_0 = 909; A_0 = 2 \times \frac{1}{1+1/909} = 1.9978 \text{ V/V}$$

$$f_B = 72 \text{ MHz}$$

$$(c) SR = \frac{1}{550 \times 2 \times 10^{-12}} = 909 \text{ V/}\mu\text{s.}$$