 


Applications Note: SY5830B Single Stage Flyback And PFC Controller With Primary Side Control For LED Lighting

General Description

The SY5830B is a single stage Flyback and PFC controller targeting at LED lighting applications. It is a primary side controller without applying any secondary feedback circuit for low cost, and drives the Flyback converter in the quasi-resonant mode to achieve higher efficiency. It keeps the Flyback converter in constant on time operation to achieve high power factor. It adopts special design to achieve quick start up and reliable protection for safety requirement.

Ordering Information



Ordering Number	Package type	Note
SY5830BABC	SOT23-6	

Typical Applications

 


Figure 1. Schematic Diagram SOT23-6



- Primary side control eliminates the opto-coupler.
- Valley turn-on of the primary MOSFET to achieve low switching loss
- Power factor >0.90 with single-stage conversion.
- Reliable short LED and Open LED protection
- Quick start up <500ms
- Low start up current:15µA typical
- Package: SOT23-6

Applications

• LED lighting


 


Figure 2. Efficiency vs Input Voltage

 

2

Pinout (top view)



Top Mark: Jyxyz (device code: Jy, x=year code, y=week code, z= lot number code)

Pin Name	SOT23-6	Pin Description	
ISEN	1	Current sense pin. Connect this pin to the source of the primary switch. Connect the sense resistor across the source of the primary switch and the GND pin. (current sense resister R : R $_{S}$ = k $\frac{V \times N}{\frac{REF}{0}}$, k=0.167) Also this pin used to detect transformer and secondary is short or not.	
GND	2	Ground pin	
COMP	3	Loop compensation pin. Connect a RC network across this pin and ground to stabilize the control loop.	
VSEN	4	Inductor current zero-crossing detection pin. This pin receives the auxiliary winding voltage by a resister divider and detects the inductor current zero crossing point. This pin also provides over voltage protection and line regulation modification function simultaneously. If the voltage on this pin is above $V_{VSEN,OVP}$, the IC would enter over voltage protection mode. Good line regulation can be achieved by adjusting the upper resistor of the divider.	
VIN	5	Power supply pin. This p n lso provides output over voltage protection along with VSEN pin.	
DRV	6	Gate driver pin. Connect this pin to the gate of primary MOSFET.	



Absolute Maximum Ratings (Note 1)

VIN, DRV	-0.3V~33V
Supply Current I _{VIN}	15mA
VSEN	$-0.3V \sim V_{IN}+0.3V$
ISEN, COMP	-0.3~3.6V
Power Dissipation, @ T _A = 25°C SOT23-6	0.6W
Package Thermal Resistance (Note 2)	
SOT23-6, θJA	170°C/W
SOT23-6, θJC	130°C/W
Junction Temperature Range	-40°C to 150°C
Lead Temperature (Soldering, 10 sec.)	260°C
Storage Temperature Range	-65°C to 150°C

Recommended Operating Conditions (Note 3)

VIN, DRV	9.5V~27V
Junction Temperature Range	-40°C to 125°C

Block Diagram

 


Figure3. Block Diagram



Electrical Characteristics

 $(V_{IN} = 12V \text{ (Note 3)}, T_A = 25^{\circ}C \text{ unless otherwise specified)}$

Parameter	Symbol	Test Conditions	Min	Тур	Max	Unit
Power Supply Section						
VIN turn-on threshold	V VIN,ON		22.5	25	27	V
VIN turn-off threshold	V VIN,OFF		7.5	8.5	9.5	V
VIN OVP voltage	V VIN,OVP		27	30	33	V
Start up Current	ST	VIN VIN,OFF	12	17	23	μA
Shunt current in OVP mode	I VIN,OVP	V VIN VIN,OVP	3.8	4.7	5.7	mA
Error Amplifier Section						
Internal reference voltage	V REF		0.294	0.3	0.306	V
Current Sense Section						
Current limit voltage	V ISEN,LIMIT		0.40	0.44	0.48	V
Protection limit for TR short	V ISEN,EX		0.85	0.9	0.97	V
CC Feedforward coefficient	K2			0.1		
CC Feedforward resistor	K2			340		Ω
COMP section						
Pre-charge value	V COMP,ST			1.4		V
VSEN pin Section						
VSEN pin OVP voltage	V					
threshold	VSEN,OVP		1.43	1.5	1.57	V
Fast start up theshold	V VSEN,ST			0.55		V
Gate Driver Section						
Gate driver voltage	V Gate		9.5	12	13	V
Maximum source current	I SOURCE			60		mA
Minimum sink current	I SINK			250		mA
Max ON Time	I ON,MAX	V _{ISEN} =0V		10		μs
Max OFF Time	OFF,MAX			150		μs
Blanking time for ON time	I ON,BLK			350		ns
Blanking time for OFF time	I OFF,BLK			2		μs
Maximum switching frequency	I MAX			125		kHz
Thermal Section						
Thermal Shutdown	Т					
Temperature	SD			150		°C

Note 1: Stresses beyond the "Absolute Maximum Ratings" may cause permanent damage to the device. These are stress ratings only. Functional operation of the device at these or any other conditions beyond those indicated in the operational sections of the s ecification is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

Note 2: f_{JA} is measured in the natural convection at $T_A = 25^{\circ}$ C on a low effective single layer thermal conductivity test board of JEDEC 51-3 thermal measurement standard. Test condition: Device mounted on 2" x 2" FR-4 substrate PCB, 2oz copper, with minimum recommended pad on top layer and thermal vias to bottom layer ground plane.

Note 3: Increase VIN pin voltage gradually higher than V_{VIN,ON} voltage then turn down to 12V.



AN_SY5830B

Operation

SY5830B is a constant current Flyback controller with primary side control and PFC function that targets at LED lighting applications.

The device provides primary side control to eliminate the opto-couplers or the secondary feedback circuits, which would cut down the cost of the system.

High power factor is achieved by constant on operation mode, with which the control scheme and the circuit structure are both simple.

Start up process is optimized inside SY5830B, and quick start up (less than 500ms) is achieved without any additional circuit

In order to reduce the switching losses and improve EMI performance, Quasi-Resonant switching mode is applied, which means to turn on the power MOSFET at voltage valley; the start up current of SY5830B is rather small (15μ A typically) to reduce the standby power loss further; the maximum switching frequency is clamped to 125kHz to reduce switching losses and improve EMI performance when the converter is operated at light load condition.

SY5830B provides reliable protections such as Short Circuit Protection (SCP), Open LED Protection (OLP), Over Temperature Protection (OTP), transformer shorted protection and power diode shorted protection, etc.


SY5830B is available with SOT23-6

Applications Information

<u>Start up</u>

After AC supply or DC BUS is powered on, the capacitor C_{VIN} across VIN and GND pin is charged up by BUS voltage through a start up resistor R_{ST} . Once V_{VIN} ises up to V_{VIN-ON} , the internal blocks start to work and PWM output is enabled.

 The output voltage is feedback by VSEN pin, which is taken as V_{FB} . If V_{FBV} is lower than certain threshold $V_{VSEN,ST}$, which means the output voltage is not built up, V_{COMP} is pulled up to high clamped; if V_{FBV} is higher than $V_{VSEN,ST}$, V_{COMP} is under charge of the internal gain modulator.



This operation is aimed to build up enough output voltage for auxiliary winding bias supply as quickly as possible. It is enabled only one time just when $V_{\rm VIN}$ is over $V_{\rm VIN,ON}$.

 v_{COMP} is pre-charged by internal current source to $v_{COMP,IC}$ and hold at this level until fast start up process is finished.

The start up resistor R_{ST} and C_{VIN} are designed by rules below:

(a) Preset start-up resistor $R_{ST},\,$ make sure that the current through R_{ST} is larger than I_{ST} and smaller than I

$$\frac{VIN OVP}{V} \frac{V}{BUS} = \frac{V}{R_{ST}} < \frac{V}{I}$$

Where V_{BUS} is the BUS line voltage.

(b) Select C_{VIN} to obtain an ideal start up time t_{ST} , and ensure the output voltage is built up at one time.

$$C_{VIN} = \frac{\left(\frac{\mathbf{v}_{BUS}}{R_{ST}} - I_{ST}\right) \times t_{ST}}{V_{VIN ON}}$$

(d) If the C_{VIN} is not big enough to build up the output voltage at one time. Increase C_{VIN} and decrease R_{ST} , go back to step (a) and redo such design flow until the ideal start up procedure is obtained.



After AC supply or DC BUS is powered off, the energy stored in the BUS capacitor will be discharged. When the auxiliary winding of Flyback transformer can not supply enough energy to VIN pin, V_{VIN} will drop down. Once V_{VIN} is below $V_{VIN-OFF}$, the IC will stop working and V_{COMP} will be discharged to zero.

Primary-side constant-current control


Primary side control is applied to eliminate secondary feedback circuit or opto-coupler, which reduces the circuit cost. The switching waveforms are shown in blow.

The output current I_{OUT} can be represented by,

$$I_{OUT} = \frac{I_{SP}}{2} \frac{t_{DIS}}{t_S}$$

Where I_{SP} is the peak current of the secondary side; t_{DIS} is the discharge time of Flyback transformer; t_S is the switching period.

 The secondary peak current is related with primary peak current, if the effect of the leakage inductor is neglected.



 $I_{SP} = N_{PS} \times I_{PP} (4)$

Where N_{PS} is the turns ratio of primary to secondary of the Flyback transformer.

Thus, IOUT can be represented by

$$\underset{2}{\overset{N\times I}{\underset{p_{S}}{\times}}} \underset{t_{S}}{\overset{p_{P}\times \text{ dis}}{\overset{p_{P}\times \text{ dis}}{\times}}}$$

The primary peak current I_{PP} and inductor current discharge time t_{DIS} can be detected by Source and VSEN pin, which is shown in blow. These singals are processed and applied to the negative input of the gain modulator. In static state, the positive and negative inputs are equal

 


Fig. Output current detection diagram

Finally, the output current I_{OUT} can represented by

$$I_{OUT} = \frac{REF}{R_S \times 2 \times k_1}$$

Where k_1 is the output current weight coefficient; V_{REF} is the internal reference voltage; R_{S} is the current sense resistor.

 k_1 , and V_{REF} are all internal constant parameters, I_{OUT} can be programmed by N_{PS} and R_S .

$$R_{s} = \frac{V \times N}{\prod_{out \times 2 \times k_{1}}}$$


then

$$R_{s} = \frac{k \times V_{REF} \times N_{PS}}{I}, k = \frac{1}{2k_{1}}$$



Quasi-Resonant Operation

 QR mode operation provides low turn-on switching losses for Flyback converter.



The voltage across drain and source of the primary MOSFET is reflected by the auxiliary winding of the Flyback transformer. VSEN pin detects the voltage across the auxiliary winding by a resistor divider. When the voltage across drain and source of the primary MOSFET is at voltage valley, the MOSFET would be turned on.

<u>Over Voltage Protection (OVP) & Open LED</u> Protection (OLP)

 


Fig. OVP&OLP

The output voltage is reflected by the auxiliary winding voltage of the Flyback transformer, and both VSEN pin and VIN pin provide over voltage protection function. When the load is null or large transient happens, the output voltage will exceed the rated value. When V_{VIN} exceeds $V_{VIN,OVP}$ or V_{VSEN} exceeds $V_{VSEN,OVP}$, the over voltage protection is triggered and the IC will discharge V_{VIN} by an internal current source $I_{VIN,OVP}$. Once V_{VIN} is below $V_{VIN,OFF}$, the IC will shut down and be charged again by BUS voltage through start up resistor. If the over voltage condition still exists, the system will operate in hiccup mode.

Thus, the turns of the auxiliary winding N_{AUX} and the resistor divider is related with the OVP function.

$$\frac{V_{\text{SEN_OVP}} = V_{\text{SEND}}}{V_{\text{OVP}} R_{\text{VSENU}} + R_{\text{VSEND}}}$$

$$\frac{V_{\text{VIN_OVP} \ge}}{V_{\text{OVP}} N_{\text{s}}}$$

Where V_{OVP} is the output over voltage specification; R_{VSENU} and R_{VSEND} compose the resistor divider. The turns ratio of N_S to N_{AUX} and the ratio of R_{VSENU} to R_{VSEND} could be induced from equation above.

Short Circuit Protection (SCP)

When the output is shorted to ground, the output voltage is clamped to zero. The voltage of the auxiliary winding is proportional to the output winding, so valley signal cannot be detected by VSEN. Without valley detection, MOSFET cannot be turned ON until maximum off time $t_{OFF,MAX}$ is matched. If MOSFET is turned ON by $t_{OFF,MAX}$ 64 times continuously, IC will be shut down and enter into hiccup mode.

If the output voltage is not low enough to disable valley detection in short condition, V_{VIN} will drop down without auxiliary winding supply. Once V_{VIN} is below $V_{VIN,OFF}$, the IC will shut down and be charged again by the BUS voltage through the start up resistor. If the short circuit condition still exists, the system will operate in hiccup mode.

Line regulation modification

The IC provides line regulation modification function to improve line regulation performance.

Due to the sample delay of ISEN pin and other internal delay, the output current increases with increasing input BUS line voltage. A small compensation voltage $\Delta V_{ISEN,C}$ is added to ISEN pin during ON time to improve such performance. This $\Delta V_{ISEN,C}$ is adjusted by the upper resistor of the divider connected to VSEN pin and external resistor R_{ISEN,C} on ISEN pin.

$$\Delta V_{\text{ISEN,C}} = V_{\text{BUS}} \times \frac{N}{N_{p}} \times \frac{1}{\kappa_{\text{VSENU}}} \times k_{2} \times (R_{k2} + R_{lSEN,C})$$

Where R_{VSENU} is the upper resistor of the divider; k_2 is an internal constant as the modification coefficient;



Rk2 is an internal feed-forward resistor; auxiliary resistor RISEN.C can be added to enhance feed-forward effects.

 


Fig. feed-forward resistor

Single fault design

If VSEN pin is shorted to GND pin or floating, valley detection is failed, which is similar to SLP, the system will operate in hiccup mode.

If the transformer or the secondary diode is shorted, VISEN will exceeds VISEN.EX, and the system will operate in hiccup mode.

Thermal fold back design

If IC junction temperature rises over T_{FB} , the output current will be decreased to regulate the junction temperature around T_{FB} . If the junction temperature is over T_{SD} , IC will be shut down and won't r cov r unless the junction temperature drops below T_{FB}.

Power Device Design

MOSFET and Diode

When the operation condition is with maximum input voltage and full load, the voltage stress of MOSFET and secondary power diode is maximized;

$$V_{\text{MOS_DS-MAX}} = \sqrt{2V} + N_{\text{ps}} \times (V_{\text{out}} + V_{\text{d_f}}) + \Delta V_{\text{s}}$$
$$V_{\text{d_f}} = \frac{\sqrt{2V} AC_{\text{MAX}}}{1N} + V_{\text{out}}$$

Where VAC.MAX is maximum input AC RMS voltage; N_{PS} is the turns ratio of the Flyback transformer; V_{OUT} is the rated output voltage; V_{D,F} is the forward voltage of secondary power diode; ΔV_S is the

overshoot voltage clamped by RCD snubber during OFF time.

When the operation condition is with minimum input voltage and full load, the current stress of MOSFET and power diode is maximized.

$$\begin{array}{c} I = I \\ I^{\text{MOS}_{PK}\text{MAX}} = I^{P_{P}K\text{MAX}} \\ I^{\text{MOS}_{RMS}\text{MAX}} = I^{P_{P}K\text{MAX}} \\ I^{\text{MOS}_{RMS}\text{MAX}} = I \\ I^{D_{PK}\text{MAX}} P^{S} P_{P}K\text{MAX} \\ I^{D_{PK}\text{MAX}} = I \\ D_{\text{AVG}} \text{OUT} \end{array}$$

1

Where IP-PK-MAX and IP-RMS-MAX are maximum primary peak current and RMS current, which will be introduced later.

Transformer (N_{PS} and L_M)

N_{PS} is limited by the electrical stress of the power MOSFET:

$$\sum_{N_{PS}} \leq \frac{V_{MOS}(BR)DS \times 90\%}{V_{AC}MAX} \cdot \Delta V_{S}$$

Whe e V_{MOS,(BR)DS} is the breakdown voltage of the power MOSFÊT.

In Quasi-Resonant mode, each switching period cycle t_S consists of three parts: current rising time t₁, current falling time t₂ and quasi-resonant time t₃ shown in blow Vg A

 


Fig. switching waveforms



The system operates in the constant on time mode to achieve high power factor. The ON time increases with the input AC RMS voltage decreasing and the load increasing. When the operation condition is with minimum input AC RMS voltage and full load, the ON time is maximized. On the other hand, when the input voltage is at the peak value, the OFF time is maximized. Thus, the minimum switching frequency

 $f_{S\text{-}MIN}$ happens at the peak value of input voltage with minimum input AC RMS voltage and maximum load condition; Meanwhile, the maximum peak current through MOSFET and the transformer happens.

Once the minimum frequency f_{S-MIN} is set, the inductance of the transformer could be induced. The design flow is shown as below:

(a)Select N_{PS}

$$\sum_{N_{PS}} \leq \frac{V_{MOS_{BR})DS} \times 90\% \sqrt{-\sqrt{2}V_{AC_{MAX}}} - \Delta V_S}{V_{OUT} + V_{D_F}}$$

(b) Preset minimum frequency f_{S-MIN}

(c) Compute relative t_S , t_1 (t_3 is omitted to simplify the design here)

$$t_{S} = \frac{1}{\sum_{S_{MIN}}}$$
$$t_{1} = \frac{t_{S} \times N_{PS} \times (V_{OUT} + V_{D-F})}{\sqrt{2}V_{AC_{MIN}} + N_{PS} \times (V_{OUT} + V_{D-F})}$$

(d) Design inductance L_M

$$L_{M} = \frac{V_{AC}^{2} MIN \times t_{1}^{2} \times \eta}{2P_{OUT} \times t_{S}}$$


(e) Compute t₃

$$t_{3} = \pi \times \sqrt{L_{M} \times C}_{Drain}$$

Where C_{Drain} is the parasitic capacitance at drain of MOSFET.

 (f) Compute primary maximum peak current $I_{P-PK-MAX}$ and RMS cu rent $I_{P-RMS-MAX}$ for the transformer fabricat on.

$$I_{P_{P}^{K}MAX} = \frac{2P_{OUT} \times \left[\sqrt{2V_{AC_{MIN}}} + \frac{N_{PS} \times (V_{OUT} + V_{DF})}{L_{M} \times \eta}\right]}{L_{M} \times \eta}$$



Where η is the efficiency; P_{OUT} is rated full load power

Adjust $t_1 \text{ and } t_S \text{ to } t_1' \text{ and } t_S' \text{ considering the effect of } t_3$

$$t' = \underbrace{\underbrace{\mathbb{N} \times \mathbb{I}_{M} \times \mathbb{I}_{p}^{-} \mathbb{P}K \operatorname{MAX}}_{\text{OUT}}$$

$$t' = \underbrace{\underbrace{\mathbb{L} \times \mathbb{I}}_{1} \times \mathbb{I}}_{\operatorname{MC_MIN}}$$

$$I_{P_{\text{RMS}_{\text{MAX}}} \approx \sqrt{\frac{\mathbb{t}_{l'}}{6t'}} \times I_{s}$$

$$P_{\text{PK}_{\text{MAX}}} \approx \sqrt{\frac{\mathbb{t}_{l'}}{6t'}} \times I_{s}$$

(g) Compute secondary maximum peak current $I_{S\text{-}PK\text{-}}_{MAX}$ and RMS current $I_{S\text{-}RMS\text{-}MAX}$ for the transformer fabrication.

$$I_{SPK_{MAX}} = N_{PS} \times I_{PPK_{MAX}}$$
$$t_{2} = t_{S}' - t_{1}' - t_{3}$$
$$I_{S_{RMS_{MAX}}} \approx \sqrt{\frac{t'_{2}}{6t'_{S}}} \times I_{S_{RMS_{MAX}}}$$

Transformer design (NP,NS,NAUX)

The design of the transformer is similar with ordinary Flyback transformer. The parameters below are necessary:

Necessary parameters	
Turns ratio	PS
Inductance	L _M
Primary maximum current	I P-PK-MAX
Primary maximum RMS current	P-RMS-MAX
Secondary maximum RMS current	I S-RMS-MAX

The design rules are as followed:

(a) Select the magnetic core style, identify the effective area A_{e} .

(b) Preset the maximum magnetic flux ΔB

ΔB=0.22~0.26T



(c) Compute primary turn N_P $L \times I$ N =

$$\Delta B \times A_e$$

(d) Compute secondary turn N_S

$$N_{S} = \frac{P^{N}}{N_{PS}}$$

(e) compute auxiliary turn NAUX

 $N_{AUX} = N_S \times \frac{V_{VIN}}{V_{OUT}}$

Where V_{VIN} is the working voltage of VIN pin

(f) Select an appropriate wire diameter

With $I_{P\text{-}RMS\text{-}MAX}$ and $I_{S\text{-}RMS\text{-}MAX}$, select appropriate wire to make sure the current density ranges from $4A/mm^2$ to $10A/mm^2$

(g) If the winding area of the core and bobbin is not enough, reselect the core style, go to (a) and redesign the transformer until the ideal transformer is achieved.

Output capacitor Cout

Preset the output current ripple $\Delta I_{OUT},\ C_{OUT}$ is induced by

$$C_{\text{out}} = \frac{\sqrt{\frac{2I}{(\frac{OUT}{\Delta i})^2 - 1}}}{4\pi f R}$$

Where I_{OUT} is the rated output current; ΔI_{OUT} is the demanded current ripple; f_{AC} is the input AC supply frequency; R_{LED} is the equivalent series resistor of the LED load.

AN_SY5830B

RCD snubber for MOSFET

The power loss of the snubber P_{RCD} is evaluated first

$$P_{_{RCD} = \underline{N_{PS} \times (V_{OUT} + V_{D F}) + \Delta V_{S}} \times \underline{L_{K}} \times P_{_{OUT}}$$

Where N_{PS}

$$\Delta V_S$$
 L_M

is the turns ratio of the Flyback transformer; V_{OUT} is the output voltage; $V_{D\text{-}F}$ is the forward voltage of the power diode; ΔV_S is the overshoot voltage clamped by RCD snubber; L_K is the leakage inductor; L_M is the inductance of the Flyback transformer; P_{OUT} is the output power.

The R_{RCD} is related with the power loss:


$$R_{_{RCD}} = \frac{\left(N_{PS} \times \left(V_{OUT} + V_{D_{-}F}\right) + \Delta V_{S}\right)^{2}}{P_{_{RCD}}}$$

The C_{RCD} is related with the voltage ripple of the snubber ΔV_{C-RCD} :

$$C_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D_F}) + \Delta V_S}{R_{RCD} f \Delta V_{C RCD}}$$

AN_SY5830BRev.0.1 Silergy Corp. Confidential- Prepared for Customer Use Only 10



 

SOT23-6 Package outline & PCB layout design

Notes: All dimensions are in millimeters. All dimensions don't include mold flash & metal burr.